

TOSHIBA

e-Learning

Basics of CMOS Logic ICs

Chapter2 Basic Operations of CMOS Logic ICs

Toshiba Electronic Devices & Storage Corporation


02

Basic operations of CMOS Logic ICs


2.1 What is a CMOS Logic IC?

A circuit that uses complementary pairs of **p-channel** and **n-channel** MOSFETs is called **CMOS** (**C**omplementary **M**OS). CMOS logic ICs combine MOSFETs in various ways to implement logic functions. A logic gate composed of a single pair of p-channel and n-channel MOSFETs is called an inverter.

Inverter

 


Logic symbol

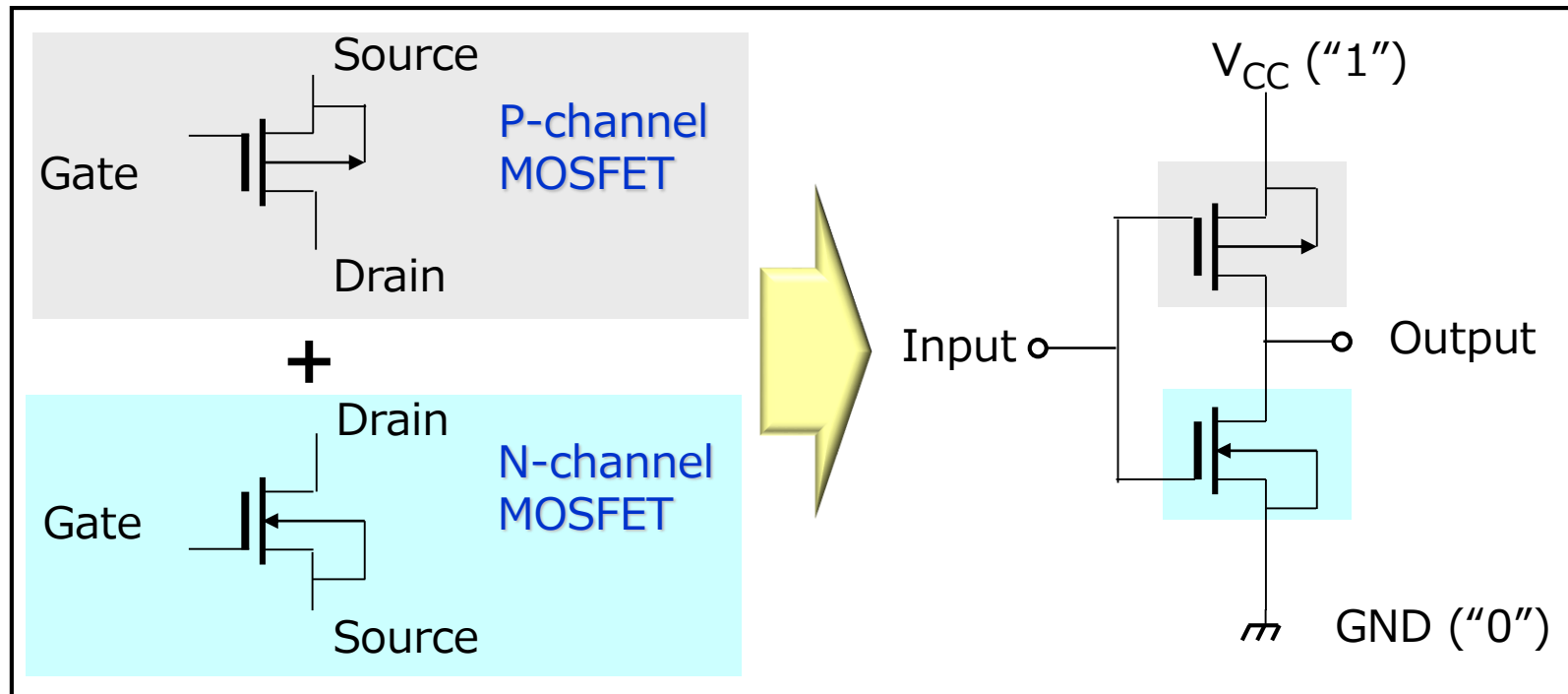

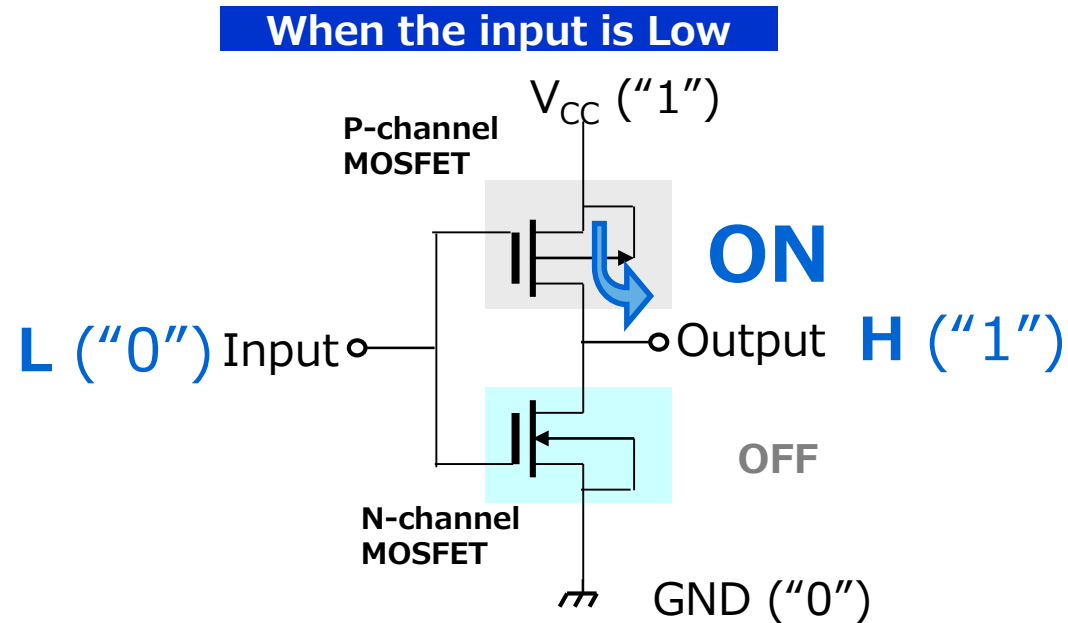2.2 Basic CMOS Logic ICs: #1

The following briefly describes the operation of an **inverter**.



* V_{CC} : Supply voltage

Truth	
Input	Output
L	H
H	L


When the input is Low, the n-channel MOSFET is **off**, and the p-channel MOSFET is **on**.

At this time, V_{CC} and the output are electrically connected.

The output signal is driven to High (V_{CC} "1").

2.2 Basic CMOS Logic ICs: # 1

When the input is High

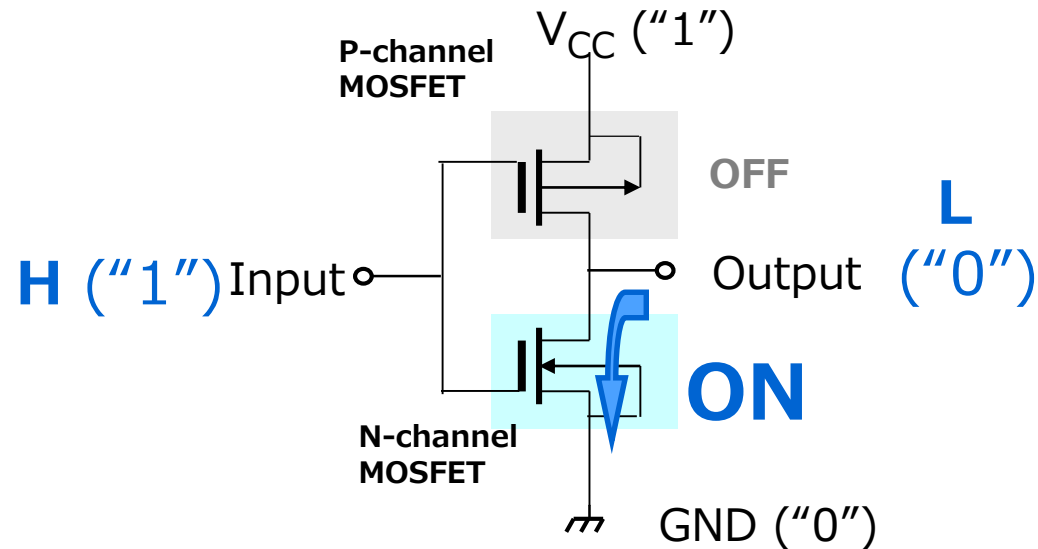

When the input is High, the n-channel MOSFET is **on**, and the p-channel MOSFET is **off**.



At this time, GND and the output are electrically connected.

The output signal is driven to Low (GND "0").



2.2 Basic CMOS Logic ICs: #2

Various logic functions can be implemented by combining p-channel and n-channel MOSFETs.

2-input NAND gate

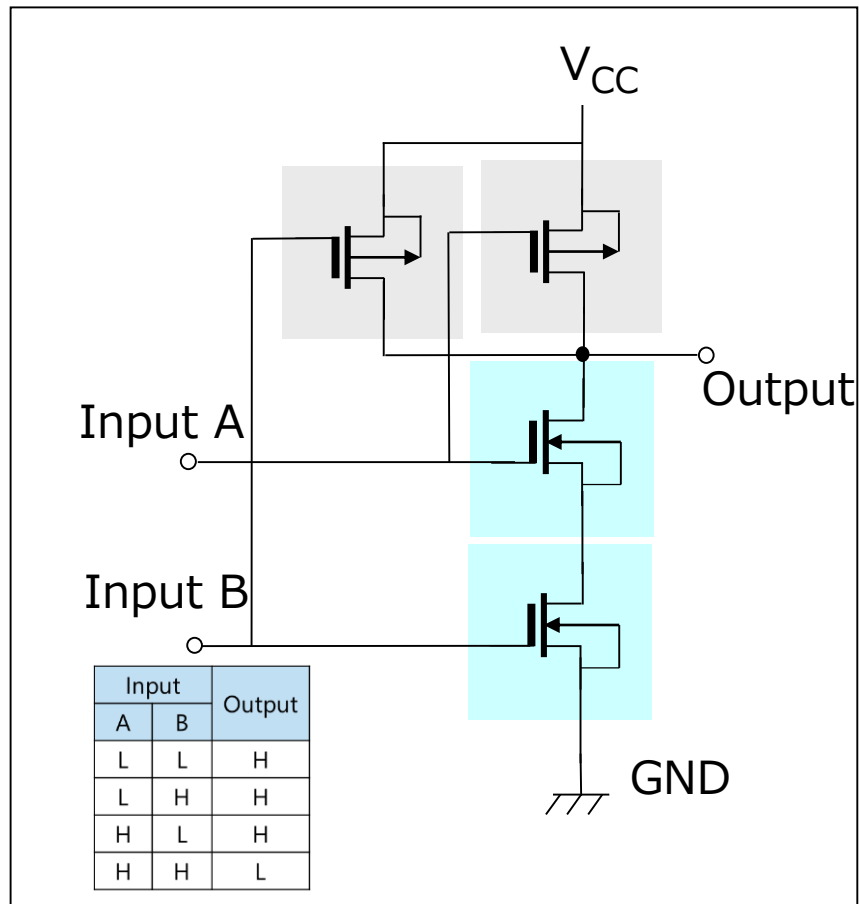 

2-input NOR gate

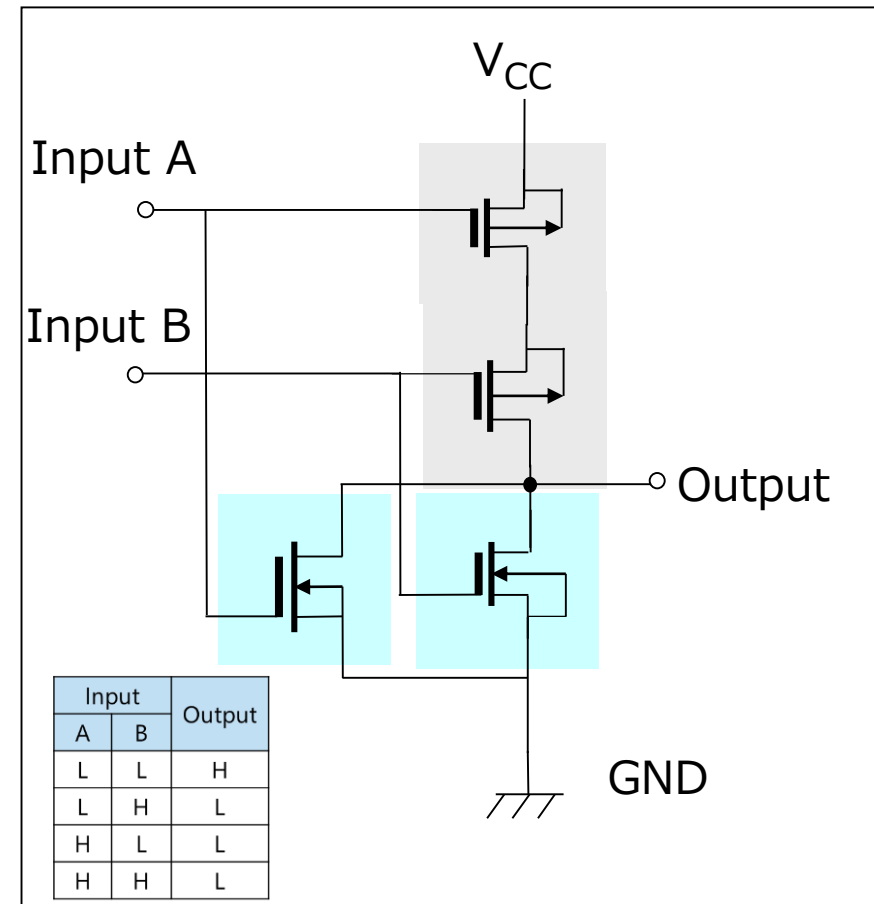 



2.3 Basic operations of CMOS Logic ICs: #1

When the gate-source voltage of a MOSFET exceeds a certain voltage (threshold voltage, $|V_{th}|$), the drain-source resistance decreases, causing the MOSFET to turn on. This drain-source resistance is called on-resistance.

The direction of the voltage applied across gate and source differs between n-channel and p-channel MOSFETs. The following figure shows the condition under which a MOSFET turns on.

N-channel MOSFET: When the gate voltage is higher than the source voltage by $|V_{th}|$, the n-channel MOSFET turns on.

Characteristics of the n-channel MOSFET

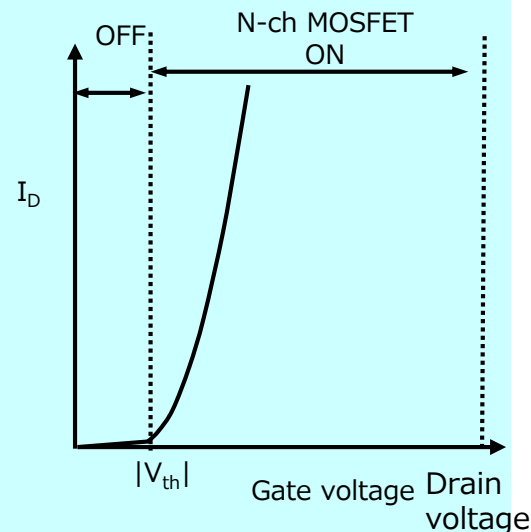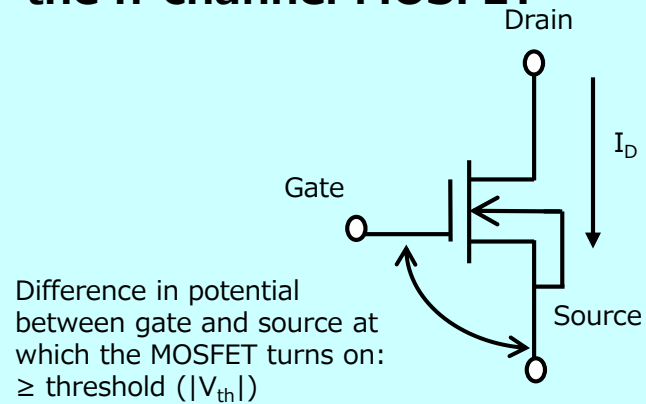



Apply positive voltage to the gate with respect to the source.

2.3 Basic operations of CMOS Logic ICs: #1

P-channel MOSFET: When the gate voltage is lower than the source voltage by $|V_{th}|$, the p-channel MOSFET turns on.

Characteristics of the p-channel MOSFET

Difference in potential between gate and source at which the MOSFET turns on: \geq threshold ($|V_{th}|$) Gate

  


Apply negative voltage to the gate with respect to the source.

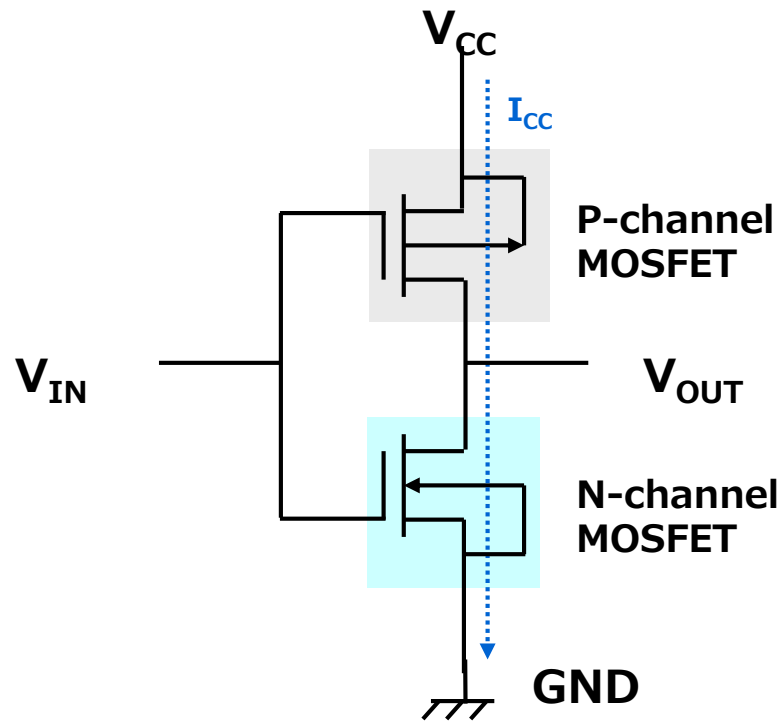2.3 Basic operations of CMOS Logic ICs: #2

The following figure shows an inverter, a basic building block of CMOS logic ICs.

When V_{IN} is at the V_{CC} or GND level, either the p-channel or n-channel MOSFET is off. Therefore, very little current (I_{CC}) flows between V_{CC} and GND. When the input is in the steady state (at the V_{CC} or GND level), I_{CC} is very low.




Building block of the CMOS logic IC (inverter)

2.3 Basic operations of CMOS Logic ICs: #2

The following figure shows the V_{IN} - I_{CC} curve of CMOS.

When V_{IN} is between 0 and $|V_{th}|$ or between $V_{CC} - |V_{th}|$ and V_{CC} , very little current (I_{CC}) flows between V_{CC} and GND. However, when V_{IN} is between $|V_{th}|$ and $V_{CC} - |V_{th}|$, shoot-through current flows from the p-channel MOSFET to the n-channel MOSFET, increasing I_{CC} . Therefore, care should be exercised to ensure that excessively slowly changing input is not applied to V_{IN} .

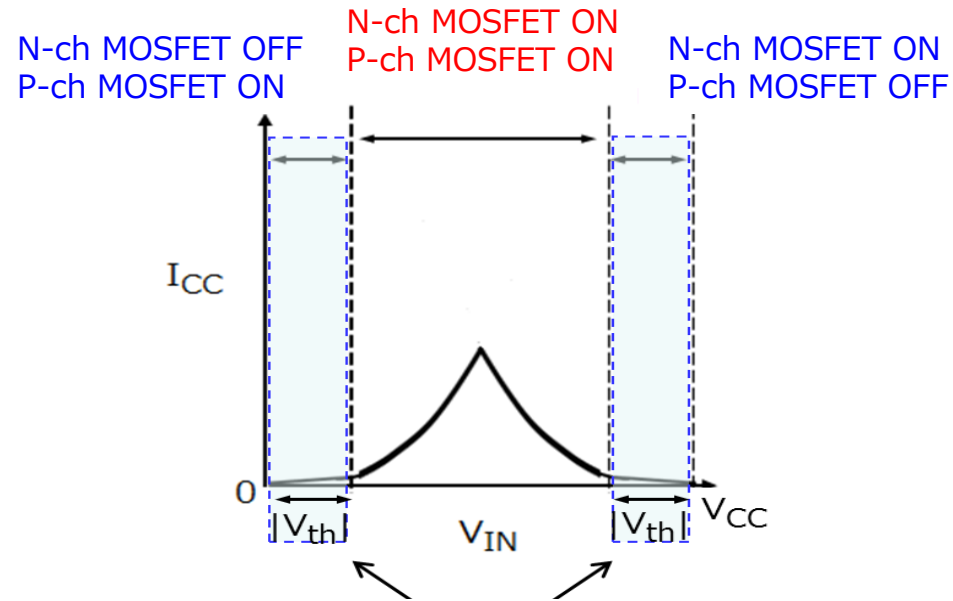


By using it in this range, I_{CC} hardly flows.

V_{IN} - I_{CC} curve of the CMOS logic IC

2.4 Basic configuration of CMOS Logic ICs

- **Example of the cross section of a CMOS logic IC**
 - > A wide diffusion region (p-well) is formed in the n-substrate.
 - > An n-channel MOSFET is formed on the p-well.
 - > A p-channel MOSFET is formed on the n-substrate.
 - > An n-well is formed on a p-substrate, depending on the process.
 - > Since the performance and integration density of MOSFETs are determined by the gate width, the manufacturing process is expressed with the gate width. For example, a CMOS process with a gate width of 1.0 μm is called a 1.0- μm CMOS process.
(In this case, the gate width is the distance between #3 and #4 and between #5 and #6.)

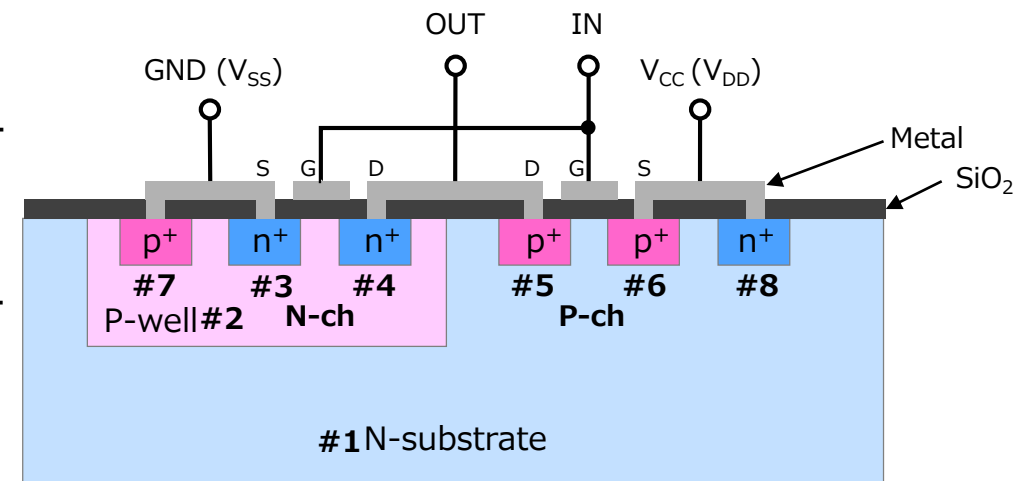- #1. N-substrate: Typically, a wafer substrate
- #2. P-well: Region for forming an n-channel MOSFET
- #3. Diffused region for the source of the n-channel MOSFET
- #4. Diffused region for the drain of the n-channel MOSFET
- #5. Diffused region for the drain of the p-channel MOSFET
- #6. Diffused region for the source of the p-channel MOSFET
- #7. Diffused region for p-well bias
- #8. Diffused region for n-substrate bias



TOSHIBA