

**Single-Output High-Side
N-Channel Power MOSFET
Gate Driver Application
and Circuit of the TPD7106F
Reference Guide**

RD178-RGUIDE-01

TOSHIBA ELECTRONIC DEVICES & STORAGE CORPORATION

Table of Contents

1. Overview	4
1.1 Target Application	5
2. Application Circuit Diagram	6
3. Bill of Materials	8
4. Application Circuit Design Guide	9
4.1 Normal Operation (Gate Drive of Power MOSFET)	9
4.1.1 Simulation Verification	9
4.2 Switching Waveform.....	11
4.3 Operation with the Power Supply Reverse Connection.....	13
4.3.1 Simulation Verification	13
4.4 Charge Pump Capacitor Selection	15
4.4.1 Simulation Verification	16
4.5 Charge Pump Voltage Drop Detection	19
4.5.1 Simulation Verification	19
5. Product Overview	21
5.1 TPD7106F	21
5.1.1 Overview.....	21
5.1.1 Appearance and Pin Assignment.....	21
5.2 TKR74F04PB	22

5.2.1 Overview..... 22

5.2.2 Appearance and Pin Assignment..... 22

1. Overview

Mechanical relays are widely known as switches that cut off and connect power supply lines from power sources such as batteries to loads. However, because mechanical relays mechanically open and connect contacts repeatedly, there is a problem with durability, and in applications where long-term reliability is required, semiconductor relays using semiconductor elements are becoming increasingly popular. Furthermore, with the increasing number of systems, the current capacitor required for semiconductor relays is increasing year by year, and by using a load switch circuit using a discrete N-channel power MOSFET with low on-resistance, a high-current semiconductor relay with low-loss and low heat generation can be realized.

TPD7106F is an N-channel power MOSFET gate driver for a single-output high-side switch with a built-in charge pump circuit. When combined with an external discrete N-channel MOSFET, a high-side switch can be configured for high-current applications. In addition, semiconductor relays have no contact wear unlike mechanical relays, so maintenance-free operation can be achieved. There are I/O terminals that control turn-off rapidly to protect MOSFET when an abnormality occurs, and they are independently controlled from the microcomputer to achieve safe operation.

This reference guide explains, the operation at the power supply reverse connection, which is important for the safe operation of the system including the high current load switch, and the application of the charge pump circuit.

Please refer to the datasheet for TPD7106F functions and detailed information.

Download TPD7106F datasheets from here →

[Click Here](#)

1.1 Target Application

- Automotive junction box
- On-board power distribution module
- Semiconductor relay

Application circuit example

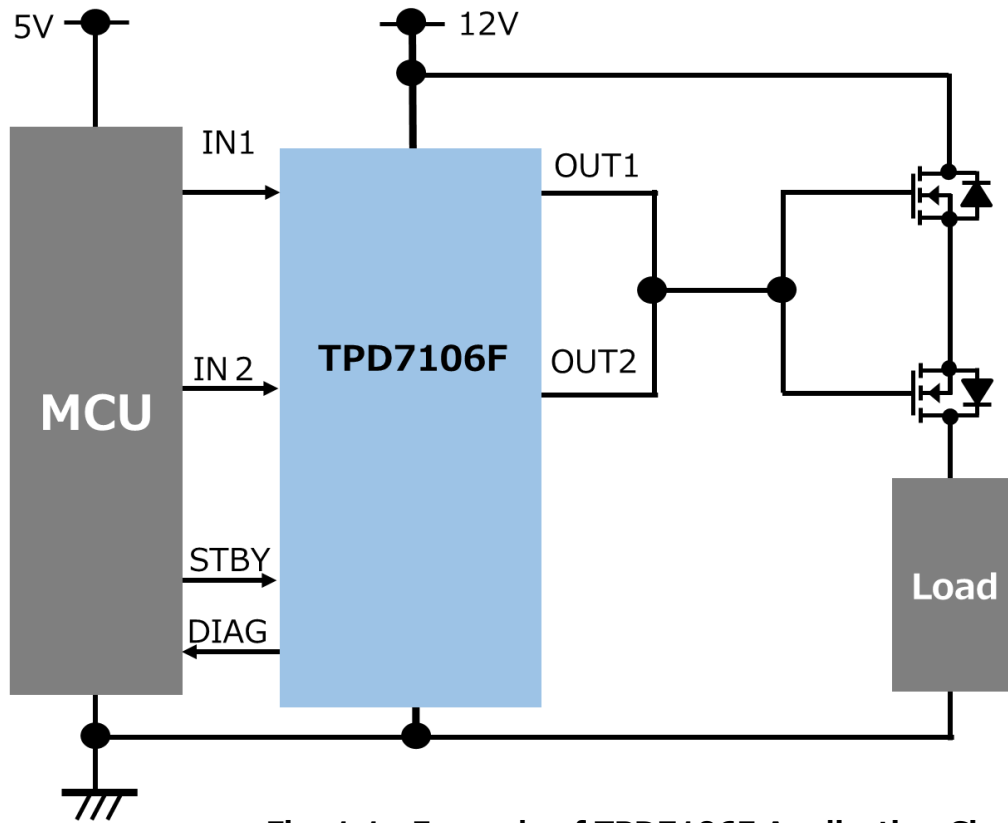


Fig. 1.1 Example of TPD7106F Application Circuit

2. Application Circuit Diagram

Fig. 2.1 is an application circuit diagram of a semiconductor-relay block composed of TPD7106F and TKR74F04PB (N-channel 40 V, 0.74 mΩ).

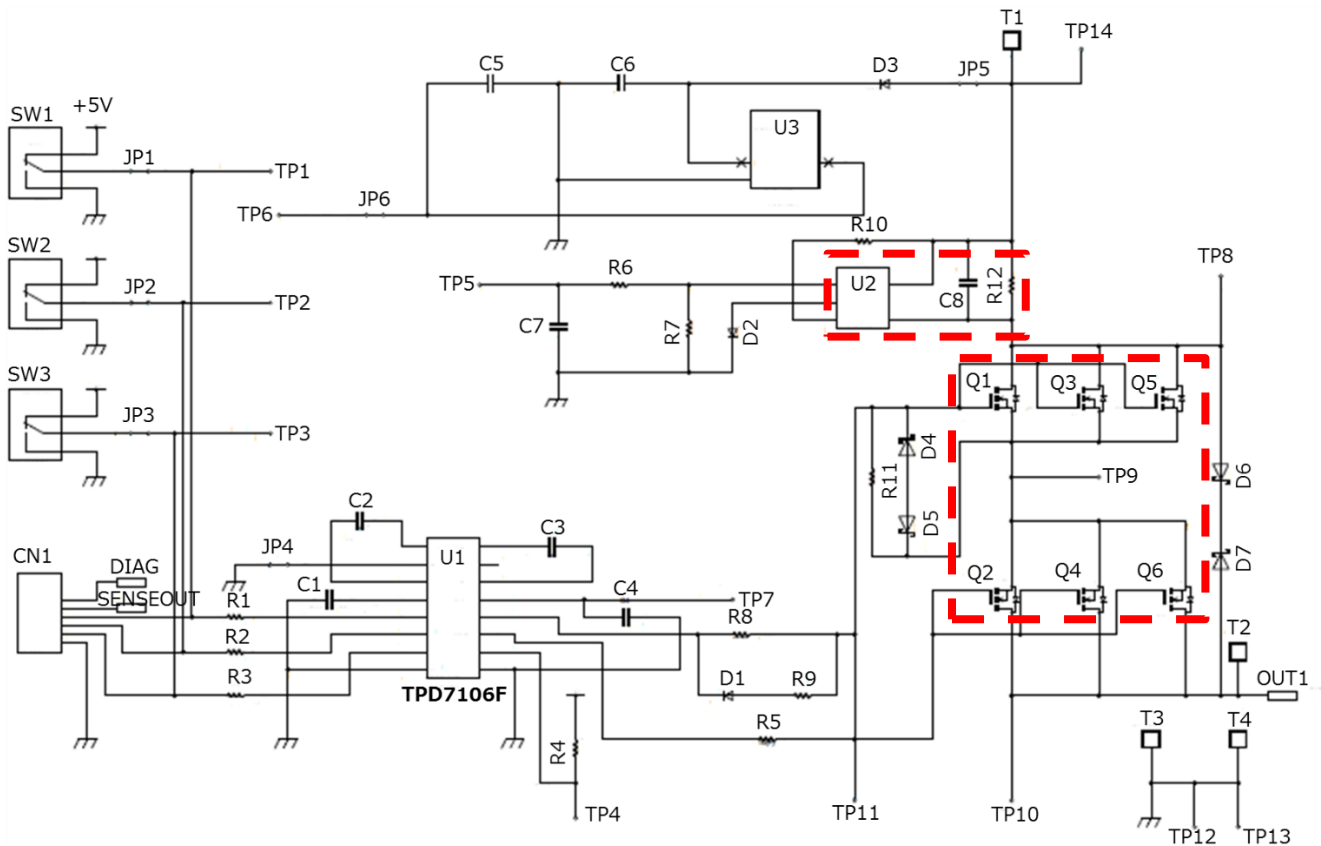


Fig. 2.1 Application Circuit Diagram (Semiconductor Relay)

MOSFET is a three-parallel connection of the source common, so TPD7106F are driving six MOSFET. The maximum load current is targeted at 200 A. The current sense amplifier uses a shunt resistor (R12) and a low-offset current sense amplifier (U2) for voltage conversion. The gate drive of the TPD7106F is described in Chapter 4.1.

The typical gate-source breakdown voltage of MOSFET is ± 20 V.

D4 and D5, a zener diode of 16 V is inserted to protect the gate-source of MOSFET. The switching time adjustment is described in Chapter 4.2.

TPD7106F has a function to keep Q₁ to Q₆ off-state at the power supply reverse connection. Chapter 4.3 describes the operation.

TPD7106F has a built-in charge pump circuitry that is combined with an external capacitance so that it can drive an external discrete N-channel MOSFET with a low on-resistance. Therefore, the capacitor is required as an external component. For capacitors C2 and C3, 0.1 μ F is selected. The selection method is described in Chapter 4.4.

TPD7106F has a built-in charge pump voltage drop detection function to check that the proper gate voltage is applied to MOSFET. The operation is described in chapter 4.5.

Please refer to the overall schematic as it is published in (RD178-SCHEMATIC-01).

The overall schematic is shown in this → [Click Here](#)

Download TKR74F04PB datasheet from here → [Click Here](#)

For more information about MOSFET, go here to → [Click Here](#)

3. Bill of Materials

Table 3.1 is a bill of materials in Application Circuit Diagram.

Table 3.1 Bill of Materials for Semiconductor Relay Circuits

No.	Ref.	Q'ty	Value	Part Number	Manufacturer	Description	Package Name	Standard Dimensions in mm (inches)
1	U1	1		TPD7106F	TOSHIBA	IPD (Gate driver)	SSOP-16	5.5×6.4
2	U2	1		LTC6101BCS5	LT	Current sense amplifier	TSOT-23	2.9×2.8
3	U3	1		TA7805F	TOSHIBA	Regulator	HSOP-3	6.5×9.5
4	Q1,Q2,Q3,Q4,Q5,Q6	6		TKR74F04PB	TOSHIBA	MOSFET	TO-220SM(W)	10.0×13.0
5	D1,D2	2		1SS352	TOSHIBA	Switching diode	SOD-323	2.5×1.25
6	D3	1		CRG09A	TOSHIBA	Rectifier diode	S-FLAT	1.6×3.5
7	D4,D5	2		CRZ16	TOSHIBA	Zener diode	S-FLAT	1.6×3.5
8	D6,D7	2		CMZ27	TOSHIBA	Zener diode	M-FLAT	2.4×4.7
9	R1,R2,R3,R4,R7	5	10k			Chip resistor, ±1%	1608	1.6×0.8 (0603)
10	R5	1	10			Chip resistor, ±1%	1608	1.6×0.8 (0603)
11	R6	1	47k			Chip resistor, ±1%	1608	1.6×0.8 (0603)
12	R8	1	1k			Chip resistor, ±1%	1608	1.6×0.8 (0603)
13	R9	1	100			Chip resistor, ±1%	1608	1.6×0.8 (0603)
14	R10	1	200			Chip resistor, ±1%	1608	1.6×0.8 (0603)
15	R11	1	200k			Chip resistor, ±1%	1608	1.6×0.8 (0603)
16	R12	1	0.5m	BVS-M-R0005	isabellenhuette	Shunt resistance, ±1%		6.35×3.05
17	C1,C4	2	1.0uF			Ceramic, 50V, ±10%	3216	3.2×1.6 (1206)
18	C2,C3,C6	3	0.1uF			Ceramic, 50V, ±10%	1608	1.6×0.8 (0603)
19	C5	1	10uF			Ceramic, 50V, ±10%	3216	3.2×1.6 (1206)
20	C7	1	1000pF			Ceramic, 50V, ±10%	1608	1.6×0.8 (0603)
21	C8	1	15pF			Ceramic, 50V, ±10%	2012	2.0×1.25
22	CN1	1		22-23-2061	molex	6-pole 1-row connector		
23	SW1,SW2,SW3	3		SS-12SDP2	NKK	Switch		
24	T1,T2,T3,T4	4		OP-486	OSADA	Terminal		
25	JP1,JP2,JP3,JP4,JP5,JP6	6		XJ8B-0211	OMRON	Jumper		
26	TP1~TP14	14		ST-2-2	MAC8	Monitor pin		

4. Application Circuit Design Guide

In addition to normal operation, this chapter describes the "operation at the power supply reverse connection" and "charge pump circuit", which are the points in designing, in chapter 4.1 to 4.5, including verification by simulation.

4.1 Normal Operation (Gate Drive of Power MOSFET)

Table 4.1 lists the truth values. The input pin IN1 is a control pin in normal operation. The input pin IN2 is a control pin in quick off mode. The quick off mode by IN2 is used to shut down MOSFET in abnormal operation such as load short circuit.

Table 4.1 Truth Table

IN1	IN2	STBY	OUT1	OUT2	State
X	X	L	Hiz	Hiz	Standby mode
L	L	H	L	Hiz	Normal operation
H	L	H	H	Hiz	
L	H	H	L	L	Quick off mode
H	H	H	L	L	

4.1.1 Simulation Verification

Check the simulation for normal operation, switching waveform (turn-on, turn-off time) and quick-off operation. Fig. 4.1 to Fig. 4.5 show the simulation circuit. Simulation is performed under the conditions and procedures in Table 4.2.

Table 4.2 Simulation Conditions and Procedures

1	V_{DD12}	12 V
2	V_{DD5}	5 V
3	V_{IN1}	0 V
4	V_{IN2}	0 V
5	Start of simulation	
6	V_{STBY}	0 to 5 V (1 ms standby mode)
7	V_{IN1}	0 to 5 V (2 ms normal operation)
8	V_{IN2}	0 to 5 V (9 ms quick-off operation)

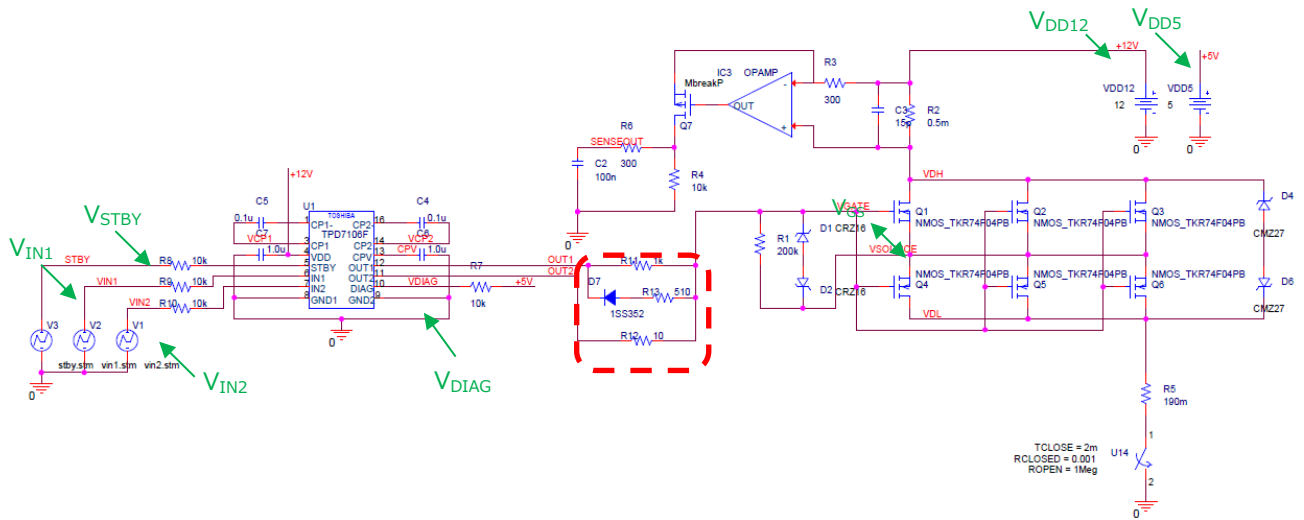


Fig. 4.1 Simulation Circuit (Normal Operation)

During the transition from standby mode to normal operation, V_{DIAG} is set to the L state (Fig. 4.2 ※1). This is because the charge pump voltage drop detection is activated. The charge pump voltage has reached the specified level and V_{DIAG} has returned to the H state. After 9 ms, $V_{IN2} = L$ to H input causes a quick off, and MOSFET (Q₁ to Q₃) is turned off briefly. This quick-off takes precedence over V_{IN1} . The switching time is described in the next section. Adjust the switching speed in the simulation-circuit R11, R13, D7 by Fig. 4.1.

 


Fig. 4.2 Simulation Waveform (Normal Operation)

4.2 Switching Waveform

Fig. 4.3 to Fig. 4.5 show the switching waveforms. The simulation waveform V_{DS} , V_{GS} are waveform of six MOSFET because MOSFET Q_1 to Q_6 are connected in parallel. The turn-on time can be adjusted by changing R11 in Fig. 4.1. On the other hand, turn-off is adjusted with R13. Fig. 4.5 shows the turn-off waveform in quick off mode.

 


Fig. 4.3 Simulation Waveform (Turn-On)

 


Fig. 4.4 Simulation Waveform (Turn-Off)

 


Fig. 4.5 Simulation Waveform (Quick Off)

4.3 Operation with the Power Supply Reverse Connection

The power supply reverse connection assumes reverse connection of the car battery.

The purpose of this application is to cut off the current generated when the power supply is connected in reverse. By using TPD7106F, MOSFET can be kept off and the current can be suppressed.

4.3.1 Simulation Verification

Check the operation of the power supply reverse connection by simulation. Fig. 4.6 shows the simulation circuit. Simulation is performed under the conditions and procedures in Table 4.3.

Table 4.3 Simulation Conditions and Procedures

1	V2	12 V
2	V _{DD5}	5 V
3	V _{IN1}	0 V
4	V _{IN2}	0 V
5	V _{STBY}	0 V
6	Start of simulation	
7	V2	12 V to -18 V (10 ms)

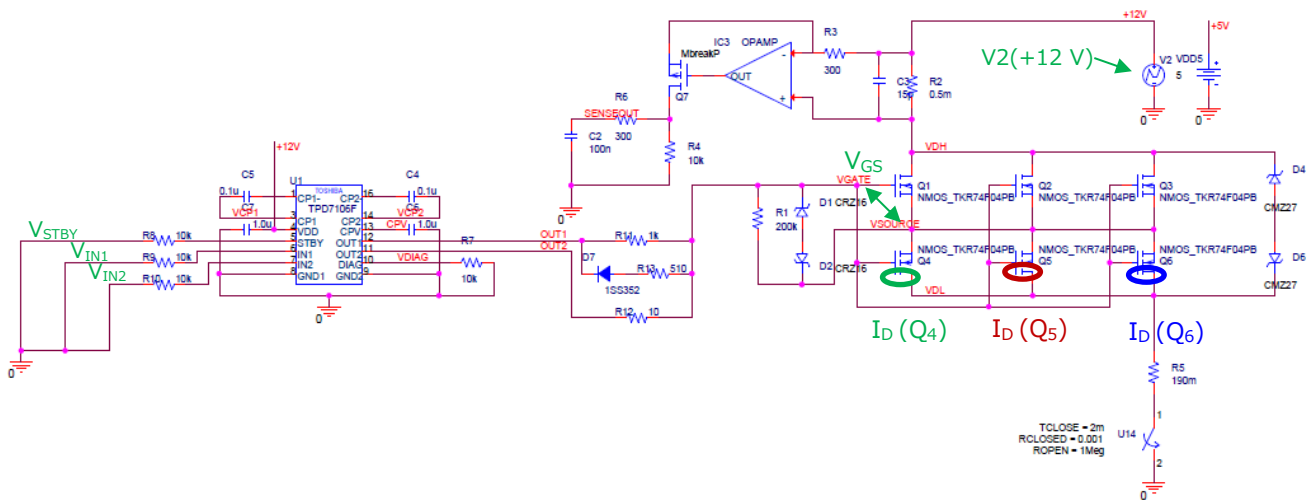


Fig. 4.6 Simulation Circuit (Power Supply Reverse Connection)

 


Fig. 4.7 Simulation Waveform (Power Supply Reverse Connection)

Fig. 4.7 shows the simulation waveform. A DC voltage source of +12 V is swept from 12 V to -18 V. The power supply reverse connection state is equivalent to the power supply voltage being at a negative potential. MOSFET Q_1 to Q_6 remains off as shown in V_{GS} waveform. Normally, a semiconductor device has a parasitic body diode. When the polarity of the power supply is reversed, current is generated from the GND. However, TPD7106F has a built-in switch that suppresses the current from the GND. When the power supply becomes negative, the switch is turned off. Therefore, the current output from OUT1, OUT2 pin are suppressed, and the external MOSFET can be kept off.

4.4 Charge Pump Capacitor Selection

Commonly used as non-isolated high-side gate drivers are the bootstrap method or the charge pump method. The bootstrap method requires periodic recharging of the bootstrapped capacitor, so operation close to 100 % duty is not possible. Therefore, the bootstrap method cannot be used for systems requiring high-duty operation, such as systems with low input voltages and high loads.

TPD7106F uses a charge pump system, so it can also be used in systems requiring high duty or DC energization. The current required for the charge pump circuitry can be obtained from V_{DD} terminal voltage, power supply voltage, and drive frequency of TPD7106F. Table 4.4 lists the conditions required for the charge pump circuit.

Table 4.4 Requirements for Charge Pump Circuits

MOSFET	TKR74F04PBx6
V_{DD} terminal voltage of TPD7106F	12 V
Power supply voltage	12 V
Drive Frequency (F_{sw})	100 Hz

 


Fig. 4.8 TKR74F04PB Dynamic Input/Output Characteristics

MOSFET charge is approximately 250 nC from V_{DD} pin voltage condition (12 V) and gate-source voltage (12 V) shown in TPD7106F in Table 4.2, as shown in Fig. 4.8. Six MOSFET are connected. In this circuit, MOSFET is driven at the maximum drive frequency (F_{sw}) = 100 Hz. Therefore, the output current of the charge pump circuit is calculated as follows.

$$I_{average} = Q_g \times F_{sw} = 1500 (nC) \times 100 (Hz) = 150 (\mu A)$$

Considering the effects of the pull-down resistor of 200 kΩ and the internal impedance of the IC, it is necessary to ensure that the output current has a sufficient margin. Capacitor values can be easily estimated using the simulation shown in Fig. 4.9.

4.4.1 Simulation Verification

Verify by simulation to confirm charge pump capacitor selection. Fig. 4.9 shows the simulation circuit. Simulation conditions and procedures in Table 4.5 are used for the execution.

Table 4.5 Simulation Conditions and Procedures

1	V _{DD12}	12 V
2	V _{DD5}	5 V
3	V _{IN1}	0 V
4	V _{IN2}	0 V
5	V _{STBY}	5 V
6	Start of simulation	
7	I ₁	0 to 100 mA (1ms step.)
8	Monitoring V _{CPV} Voltage	

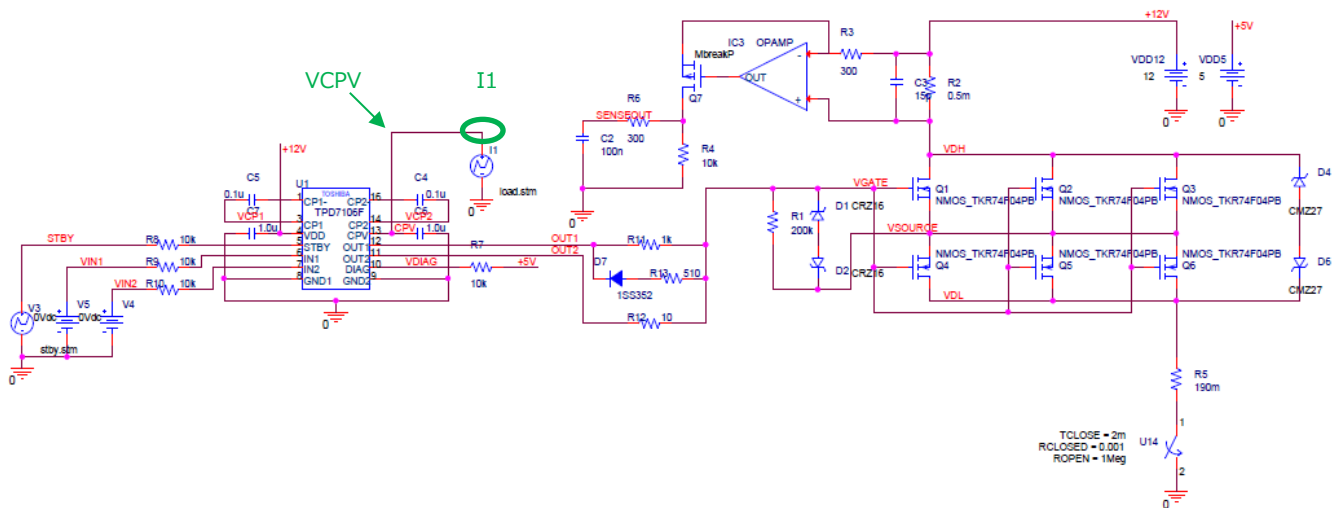


Fig. 4.9 Simulation Circuit (Charge Pump Capacitor Selection)

 


Fig. 4.10 Simulation Waveform (Charge Pump Capacitor Selection)

Fig. 4.11 shows the simulation results. Depending on the nature of MOSFET, V_{GS} typically requires at least 10 V. Therefore, the area where the CPV pin voltage is 22 V or less becomes an unstable area with bias application. The results also show that the output characteristics vary depending on the charge pump capacities $C4$ and $C5$. It is possible to estimate the selectable capacitor value from this result.

However, environmental temperatures, power supply voltage conditions, and characteristics of peripheral components such as diodes will also affect the product. Therefore, we recommend that you conduct actual measurements. 0.1 μF is selected for this circuit in consideration of sufficient margin for design. In addition, the capacitors in the charge pump circuitry of TPD7106F are supplied with voltages typically 12 V higher than V_{DD} , so care must be taken in withstanding voltage of the capacitors. In this circuit, the voltage at the VDH pin is boosted to 24 V for $V_{DD} = 12$ V. Therefore, a 50 V withstanding voltage product is selected.

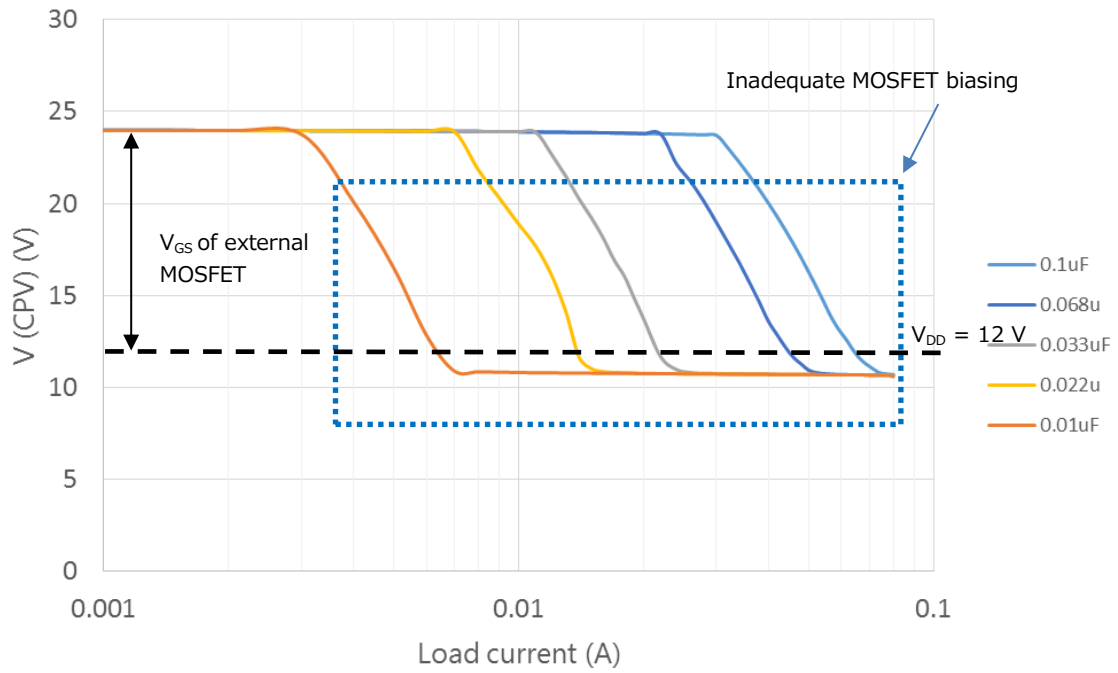


Fig. 4.11 Simulation Results (Charge Pump Capacitor Dependent)

The charge pump voltage V_{CPV} is reduced by increasing the load current from the normal operating condition. If the charge pump voltage returns to normal without stopping the output, it can be confirmed that the diagnostic output also returns to the normal state.

The power control must be operated with IN1, IN2.

 


Fig. 4.13 Simulation Waveform (Charge Pump Voltage Drop Detection)

5.2 TKR74F04PB

5.2.1 Overview

TKR74F04PB uses our latest low-voltage MOSFET processing U-MOSIX-H to achieve low on-resistance and high current ratings.

- AEC-Q101 qualified products for automotive applications
- Low on-resistance: $R_{DS(ON)} = 0.6 \text{ m}\Omega$ (Typ.) ($V_{GS} = 10 \text{ V}$)
- Low Leakage Current: $I_{DSS} = 10 \text{ }\mu\text{A}$ (Max.) ($V_{DS} = 40 \text{ V}$)
- Easy-to-handle enhancement type: $V_{th} = 2.0 \text{ to } 3.0 \text{ V}$ ($V_{DS} = 10 \text{ V}$, $I_D = 1 \text{ mA}$)
- Maximum current rating : $I_D = 250 \text{ A}$ (DC)
- Maximum voltage rating: $V_{DSS} = 40 \text{ V}$
- Small TO-220SM (W) Packaging

5.2.2 Appearance and Pin Assignment

 


Fig. 5.2 Appearance and Pin Assignment

Terms of Use

This terms of use is made between Toshiba Electronic Devices and Storage Corporation ("We") and customers who use documents and data that are consulted to design electronics applications on which our semiconductor devices are mounted ("this Reference Design"). Customers shall comply with this terms of use. Please note that it is assumed that customers agree to any and all this terms of use if customers download this Reference Design. We may, at its sole and exclusive discretion, change, alter, modify, add, and/or remove any part of this terms of use at any time without any prior notice. We may terminate this terms of use at any time and for any reason. Upon termination of this terms of use, customers shall destroy this Reference Design. In the event of any breach thereof by customers, customers shall destroy this Reference Design, and furnish us a written confirmation to prove such destruction.

1. Restrictions on usage

1. This Reference Design is provided solely as reference data for designing electronics applications. Customers shall not use this Reference Design for any other purpose, including without limitation, verification of reliability.
2. This Reference Design is for customer's own use and not for sale, lease or other transfer.
3. Customers shall not use this Reference Design for evaluation in high or low temperature, high humidity, or high electromagnetic environments.
4. This Reference Design shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.

2. Limitations

1. We reserve the right to make changes to this Reference Design without notice.
2. This Reference Design should be treated as a reference only. We are not responsible for any incorrect or incomplete data and information.
3. Semiconductor devices can malfunction or fail. When designing electronics applications by referring to this Reference Design, customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of semiconductor devices could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Customers must also refer to and comply with the latest versions of all relevant our information, including without limitation, specifications, data sheets and application notes for semiconductor devices, as well as the precautions and conditions set forth in the "Semiconductor Reliability Handbook".
4. When designing electronics applications by referring to this Reference Design, customers must evaluate the whole system adequately. Customers are solely responsible for all aspects of their own product design or applications. **WE ASSUME NO LIABILITY FOR CUSTOMERS' PRODUCT DESIGN OR APPLICATIONS.**
5. No responsibility is assumed by us for any infringement of patents or any other intellectual property rights of third parties that may result from the use of this Reference Design. No license to any intellectual property right is granted by this terms of use, whether express or implied, by estoppel or otherwise.
6. **THIS REFERENCE DESIGN IS PROVIDED "AS IS". WE (a) ASSUME NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (b) DISCLAIM ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO THIS REFERENCE DESIGN, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.**

3. Export Control

Customers shall not use or otherwise make available this Reference Design for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). This Reference Design may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export and re-export of this Reference Design are strictly prohibited except in compliance with all applicable export laws and regulations.

4. Governing Laws

This terms of use shall be governed and construed by laws of Japan.