

Application Circuit of Low Power Consumption Op-Amp TC75S102F

Design guide

RD229-DGUIDE-01

TOSHIBA ELECTRONIC DEVICES & STORAGE CORPORATION

Table of Contents

1. Introduction	3
2. Components Used	4
2.1. Operational Amplifier TC75S102F.....	4
2.2. Low Dropout Regulator (LDO) TCR3UF20A	5
2.3. Schottky Barrier Diode 1SS389.....	5
2.4. Zener Diode CEZ5V6	6
2.5. N-ch MOSFET SSM3K15AFU.....	6
3. Specifications and Block Diagram	7
3.1. Specifications	7
4. Circuit Design	8
4.1. Light Sensor Circuit (Design A1, A2, A3).....	8
4.1.1. Power Supply Circuit	8
4.1.2. I-V Converter	9
4.1.3. Astable Multivibrator Circuit	9
4.1.4. LED Drive Circuit	12
4.2. Pressure Sensor Circuit (Design B1, B2, B3)	13
4.2.1. Voltage Follower Circuit	13
4.3. Sound Sensor Circuit (Design C1, C2, C3)	15
4.3.1. Amplifier Circuit	15
4.3.2. DC Servo Circuit	15
4.4. Estimation of Operation Time Duration (Design A1).....	16
5. PCB Design	17
5.1. Component Layout Example	17

1. Introduction

This Design Guide describes the design of the Application Circuit of Low Power Consumption Op-Amp TC75S102F (hereafter referred to as this Reference Design).

This reference design uses low-power op amp(s) [TC75S102F](#) to achieve various functions. Schottky barrier diodes [1SS389](#) are used to prevent reverse current flow to the power supply terminal, a Zener diode [CEZ5V6](#) is used to protect from overvoltage, a MOSFET [SSM3K15AFU](#) is used for driving LED, and a low dropout regulator (LDO) [TCR3UF20A](#) is used as a power supply IC.

2. Components Used

2.1. Operational Amplifier TC75S102F


This reference design uses the op-amp [TC75S102F](#) manufactured by Toshiba Corporation. This op-amp is used for implementing various circuits in this reference design. TC75S102F is an CMOS op-amp featuring ultra-low current consumption. It is ideal for devices requiring long battery life, for example IoT devices.

The features of TC75S102F are as follows.

Features

- I/O full range (I/O Rail to Rail)
- Ultra-Low current consumption 0.27 μA (Typ.) @ $V_{\text{DD}} = 1.5 \text{ V}$
- Low input offset voltage 1.3 mV (Max.) @ $V_{\text{DD}} = 1.5 \text{ V}$
- Can be used with low power supply voltage $V_{\text{opr}} = 1.5 \text{ V}$ to 5.5 V

External View and Pinout (Top View)

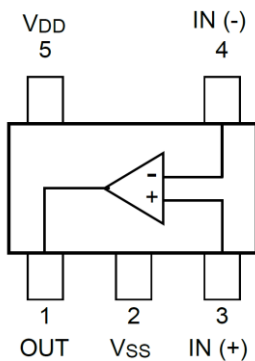

2.2. Low Dropout Regulator (LDO) TCR3UF20A

This reference design uses a low dropout regulator (LDO) [TCR3UF20A](#) in the power supply circuit. TCR3UF20A LDO features low current consumption. Thus, it is ideal for driving of IoT and mobile devices for long duration.


The features of TCR3UF20A are as follows.

Features

- Ultra low current consumption 0.34 μA (Typ.) @ $I_{\text{OUT}} = 0 \text{ mA}$
- Fast load transient response -51/+36 mV @0.8 V output, $I_{\text{OUT}} = 1 \text{ mA} \Leftrightarrow 50 \text{ mA}$
- High ripple rejection ratio = 70 dB (Typ.) @0.8 V Power
- Overcurrent protection, thermal shutdown, auto-discharge, and inrush current reduction circuit

External View and Pinout (Top View)

SMV(SOT-25)(SC-74A)

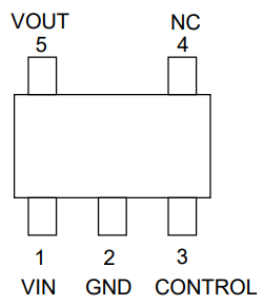

2.3. Schottky Barrier Diode 1SS389

This reference design uses a Schottky barrier diode [1SS389](#) in the power supply circuit. It features low V_F (forward voltage). The features of 1SS389 are as follows.

Features

- Compact two pin package (ESC, SOD-523: 1.6 x 0.8 x 0.6 mm)
- Low forward voltage $V_F = 0.23 \text{ V}$ (Typ.) @ $I_F = 5 \text{ mA}$

2.4. Zener Diode CEZ5V6

This reference design uses a Zener diode [CEZ5V6](#) in the power supply circuit. Suitable for overvoltage protection. The features of CEZ5V6 are as follows.

Features

- Compact two pin package (ESC, SOD-523:1.6 x 0.8 x 0.6 mm)
- Zener voltage $V_Z = 5.6 \text{ V}$ (Typ.) @ $I_Z = 5 \text{ mA}$

2.5. N-ch MOSFET SSM3K15AFU

This reference design uses a N-ch MOSFET [SSM3K15AFU](#) in LED drive circuit. Ideal for load switch applications. The features of SSM3K15AFU are as follows.

Features

- Compact package (USM, SOT-323:2.0 x 2.1 x 0.9 mm)
- Low on-resistance $R_{DS(ON)} = 3.6 \Omega$ (Max.) @ $V_{GS} = 4 \text{ V}$
- $R_{DS(ON)} = 6.0 \Omega$ (Max.) @ $V_{GS} = 2.5 \text{ V}$

3. Specifications and Block Diagram

3.1. Specifications

Table 3.1 lists the main specifications of various circuit designs in this reference design, and Fig. 3.1 shows a block diagram.

Table 3.1 Specifications of various Circuit Designs

Design Name	Onboard Sensor	Charging Method	Op-Amp 1 (OP1) Function	Op-Amp 2 (OP2) Function	Operation
A1	Light sensor (photodiode)	USB Type-C®	I-V converter	(not used)	LED turns on after sensor detection
A2				Astable multivibrator circuit	LED blinking interval changes according to the sensor value
A3					
B1	Pressure sensor (Polymer thick film)	USB Type-C®	Voltage follower circuit	(not used)	LED turns on after sensor detection
B2				Astable multivibrator circuit	LED blinking interval changes according to the sensor value
B3					
C1	Sound sensor (MEMS microphone)	USB Type-C®	Amplifier circuit	(not used)	LED turns on after sensor detection
C2				DC servo circuit (Offset cancel)	LED turns on after sensor detection (equipped with Op-Amp offset cancelling DC servo function)
C3					

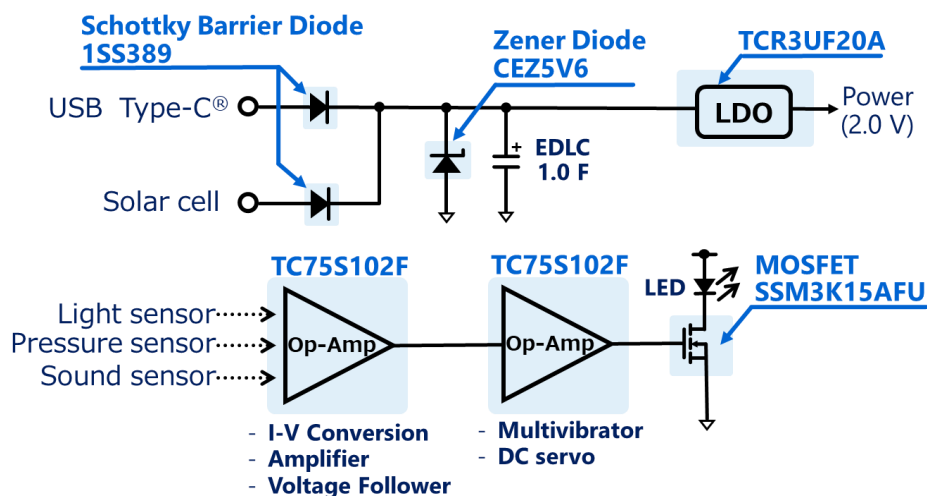


Fig. 3.1 Block Diagram of Low Power Op-Amp TC75S102F Application Circuit

4. Circuit Design

4.1. Light Sensor Circuit (Design A1, A2, A3)

Fig. 4.1 shows the light sensor circuit.

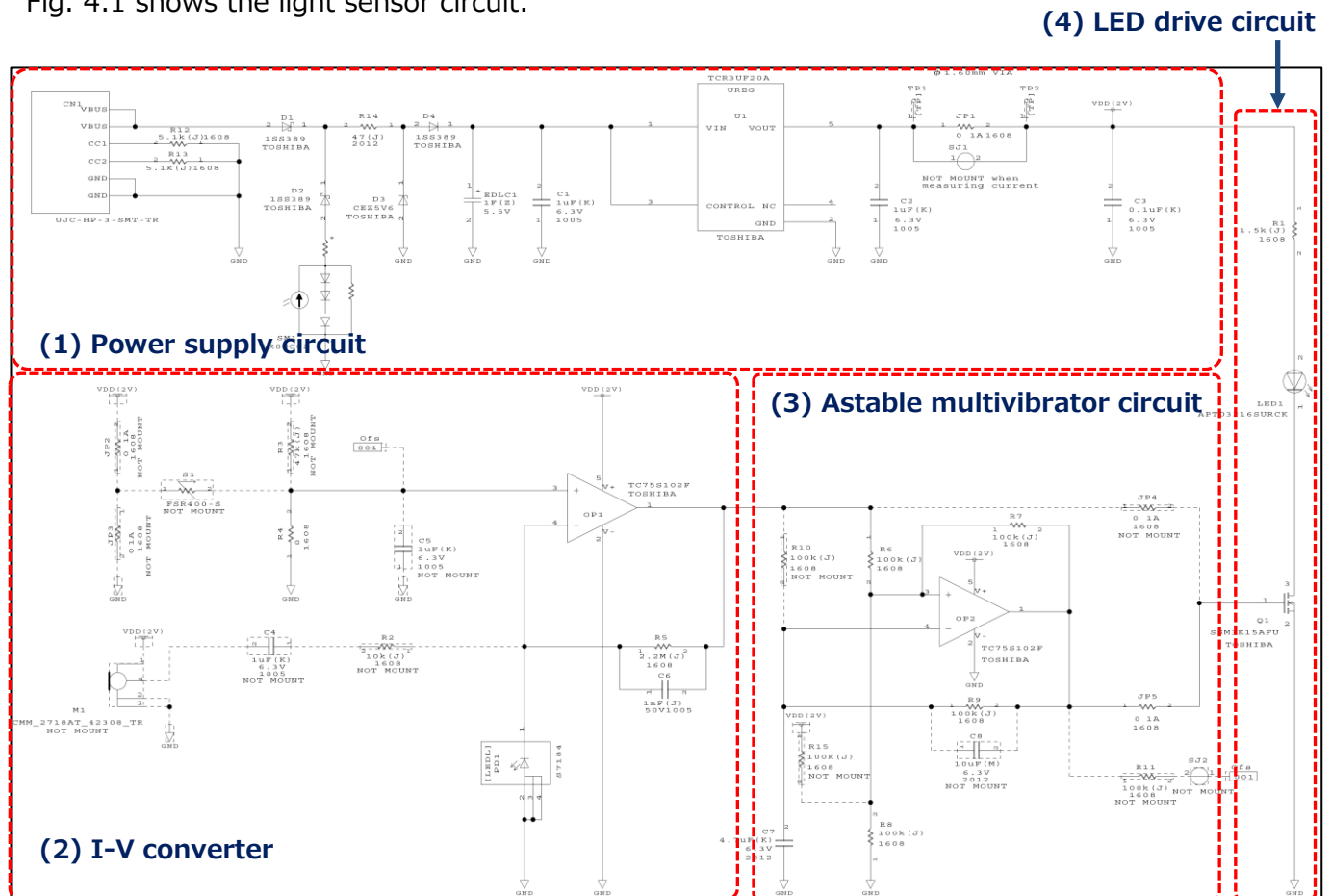


Fig. 4.1 Light Sensor Circuit (for Design A3)

4.1.1. Power Supply Circuit

The electric double layer capacitor (EDLC1) can be charged by either connecting the USB charger to USB Type-C® connector (CN1), or by irradiating the solar cell (SM1) with sunlight. The USB charger can be disconnected after the electric double layer capacitor is charged and now the board can be used standalone. The LDO, TCR3UF20A (U1) takes input from the electric double layer capacitor and produces a stable 2.0V output which is used as power supply on this board. Solar cell module is mounted on A3, B3 and C3 designs.

In order to supply 5.0 V power from the USB Type-C® connector (CN1), the CC1 and CC2 pins of CN1 detect the receptacle on the voltage sink side when an external plug is inserted based on the USB Type-C® configuration, thus these pins are pulled down with 5.1 kΩ. This board can be charged from either the solar cell (SM1) or USB Type-C® connector (CN1), so it is equipped with Schottky barrier diodes 1SS389 (D1, D2) to configure ORing circuit to prevent reverse current flow. Resistor 47 Ω (R14), Zener Diode CEZ5V6 (D3), and Schottky Barrier Diode 1SS389 (D4) are used to limit the inrush current caused by pre-charging when EDLC1 charge is zero. They also prevent the application of voltage more than the rated voltage of 5.5 V to the electric double layer capacitor (EDLC1).

The voltage is limited by the zener diode D3 which is present after ORing circuit consisting of D1 and D2. The forward voltage drop of the Schottky barrier diode 1SS389 (D4) is approximately 0.3 V, thus the electric double layer capacitor is protected from overvoltage.

Resistor 47 Ω (R14) limits the current going to the electric double layer capacitor. When the charge voltage is 5.0 V and the charge of the electric double layer capacitor is zero, approximately 0.3 V voltage drops at 1SS389 (D1) and approximately 0.3 V voltage drops at 1SS389 (D4), so that approximately 4.4 V is applied to the electric double layer capacitor (EDLC1). At this time, the inrush current caused by pre-charging is limited to approximately 4.4 V/47 $\Omega \approx 94$ mA or less.

4.1.2. I-V Converter

This unit is equipped with a light-sensor (photodiode, PD1). The light-sensor output current I_L is converted to the voltage by I-V (current-voltage) converter consisting of an op-amp OP1, a resistor of 2.2 M Ω (R5), and a capacitor of 1 nF (C6). Output voltage V_{OUT} of OP1 is as follows:

$$V_{OUT} = -I_L \times 2.2 \times 10^6 (V)$$

A low-pass filter (LPF) with a cutoff frequency f_z is also used to prevent oscillation and eliminate unwanted high-frequency components. The cutoff frequency f_z is as follows:

$$f_z = \frac{1}{2 \times \pi \times C6 \times R5} = \frac{1}{2 \times \pi \times 1 \times 10^{-9} \times 2.2 \times 10^6} \approx 72 (Hz)$$

In design A1, the output voltage V_{OUT} (0 V to 2.0 V) of I-V converter OP1 is used to control the gate-pin of the subsequent MOSFET (Q1) to turn on the LED. Designs A2 and A3 consist of another op-amp OP2 which is used as an astable multivibrator for changing the LED blinking interval.

4.1.3. Astable Multivibrator Circuit

Designs A2, A3, B2 and B3 are equipped with an astable multivibrator circuit.

The astable multivibrator circuit consists of a hysteresis comparator circuit configured using R6, R7 and R8. When the reference voltage of the non-inverting input pin of the op-amp OP2 is V_+ and the voltage of the inverting input pin is V_- , then immediately after power-on if $V_+ > V_-$ the output voltage V_{Output} of the op-amp becomes High. At this time, the capacitor C7 of 4.7 μ F is charged by V_{Output} voltage via the feedback resistor R9. When C7 is charged and $V_- > V_+$, OP2's output voltage V_{Output} becomes Low and C7 starts discharging. Therefore, this astable multivibrator circuit repeatedly charges and discharges the capacitor C7.

The threshold voltage of the inverting input pin (V-) of OP2 constituting the hysteresis comparator circuit can be expressed as shown below.

$$a = \frac{1}{\frac{1}{R6} + \frac{1}{R7} + \frac{1}{R8}}$$

$$V_{thH} = \frac{a}{R6} \times V_{Input} + \frac{a}{R7} \times V_{OH}$$

$$V_{thL} = \frac{a}{R6} \times V_{Input} + \frac{a}{R7} \times V_{OL}$$

Where V_{thH} is the threshold for High level, V_{thL} is the threshold for Low level, V_{OH} is the output voltage for High level, and V_{OL} is the output voltage for Low level of the op-amp OP2. If TC75S102F is powered by 2.0 V, $V_{OH}=1.9$ V (Min.), $V_{OL} = 0.1$ V (Max.).

When the V_{Input} line is used as the input of astable multivibrator,

•When V_{Input} is 2.0 V

$$a = \frac{1}{\frac{1}{100 \times 10^3} + \frac{1}{100 \times 10^3} + \frac{1}{100 \times 10^3}} \approx 33.3 \times 10^3 (\Omega)$$

$$V_{thH} = \frac{33.3 \times 10^3}{100 \times 10^3} \times 2 + \frac{33.3 \times 10^3}{100 \times 10^3} \times 1.9 \approx 1.3(V)$$

$$V_{thL} = \frac{33.3 \times 10^3}{100 \times 10^3} \times 2 + \frac{33.3 \times 10^3}{100 \times 10^3} \times 0.1 \approx 0.7(V)$$

As a result, the capacitor C7 connected to V-pin is repeatedly charged and discharged between 1.3 V and 0.7 V.

Since the power supply voltage of the op-amp OP2 is 2.0 V, and if the discharge starting time is t_1 , and the discharge ending time is t_2 , then

$$V_{thH} = 1.3 = 2.0 \times e^{\frac{-t_1}{C7 \times R9}}$$

$$V_{thL} = 0.7 = 2.0 \times e^{\frac{-t_2}{C7 \times R9}}$$

And the discharge time,

$$t_2 - t_1 = -C7 \times R9 \times \left(\ln \frac{0.7}{2.0} - \ln \frac{1.3}{2.0} \right)$$

$$= -4.7 \times 10^{-6} \times 100 \times 10^3 \times \left(\ln \frac{0.7}{2.0} - \ln \frac{1.3}{2.0} \right)$$

$$\approx 0.29(s)$$

Since the charge time is same as the discharge time, so when $V_{\text{Input}}=2.0$ V, the period T and the frequency f are as follows.

$$T = 0.29 \times 2 \approx 0.58(s)$$

$$f = \frac{1}{T} \approx 1.72(\text{Hz})$$

•When V_{Input} is 0 V

$$V_{thH} = \frac{33.3 \times 10^3}{100 \times 10^3} \times 0 + \frac{33.3 \times 10^3}{100 \times 10^3} \times 1.9 \approx 0.633(V)$$

$$V_{thL} = \frac{33.3 \times 10^3}{100 \times 10^3} \times 0 + \frac{33.3 \times 10^3}{100 \times 10^3} \times 0.1 \approx 0.033(V)$$

As a result, the capacitor C7 connected to V-pin is repeatedly charged and discharged between 0.63 V and 0.03 V.

Since the power supply of the op-amp OP2 is 2.0 V, and if the discharge starting time is t1, and the discharge ending time is t2,

$$V_{thH} = 0.633 = 2.0 \times e^{\frac{-t1}{C7 \times R9}}$$

$$V_{thL} = 0.033 = 2.0 \times e^{\frac{-t2}{C7 \times R9}}$$

And the discharge time,

$$\begin{aligned} t2 - t1 &= -C7 \times R9 \times \left(\ln \frac{0.033}{2.0} - \ln \frac{0.633}{2.0} \right) \\ &= -4.7 \times 10^{-6} \times 100 \times 10^3 \left(\ln \frac{0.033}{2.0} - \ln \frac{0.633}{2.0} \right) \\ &\approx 1.39(s) \end{aligned}$$

Since the charge time is same as the discharge time the period T and the frequency f during $V_{\text{Input}} = 0$ V are as follows.

$$T = 1.39 \times 2 \approx 2.78(s)$$

$$f = \frac{1}{T} \approx 0.36(\text{Hz})$$

Therefore, in the circuit consisting of OP1, OP2, the photocurrent I_L of the photodiode PD1 is converted from current to voltage by the op-amp OP1, and then this output voltage (0 V to 2.0 V) is used by OP2 to change the blinking frequency of LED (LED1) within the range of approximately 0.36 Hz to 1.72 Hz . The actual blinking period may not match with the calculated value due to variations in the characteristics of components, etc.

4.1.4. LED Drive Circuit

LED drive circuit consists of a LED (LED1), a current limiting resistor R1, and a low-side switch MOSFET (Q1) to control the circuit. This LED drive circuit is used in all designs in this reference design. The output voltage of LDO (U1) is 2.0 V, the forward voltage V_F of LED is 1.85 V, the drain-source on resistance ($R_{DS(ON)}$) of MOSFET when $V_{GS} = 2.0$ V is 6 Ω , so in order to keep LED forward current $I_F = 100 \mu A$, the value of current limiting resistor R1 is selected to be 1.5 k Ω . Thus I_F can be calculated as shown below.

$$I_F = \frac{(2.0 - 1.85)}{(1.5 \times 10^3 + 6)} \approx 100(\mu A)$$

LED is turned on and driven by applying a High voltage to the gate pin of MOSFET (Q1).

4.2. Pressure Sensor Circuit (Design B1, B2, B3)

Fig. 4.2 shows the pressure sensor circuit.

(4) LED drive circuit

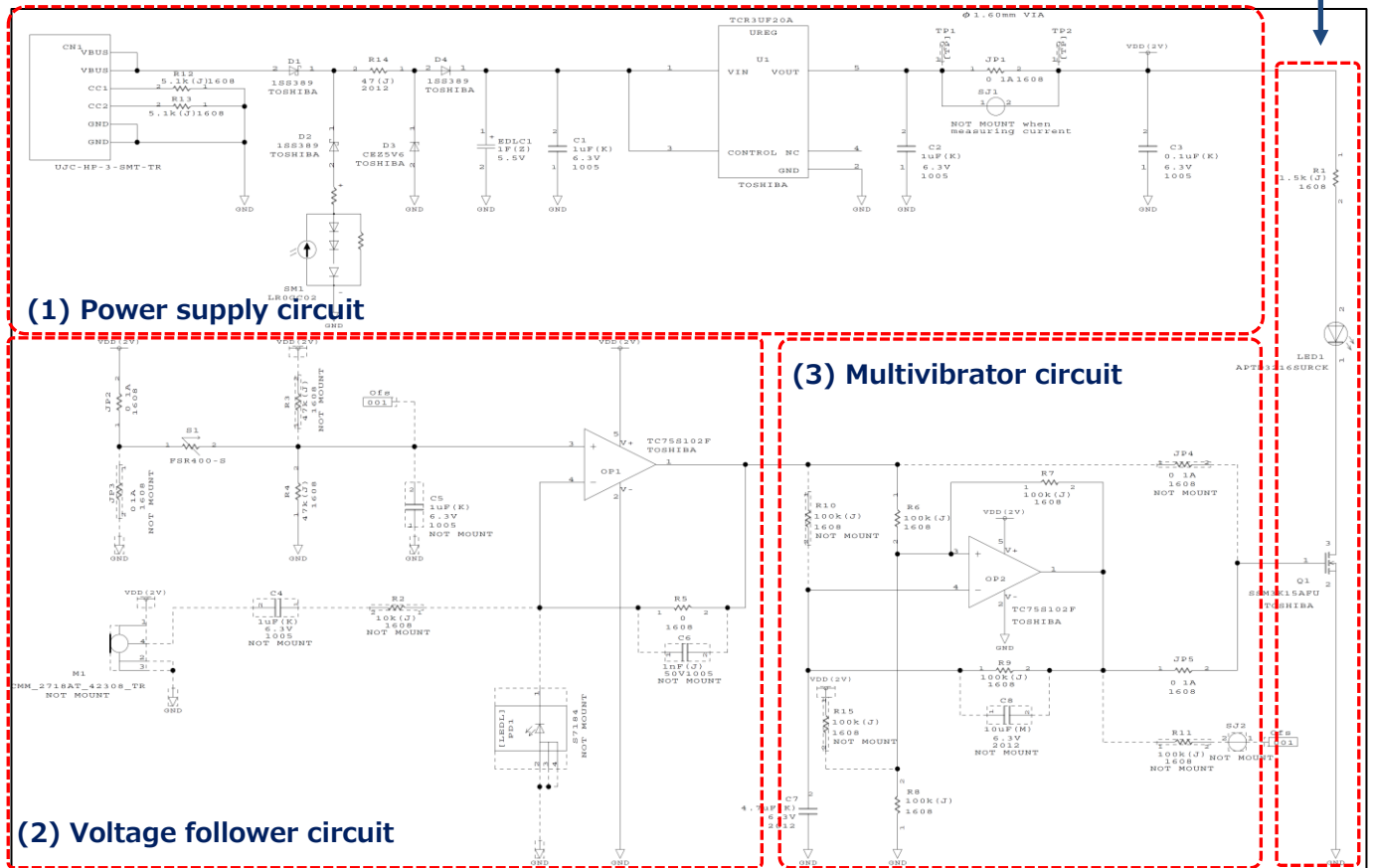


Fig. 4.2 Pressure Sensor Circuit (for Design B3)

4.2.1. Voltage Follower Circuit

The pressure sensor circuit uses FSR400-S (Interlink Electronics) as a pressure sensor. When no pressure is applied this sensor has high resistance (more than 100 kΩ), however when the pressure of more than 20 g is applied, it's resistance decreases gradually as the applied pressure increases (Fig. 4.3).

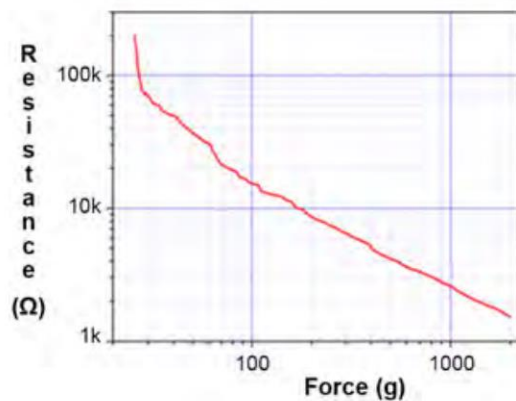


Fig. 4.3 FSR400 Resistance-Pressure Characteristic (quoted from Interlink's FSR400 datasheet)

A voltage follower circuit is configured using op-amp OP1 and a 0 Ω resistor (R5). A voltage obtained by dividing the power supply voltage 2.0 V by FSR400 and 47 k Ω (R4) is applied to the non-inverting input pin. This causes the output voltage of OP1 to be same as the voltage generated by applying pressure on the sensor.

4.3. Sound Sensor Circuit (Design C1, C2, C3)

Fig. 4.4 shows the sound sensor circuit.

(4) LED drive circuit

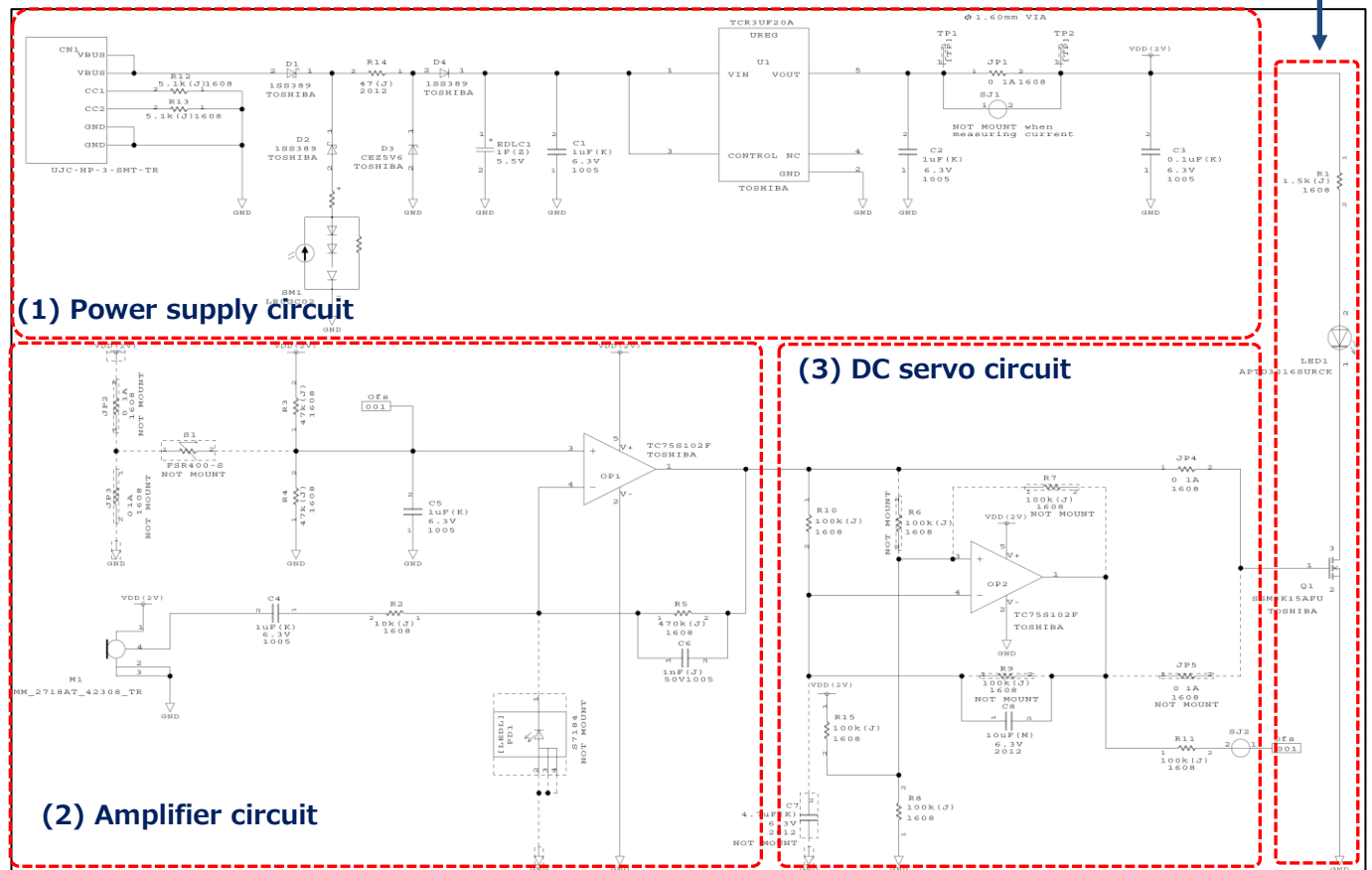


Fig. 4.4 Sound Sensor Circuit (for Design C3)

4.3.1. Amplifier Circuit

It is equipped with a MEMS microphone CMM-2718AT-42308-TR (CUI DEVICES) as a sound sensor. The op-amp OP1 with resistors 10 kΩ (R2) and 470 Ω (R5) acts as an inverting amplifier with an gain of -47 (gain $A_v = -R_5/R_2 = -470k/10k = 33$ dB). A 1.0 V bias obtained by dividing the supply voltage 2.0 V by the resistors of 47 kΩ (R3) and 47 kΩ (R4) is applied to the non-inverting input pin of the op-amp. Therefore, output of the op-amp is the voltage obtained by amplifying the output of MEMS microphone by 33 dB around 1.0 V bias.

4.3.2. DC Servo Circuit

In the designs C2 and C3, after OP1, an op-amp OP2 is also connected. Op-amp OP2 is configured as a DC servo circuit that inverts only DC offset component of the output and then feeds back to the non-inverting input pin of OP1. And because this circuit cancels DC input offset voltage of the op-amp OP1, it becomes a highly accurate amplifier circuit.

Calculation of 3 dB cutoff frequency f_{CL} of the DC servo circuit is as follows.

$$f_{CL} = \frac{1}{(2 \times \pi \times C8 \times R10)} \times \frac{R4}{R4 + R11} \times \frac{R2 + R5}{R2}$$

$$= \frac{1}{2 \times \pi \times 10 \times 10^{-6} \times 100 \times 10^3} \times \frac{47 \times 10^3}{47 \times 10^3 + 100 \times 10^3} \times \frac{4.7 \times 10^3 + 470 \times 10^3}{4.7 \times 10^3}$$

$$= 5.14(\text{Hz})$$

This circuit feeds back frequencies below f_{CL} to the inverting amplifier circuit.

In addition, OP1 and OP2 are operated with a single power supply of 2.0 V, so the AC signal output of the MEMS microphone is biased with 1.0 V at OP1 as described above. In the DC servo circuit, the power supply voltage is divided by R8 and R15 at the non-inverting input pin of OP2, creating a 1.0 V bias, and then the DC component of OP2 output is fed back into OP1.

4.4. Estimation of Operation Time Duration (Design A1)

The operation time duration of this circuit is estimated by referring to the design A1. Let's assume that the electric double layer capacitor voltage is 5.0 V, the capacitance value is 1.0 F, and the output LED turns on for a total of 5 seconds in every 1 hour according to the sensor input.

The current consumption of the main elements of the circuit,

Current draw of op-amp TC75S102F (OP1) approx. 0.27 μA

Current draw of LDO TCR3UF20A (U1) approx. 0.4 μA

Current draw of LED (LED1) approx. 100 μA (when turned on 100 %)

Since LED has a forward current of 100 μA and it turns on for a total of 5 seconds in every 1 hour, the average consumption current of LED is 0.139 μA , so the average consumption current I of the main elements of the Circuit becomes:

$$I = 0.27 + 0.4 + 0.139 \approx 0.809(\mu\text{A})$$

When the operation starting voltage of the electric double layer capacitor is 5.0 V and the operation ending voltage is 2.0 V,

$$Q = C \times V = \int Idt = I \times t$$

Thus,

$$Q = 1.0 \times (5.0 - 2.0) = 0.809(\mu\text{A}) \times t$$

$$t = \frac{1.0 \times 3.0}{0.809 \times 10^{-6}} \approx 3.71 \times 10^6(\text{s}) \approx 42.9(\text{days})$$

Therefore, according to the calculation this circuit can operate for about 42.9 days using the electric charge stored in the electric double layer capacitor.

5. PCB Design

5.1. Component Layout Example

Fig. 5.1 and Fig. 5.2 show examples of component arrangement.

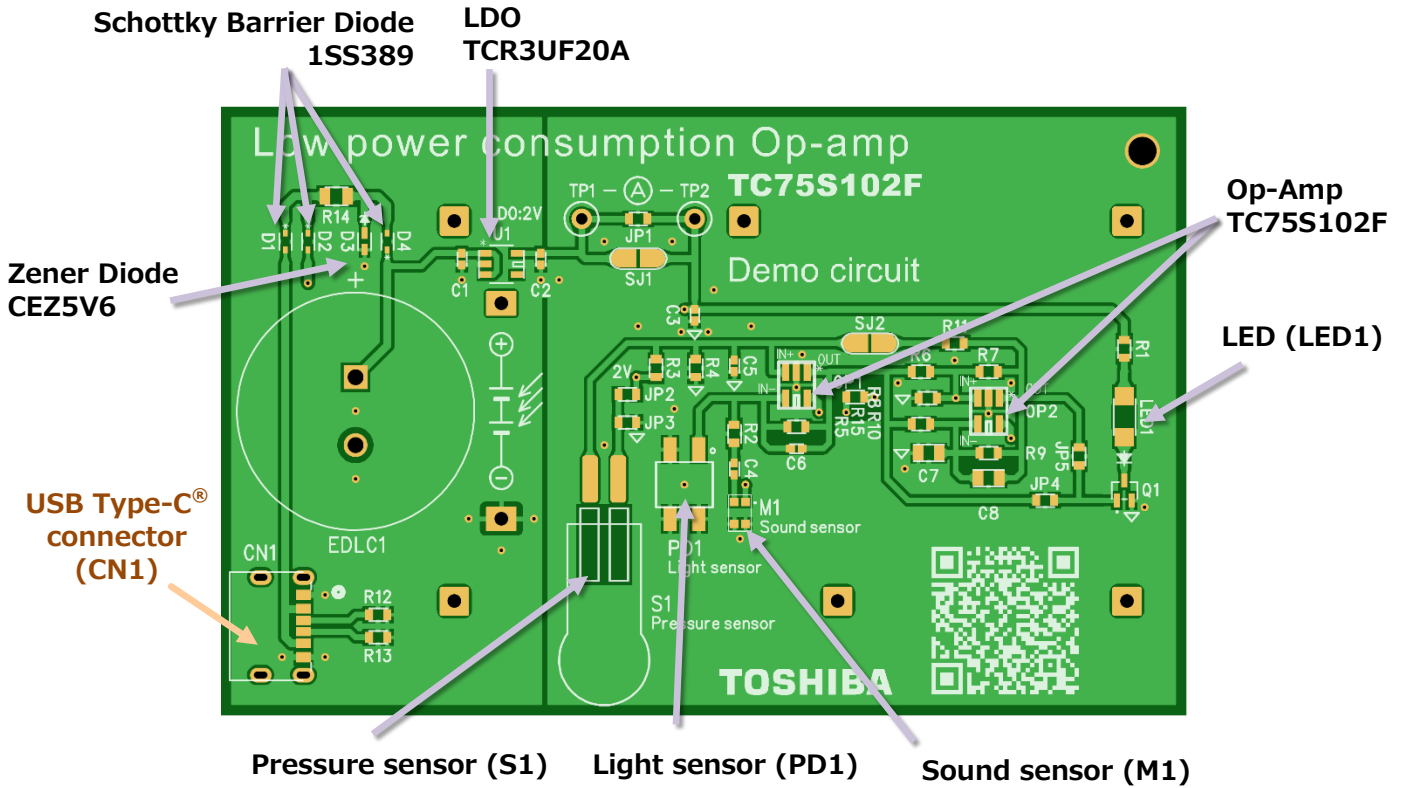


Fig. 5.1 PCB Component Layout (Front Side)

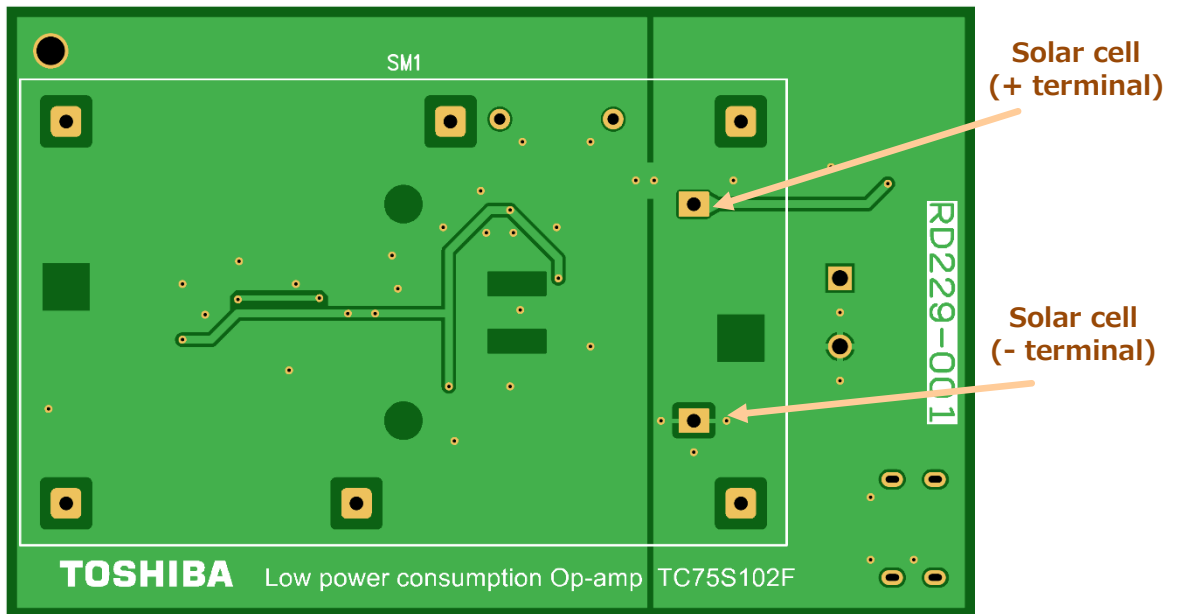


Fig. 5.2 PCB Component Layout (Back Side)

- ※ USB Type-C[®], USB-C[®] is a registered trademark of USB Implementers Forum.
- ※ Company names, product names, and service names may be trademarks of their respective companies.

Terms of Use

This terms of use is made between Toshiba Electronic Devices and Storage Corporation ("We") and customers who use documents and data that are consulted to design electronics applications on which our semiconductor devices are mounted ("this Reference Design"). Customers shall comply with this terms of use. Please note that it is assumed that customers agree to any and all this terms of use if customers download this Reference Design. We may, at its sole and exclusive discretion, change, alter, modify, add, and/or remove any part of this terms of use at any time without any prior notice. We may terminate this terms of use at any time and for any reason. Upon termination of this terms of use, customers shall destroy this Reference Design. In the event of any breach thereof by customers, customers shall destroy this Reference Design, and furnish us a written confirmation to prove such destruction.

1. Restrictions on usage

1. This Reference Design is provided solely as reference data for designing electronics applications. Customers shall not use this Reference Design for any other purpose, including without limitation, verification of reliability.
2. This Reference Design is for customer's own use and not for sale, lease or other transfer.
3. Customers shall not use this Reference Design for evaluation in high or low temperature, high humidity, or high electromagnetic environments.
4. This Reference Design shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.

2. Limitations

1. We reserve the right to make changes to this Reference Design without notice.
2. This Reference Design should be treated as a reference only. We are not responsible for any incorrect or incomplete data and information.
3. Semiconductor devices can malfunction or fail. When designing electronics applications by referring to this Reference Design, customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of semiconductor devices could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Customers must also refer to and comply with the latest versions of all relevant our information, including without limitation, specifications, data sheets and application notes for semiconductor devices, as well as the precautions and conditions set forth in the "Semiconductor Reliability Handbook".
4. When designing electronics applications by referring to this Reference Design, customers must evaluate the whole system adequately. Customers are solely responsible for all aspects of their own product design or applications. WE ASSUME NO LIABILITY FOR CUSTOMERS' PRODUCT DESIGN OR APPLICATIONS.
5. No responsibility is assumed by us for any infringement of patents or any other intellectual property rights of third parties that may result from the use of this Reference Design. No license to any intellectual property right is granted by this terms of use, whether express or implied, by estoppel or otherwise.
6. THIS REFERENCE DESIGN IS PROVIDED "AS IS". WE (a) ASSUME NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (b) DISCLAIM ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO THIS REFERENCE DESIGN, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.

3. Export Control

Customers shall not use or otherwise make available this Reference Design for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). This Reference Design may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export and re-export of this Reference Design are strictly prohibited except in compliance with all applicable export laws and regulations.

4. Governing Laws

This terms of use shall be governed and construed by laws of Japan.