

**Automotive Buck-Boost DC-DC Converter  
for USB PD**

**Reference Guide**

**RD227-RGUIDE-01**

---

**TOSHIBA ELECTRONIC DEVICES & STORAGE CORPORATION**

## Table of Contents

<b>1. Introduction</b>	<b>3</b>
<b>2. Specifications</b>	<b>4</b>
2.1. Circuit Block Diagram	4
2.2. Appearance and Component Arrangement	5
<b>3. Schematic, Bill of Material, and PCB Pattern</b>	<b>9</b>
3.1. Schematic	9
3.2. Bill of Material	9
3.3. PCB Pattern	9
<b>4. Operation</b>	<b>14</b>
4.1. Name and Function of Components	14
4.1.1. Power Input Connector (CN101, CN201)	14
4.1.2. Power Output Connector (CN103, CN203)	14
4.1.3. Host Connector (CN102, CN202)	15
4.2. Operation Checking Procedure	16
4.2.1. Preparation	16
4.2.2. Operation Procedure	16
4.2.3. Operation During Error Detection	16
4.3. Precautions (To Prevent Electric Shock, Burn Injury, etc.)	16

## 1. Introduction

This Reference Guide (hereafter referred to as this Guide) describes the specifications and operation procedures of the Automotive Buck-Boost DC-DC Converter for USB PD (hereafter referred to as this Power Supply).

Recently, USB Power Delivery (hereafter referred to as USB PD) power supply (for recharging) has become popular for smart phones, tablets, laptop PC, etc. In response to the growing demand for power supply not only indoors but also inside vehicles, USB Type-C<sup>®</sup> connectors have been installed, and power supply by USB PD has become popular. Since the output voltage is determined by the power receiving device in USB PD, DC-DC converter for automotive USB PD requires a buck-boost converter to generate the output voltage from the vehicle battery voltage. This power supply is an H-bridge type buck-boost DC-DC converter with four switching elements. By using our small-package automotive MOSFETs as switching devices, we have realized an automotive buck-boost DC-DC converter that is highly efficient and has a small board mounting area.

We have prepared two types of automotive MOSFETs which are used in the H-bridge buck-boost DC-DC converter section of this power supply. Option 1 uses a [XPN7R104NC](#), and Option 2 uses a [SSM6K804R](#). In addition, our automotive MOSFET [XPN3R804NC](#) is used as a switching device in reverse-connection protection circuit and shield short-circuit protection circuit.

## 2. Specifications


Table 2.1 lists the main specifications of this power supply.

**Table 2.1 Specifications of Automotive Buck-Boost DC-DC Converter for USB PD**

Item	Specifications
Power Topology	H-bridge buck-boost circuit
Input Voltage	DC 5 to 18 V, 12.6 V (Typ.)
Output Voltage	DC 3.3 to 21 V
Rated Power	60 W (Max.)
Switching Frequency	400 kHz (Typ.)
Protective Function	Reverse connection protection Overvoltage, overcurrent, and shield short-circuit protection (controlled by the controller)
Cooling System	Convection cooling
Board Size	90 x 40 mm
Substrate Layer Configuration	Four-layer through-hole (surface layer: 70 μm, inner layer: 70 μm)

### 2.1. Circuit Block Diagram


Fig. 2.1 shows the block diagram of this power supply.

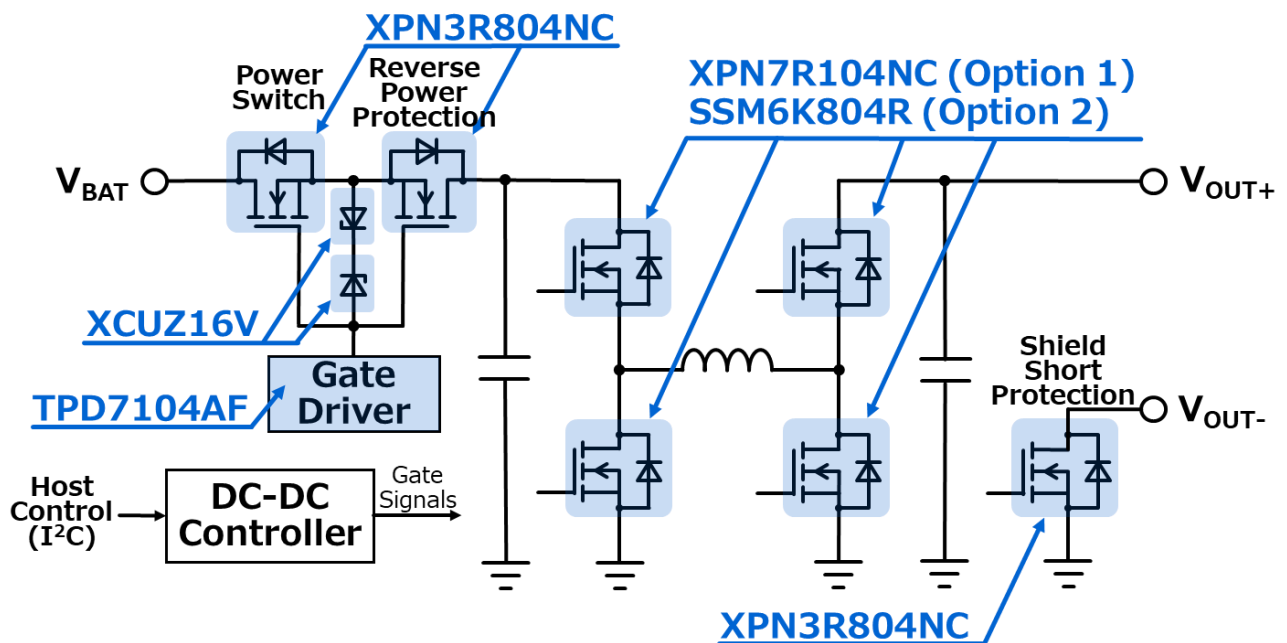


**Fig. 2.1 Block Diagram of Automotive Buck-Boost DC-DC Converter for USB PD**

### 2.2. Appearance and Component Arrangement

Fig. 2.2 and Fig. 2.3 show the appearance of this power supply, and Figs. 2.4 and 2.5 show the layout of main components.

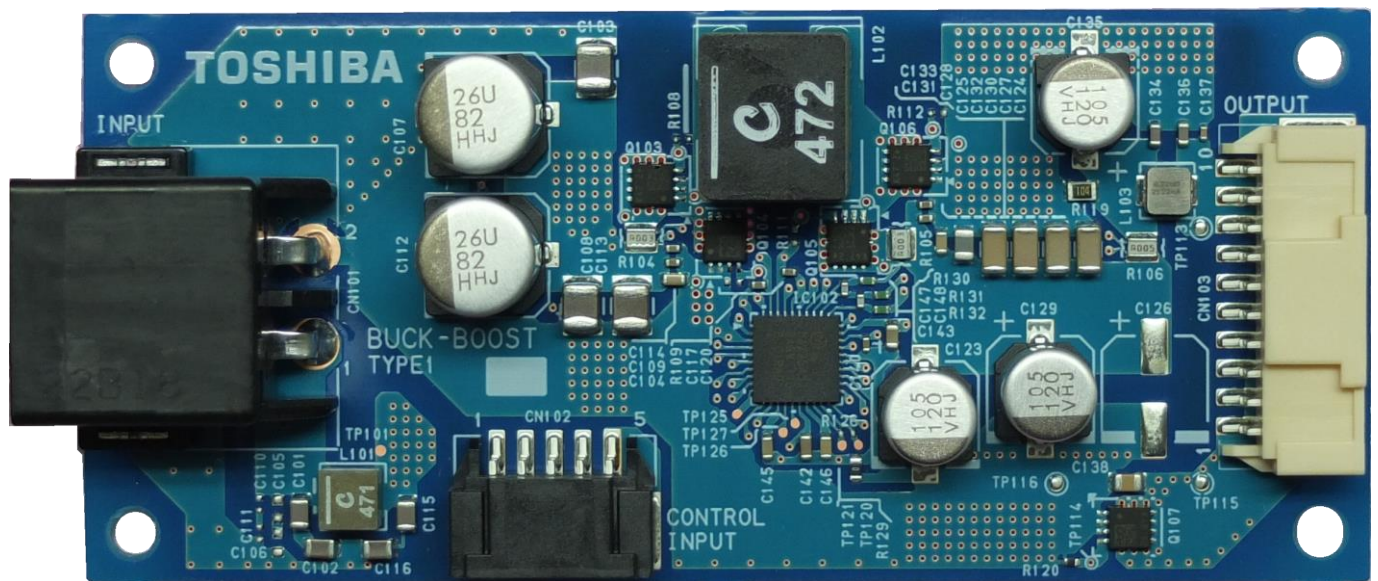


<Front>

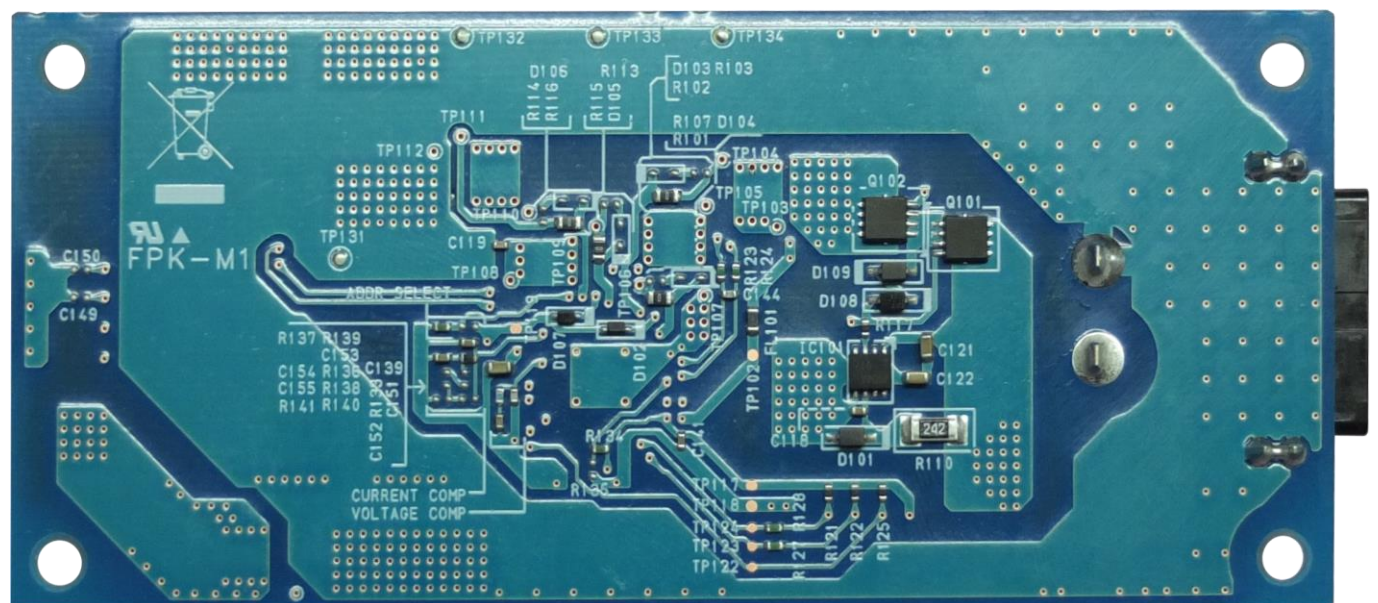


<Back>

**Fig. 2.2 Board Appearance (Option 1)**

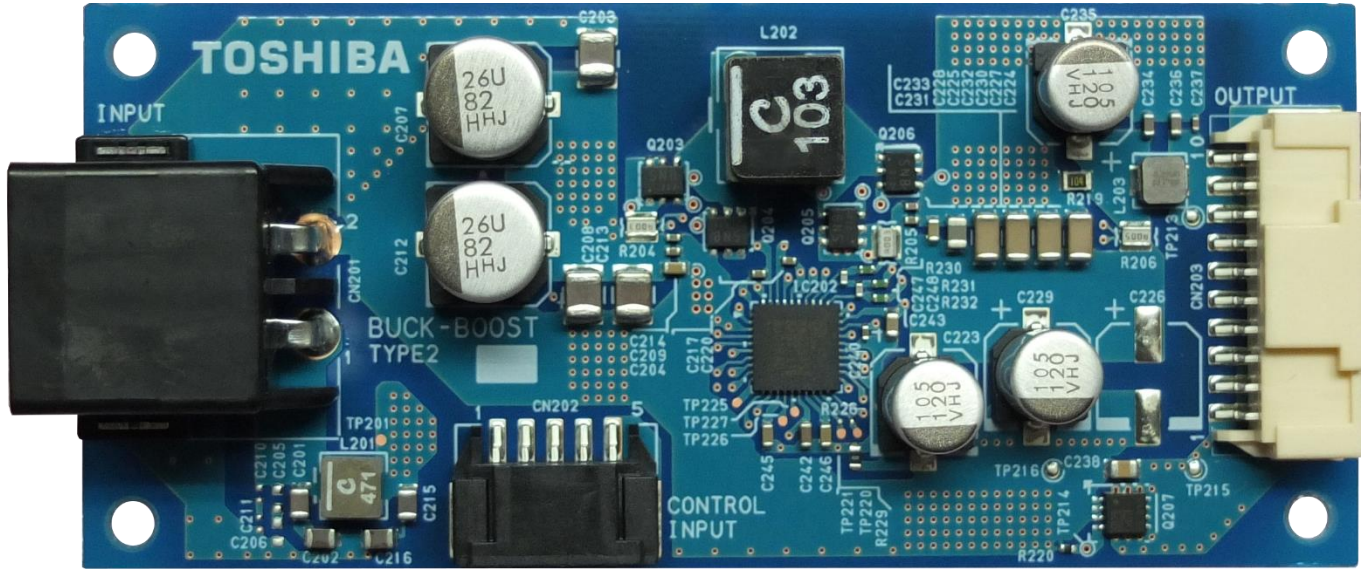


<Front>

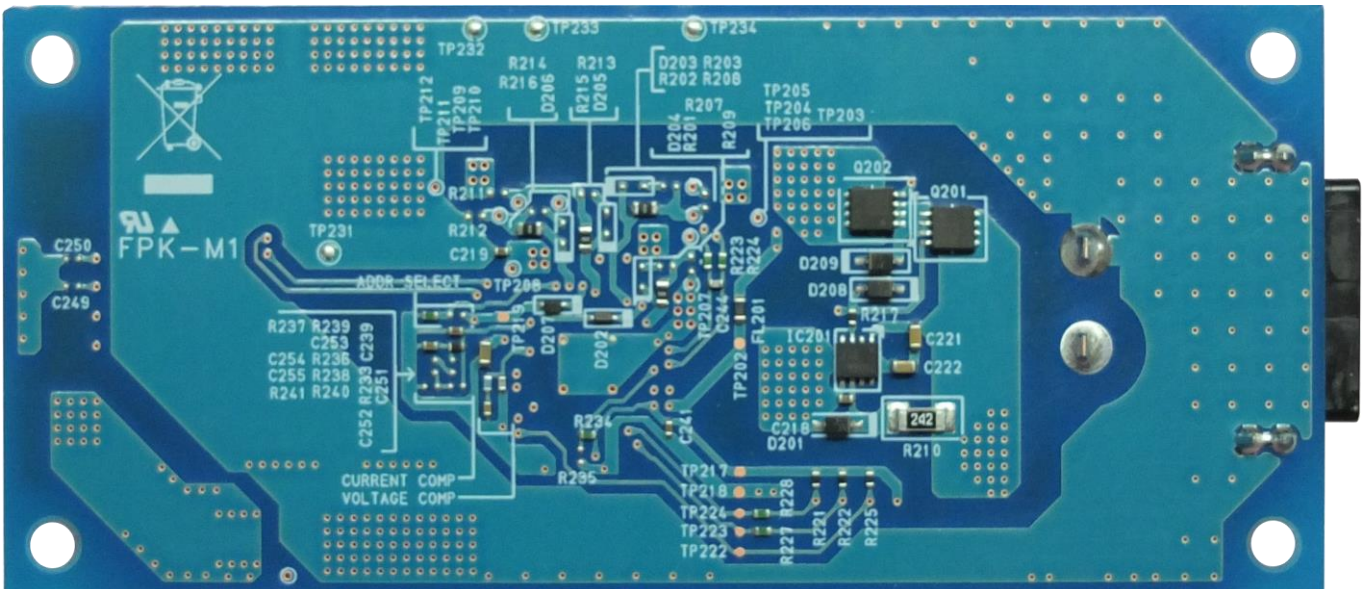


<Back>

Fig. 2.3 Board Appearance (Option 2)

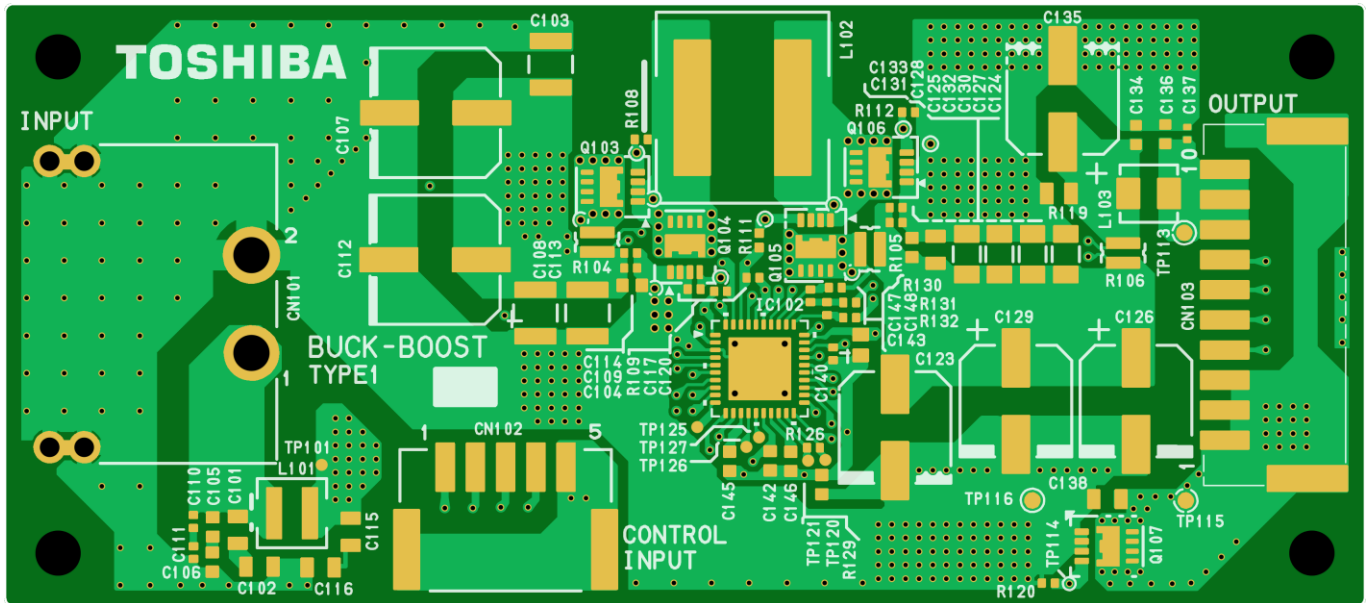

<Front>

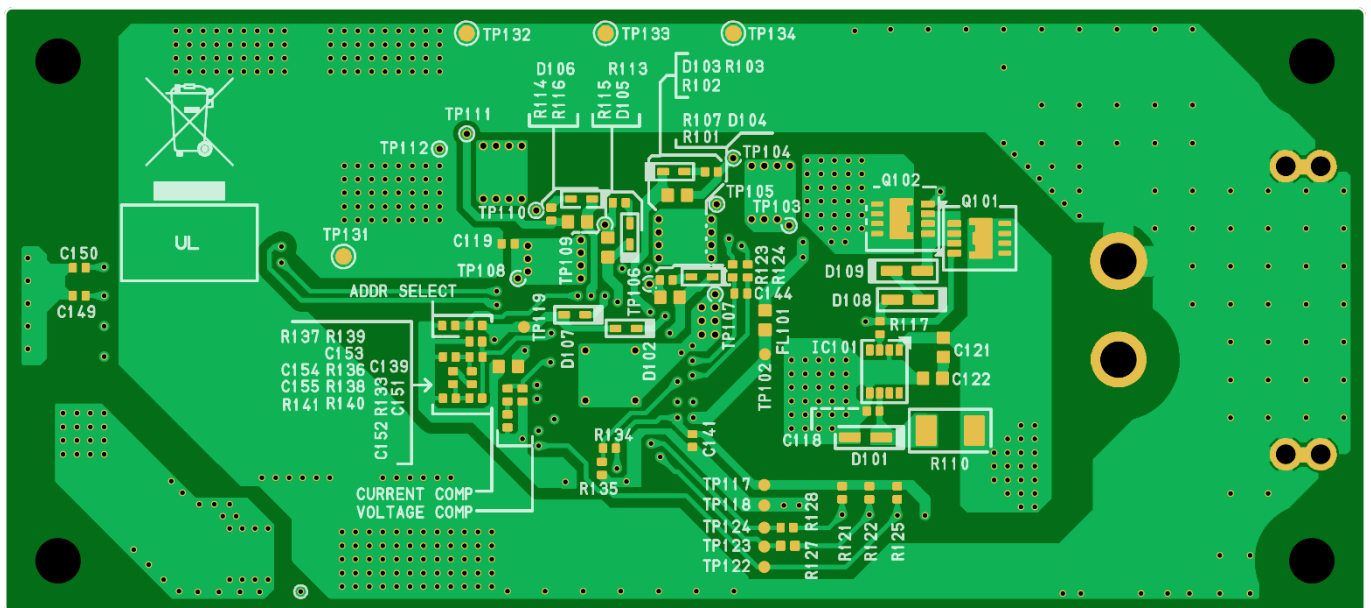

<Back>

Fig. 2.4 Main Component Layout (Option 1)





## **3. Schematic, Bill of Material, and PCB Pattern**

### **3.1. Schematic**

Refer to the following files:

RD228-SCHEMATIC1-xx.pdf (optional 1, using XPN7R104NC)

RD228-SCHEMATIC2-xx.pdf (optional 2, using SSM6K804R)

(xx is the revision number.)

### **3.2. Bill of Material**

Refer to the following files:

RD228-BOM1-xx.pdf (optional 1, using XPN7R104NC)

RD228-BOM2-xx.pdf (optional 2, using SSM6K804R)

(xx is the revision number.)

### **3.3. PCB Pattern**


Fig. 3.1 and Fig. 3.2 show the PCB pattern of this power supply.

Also, refer to the following files:


RD228-LAYER1-xx.pdf (optional 1, using XPN7R104NC)

RD228-LAYER2-xx.pdf (optional 2, using SSM6K804R)


(xx is the revision number.)

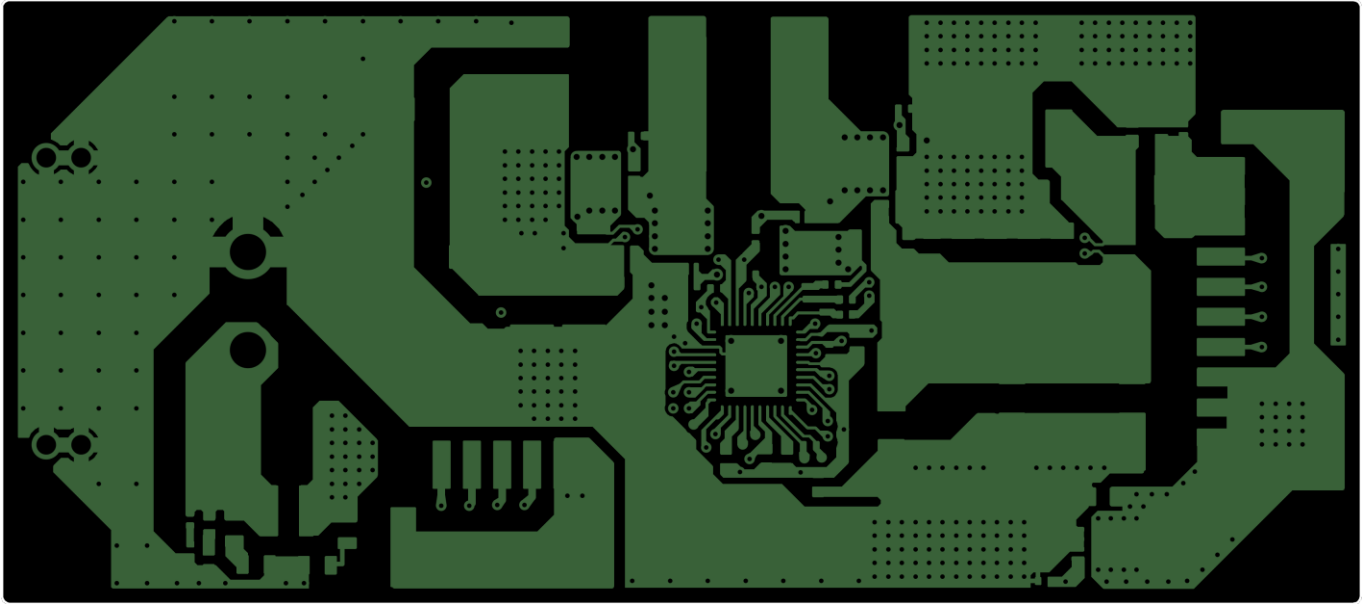


<Layer 1 Front>

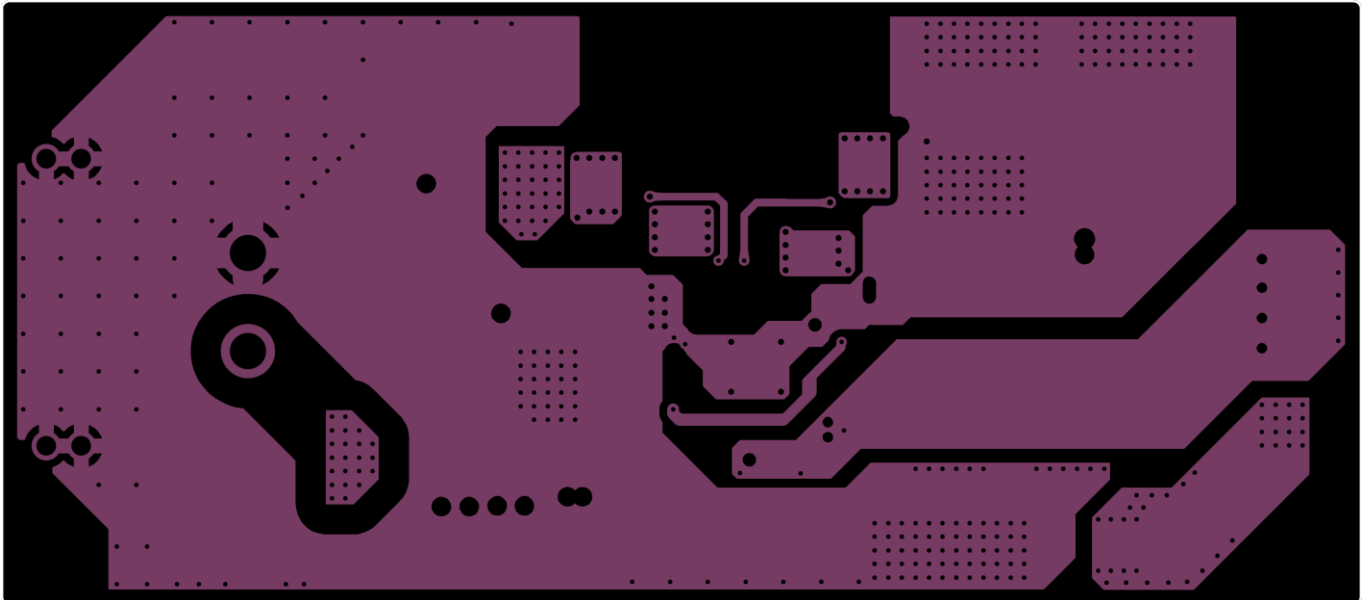

<Layer 2>

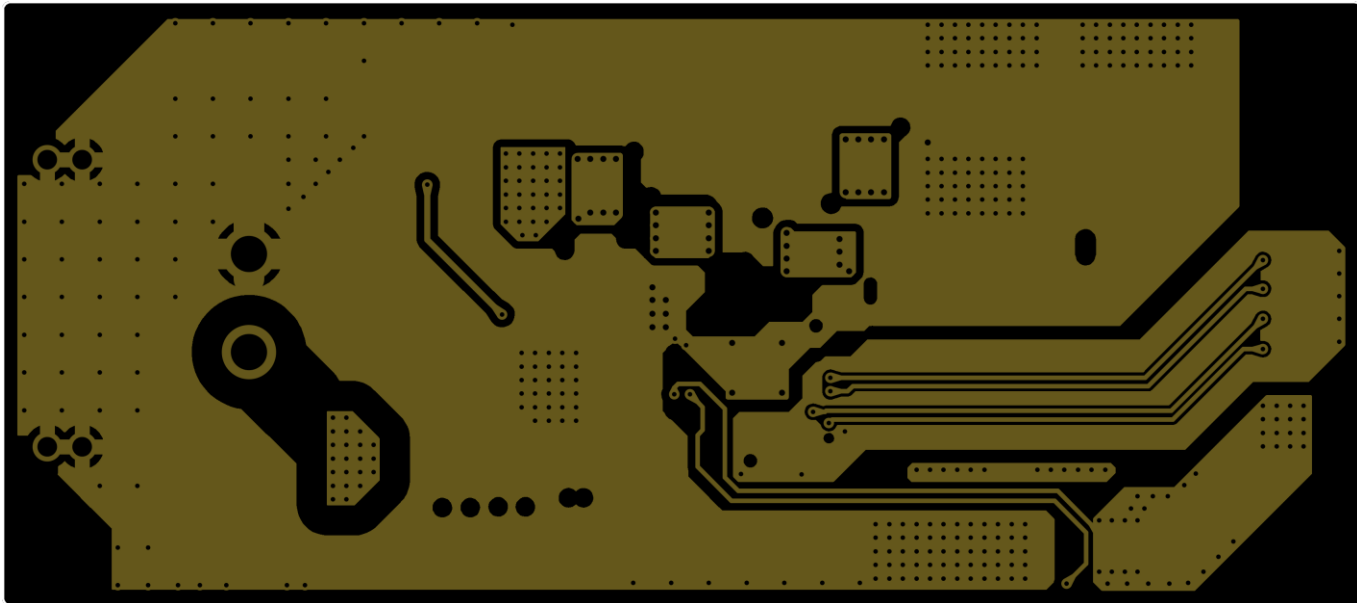


<Layer 3>

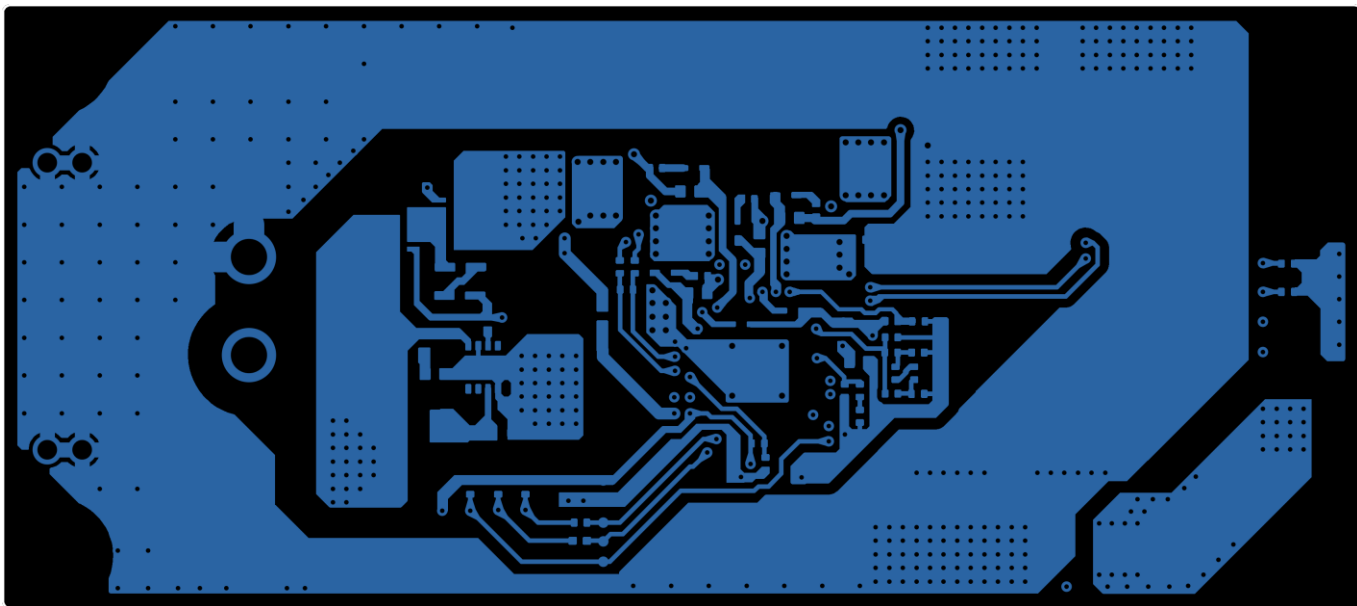


<Layer 4 Back>


**Fig. 3.1 PCB Pattern (Front View) (Option 1)**

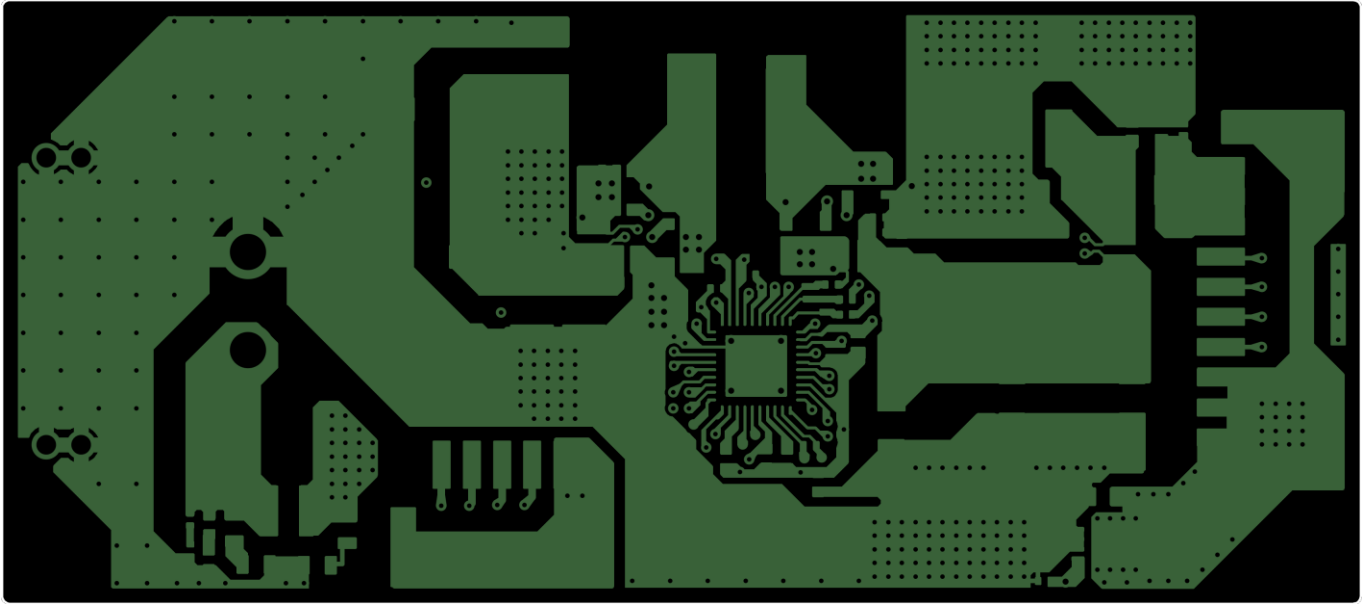


<Layer 1 Front>

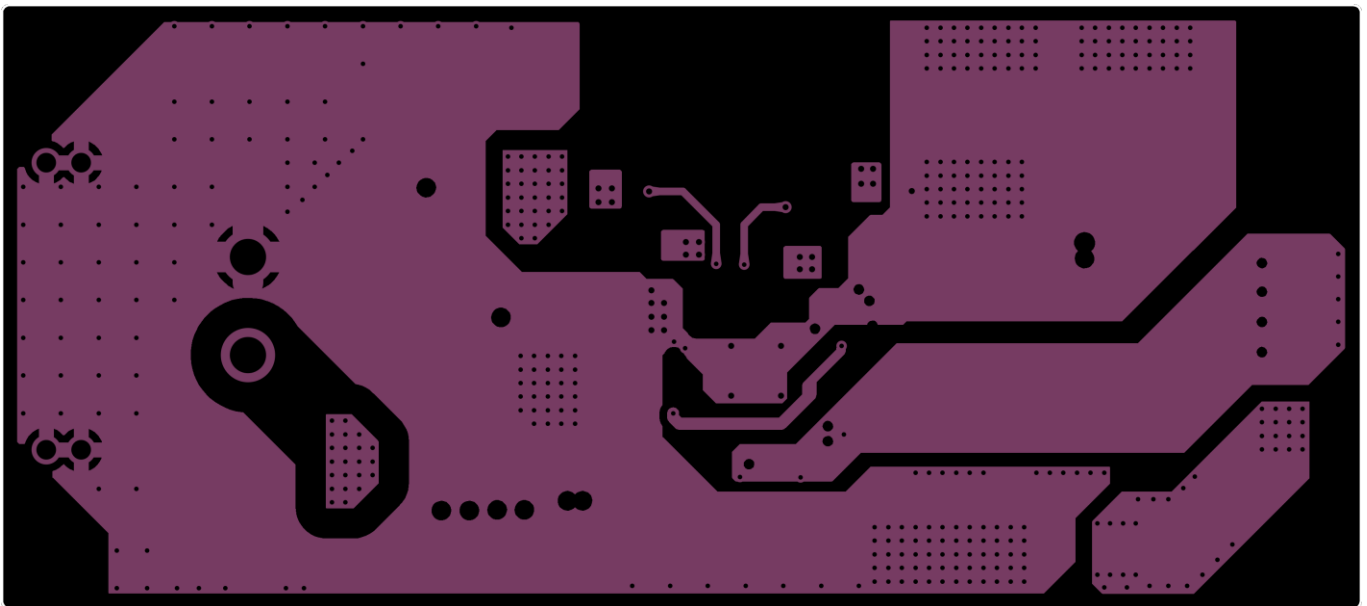

<Layer 2>

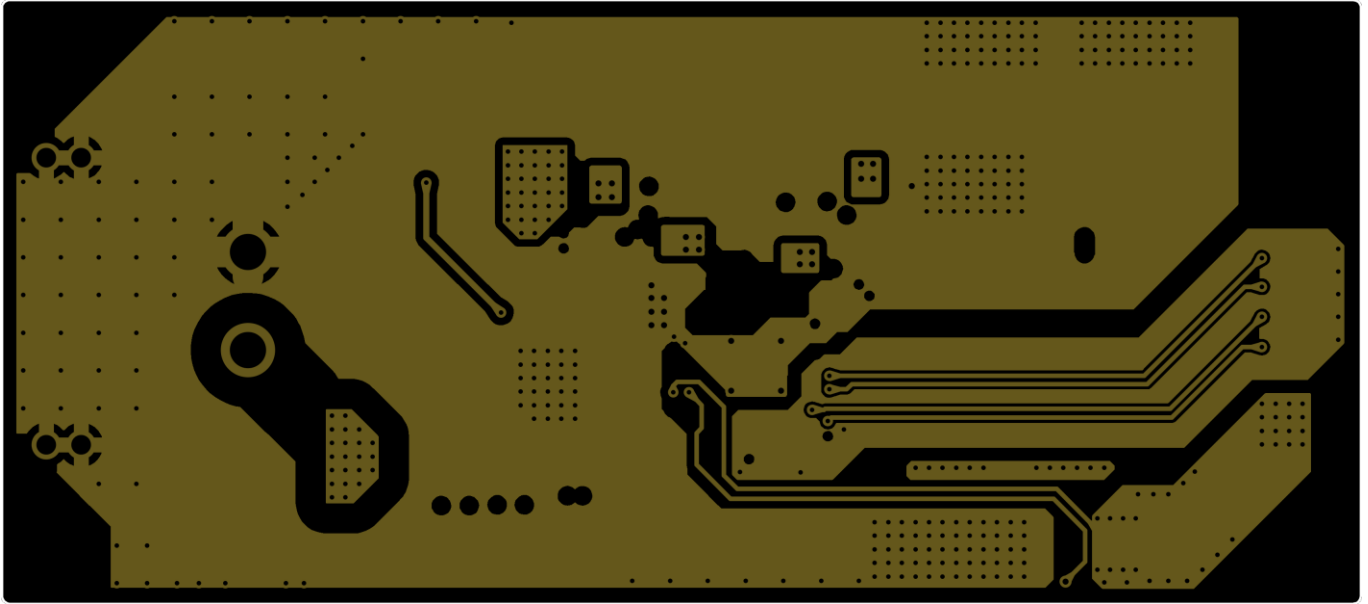

<Layer 3>

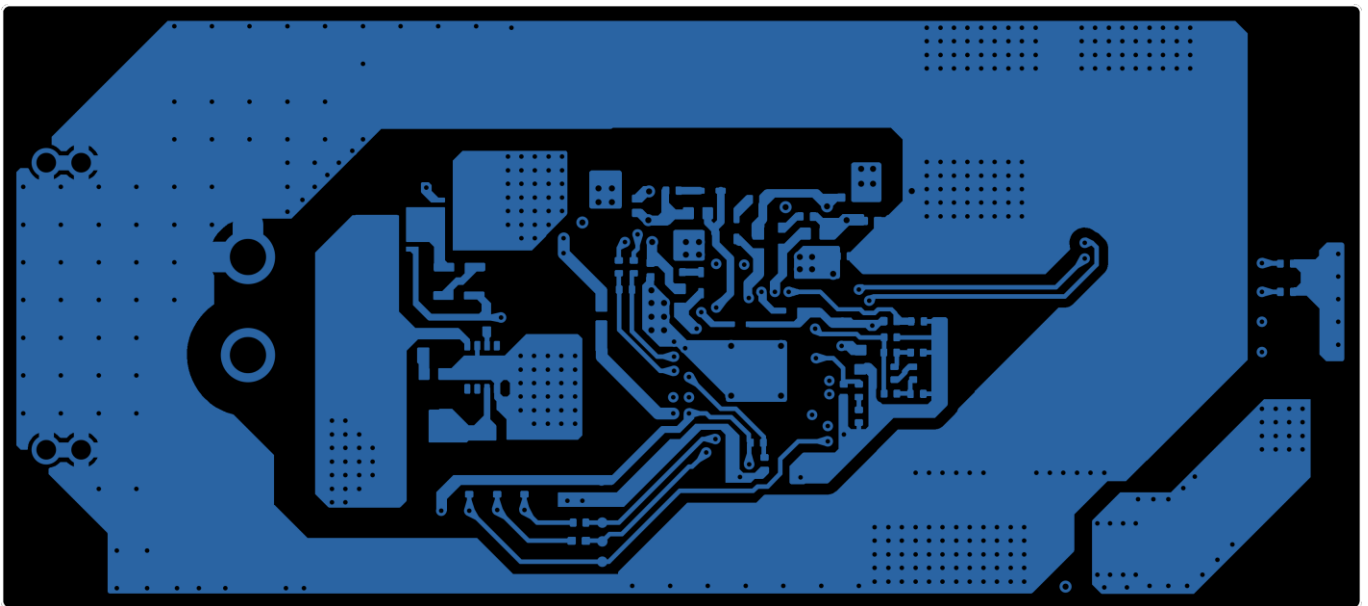

<Layer 4 Back>

**Fig. 3.2 PCB Pattern (Front View) (Option 2)**

## 4. Operation

### 4.1. Name and Function of Components

#### 4.1.1. Power Input Connector (CN101, CN201)

This connector is used to input power. HVH-280-2P-6.5DS (Hirose) is being used.



Fig. 4.1 Power Input Connector

Table 4.1 Power Input Connector Specifications

Pin	Net name	Description
1	VIN	Power input (+)
2	GND_P	Power Input (-)

#### 4.1.2. Power Output Connector (CN103, CN203)

This connector is used to output power. 502352-1000 (Molex) is being used. To control the power with USB Power Delivery, connection to the specified terminal of the external USB Type-C<sup>®</sup> connector is required.




Fig. 4.2 Power Output Connector

Table 4.2 Power Output Connector Specifications

Pin	Net name	Description
1	SHLD_SNS	Power Output (-)
2		
3		
4	HVDP	Connect to USB Type-C <sup>®</sup> connector D+ terminal
5	HVDM	Connect to USB Type-C <sup>®</sup> connector D- terminal
6	HVCC2	Connect to USB Type-C <sup>®</sup> connector CC2 terminal
7	HVCC1	Connect to USB Type-C <sup>®</sup> connector CC1 terminal
8	VBUS	Power Output (+)
9		
10		

### 4.1.3. Host Connector (CN102, CN202)

It is used to connect to a host such as an external MCU. 502352-0501 (Molex) is being used. It connects I<sup>2</sup>C interface between the host and the controller mounted on the power supply. I<sup>2</sup>C address defaults to 50 (hexadecimal), but I<sup>2</sup>C address can be changed by setting the resistor on the board. A control power supply (3.3 V or 5 V) is required to operate the controller installed in this power supply.

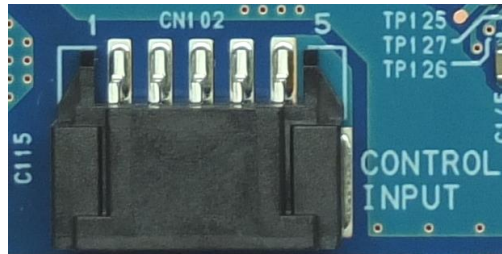

**Fig. 4-3 Host Connector**

**Table 4-3 Host Connector Specifications**

Pin	Net name	Description
1	VDD	Control power (3.3 V or 5.5 V)
2	ALERT	Error signal output (L output at error)
3	SCL	I2C Clock-Signal Input (SCL)
4	SDA	I2C Input/Output (SDA)
5	GND_A	Control Power/Signal Ground

## **4.2. Operation Checking Procedure**

### **4.2.1. Preparation**

Connect a host device to the host connector. A host device could be a MCU board that controls the controller mounted on this power supply. For details, refer to the data sheet of the installed controller. Connect the battery or other input power to the power input connector. Connect USB Type-C<sup>®</sup> connector to the power output connector.

### **4.2.2. Operation Procedure**

Apply control power (3.3 V or 5 V) to pin 1 of the host connector. Initialize the controller mounted on this power supply from the host. By connecting a USB Power Delivery load device (Sink Device) to USB Type-C<sup>®</sup> connector connected to the power output connector, the power is controlled by USB Power Delivery and the required power is supplied to the load device.

### **4.2.3. Operation During Error Detection**

When the controller mounted on this power supply detects an error, the ALERT (pin 2) of the host connector is set to low.

## **4.3. Precautions (To Prevent Electric Shock, Burn Injury, etc.)**

Pay special attention to the following when operating.

- Make sure the polarity of the connector is correct before supplying power.
- When checking the operation, cover the BOARD with an acrylic case for safety.
- MOSFET and other components generate heat during operation. Some components of the circuit board contain high voltage. Be very careful of burns and electric shocks when handling the circuit board.

※ USB Type-C<sup>®</sup>, USB-C<sup>®</sup> are registered trademarks of USB Implementers Forum.

※ Company names, product names, and service names may be trademarks of their respective companies.



## Terms of Use

This terms of use is made between Toshiba Electronic Devices and Storage Corporation ("We") and customers who use documents and data that are consulted to design electronics applications on which our semiconductor devices are mounted ("this Reference Design"). Customers shall comply with this terms of use. Please note that it is assumed that customers agree to any and all this terms of use if customers download this Reference Design. We may, at its sole and exclusive discretion, change, alter, modify, add, and/or remove any part of this terms of use at any time without any prior notice. We may terminate this terms of use at any time and for any reason. Upon termination of this terms of use, customers shall destroy this Reference Design. In the event of any breach thereof by customers, customers shall destroy this Reference Design, and furnish us a written confirmation to prove such destruction.

### 1. Restrictions on usage

1. This Reference Design is provided solely as reference data for designing electronics applications. Customers shall not use this Reference Design for any other purpose, including without limitation, verification of reliability.
2. This Reference Design is for customer's own use and not for sale, lease or other transfer.
3. Customers shall not use this Reference Design for evaluation in high or low temperature, high humidity, or high electromagnetic environments.
4. This Reference Design shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.

### 2. Limitations

1. We reserve the right to make changes to this Reference Design without notice.
2. This Reference Design should be treated as a reference only. We are not responsible for any incorrect or incomplete data and information.
3. Semiconductor devices can malfunction or fail. When designing electronics applications by referring to this Reference Design, customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of semiconductor devices could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Customers must also refer to and comply with the latest versions of all relevant our information, including without limitation, specifications, data sheets and application notes for semiconductor devices, as well as the precautions and conditions set forth in the "Semiconductor Reliability Handbook".
4. When designing electronics applications by referring to this Reference Design, customers must evaluate the whole system adequately. Customers are solely responsible for all aspects of their own product design or applications. WE ASSUME NO LIABILITY FOR CUSTOMERS' PRODUCT DESIGN OR APPLICATIONS.
5. No responsibility is assumed by us for any infringement of patents or any other intellectual property rights of third parties that may result from the use of this Reference Design. No license to any intellectual property right is granted by this terms of use, whether express or implied, by estoppel or otherwise.
6. THIS REFERENCE DESIGN IS PROVIDED "AS IS". WE (a) ASSUME NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (b) DISCLAIM ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO THIS REFERENCE DESIGN, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.

### 3. Export Control

Customers shall not use or otherwise make available this Reference Design for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). This Reference Design may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export and re-export of this Reference Design are strictly prohibited except in compliance with all applicable export laws and regulations.

### 4. Governing Laws

This terms of use shall be governed and construed by laws of Japan.