

**Smart gate driver coupler**  
**TLP5214A/TLP5214/TLP5212/TLP5222**  
**Application Note -Introduction-**

**Outline**

This document provides an overview of the features of the Smart Gate Driver coupler TLP5214A/TLP5214/TLP5212/TLP5222 as an introduction.

**Table of contents**

Introduction .....	2
1. What is overcurrent protection? .....	3
2. Cause of overcurrent .....	4
2-1. Output short circuit.....	4
2-2. Arm short circuit.....	4
3. Type of overcurrent protection.....	5
4. Example of protection circuitry using general-purpose / SGD couplers .....	6
5. Functional explanation of the SGD coupler .....	7
5-1. Outline of protection operation .....	7
5-2. Fault signal reset method .....	8
5-3. Normal operation .....	9
5-4. Malfunction due to miller capacity, and the prevention .....	10
5-5. Active Miller Clamp Function.....	12
6. Application .....	13
RESTRICTIONS ON PRODUCT USE.....	15



### Introduction

TLP5214A/TLP5214/TLP5212/TLP5222 are smart gate driver (hereinafter SGD) couplers with a  $V_{CE(sat)}$  detecting function, miller clamping function, FAULT outputting function in addition to a general-purpose gate driver coupler to protect IGBT from overcurrent generated in the inverter applications, etc.

To accommodate multi-functionality, 16-pin SO16L package is used for these products.

In this document, the functional outline of TLP5214A/TLP5214/TLP5212/TLP5222 will be explained.

**Table 1. Comparison table of general-purpose gate driver couplers and SGD couplers**

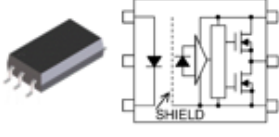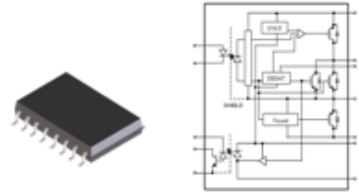	General-purpose gate driver coupler	SGD coupler
Model	TLP5702, TLP5754など	TLP5214A/TLP5214/TLP5212/TLP5222
Package/Internal circuit diagram	SO6L 	SO16L 
Pin count	6pin	16pin
Direct driving of the IGBT gate	✓	✓
UVLO function	✓	✓
$V_{CE(sat)}$ detecting function	-	✓
Active miller clamp	-	✓
FAULT outputting function	-	✓

## 1. What is overcurrent protection?

Overcurrent protection is to detect abnormal current flowing in the circuit and prevent damage to the circuit.

In particular, if an overcurrent is applied to IGBT used in the inverter circuit, the collector-emitter voltage ( $V_{CE}$ ) will rise, and destroy IGBT due to that excessive power is applied. Therefore, the overcurrent must be shut off in as short a time as possible. The time from when an overcurrent flows to IGBT until it is destroyed is called the short-circuit tolerance, and the overcurrent must be interrupted within the short-circuit tolerance. Although the short-circuit tolerance varies depending on the product, the design must be made so that the overcurrent is cut off within at least  $10\mu s$ . In addition, for the safety of humans, many electrical equipment must be equipped with an overcurrent protection function according to safety standards.

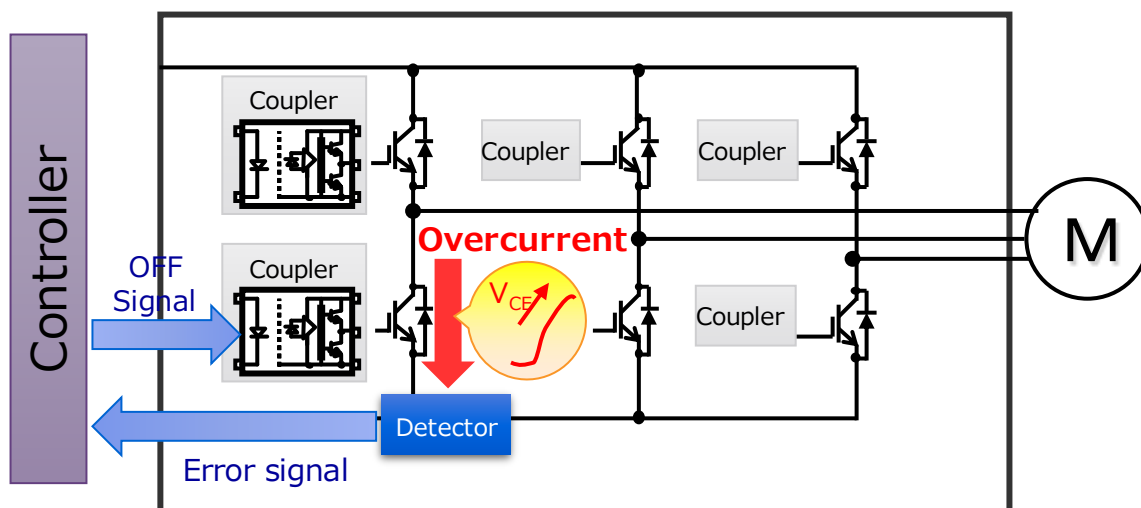


Figure 1. Example of inverter circuit

## 2. Cause of overcurrent

There are various causes of overcurrent, but some typical examples are given here.

### 2-1. Output short circuit

Excessive current flows between separate arms due to human-induced connection errors or load breakage. Overcurrent also flows when the motor is mechanically constrained by external factors.

### 2-2. Arm short circuit

The upper and lower arms are short-circuited and overcurrent flows, due to malfunction caused by noise or IGBT malfunction caused by miller current during switching.

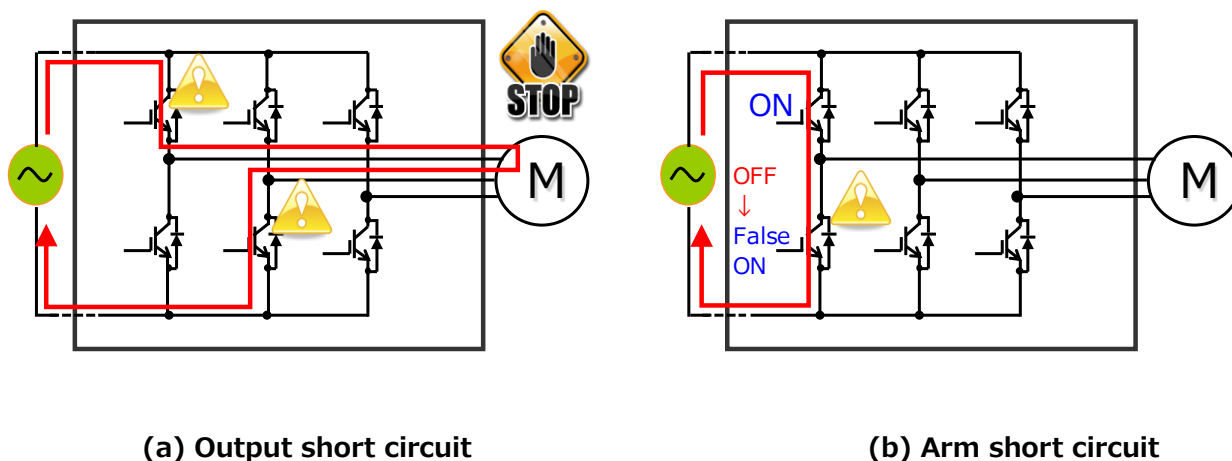


Figure 2. Examples of overcurrent generation causes

### 3. Type of overcurrent protection

There are several ways to prevent IGBT destruction caused by overcurrent. Each of them has different advantages, but especially, the method of monitoring the saturation voltage  $V_{CE(sat)}$  shown in Fig. 3(c) have the merits of lower power dissipation and faster operation because the protective operations are performed in IGBT driving circuitry.

TLP5214A/TLP5214/TLP5212/TLP5222 are IGBT driver photocouplers with a built-in protective circuitry that monitors  $V_{CE(sat)}$ .

a) Current transformer

Current transformer is used to monitor the currents in inverter circuitry. Electrical isolation is not necessary, but it may be physically too large.

b) Current sense resistor

A metallic resistor for sensing the current is used to monitor the current. Insulation is needed. Although relatively small, it produces large power losses due to the load current.

c)  $V_{CE(sat)}$  monitor

A high voltage diode is used to monitor the collector-emitter voltage. This method provides low power loss, relatively inexpensive, and fast operation.

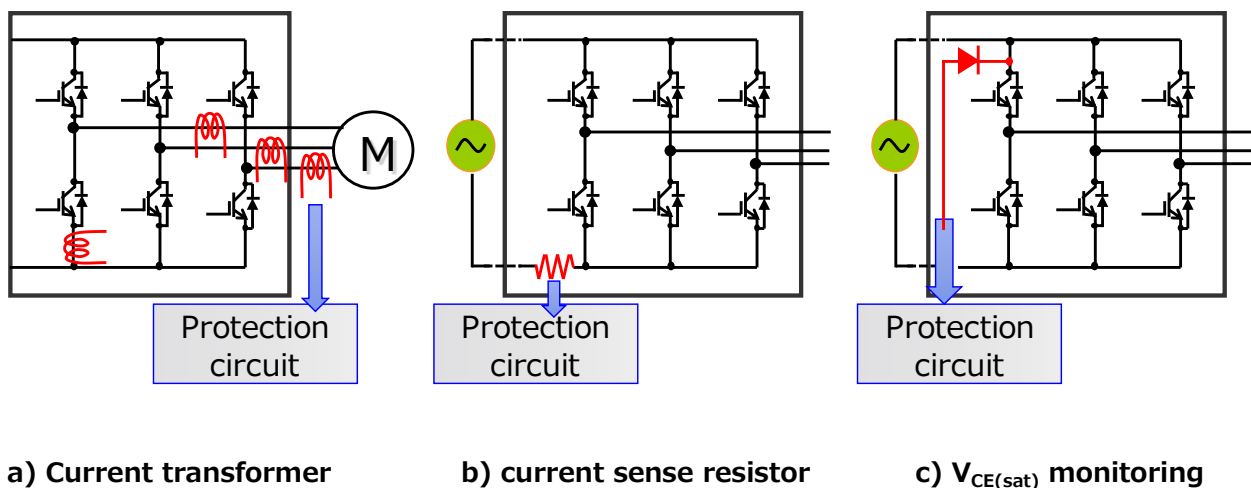


Figure 3. Type of overcurrent protection

## 4. Example of protection circuitry using general-purpose / SGD couplers

### couplers

Fig. 4 shows an illustration of the example of protective circuitry by Fig. 3(c)  $V_{CE(sat)}$  monitoring using a general-purpose driver-coupler TLP5702.

In the protective circuit,  $V_{CE(sat)}$  is monitored through diode  $D_1$ , and when an overcurrent occurs, the gate signal of IGBT is softly turned OFF.

A 1Mbps high-speed coupler is used to transmit FAULT signals to the controller. External component in the protection circuits are complex and use much areas in the board, but SGD couplers are the photo couplers that integrate these functions into one package, and offers smart gate-drive and protection circuitry.

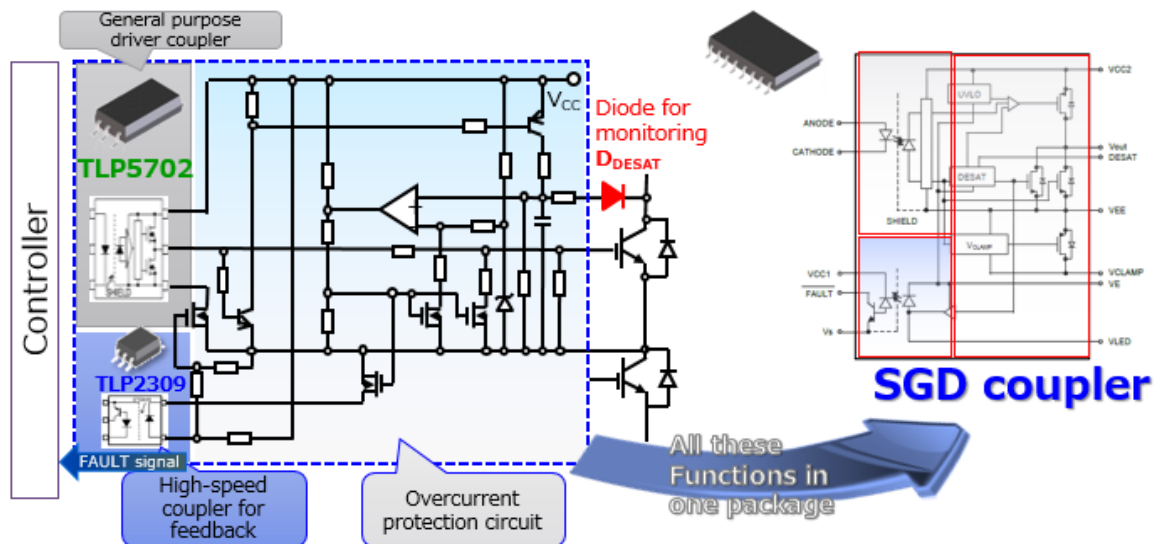


Figure 4. Example of protection circuitry using general-purpose / SGD couplers

## 5. Functional explanation of the SGD coupler

### 5-1. Outline of protection operation

TLP5214A/TLP5214/TLP5212/TLP5222 monitors IGBT collector-emitter voltage ( $V_{CE}$ ) on DESAT pins. Normally, when IGBT is ON,  $V_{CE(sat)}$  is about 2V. In the event of overcurrent,  $V_{CE(sat)}$  increasing causes the DESAT – VE pin-to-pin voltage ( $V_{DESAT}$ ) exceeds the threshold of 6.5 V (Typ.), and the following two-stage overcurrent protection sequence will be carried out by the SGD couplers.

- ① Soft shutdown of  $V_{OUT}$  (gradual transition to OFF status) to prevent IGBT breakdown due to the overcurrent;
- ② Fault signal transfer to controller.

While most driver couplers take several microseconds to generate the fault signal to the controller and shut down LED signal/coupler output, the TLP5214A/TLP5214/TLP5212/TLP5222 are able to initiate the  $V_{OUT}$  shutdown in less than 500 ns, and are therefore suitable for designing quick and safety circuits.

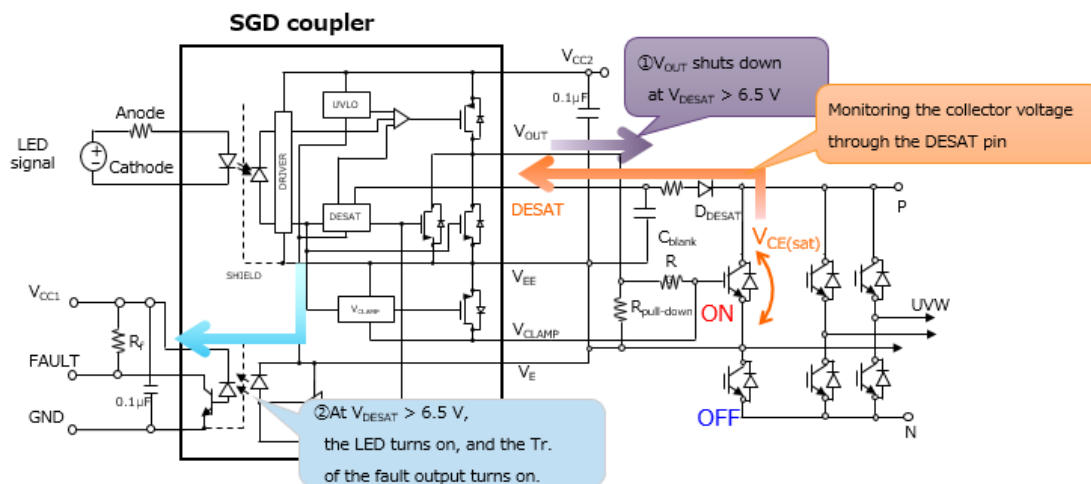


Figure 5. Outline of the protective function of SGD coupler


### 5-2. Fault signal reset method

Once the protection operation is triggered, the LED signal is not received by SGD couplers for a preset period. This period is denoted  $t_{DESAT(MUTE)}$ . There are two types of resetting methods for Fault signal during protection operation.

- ① LED trigger: The New LED signal, arising after  $t_{DESAT(MUTE)}$ , initiates reset procedure. TLP5214A/TLP5214/TLP5212 are applicable.
- ② Automatic: Automatically initiates reset procedure after  $t_{DESAT(MUTE)}$ . TLP5222 is applicable.

The timing chart of Protection and fault signal reset are shown in Table 2

**Table 2. Protection and Fault signal reset procedure timing chart**

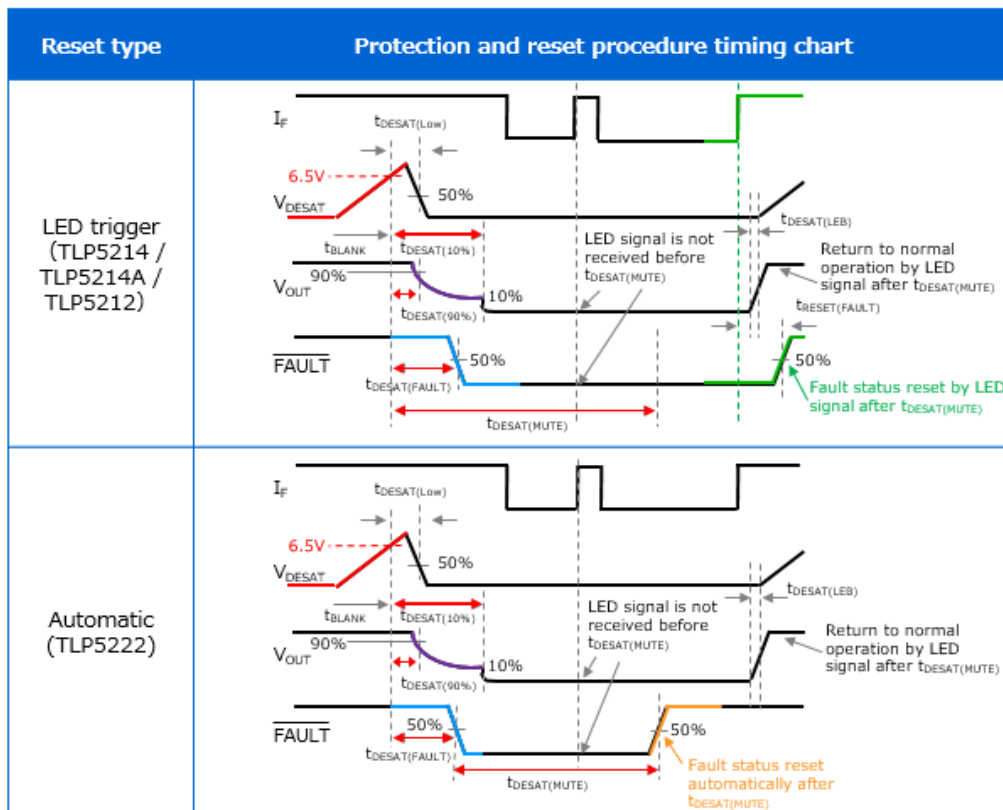

For the LED trigger reset type, resetting Fault signal is linked with LED signal. Therefore, a command from the controller is required. On the other hand, for the automatic reset type, Fault signal is automatically reset over time, which simplifies the sequencing setting in the controller.




### 5-3. Normal operation

a) When the LED signal is OFF

$V_{OUT}$  is Low and DESAT pin is inactive. FAULT isn't sent even if more than the  $V_{DESAT}$  voltage is applied to the DESAT pin.

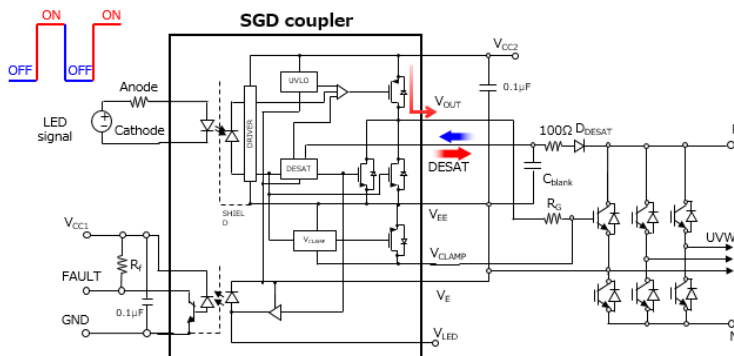b) When the LED signal is ON

$V_{OUT}$  is High and the DESAT pin is active. The above protection operation is triggered when an overcurrent condition occurs.



LED	DESAT terminal	FAULT output	$V_{OUT}$
OFF	Inactive	High	Low
ON	Active Low ( $< V_{DESAT}$ )	High	High
ON	Active High ( $> V_{DESAT}$ )	Low (FAULT)	Low


Figure 7. List of DESAT Pin Operation in Normal Operation

**5-4. Malfunction due to miller capacity, and the prevention**

Malfunctions caused by a parasitic miller capacitance between the collector and gate of IGBT  $C_{CG}$ , should be mentioned as one of the malfunctions due to switching noise in the inverter circuitry. This malfunction mechanism and the active miller clamp function on the SGD coupler are explained here.

When IGBT of the upper arm in the inverter circuitry is turned on, the  $V_{CE}$  of the IGBT of the lower arm rises sharply.

At this time, the displacement current  $I_S = C_{CG} \times (dV_{CG}/dt)$  is generated via  $C_{CG}$  of IGBT of the lower arm and flows toward the output of the photocoupler, and the gate voltage of IGBT rises due to that  $I_S$  flows through  $R_G$ . Due to this voltage rising of gate, IGBT will be erroneously turned on, and this induces a short circuit in the upper and lower arms.

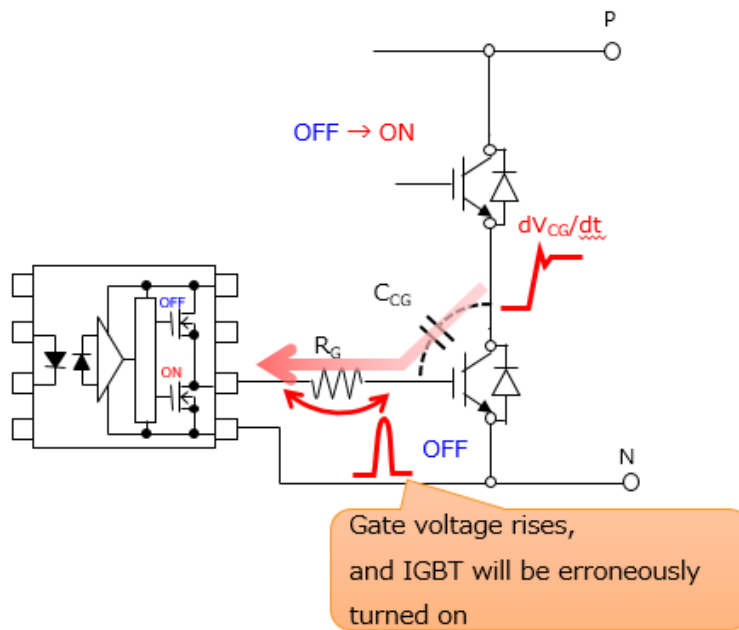

**Figure 8. Illustration of malfunction due to miller capacity**


Below are two methods to prevent a malfunction due to miller capacitance. The 1st involves using a negative power source. The 2nd involves adjusting the gate resistance.

a) Use of negative power supply

Using a negative supply voltage for the photocoupler's power source prevents this malfunction because the gate has a negative voltage when the IGBT is off. Since this solution requires a negative power supply circuit, cost and size can be an issue.

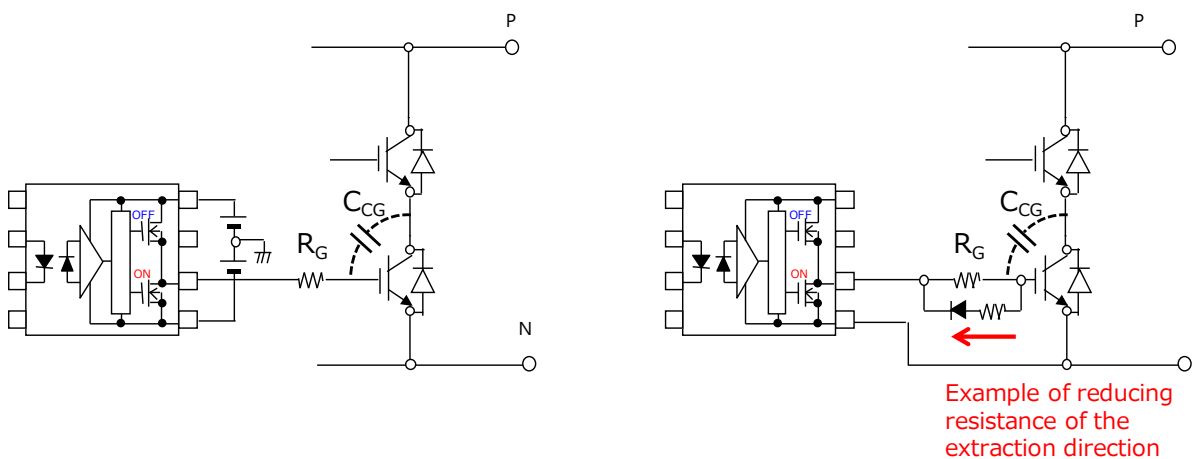b) Adjusting the gate resistance

The increasing in gate potential can be minimized by using a smaller gate resistance. Although this solution is less inexpensive than using a negative power supply, switching noise may increase.



a) Use of negative power supply


b) Adjusting the gate resistance

Figure 9. Example of prevention of malfunction due to miller capacity



## 6. Application

TLP5214A/TLP5214/TLP5212/TLP5222 are suitable for applications which need inverter such as industrial inverters, PV inverters, UPSs, BMSs, etc.

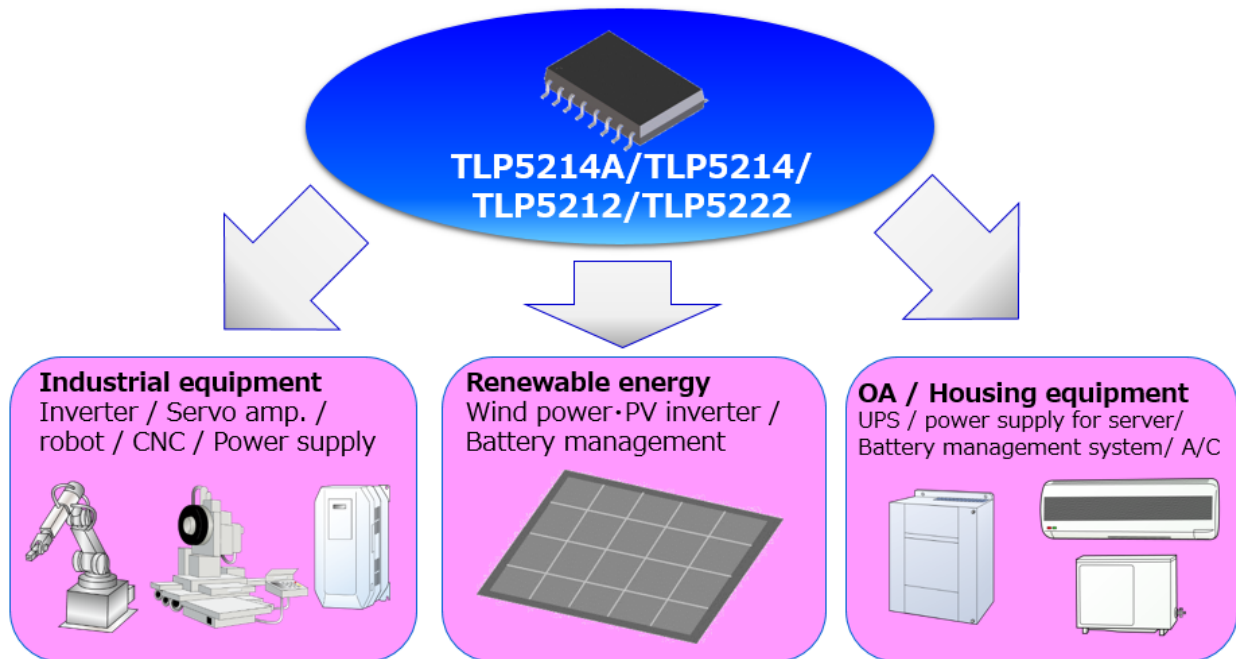

**Figure 11. Application example of TLP5214A/TLP5214/TLP5212/TLP5222**

**Revision History**

Revision	Date	Page	Description
Rev. 1.0	2014-8-12	-	1st edition
Rev. 1.1	2014-9-9	P2,9	Revision due to the correction of errors
Rev. 2.0	2021-3-2	All pages	Revision due to the format changes
Rev. 2.1	2021-5-19	P2, 4, 10, 11, 12	Revision due to the correction of errors
Rev. 3.0	2022-4-21	All pages	Postscript for TLP5212/TLP5222 and protection operation reset type

## RESTRICTIONS ON PRODUCT USE

Toshiba Corporation and its subsidiaries and affiliates are collectively referred to as "TOSHIBA". Hardware, software and systems described in this document are collectively referred to as "Product".

- TOSHIBA reserves the right to make changes to the information in this document and related Product without notice.
- This document and any information herein may not be reproduced without prior written permission from TOSHIBA. Even with TOSHIBA's written permission, reproduction is permissible only if reproduction is without alteration/omission.
- Though TOSHIBA works continually to improve Product's quality and reliability, Product can malfunction or fail. Customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of Product could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Before customers use the Product, create designs including the Product, or incorporate the Product into their own applications, customers must also refer to and comply with (a) the latest versions of all relevant TOSHIBA information, including without limitation, this document, the specifications, the data sheets and application notes for Product and the precautions and conditions set forth in the "TOSHIBA Semiconductor Reliability Handbook" and (b) the instructions for the application with which the Product will be used with or for. Customers are solely responsible for all aspects of their own product design or applications, including but not limited to (a) determining the appropriateness of the use of this Product in such design or applications; (b) evaluating and determining the applicability of any information contained in this document, or in charts, diagrams, programs, algorithms, sample application circuits, or any other referenced documents; and (c) validating all operating parameters for such designs and applications. **TOSHIBA ASSUMES NO LIABILITY FOR CUSTOMERS' PRODUCT DESIGN OR APPLICATIONS.**
- **PRODUCT IS NEITHER INTENDED NOR WARRANTED FOR USE IN EQUIPMENTS OR SYSTEMS THAT REQUIRE EXTRAORDINARILY HIGH LEVELS OF QUALITY AND/OR RELIABILITY, AND/OR A MALFUNCTION OR FAILURE OF WHICH MAY CAUSE LOSS OF HUMAN LIFE, BODILY INJURY, SERIOUS PROPERTY DAMAGE AND/OR SERIOUS PUBLIC IMPACT ("UNINTENDED USE").** Except for specific applications as expressly stated in this document, Unintended Use includes, without limitation, equipment used in nuclear facilities, equipment used in the aerospace industry, lifesaving and/or life supporting medical equipment, equipment used for automobiles, trains, ships and other transportation, traffic signaling equipment, equipment used to control combustions or explosions, safety devices, elevators and escalators, and devices related to power plant. **IF YOU USE PRODUCT FOR UNINTENDED USE, TOSHIBA ASSUMES NO LIABILITY FOR PRODUCT.** For details, please contact your TOSHIBA sales representative or contact us via our website.
- Do not disassemble, analyze, reverse-engineer, alter, modify, translate or copy Product, whether in whole or in part.
- Product shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.
- The information contained herein is presented only as guidance for Product use. No responsibility is assumed by TOSHIBA for any infringement of patents or any other intellectual property rights of third parties that may result from the use of Product. No license to any intellectual property right is granted by this document, whether express or implied, by estoppel or otherwise.
- **ABSENT A WRITTEN SIGNED AGREEMENT, EXCEPT AS PROVIDED IN THE RELEVANT TERMS AND CONDITIONS OF SALE FOR PRODUCT, AND TO THE MAXIMUM EXTENT ALLOWABLE BY LAW, TOSHIBA (1) ASSUMES NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (2) DISCLAIMS ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO SALE, USE OF PRODUCT, OR INFORMATION, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.**
- Do not use or otherwise make available Product or related software or technology for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). Product and related software and technology may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export and re-export of Product or related software or technology are strictly prohibited except in compliance with all applicable export laws and regulations.
- Please contact your TOSHIBA sales representative for details as to environmental matters such as the RoHS compatibility of Product. Please use Product in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. **TOSHIBA ASSUMES NO LIABILITY FOR DAMAGES OR LOSSES OCCURRING AS A RESULT OF NONCOMPLIANCE WITH APPLICABLE LAWS AND REGULATIONS.**