

**DC 300 V Input BLDC Motor
Sensorless Control Circuit
Using TPD4165K**

Design Guide

RD179d-DGUIDE-01

Toshiba Electronic Devices & Storage Corporation

Table of Contents

1. Introduction	3
2. Components Used	4
2.1. Microcontroller TMPM374FWUG	4
2.2. Intelligent Power Device TPD4165K	5
3. Circuit Design	6
3.1. MCU Peripheral Circuit	7
3.2. Motor Drive Circuit	9
3.3. Shunt Current Measurement Circuit	10
3.4. Error Detection Circuit	11
3.5. Motor Voltage Detection Circuit	12

1. Introduction

This Design Guide (hereinafter referred to as this Guide) describes the designs of DC 300 V Input BLDC Motor Sensorless Control circuit (hereinafter referred to as this reference design).

In this reference design, [TMPM374FWUG](#) microcontroller is used as motor controller, and vector control without sensor is realized. An intelligent power device for a three-phase inverter, which contains switching element and gate driver in a small package is used as motor driver. The intelligent power device used in this design (RD179-4) is as follows:

- [TPD4165K](#) (built-in IGBT type, 600 V withstand voltage, 3.0 A maximum output current, and HDIP30 package).


2. Components Used

2.1. Microcontroller TPM374FWUG


This reference uses the Toshiba microcontroller [TPM374FWUG](#) for controlling the motor.

The main features of TPM374FWUG are as follows:

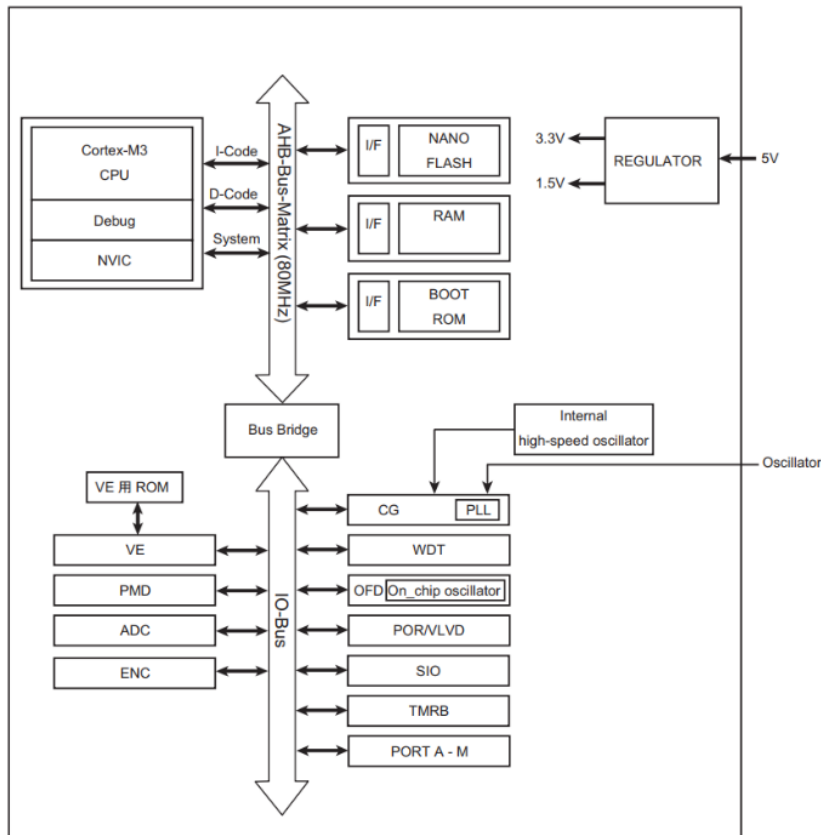- Equipped with high-speed Arm Cortex-M3 and which can operate up to 80 MHz (operating temp. range -40 to 80 °C)
- Equipped with functions suitable for motor control such as A/D converter, programmable motor driver, vector engine, and encoder
- Supports 5 V voltage operation
- Small LQFP44 package



Internal Block Diagram

 


LQFP44 Package

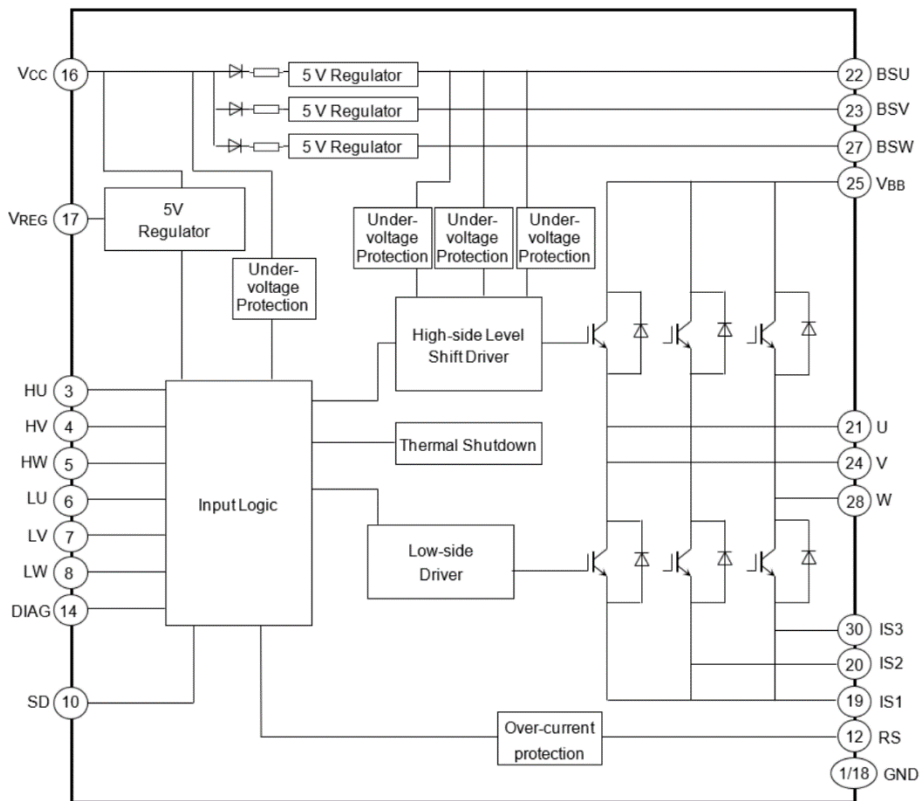
2.2. Intelligent Power Device TPD4165K

This reference (RD179-4) uses the Intelligent Power Device [TPD4165K](#). TPD4165K is a high-voltage, three-phase brushless motor driver with a built-in IGBT rated at 600 V, and supports 3-shunt resistor current sensing. It also incorporates level-shifted high-side driver, low-side driver, overheat protection circuit, under-voltage protection circuit, overcurrent protection, shutdown (SD) function. Therefore, a three-phase brushless motor can be driven directly by taking control signal input from a microcontroller. The main features are as follows.

- Output tolerance V_{BB} 600 V (Max.)
- Current I_{out} 3.0 A (Max.)
- HDIP30 package



Internal Block Diagram

 

HDIP30 Package

3. Circuit Design

This section explains the main points of circuit design. Refer to RD179-SCHEMATIC4 for the schematics and to RD179-BOM4 for the bill of materials.

Fig. 3.1 shows the block diagram of this reference.

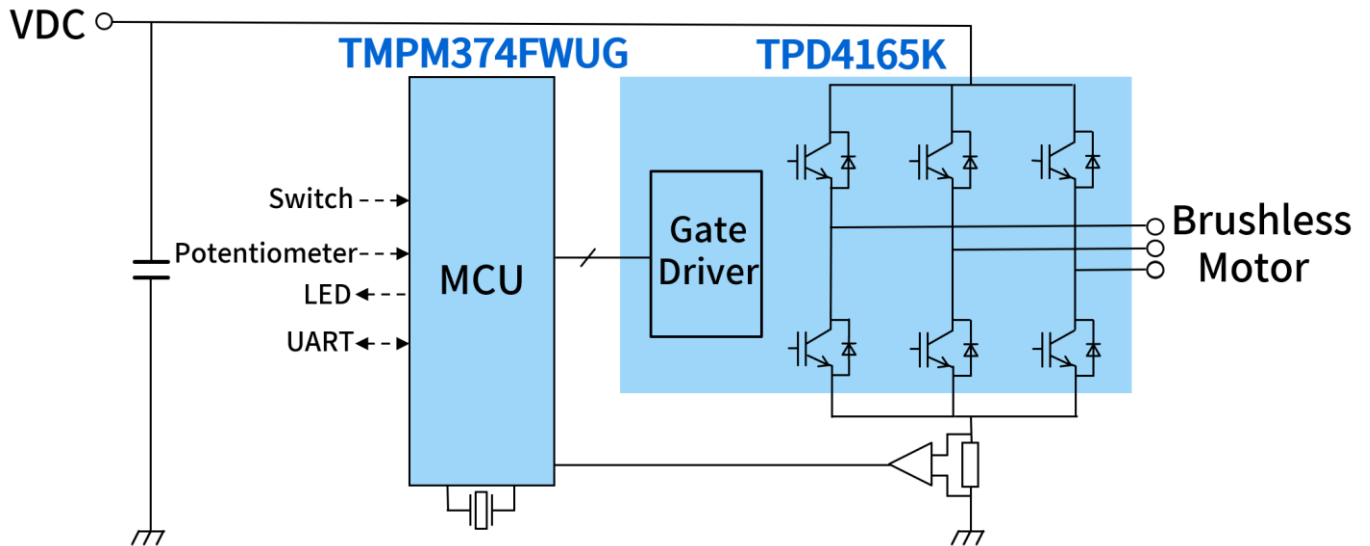


Fig. 3.1 Block Diagram of DC 300 V Input BLDC Motor Sensorless Control Circuit

3.1. MCU Peripheral Circuit

Fig. 3.2 shows the MCU peripheral circuit.

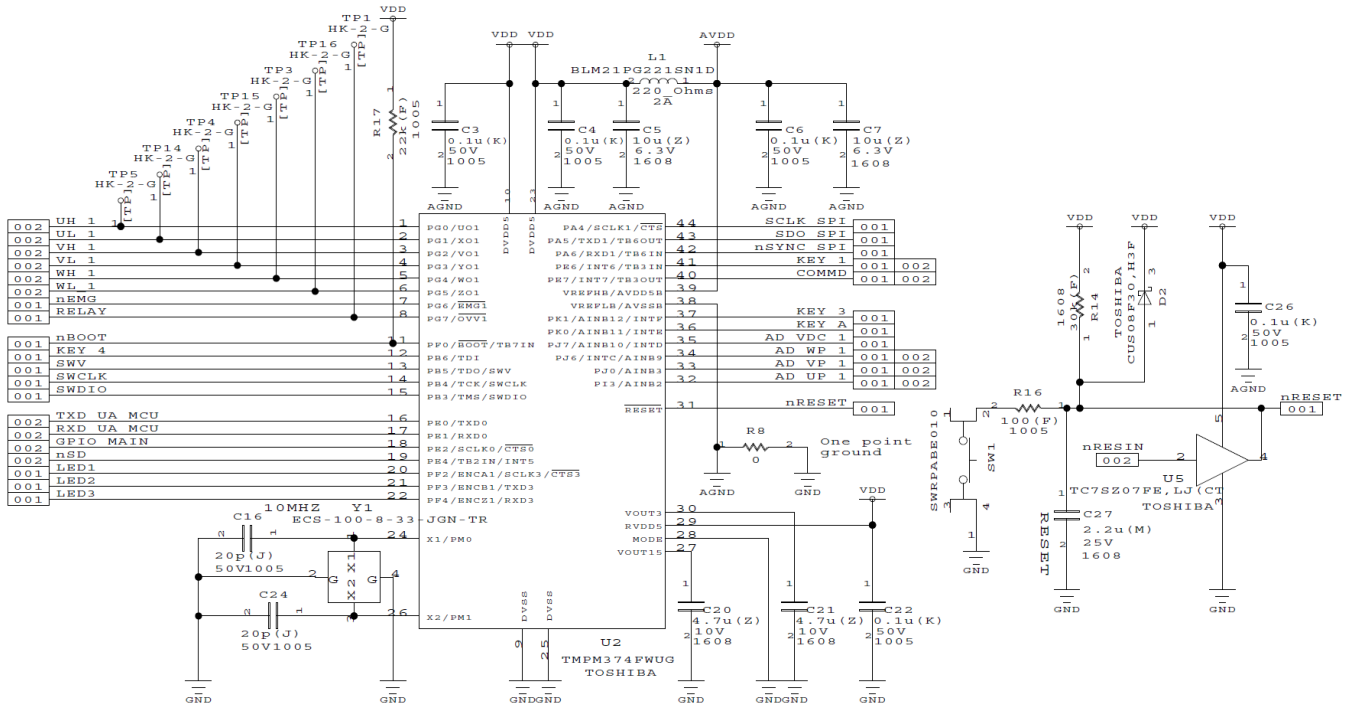


Fig. 3.2 MCU Peripheral Circuit

VDD (5 V) connected to the control power input terminal (J10) is supplied to the digital power supply used in MCU, etc. Bypass capacitors (C3, C4, C5, etc.) are required to eliminate power supply noise, etc. The 5 V analogue power supply (AVDD) of this reference design is generated from the 5V control power supply (VDD) and is received from the control power supply input pin (J10) via the ferrite bead (L1). The ground (GND) of the control power supply is connected to the ground (AGND) of the analogue power supply at a single point. VOUT3 pin (pin 30) and VOUT15 pin (pin 27) of the MCU must have the same capacitance of 3.3 to 4.7 μ F as the stabilizing capacitor of the power supply in the MCU. This reference design uses a 4.7 μ F capacitor for C20 and C21.

The capacitance of the load capacitors (C16 and C24) used in the resonator circuit of the microcontroller is selected so that the sum of equivalent capacitances of these capacitors in series (C16, C24), and the capacitance of resonator circuit in the MCU, and the pattern capacitance (approximately 10 pF) becomes the load capacitance of the resonator (X1). Since the load capacitance of the resonator (crystal resonator) used in this reference is 20 pF (Typ.), the capacitance of C16 and C24 is set to be 20 pF. The patterns to the resonator (X1) and the capacitors (C20 and C21) connected from the MCU should be as short as possible, and consideration should be given to minimizing the effect of noise on the surrounding signals. The 10 MHz clock generated by the crystal resonator circuit is used by the internal PLL to generate a system clock of up to 80 MHz.

The reset signal (nRESET) to the MCU is generated by the logical OR of the push switch (S1) and the external reset signal (nRESIN).

Each pin of the MCU is multiplexed, and the pin assignment is decided by the software setting. Table 3.1 lists the pin assignments used in this reference design. The function of each pin used in this reference is indicated by orange color.

Table 3.1 MCU Pin Assignment

Pin Number	Functions				Direction	Description
1	PG0	UO1			Out	U-phase high-side switch
2	PG1	XO1			Out	U-phase low-side switch
3	PG2	V01			Out	V-phase high-side switch
4	PG3	YO1			Out	V-phase low-side switch
5	PG4	WO1			Out	W-phase high-side switch
6	PG5	ZO1			Out	W-phase low-side switch
7	PG6	EMG1#			In	Emergency signal input
8	PG7	OVV1#			Out	GPIO-Relay control (not used)
9	DVSS				-	GND
10	DVDD5				-	Digital power (5 V)
11	PF0	BOOT#	TB7IN		In	Boot mode (usually connected to ground)
12	PB6	TDI			In	GPIO-S SW4 (not Used)
13	PB5	TDO	SWV		In/Out	SWD-SWV
14	PB4	TCK	SWCLK		Out	SWD-SWCLK
15	PB3	TMS	SWDIO		In/Out	SWD-SWDIO
15	PE0	TXD0			Out	UART-TXD0 (for host communication)
17	PE1	RXD0			In	UART-RXD0 (for host communication)
18	PE2	SCLK0	CTS0#		In/Out	GPIO-Reserved (for host communication)
19	PE4	TB2IN	INT5		Out	GPIO-IPD Shutdown (not used)
20	PF2	ENCA1	SCLK3	CTS3#	Out	GPIO-LED1
21	PF3	ENCB1	TXD3		Out	GPIO-LED2
22	PF4	ENCZ1	RXD3		Out	GPIO-LED3
23	DVDD5				-	Digital power (5 V)
24	PM0	X1			-	10 MHz resonator
25	DVSS				-	GND
26	PM1	X2			-	10 MHz resonator
27	VOOUT15				-	(Connected to capacitor)
28	MODE				In	(Connected to GND)
29	RVDD5				-	Digital power (5 V)
30	VOOUT3				-	(Connected to capacitor)
31	RESET#				In	Reset
32	PI3	AINB2			Analog In	U-phase shunt current
33	PJ0	AINB3			Analog In	V-phase shunt current
34	PJ6	AINB9	INTC		Analog In	W-phase shunt current
35	PJ7	AINB10	INTD		Analog In	Inverter DC bus voltage
36	PK0	AINB11	INTE		Analog In	Voltage of Potentiometer(VR1)
37	PK1	AINB12	INTF		In	GPIO-S SW3 (for CW-CCW switch)
38	AVSSB/VREFLB				-	Analog GND
39	AVDD5B/VREFHB				-	Analog power (5 V)
40	PE7	TB3OUT	INT7		In	GPIO-S SW2 (for host communication)
41	PE6	TB3IN	INT6		In	GPIO-S SW1 (not used)
42	PA6	TB6IN	RXD1		Out	SYNC# for external DAC
43	PA5	TB6OUT	TXD1		Out	SDO for external DAC
44	PA4	CTS1#	SCLK1		Out	SCLK for external DAC

3.2. Motor Drive Circuit

Fig. 3.3 shows the motor drive circuit (for RD179-4 using TPD4165K).

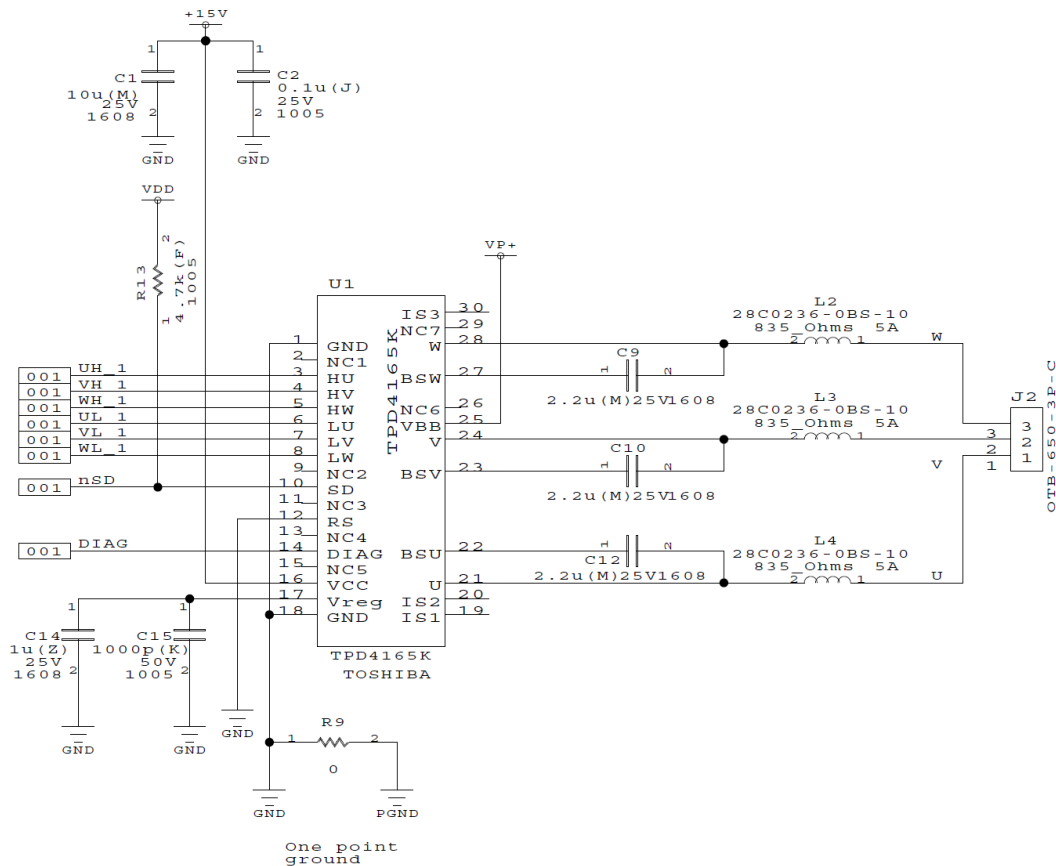


Fig. 3.3 Motor Drive Circuit (For RD179-4 using TPD4165K)

The intelligent power device (U1, TPD4165K in RD179-4) has built-in gate driver, and the 5 V level inverter control signals (UH_1, VH_1, WH_1, UL_1, VL_1, WL_1) output from the MCU can be directly connected to the HU pin, HV pin, HW pin, LU pin, LV pin, and LW pin. The inverter output from the U, V, and W pins are output to the motor connection terminals (J2) via filters (L2, L3, and L4).

The motor power (VP+) is supplied from the motor power input terminal (J1) to V_{BB} pins. The motor power ground (PGND) is connected to the control power ground (GND) at a single point. The 15 V control power is supplied from the control power input terminal (J3) to V_{CC} pin. A power supply stabilizing capacitor (C1) and a surge absorbing capacitor (C2) are connected to the control power supply.

The intelligent power device has a built-in bootstrap diode required for level shifting of the high-side gate driver. Connect a bootstrap capacitor (C9, C10, C12, 2.2 μF 25 V each) between U-pin and BSU-pin, between V-pin and BSV pin, and between W-pin and BSW pin.

The U1 has a built-in regulator and can output 5 V (for RD179-4) to V_{REG} pin, but it is not used in this reference design. Regardless of the use of the internal regulator output, connect a power supply stabilizing capacitor (C14) and a surge absorbing capacitor (C15) to V_{REG} pin of U1.

The SD pin of U1 is the shutdown control signal input. When the L level is input, all inverter outputs are shut off. This reference is connected to the MCU and is pulled up to VDD (5 V) by R13.

The input-side control pin and output-side step-down large current pin of the U1 are separated on both sides of the package. However, it is necessary to consider the creepage distances, etc., while designing the pattern.

3.3. Shunt Current Measurement Circuit

Fig. 3.4 shows the shunt current measurement circuit (for RD179-4 using TPD4165K).

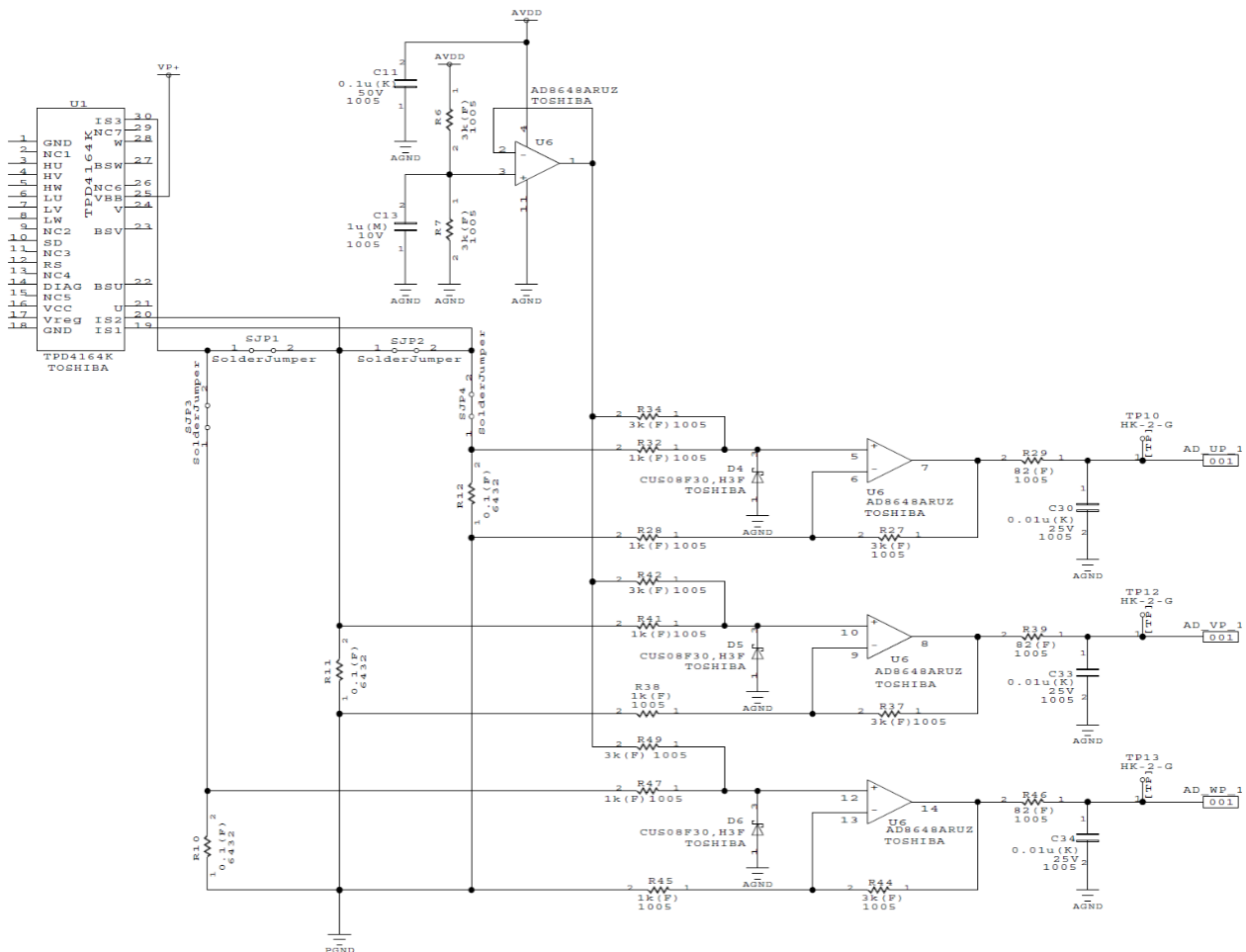


Fig. 3.4 Shunt Current Measurement Circuit (for RD179-4 using TPD4165K)

Intelligent power devices have shunt resistor connection pins for each half-bridge of the output inverter. IS1 pin corresponds to the U-phase output bridge, IS2 pin corresponds to the V-phase output bridge, and IS3 pin corresponds to the W-phase output bridge. In this design, a shunt resistor (R12, R11, R10, 0.1 Ω respectively) is connected to each pin, and amplified with 3 times gain by the operational amplifier (U6).

Bias voltage is added so that the output voltage becomes 2.5 V when the shunt current is 0 A. The op-amp with pin 1, pin 2, and pin 3 of U6 operates as a voltage follower of 2.5 V generated by the voltage divider circuit made of R6 and R7, and provides a bias voltage to the op-amps of each phase.

The shunt current measurement signals (AD_UP_1, AD_VP_1, AD_WP_1) are input to the A/D converter of the MCU via RC LPF (R29 and C30, R39 and C33, R46 and C34). The cutoff frequency f_c of this LPF is as follows.

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 82 \times 0.01 \times 10^{-6}} \approx 200 \text{ kHz}$$

The three-shunt configuration and one-shunt configuration can be changed in this reference design. Three-shunt configuration is selected by opening the solder jumper SJP1 and SJP2, shorting SJP3 and SJP4, and one-shunt configuration is selected by shorting the solder jumper SJP1 and SJP2, and opening SJP3 and SJP4. Only the V-phase shunt current measurement signal (AD_VP_1) is used in the 1-shunt configuration.

3.4. Error Detection Circuit

Fig. 3.5 shows the error detection circuit.

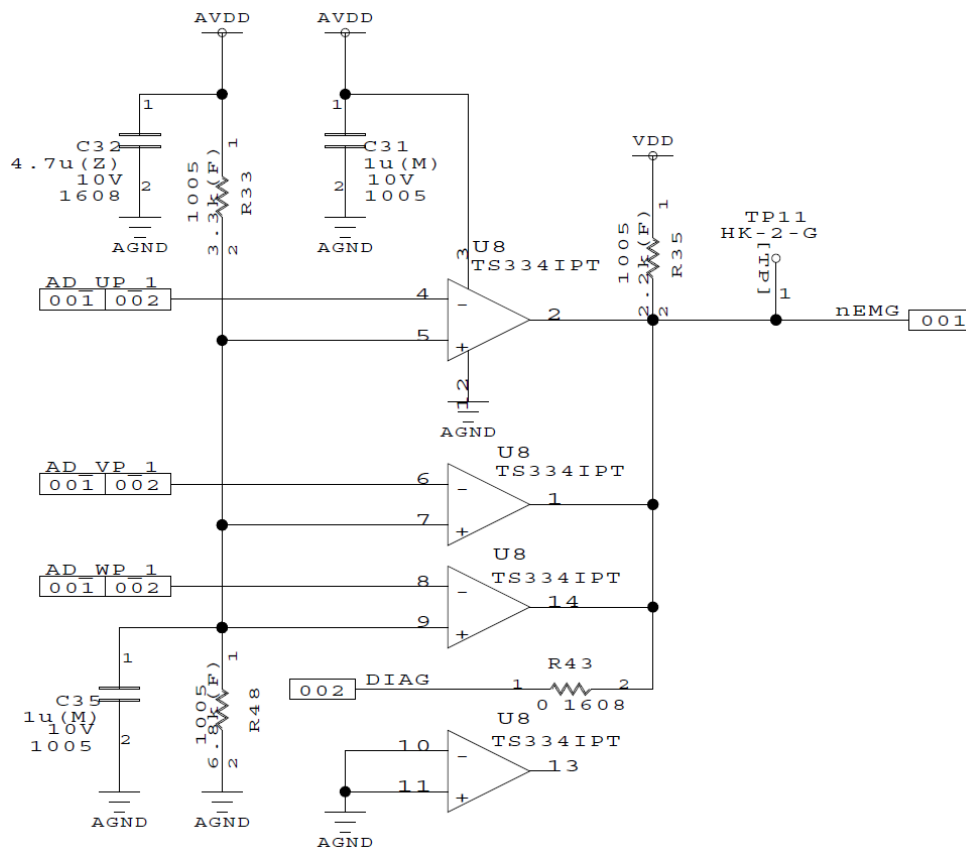


Fig. 3.5 Error Detection Circuit

The shunt current measurement signals (AD_UP_1, AD_VP_1, AD_WP_1) of each phase are used to detect an overcurrent error by using the comparator (U8). Since the overcurrent error output of each phase from the comparator and the diagnostic output (DIAG) signal of the intelligent power device (U1) are either open collector or open drain output, a wired OR output is generated by using the pull-up resistor (R35), and the resulting error detection signal (nEMG) is connected to

the EMG pin of the MCU. Whenever an error occurs in either one of them, nEMG signal is sent to the EMG pin of the MCU.

The + side reference voltage (approx. 3.37 V) of the comparator is produced by dividing AVDD (5 V) using R48 and R33. When the shunt current of each phase is i , the shunt current measurement voltage v input to each comparator is

$$v = 2.5 + i \times 0.1 \times \text{OpAmpGain}(3.0)$$

Therefore, when the shunt current of each phase becomes about 2.89 A or more, an error detection signal is output.

3.5. Motor Voltage Detection Circuit

Fig. 3.6 shows the motor voltage detection circuit.

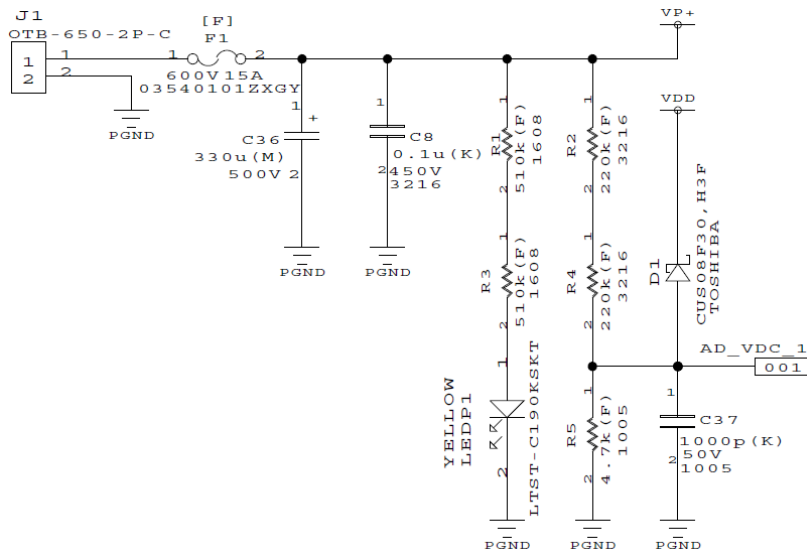


Fig. 3.6 Motor Voltage Detection Circuit

The motor voltage ($VP +1$) input from the motor power terminal (J1) is divided by the resistors (R2, R4, R5) and is input to the A/D converter of the MCU as the motor voltage signal (AD_VDC_1). The motor voltage signal input to the A/D converter is approximately $0.01 \times (VP+)$, i.e. approximately 1 % of the motor voltage.

Terms of Use

This terms of use is made between Toshiba Electronic Devices and Storage Corporation ("We") and Customer who downloads or uses this Reference Design. Customer shall comply with this terms of use. This Reference Design means all documents and data in order to design electronics applications on which our semiconductor device is embedded.

Section 1. Restrictions on usage

1. This Reference Design is provided solely as reference data for designing electronics applications. Customer shall not use this Reference Design for any other purpose, including without limitation, verification of reliability.
2. Customer shall not use this Reference Design for sale, lease or other transfer.
3. Customer shall not use this Reference Design for evaluation in high or low temperature, high humidity, or high electromagnetic environments.
4. This Reference Design shall not be used for or incorporated into any product or system whose manufacture, use, or sale is prohibited under any applicable laws or regulations.

Section 2. Limitations

1. We reserve the right to make changes to this Reference Design without notice.
2. This Reference Design should be treated as a reference only. WE ARE NOT RESPONSIBLE FOR ANY INCORRECT OR INCOMPLETE DATA AND INFORMATION.
3. Semiconductor devices can malfunction or fail. When designing electronics applications by referring to this Reference Design, Customer is responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of semiconductor devices could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Customer must also refer to and comply with the latest versions of all relevant our information, including without limitation, specifications, data sheets and application notes for semiconductor devices, as well as the precautions and conditions set forth in the "Semiconductor Reliability Handbook".
4. Designing electronics applications by referring to this Reference Design, Customer must evaluate the whole system sufficiently. Customer is solely responsible for applying this Reference Design to Customer's own product design or applications. WE ASSUME NO LIABILITY FOR CUSTOMER'S PRODUCT DESIGN OR APPLICATIONS.
5. WE SHALL NOT BE RESPONSIBLE FOR ANY INFRINGEMENT OF PATENTS OR ANY OTHER INTELLECTUAL PROPERTY RIGHTS OF THIRD PARTIES THAT MAY RESULT FROM THE USE OF THIS REFERENCE DESIGN. NO LICENSE TO ANY INTELLECTUAL PROPERTY RIGHT IS GRANTED BY THIS TERMS OF USE, WHETHER EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE.
6. THIS REFERENCE DESIGN IS PROVIDED "AS IS". WE (a) ASSUME NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (b) DISCLAIM ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO THIS REFERENCE DESIGN, INCLUDING WITHOUT LIMITATION, WARRANTIES OR CONDITIONS OF FUNCTION AND WORKING, WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.

Section 3. Terms and Termination

It is assumed that Customer agrees to any and all this terms of use if Customer downloads or uses this Reference Design. We may, at its sole and exclusive discretion, change, alter, modify, add, and/or remove any part of this terms of use at any time without any prior notice. We may terminate this terms of use at any time and without any cause. Upon termination of this terms of use, Customer shall eliminate this Reference Design. Furthermore, upon our request, Customer shall submit to us a written confirmation to prove elimination of this Reference Design.

Section 4. Export Control

Customer shall not use or otherwise make available this Reference Design for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). This Reference Design may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Act and the U.S. Export Administration Regulations. Export and re-export of this Reference Design is strictly prohibited except in compliance with all applicable export laws and regulations.

Section 5. Governing Laws

This terms of use shall be governed and construed by laws of Japan, without reference to conflict of law principle.

Section 6. Jurisdiction

Unless otherwise specified, Tokyo District Court in Tokyo, Japan shall be exclusively the court of first jurisdiction for all disputes under this terms of use.