

**1.6kW LLC Resonant  
AC-DC Converter for Servers**

**Design Guide**

**RD212-DGUIDE-01**

---

**Toshiba Electronic Devices & Storage Corporation**

## Table of Contents

<b>1. Introduction .....</b>	<b>4</b>
<b>2. Main Components Used .....</b>	<b>5</b>
2.1. Power MOSFET TK024N60Z1 .....	5
2.2. Power MOSFET TK080N60Z1 .....	6
2.3. Power MOSFET TK125A60Z1 .....	7
2.4. Power MOSFET TPH2R408QM .....	8
2.5. SiC Schottky Barrier Diode TRS8E65H .....	9
2.6. Microcontroller TPM372FWUG.....	10
<b>3. Outline of Interleaved PFC Circuit and 3-Phase LLC Resonant DC-DC Converter .....</b>	<b>11</b>
3.1. Interleaved PFC Circuit .....	11
3.2. 3-Phase LLC Resonant DC-DC Converter Circuit .....	14
<b>4. 1.6kW LLC Resonant AC-DC Converter for Servers for Servers .....</b>	<b>16</b>
4.1. Specifications .....	17
4.2. AC Line Circuit .....	18
4.3. Active Bridge Circuit.....	20
4.4. Interleaved PFC Circuit .....	21
4.5. LLC Circuit Design .....	27
4.6. 3-Phase LLC Resonant DC-DC Converter Design.....	34

4.6.1. Calculation of Output Voltage and Output Power of Individual Transformers.....	34
4.6.2. Transformer Design (Resonant Design) .....	35
4.6.3. Resonant Circuit Voltage Gain Confirmation.....	41
4.6.4. Resonant Transformer Current Calculation and ZVS (Zero Volt Switching) Confirmation .....	46
4.7. ORing Circuit .....	48

## 1. Introduction

This Design Guide describes the design methodology of the 1.6kW LLC Resonant AC-DC Converter for Servers (hereinafter referred to as "this design").

With the increase in the amount of information handled daily, the number of data centers is increasing, and the size of data centers is also increasing. Therefore, reducing the power consumption of data centers has become a global issue. Various measures are being considered to reduce power consumption in data centers, and one of them is the use of 48V bus voltages in servers used in data centers, and 48V servers have become increasingly popular in recent years. This design is an AC-DC converter that takes 100V/200V AC input and outputs 54.5V DC to a 48V server.

In order to improve power supply efficiency, following topologies have been used, an active bridge circuit that uses MOSFETs instead of a diode bridge, an interleaved PFC circuit, and a 3-phase LLC resonant DC-DC converter. This allowed to achieve an efficiency that exceeds the Titanium standard of 80 PLUS\* at 230V input condition.

Toshiba's latest power MOSFETs like [TK024N60Z1](#) mounted on the active bridge section, [TK080N60Z1](#) mounted on the interleaved PFC section, [TK125A60Z1](#) mounted on the primary side of the 3-phase LLC resonant DC-DC converter, and [TPH2R408QM](#) mounted on the secondary side of the 3-phase LLC resonant DC-DC converter and ORing section, and 650V SiC Schottky barrier diodes [TRS8E65H](#) mounted on the interleaved PFC contributes to reduced losses and high-efficiency operation.

Toshiba's [TMPM372FWUG](#) microcontroller is used to generate the 3-phase control signal for the LLC resonant DC-DC converter.

\*80 PLUS: It is the efficiency standard for power supply units for computers such as servers, and Titanium is the name of the highest standard.

## 2. Main Components Used


This chapter describes the main components used in this design.

### 2.1. Power MOSFET TK024N60Z1

600V withstand voltage N-channel MOSFETs [TK024N60Z1](#) are used as switching elements of active bridge circuit instead of the diode bridge circuits. The main features of TK024N60Z1 are as follows.

- Low drain-source on-resistance:  $R_{DS(ON)} = 0.02\Omega$  (Typ.)
- High-speed switching properties with lower capacitance.
- Enhancement mode:  $V_{th} = 3$  to  $4V$  ( $V_{DS} = 10V$ ,  $I_D = 3.84mA$ )

#### Appearance and Terminal Layout

 


**Fig. 2.1 Appearance and Terminal Layout of TK024N60Z1**

### 2.2. Power MOSFET TK080N60Z1

600V withstand voltage N-channel MOSFETs [TK080N60Z1](#) are used as the switching elements of the PFC circuit. The main features of TK080N60Z1 are as follows.

- Low drain-source on-resistance:  $R_{DS(ON)} = 0.067\Omega$  (Typ.)
- High-speed switching properties with lower capacitance.
- Enhancement mode:  $V_{th} = 3$  to  $4V$  ( $V_{DS} = 10V$ ,  $I_D = 1.17mA$ )

#### Appearance and Terminal Layout

 


**Fig. 2.2 Appearance and Terminal Layout of TK080N60Z1**

### 2.3. Power MOSFET TK125A60Z1

600V withstand voltage N-channel MOSFETs [TK125A60Z1](#) are used as the primary-side switching elements of the LLC resonant DC-DC converter circuit. The main features of TK125A60Z1 are as follows.

- Low drain-source on-resistance:  $R_{DS(ON)} = 0.105\Omega$  (Typ.)
- High-speed switching properties with lower capacitance.
- Enhancement mode:  $V_{th} = 3$  to  $4V$  ( $V_{DS} = 10V, I_D = 0.73mA$ )

#### Appearance and Terminal Layout

 


**Fig. 2.3 Appearance and Terminal Layout of TK125A60Z1**

### 2.4. Power MOSFET TPH2R408QM

80V withstanding voltage N-channel MOSFETs [TPH2R408QM](#) are used as the secondary-side switching elements of the LLC Resonant DC-DC converter circuit and the switching element of the output ORing circuit. The main features of TPH2R408QM are as follows.

- High-speed switching.
- Small gate charge:  $Q_{SW} = 28\text{nC}$  (Typ.)
- Small output charge:  $Q_{OSS} = 90\text{nC}$  (Typ.)
- Low drain-source on-resistance:  $R_{DS(ON)} = 1.9\text{n}\Omega$  (Typ.) ( $V_{GS} = 10\text{V}$ )
- Low leakage current:  $I_{DSS} = 10\mu\text{A}$  (Max.) ( $V_{DS} = 80\text{V}$ )
- Enhancement mode:  $V_{th} = 2.5$  to  $3.5\text{V}$  ( $V_{DS} = 10\text{V}$ ,  $I_D = 1.0\text{mA}$ )

#### Appearance and Terminal Layout

 


**Fig. 2.4 Appearance and Terminal Layout of TPH2R408QM**



## 2.5. SiC Schottky Barrier Diode TRS8E65H

650V system diodes [TRS8E65H](#) are used as the rectifiers in the PFC circuit. The main features of TRS8E65H are as follows.

 - Chip design of 3<sup>rd</sup> generation
- Low forward voltage:  $V_F = 1.2V$  (Typ.)
- Low total capacitive charge :  $Q_c = 22nC$  (Typ.)
- Low reverse current:  $I_R = 1.5\mu A$  (Typ.)


 


**Fig. 2.5 Appearance and Terminal Layout of TRS8E65H**

### 2.6. Microcontroller TPM372FWUG

Microcontroller [TPM372FWUG](#) is used in the 3-phase control-signal generator of the 3-phase LLC resonant DC-DC converter. The main features of TPM372FWUG are as follows.

- Arm Coretex-M3 core-equipped, maximum operating frequency: 80MHz (operating temperature - 40 to 85°C)
- 16-bit timer/event counter: 8 channels
- 5V voltage-operation
- Tiny package: LQFP44

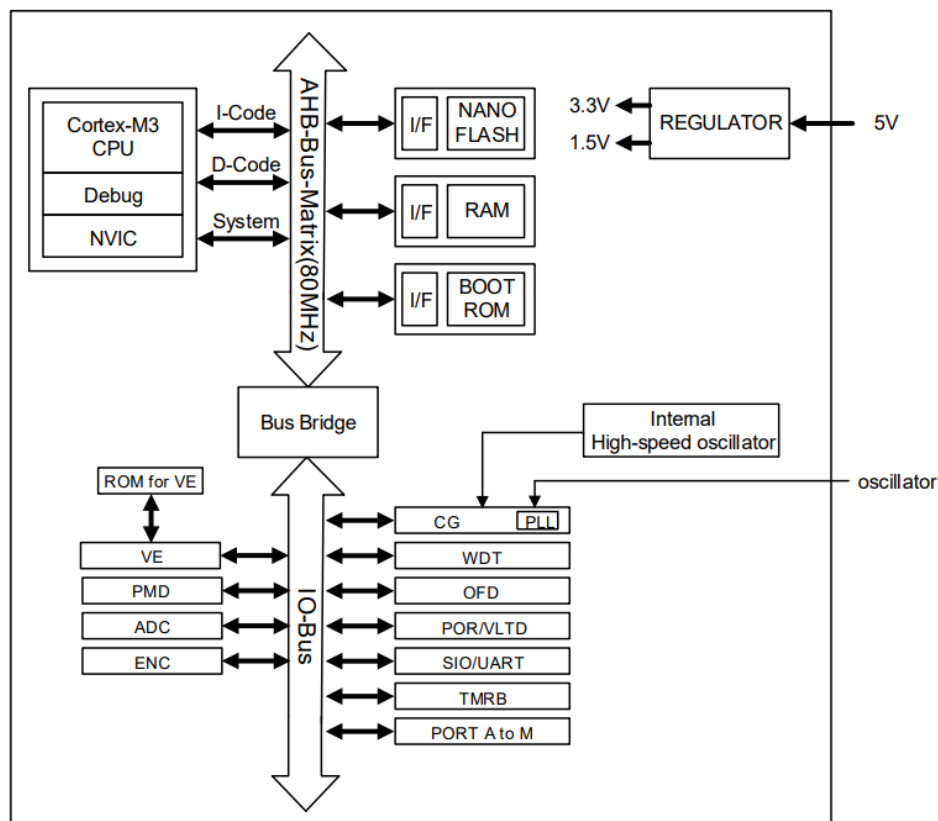

**Fig. 2.6 Appearance and Block Diagram of TPM372FWUG**

## 3. Outline of Interleaved PFC Circuit and 3-Phase LLC Resonant DC-DC Converter

This chapter describes the basic concepts of the interleaved PFC and 3-phase LLC resonant DC-DC converters used in this design.

### 3.1. Interleaved PFC Circuit

Interleaved PFC circuits, in which multiple step-up converter circuits are arranged in parallel, are becoming increasingly popular in medium to large power supplies that exceed 500W. In principle, three or more phases are possible, but a two-phase system as shown in Fig. 3.1 is common. Here, a circuit consists with  $L_1$ ,  $Q_1$  and  $D_5$  on the Fig. 3.1 is named PFC Circuit 1, and a circuit consists with  $L_2$ ,  $Q_2$  and  $D_6$  on the Fig. 3.1 is named PFC Circuit 2. Since each phase is switched by shifting the phase by 180 degrees, the frequency of the synthesized inductor current is apparently double the frequency of the switching element.

Fig. 3.1 shows the current paths when the input AC voltage is positive (Fig. 3.1 (a) and (b)), and the current paths when it is negative (Fig. 3.1 (c) and (d)). The input current is always the sum of the currents of the two  $L_1$ ,  $L_2$ , and the input ripple current is reduced because the phase is shifted by 180 degrees. The interleaving method enables loss to be dispersed into two elements, facilitating thermal design.


The following describes the operation of the interleaved PFC circuit. For simplicity, consider the case where the on-duty of each phase is less than 50% (when the switching element of one phase is on, and the switching element of the other phase is off).

#### During Positive AC Input


The PFC Circuit 1 stores energy on  $L_1$  when  $Q_1$  is on (and  $Q_2$  is off). At this time, the PFC circuit 2 draws current from the energy stored in  $L_2$  (Fig. 3.1 (a)). And PFC circuit 2 stores energy in  $L_2$  when  $Q_2$  is on ( $Q_1$  is off). At this time, the PFC circuit 1 draws current from the energy stored in  $L_1$  (Fig. 3.1 (b)).

#### During Negative AC Input

The operation after rectification of AC input is the same as the operation during positive AC input. Fig. 3.1 (c) shows the operation when  $Q_1$  is on ( $Q_2$  is off), and Fig. 3.1 (d) shows the operation of when  $Q_2$  is on (and  $Q_1$  is off).

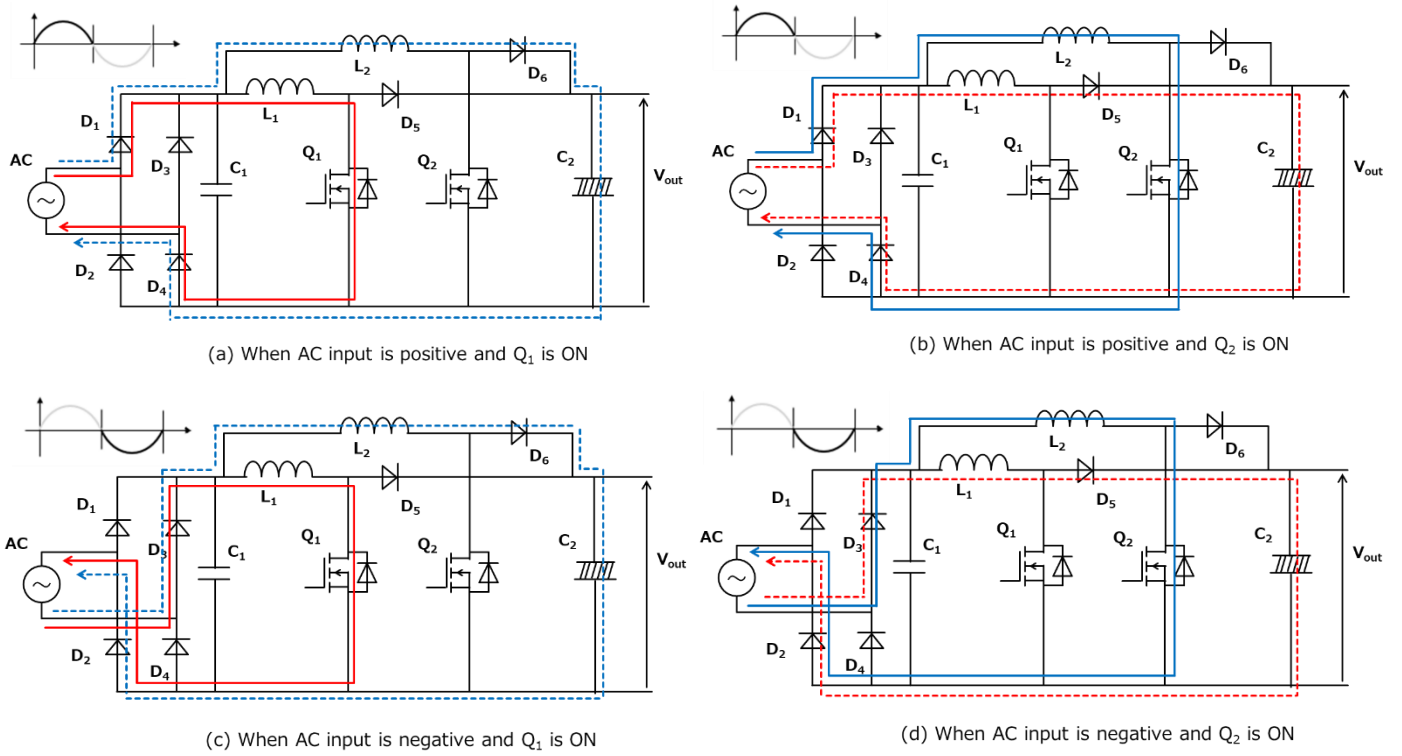

**Fig. 3.1 Interleaved PFC Circuit Operation**

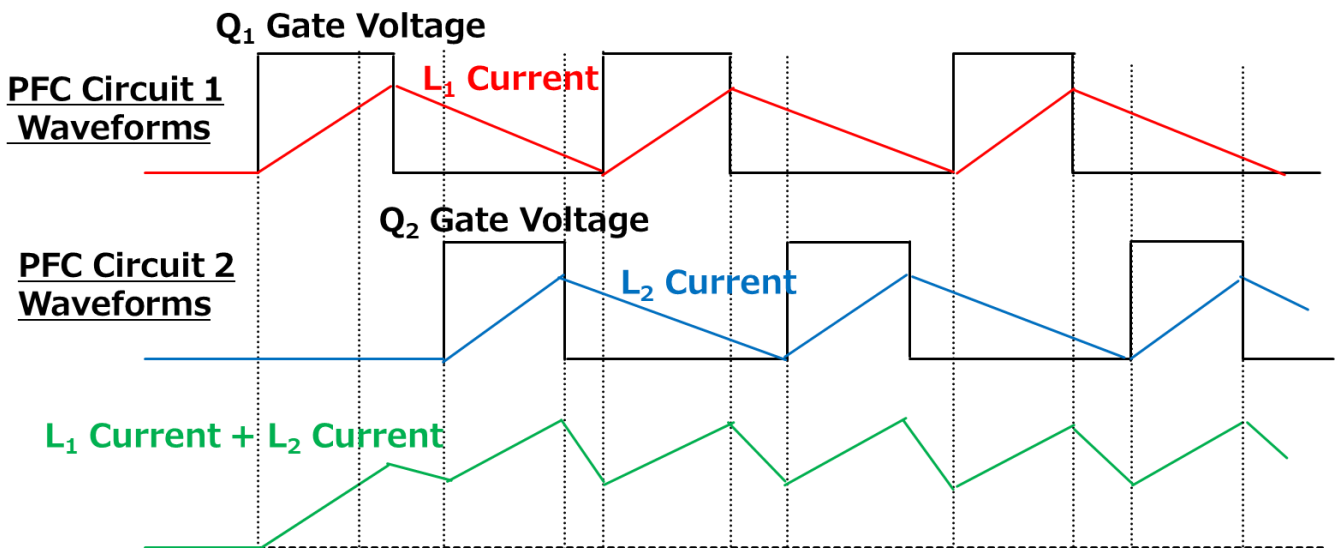


**Fig. 3.2 Interleaved PFC Current Waveforms**



### 3.2. 3-Phase LLC Resonant DC-DC Converter Circuit


Fig. 3.3 shows the configuration of the 3-phase LLC resonant DC-DC converter used in this design. Three half-bridge LLC converters are arranged in parallel on the primary-side, and the secondary-side terminals of the transformer are connected in Y configuration. By adopting this configuration, a 1U sized system using a general-purpose transformer achieves 1.6kW power.

 


**Fig. 3.3 3-phase LLC Resonant DC-DC Converter**

This section outlines the operation of the 3-phase LLC resonant DC-DC converter. Each phase operates at a phase difference of 120 degrees, and the current on the primary-side of the transformer has a waveform equivalent to 3-phase AC. Fig. 3.4 (a) shows an image of the transformer's primary-side current. The actual current waveform is not a sine wave, but it will be described with an image of 3-phase AC. The positive and negative currents shown here indicate the direction of the current flowing in the transformer's primary-side (the direction in which the primary-side high-side MOSFET turns on and the current flows from the top to the bottom of the primary-side transformer winding is assumed to be positive). Fig. 3.4 (b) shows the current paths of secondary-side rectifiers #1, #2, and #3 when LLC circuit #1 is positive and circuits #2 and #3 are negative, as shown in Fig. 3.4 (a). The primary-side and secondary-side high-side/low-side MOSFETs are switched on and off in conjunction, while the secondary-side rectifier circuits #1, #2, and #3 operate in conjunction with one another.

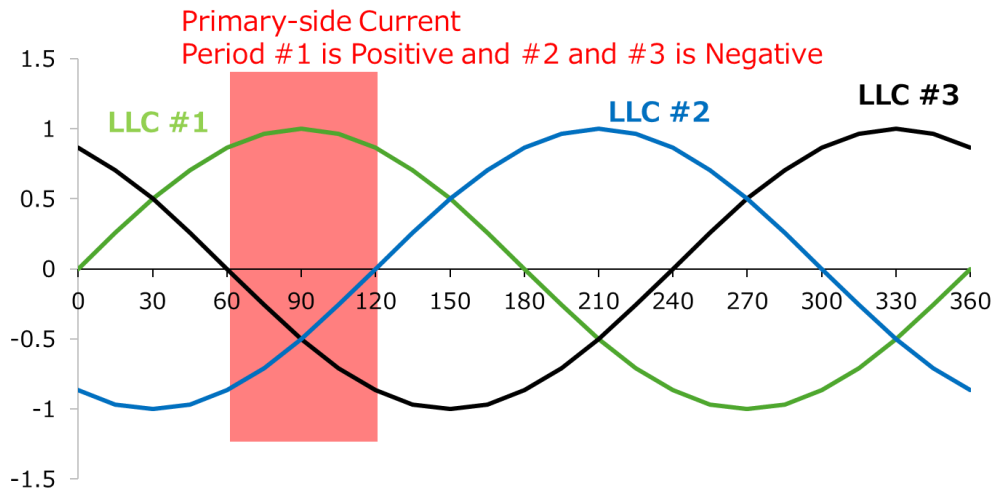The output voltage is twice the voltage between the transformer secondary windings. The voltage applied to the secondary-side MOSFETs is 1/2 of the output voltage, and devices with lower withstand voltage than typical LLC resonant DC-DC converters can be used.



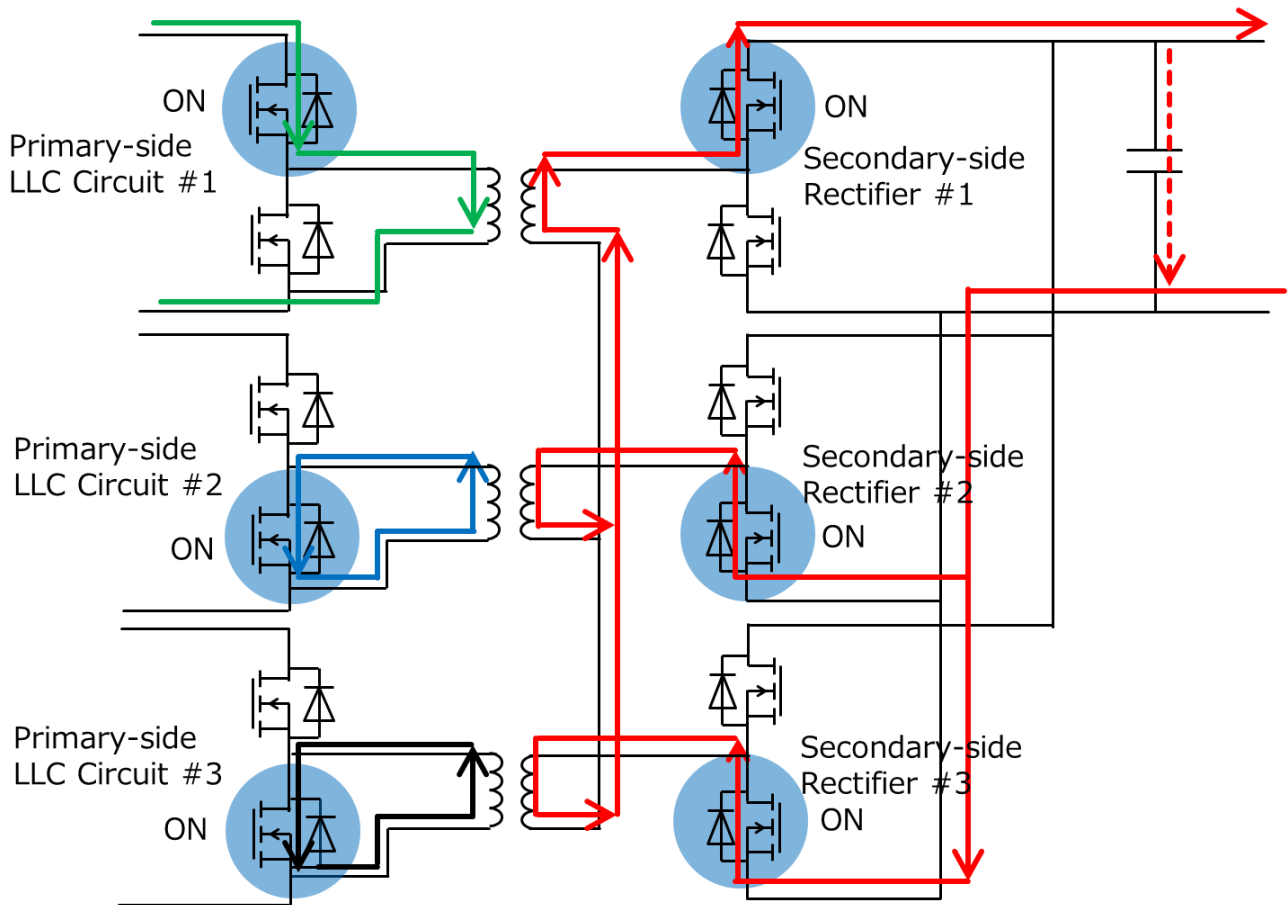(a) Image of Transformer's Primary-Side Current




(b) Current Path in Secondary-Side Rectifiers

Fig. 3.4 Operation of 3-phase LLC Resonant DC-DC Converter


## 4. 1.6kW LLC Resonant AC-DC Converter for Servers for Servers

This chapter provides an overview of the configuration of this design and the circuit design of each part. Fig. 4.1 shows the functional configuration diagram of this design, and Fig. 4.2 shows the circuit block diagram.

DC 390V is generated from the AC power supplies of 100V and 200V systems through an active-bridge circuit that uses MOSFET and an interleaved PFC circuit in a two-phase configuration. And this DC 390V is converted into DC 54.5V using a 3-phase LLC resonant DC-DC converter which is then outputs it via an ORing circuit. The 3-phase LLC resonant DC-DC converter is controlled using a conventional single-phase LLC controller, and its output is used by a MCU to generate MOSFET drive signals that differ in phase by 120 degrees.

 

**Fig. 4.1 Functional Configuration Diagram**

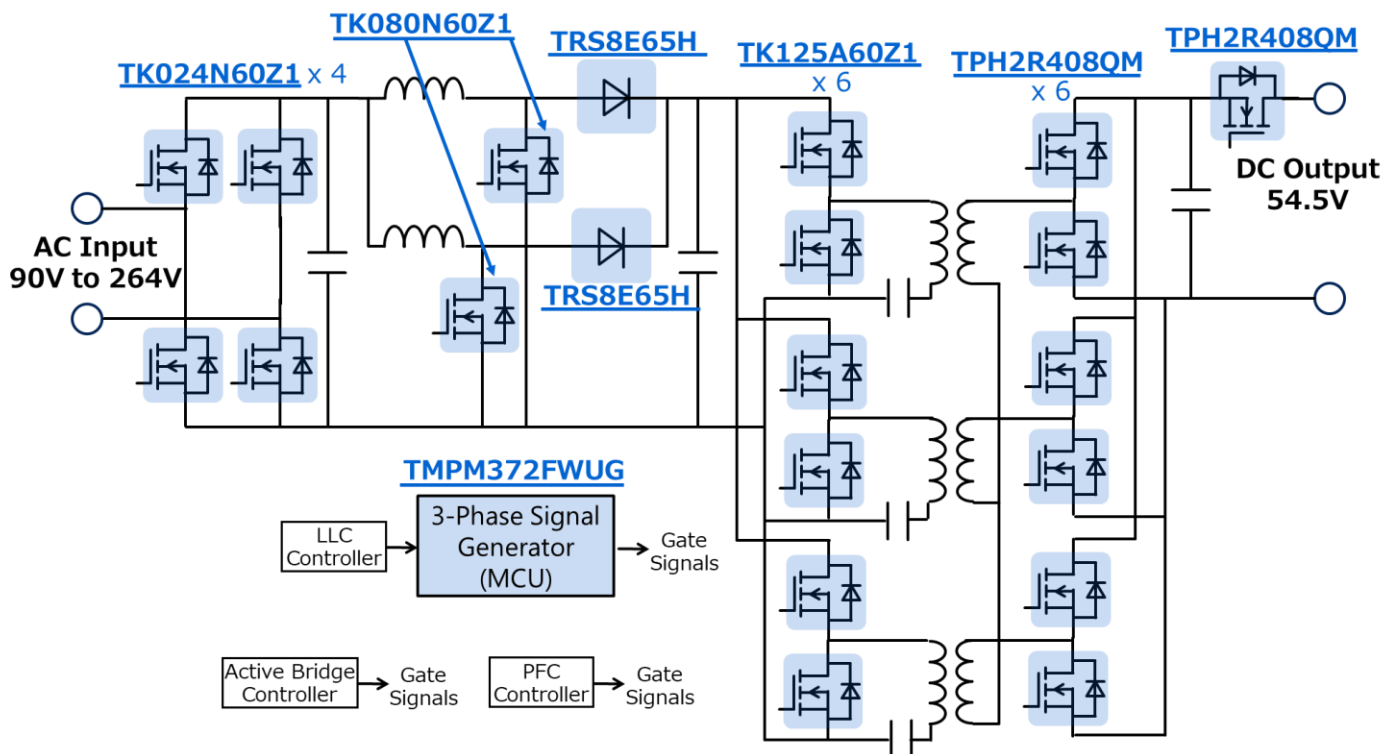

**Fig. 4.2 Circuit Block Diagram**



### 4.1. Specifications


Table 4.1 lists the main specifications of this design.

**Table 4.1 Specifications of This Design**

Item	Conditions	Min.	Typ.	Max.	Unit
<b>Input characteristics</b>					
AC input voltage (rms)		90		264	V
AC input current (rms)	Vin = AC 90V, Iout = 20A			12	A
Input frequency		47		63	Hz
<b>Internal characteristics (Interleaved PFC circuit)</b>					
Output voltage			390		V
Maximum output power	Vin = AC 230V			1.77	kW
	Vin = AC 115V			0.89	kW
Switching frequency			62.5		kHz
<b>Output characteristics (3-phase LLC resonant DC-DC converter circuit)</b>					
Output voltage		51.7	54.5	57.3	V
Output current	Vin = AC 230V			29.4	A
	Vin = AC 115V			14.7	A
Maximum output power	Vin = AC 230V			1.6	kW
	Vin = AC 115V			0.8	kW
Output ripple voltage	Ta = 25°C			2180	mV
<b>Other</b>					
Protective functions	Output overvoltage protection, output overcurrent protection, output short-circuit protection, and overheat protection				
Board layer configuration	Main board: FR-4 4-layer structure, copper foil thickness 70μm (all layers) Active bridge circuit board: FR-4 2-layer configuration, copper foil thickness 70μm PFC control board, LLC control board: FR-4 2-layer configuration, copper foil thickness 35μm				

### 4.2. AC Line Circuit

This section describes the design of AC line-circuits. Fig. 4.3 shows AC line-circuit.

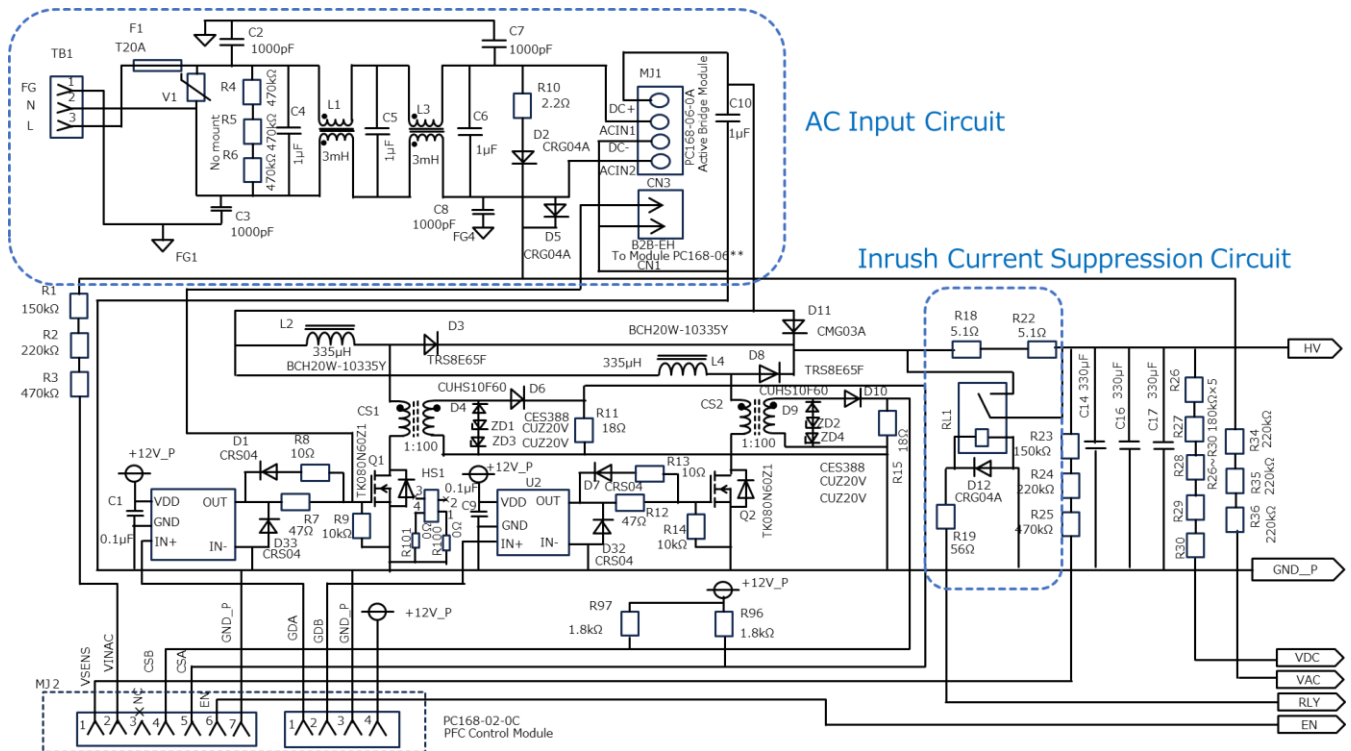

**Fig. 4.3 AC Line Circuit**

#### Fuse

To cut-off AC line when excessive current flows through AC line, the fuse F1 is installed. Select a fuse using the max. value of the rms current value of AC line  $ACin_{peakrms}$ . The maximum power  $P_{out}$ , total power supply efficiency  $\eta$ , the power factor PF, and the minimum value of the rms value of AC line voltage  $VinAC_{min}$  are used to calculate the maximum value of the rms current value of AC line  $ACin_{peakrms}$  using the following equation.

$$ACin_{peakrms} = \frac{P_{out}}{\eta \times PF \times VinAC_{min}}$$

If  $VinAC_{min} = 90V$ ,  $P_{out} = 800W$ ,  $\eta = 90\%$ , and  $PF = 99\%$ , then  $ACin_{peakrms} = 10A$ .

In this design, 20A fuse is selected considering the margins.

When selecting a fuse, in addition to the above max. current, the inrush current which flows when AC power supply is turned on, and whether the product has acquired the safety standard to be complied with, etc. must also be considered.

**Varistor**

A metal-oxide varistor (V1) is used for protection from the surge-voltage that might appear on the AC line because of inductive lightning. A varistor is selected based on the AC line voltage. Since the maximum AC line voltage of this design is 264V in rms value and 373V in peak value, a varistor with the maximum allowable circuit voltage of 420V (AC rms value) and the varistor voltage of 680V is selected considering the margins.

When selecting a varistor, it is necessary to consider not only the maximum allowable circuit voltage and varistor voltage, but also the surge current tolerance, energy tolerance, etc. In addition, since the varistor failure mode has many short modes, a fuse is inserted before the varistor (on the AC input side).

**EMI suppression components**

The Y capacitors (C2, C3, C7, C8) and the common mode chokes (L1, L3) are installed to suppress common mode noise, and the X capacitors (C4, C5, C6) are installed to suppress differential noise. Since the noise-levels are affected by PCB layout/enclosure construction, thus these components must be changed, removed, or added according to the requirement. Note that this design does not have an adequate Y capacitor because there is no enclosure. When designing a system with a chassis, install a sufficient Y capacitor as a countermeasure against common mode noise. Increasing the capacitance of the Y capacitor will increase the leakage current, so it is necessary to check whether the system satisfies the required safety standards.


**Inrush current suppression component**

The fuse resistors (R18, R22) and the relay (RL1) are installed to suppress inrush current when AC power is turned on. When AC power is turned on, RL1 opens and AC current flows to R18, R22, suppressing the inrush current. After AC power supply is turned on, RL1 closes when the specified conditions are met. When RL1 conducts, R18, R22 that was suppressing AC current are short-circuited, reducing power dissipation during operation. It is necessary to select a fuse resistor that can withstand the inrush current. Also, confirm that the conditions and timing for opening and closing the relay satisfy the required specifications.

**4.3. Active Bridge Circuit**

For full-wave rectification before PFC circuit, an active-bridge circuit using four power MOSFETs TK024N60Z1 was adopted to improve the power supply efficiency. Fig. 4.4 shows the active bridge circuit.

MOSFETs are controlled by the TEA2209T (made by NXP, hereinafter referred to as the active bridge controller). For more information about the Active Bridge Controller, refer to TEA2209T datasheet and related documentation. The active bridge controller senses the polarity of AC power supply between terminals L and R and turns on/off the diagonal-pair MOSFETs according to the polarity.

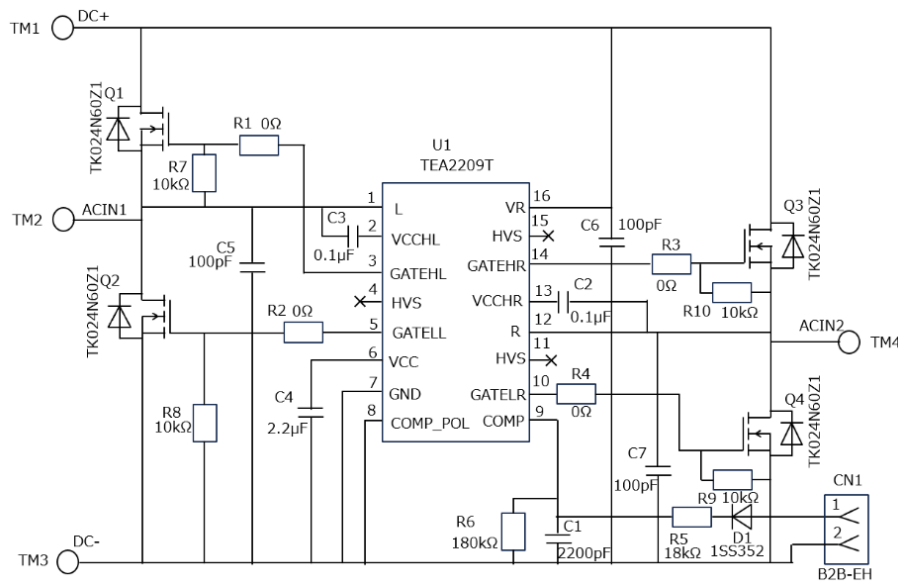

**Fig. 4.4 Active Bridge Circuit**

**X capacitor discharge**

The discharging resistors  $R_{dis}$  (R4, R5, R6) of the X capacitors  $C_x$  (C4, C5, C6) shown in Fig. 4.3 are not mounted. Discharging of the X capacitors  $C_x$  is performed by the active bridge controller mentioned above. When the mains voltage is disconnected from the power supply, the capacitor  $C_{VCC}$  (C4 in Fig. 4.3) that has been charged to  $V_{reg}$ , is discharged with an internal biased current  $I_{bias}$  (23μA). When VCC pin drops below  $V_{dis}$  (disable voltage 9.7V), the X capacitor starts discharging at 2mA current. The following table shows  $t_d$  waiting time before the X capacitor starts discharging.


$$t_d = \frac{C_{VCC}(V_{reg} - V_{dis})}{23 \mu A} = 0.11E6 \times C_{VCC}$$

Since  $C_{VCC}$  in this design uses the default value of 2.2μF,  $t_d$  is approximately 0.24 seconds.


**4.4. Interleaved PFC Circuit**

In this design, interleaved PFC circuit is configured using UCC28070 (made by Texas Instruments, hereinafter referred to as PFC controller). The basic design items are described below. Refer to UCC28070 datasheet and related documentation for detailed description of design around PFC controller.

Fig. 4.5 shows the interleaved PFC circuit on the mainboard and Fig. 4.6 shows PFC controller peripherals on the PFC control board.

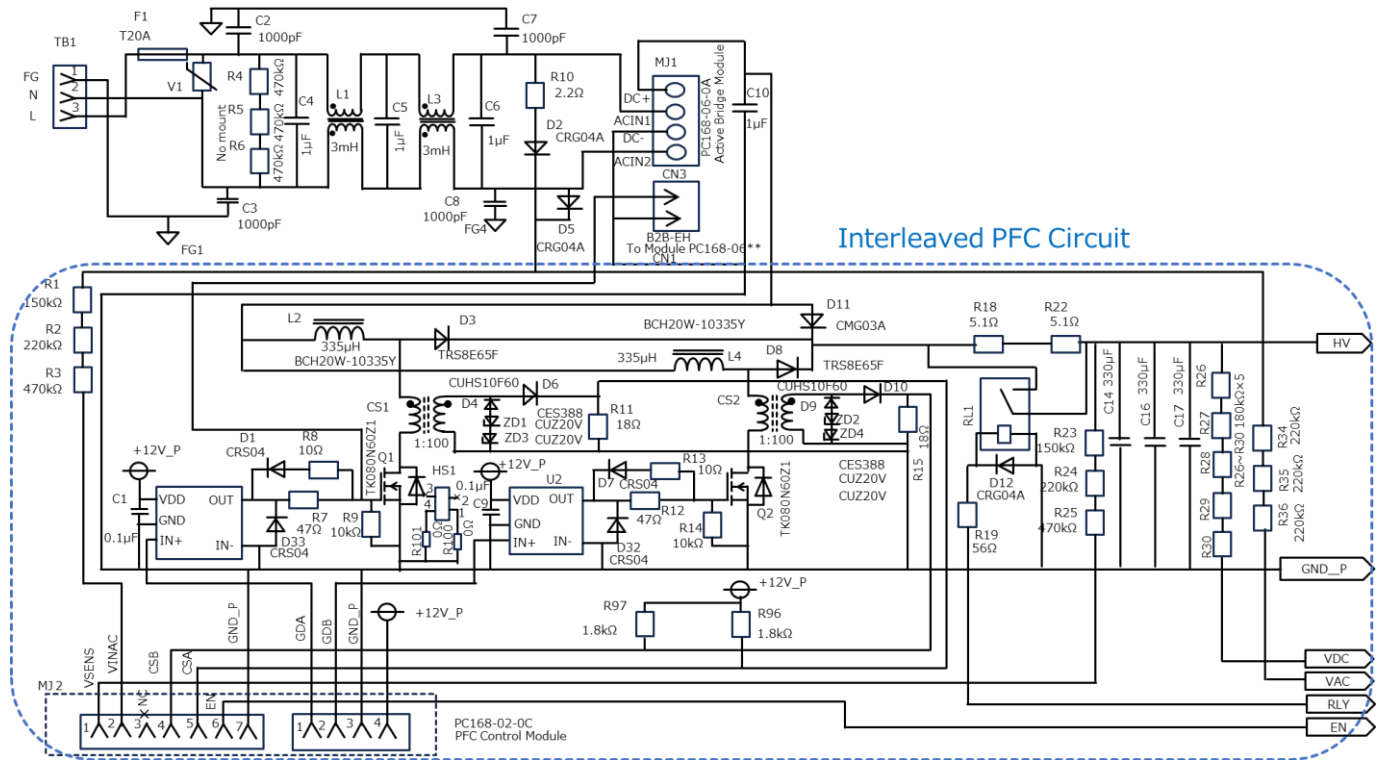

**Fig. 4.5 Interleaved PFC Circuit**

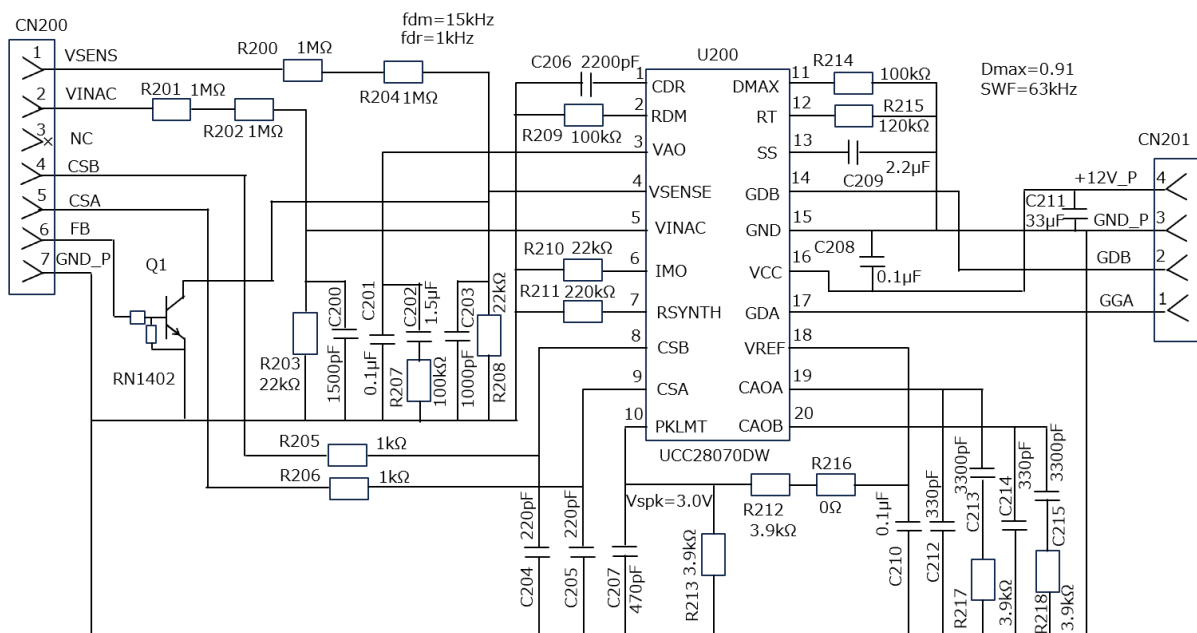


**Fig. 4.6 PFC Controller Peripheral Circuit**

### Output voltage setting

The output voltage setting circuit is shown in Fig. 4.7. Set the output-voltage ( $V_{out\_PFC}$ ) with the resistors (R23, R24, R25, R200, R204, R208) located on the main board and PFC control board. PFC control ensures that the output-sense-voltage ( $V_{VSENSE}$ ) divided by these resistors matches  $V_{SENSE}$  voltage (3V) of the PFC controller. The output voltage ( $V_{out\_PFC}$ ) at  $T_a = 25\text{ }^\circ\text{C}$  is calculated using the following equation by using the bias current  $I_{bias\_PFC}$  (250nA).

$$V_{out\_PFC} = \frac{V_{SENSE} \text{ voltage} \times (R23 + R24 + R25 + R200 + R204 + R208)}{R208} + I_{bias\_PFC} \times (R23 + R24 + R25 + R200 + R204)$$

In this design, 840k $\Omega$  is used for total resistance of R23 to R25, 1M $\Omega$  for R200, 1M $\Omega$  for R204, and 22k $\Omega$  for R208, and therefore  $V_{out\_PFC}$  is set as 390V. The above resistance can be changed as necessary to set the desired output voltage.

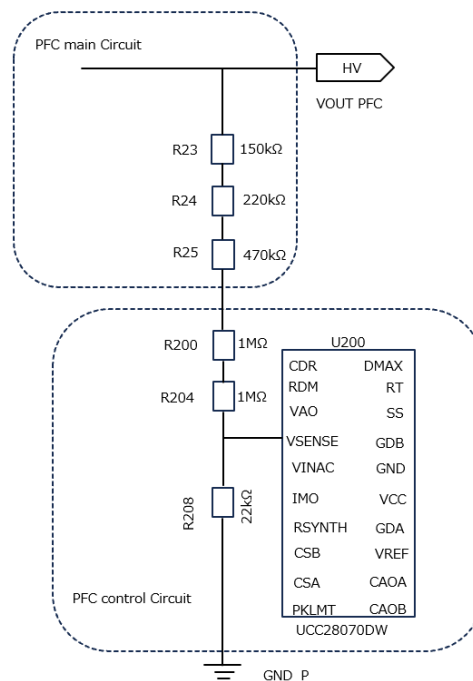

**Fig. 4.7 Output Voltage Setting Circuit**

### Switching frequency, maximum duty setting

The switching frequency and the max duty of PWM are set by RT pin and the resistor connected to DMAX pin shown in Fig. 4.8. RT Resistor R<sub>RT</sub> (R215) sets PWM Frequency (f<sub>PWM</sub>) and is calculated by the following equation:

$$R_{RT}(k\Omega) = \frac{7500}{f_{PWM}(kHz)}$$


$$f_{PWM}(kHz) = \frac{7500}{R_{RT}(k\Omega)}$$

This design uses 120kΩ for R215 and sets f<sub>PWM</sub> = 62.5kHz.

The max. duty D<sub>MAX</sub> of PWM is calculated from R<sub>RT</sub> and D<sub>MAX</sub> resistor R<sub>DMX</sub> (R214) by the following equation.

$$R_{DMX} = R_{RT} \times (2 \times D_{MAX} - 1)$$


This design uses 100kΩ for R214 and therefore sets D<sub>MAX</sub> = 0.916.

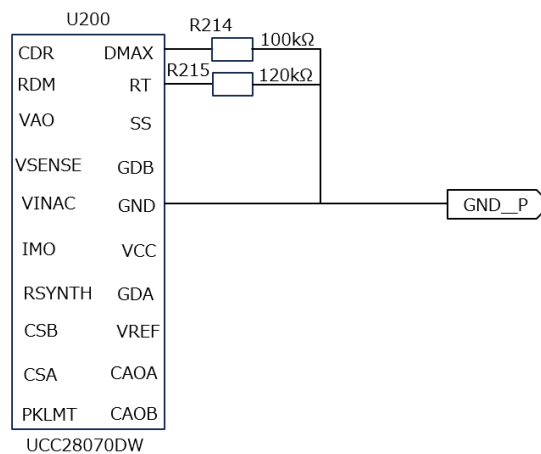

**Fig. 4.8 Switching Frequency and Maximum Duty Setting Circuit**

### Gate drive circuit

Fig. 4.9 shows the gate drive circuit. The gate-driver design affect power-efficiency and EMI (noises). Generally, there is a trade-off between power supply efficiency and EMI, and both need to be well balanced. To adjust EMI, adjust the resistance of the gate-series resistor (R7, R8). The turn-on speed of MOSFET is determined by R7. During turn on, R8 will not have any effect because of D1. And the turn-off speed is determined by the parallel resistances of R7 and R8. If only turn-on speed needs to be changed, both R7 and R8 must be adjusted. If only turn-off speed needs to be changed, and if it is possible to adjust it only using R8, then the turn-on speed will not be affected. Increasing the gate-resistance may reduce the switching speed of MOSFET, which may also reduce the power-supply efficiency. Check that the power supply efficiency specification and heat radiation specification satisfy the required specification.

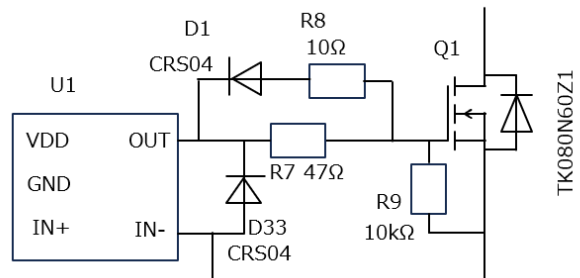

**Fig. 4.9 Gate Drive Circuit**

### Inductor

In the interleaved PFC circuit shown in Fig. 4.5, the inductance value L of the inductor L2 is set using the following items in the input 100V system. The same applies to the inductor L4.

1. Maximum output power ( $P_{out}$ ): 800W
2. Min. input AC rms ( $V_{inAC_{min}}$ ): 90V
3. Total power conversion efficiency of this design: 90%
4. Power factor (PF) of this design: 99%
5. PFC output-voltage ( $V_{out\_PFC}$ ): 390V
6. Switching frequency ( $f_{PWM}$ ): 63kHz

The peak input current  $ACin_{peak}$  of the input AC is calculated by the following equation.

$$\begin{aligned}
 ACin_{peak} &= \frac{P_{out} \times \sqrt{2}}{\eta \times PF \times V_{inAC_{min}}} \\
 &= \frac{800 \times \sqrt{2}}{0.9 \times 0.99 \times 90} = 14.11
 \end{aligned}$$



Assuming that  $\Delta IL$  is the allowable current ripple of the inductor in each phase, L is calculated as follows:

$$L = \frac{\sqrt{2} \times VinAC_{min} - \frac{2 \times VinAC_{min}^2}{Vout\_PFC}}{f_{PWM} \times \Delta IL}$$

Here, if the  $\Delta IL$  is 60% of the peak current i.e. 7.06A, then L is calculated to be 193 $\mu$ H from the above equation. A 335 $\mu$ H inductor is selected for this design.

In addition, the peak current  $IL_{peak}$  flowing through the inductor is calculated using AC line peak input current  $ACin_{peak}$  as follows.

$$IL_{peak} = \frac{ACin_{peak}}{2} + \frac{\Delta I}{2}$$

Since  $ACin_{peak} = 14.11A$  and  $\Delta I = 4.01A$ ,  $IL_{peak}$  becomes 9.06A. Therefore, a 10A rated inductor is selected in this design.

### Output capacitors

Fig. 4.10 shows the position of the output capacitor. The output capacitance  $Cout\_PFC$  (C14, C16, C17) is calculated based on holdup time requirements.

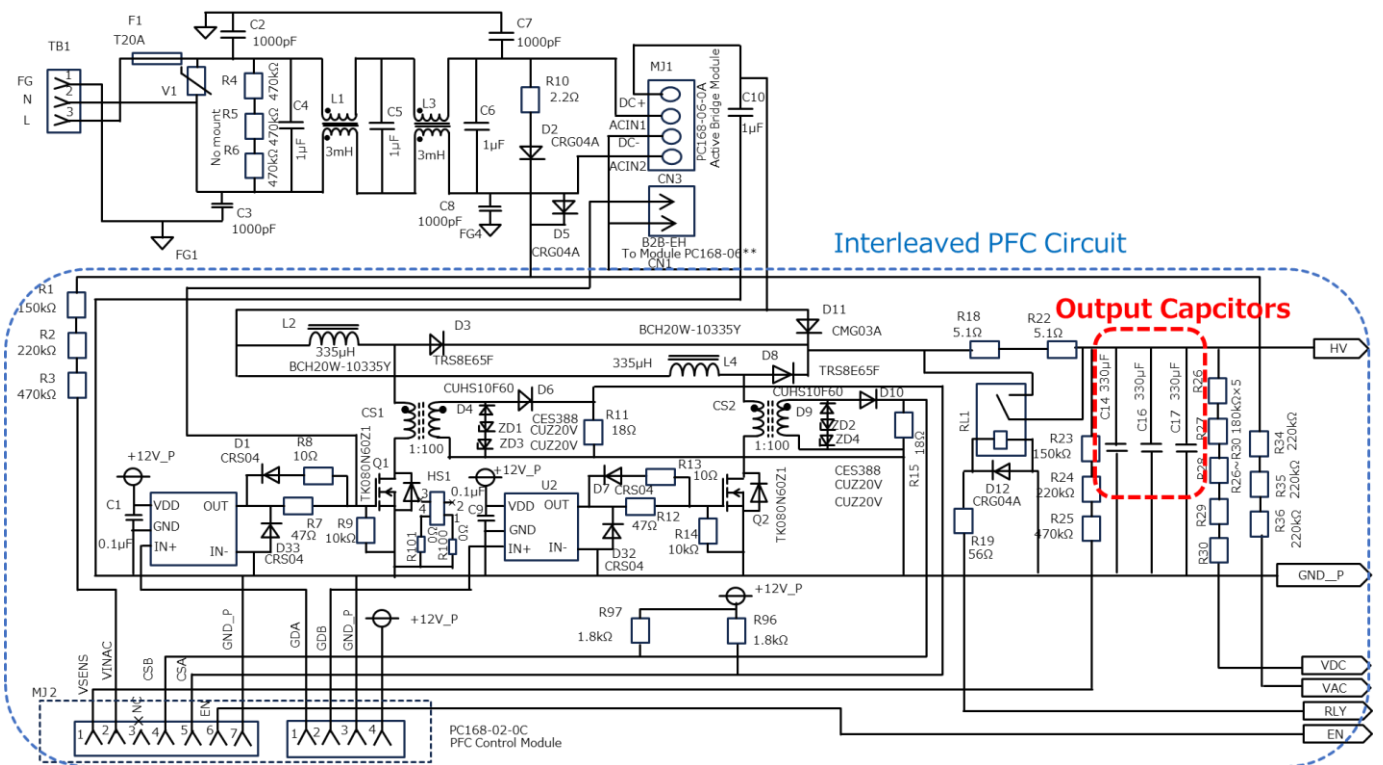


Fig. 4.10 Output Capacitors

The hold-up time  $T_{hold}$  is calculated using  $C_{out\_PFC}$ , output voltage  $V_{out\_PFC}$ , output lower limit voltage  $V_{out\_PFC\_min}$ , maximum output power  $P_{out\_max}$ , and LLC power supply efficiency  $\eta_2$  using the following equation.

$$T_{hold} = C_{out\_PFC} \times \frac{(V_{out\_PFC}^2 - V_{out\_PFC\_hold}^2) \times \eta_2}{2 \times P_{out\_max}}$$

When  $V_{out\_PFC} = 390V$ ,  $V_{out\_PFC\_min} = 300V$ ,  $\eta_2 = 94\%$ ,  $P_{out\_max} = 1600W$ , and  $T_{hold}$  is 10ms which is the half cycle of AC 50Hz, the  $C_{out\_PFC}$  becomes 549 $\mu F$ . In this design, three 330 $\mu F$  capacitors are arranged in parallel to make 990 $\mu F$ .

In addition, if there is the required specification for the output ripple, set it by the following method.

1. Find the capacitance value of the output capacitor ( $C_{out\_PFC}$ ) that satisfies the output ripple specification.
2. Find the capacitance value of the output capacitor ( $C_{out\_PFC}$ ) that satisfies the hold-up time.
3. The capacitance values of both are compared and a large value is used.


When selecting an output capacitor ( $C_{out\_PFC}$ ), consider the tolerance and aging.

### 4.5. 3-Phase LLC resonant DC-DC Converter Circuit Design

Fig. 4.11 shows the schematic of the 3-phase LLC resonant DC-DC converter section of this design. In this 3-phase configuration, each phase operates with a phase difference of 120 degrees.

This design uses a NCP1397 (made by onsemi, hereinafter referred to as LLC controller) to control the power supply. Control signals generated by LLC controller are fed to MCU TPM372FWUG through a level shifter. MCU generates the control signals (MOSFET drive signals) with the phase differential of 120 degrees and outputs to the gate driver of each phase. Fig. 4.12 shows the circuit diagram of 3-phase LLC resonant DC-DC converter circuit.

The following describes the basic designs of the 3-phase LLC resonant DC-DC converter. For detailed designs around LLC controller, refer to NCP1397 datasheet and related documentation.

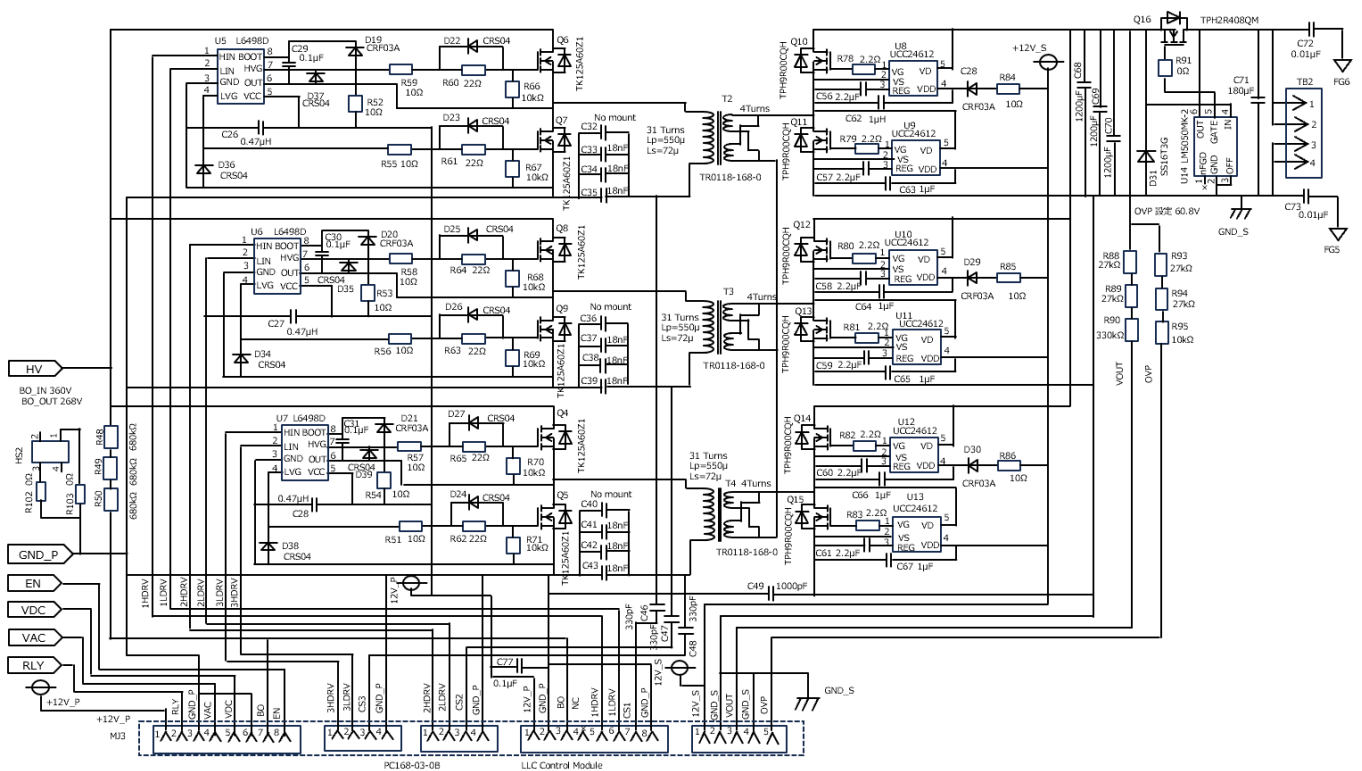

**Fig. 4.11 3-Phase LLC resonant DC-DC Converter Circuit**

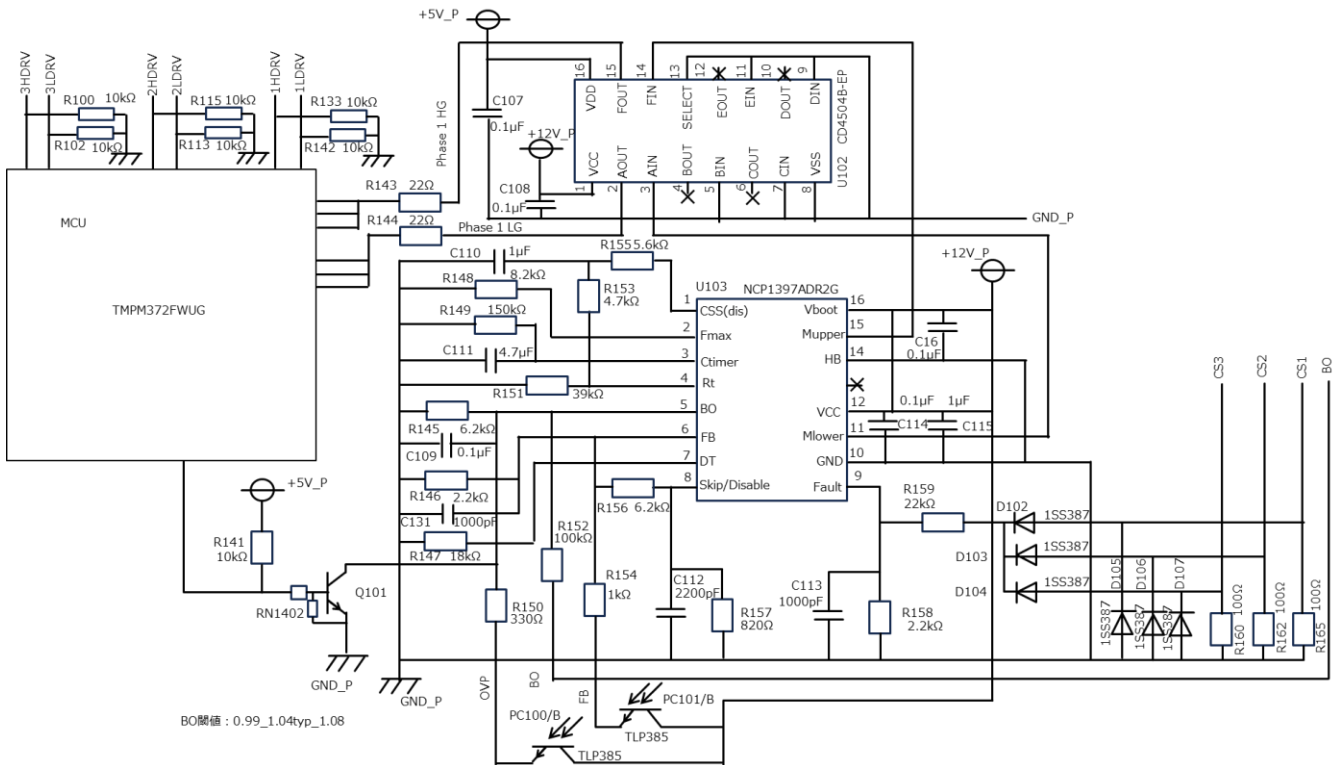


Fig. 4.12 3-Phase LLC resonant DC-DC Converter Control Circuit

**Input voltage drop protection circuit**

Input voltage drop protection function protects the DC-DC converter when the input voltage of DC-DC converter section is low. LLC controller will deactivate the output-pulse when the input-voltage is lower than the pre-set level. LLC controller controls the operation using the voltage generated by the input voltage divided made up of resistors  $R_{upper}$  and  $R_{lower}$ . This voltage is input to the BO pin.

Fig. 4.13 shows the resistor divider used for this function. In this design, the protection voltage is set to 360V and the hysteresis when the input voltage drops is set to 60V, and therefore  $R_{upper} = 2.21M\Omega$ ,  $R_{lower} = 6.2k\Omega$  are selected.

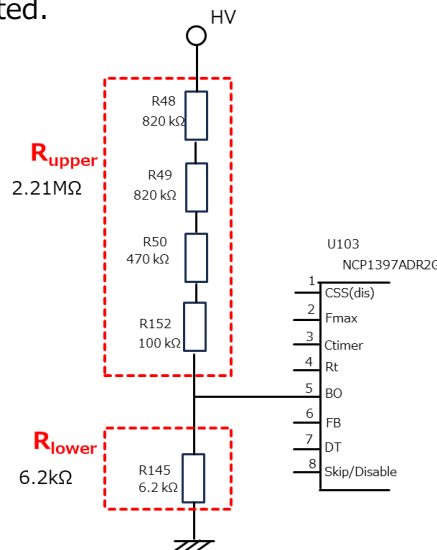


Fig. 4.13 Input Voltage Drop Protection Setting Circuit


### Output voltage setting

Fig. 4.14 shows the output voltage setting circuit. The output-voltage  $V_{out\_LLC}$  of this design is set using the external resistors (R88, R89, R90, R167 and R166) and the shunt regulator (U104). The shunt regulator controls the photocoupler (PC101) current so that the voltage obtained by dividing  $V_{out\_LLC}$  by the resistor above matches the reference voltage  $V_{ref\_LLC}$  (2.5V). LLC controller operates to keep  $V_{out\_LLC}$  constant according to the amount of current fed back from PC101 to FB terminals.

If the bias current to the shunt regulator's REF pin voltage is  $I_{bias\_LLC}$  (30nA),  $V_{out\_LLC}$  is calculated using the following equation.

$$V_{out\_LLC} = \frac{V_{ref\_LLC} \times (R88 + R89 + R90 + R167 + R166)}{R166} + I_{bias\_LLC} \times (R88 + R89 + R90 + R166)$$

In this design,  $V_{out\_LLC}$  is set as 54.6V considering voltage drop of output circuit then  $R88 = 27k\Omega$ ,  $R89 = 27k\Omega$ ,  $R90 = 330\Omega$ ,  $R167 = 330\Omega$ ,  $R166 = 3.9k\Omega$  are selected.

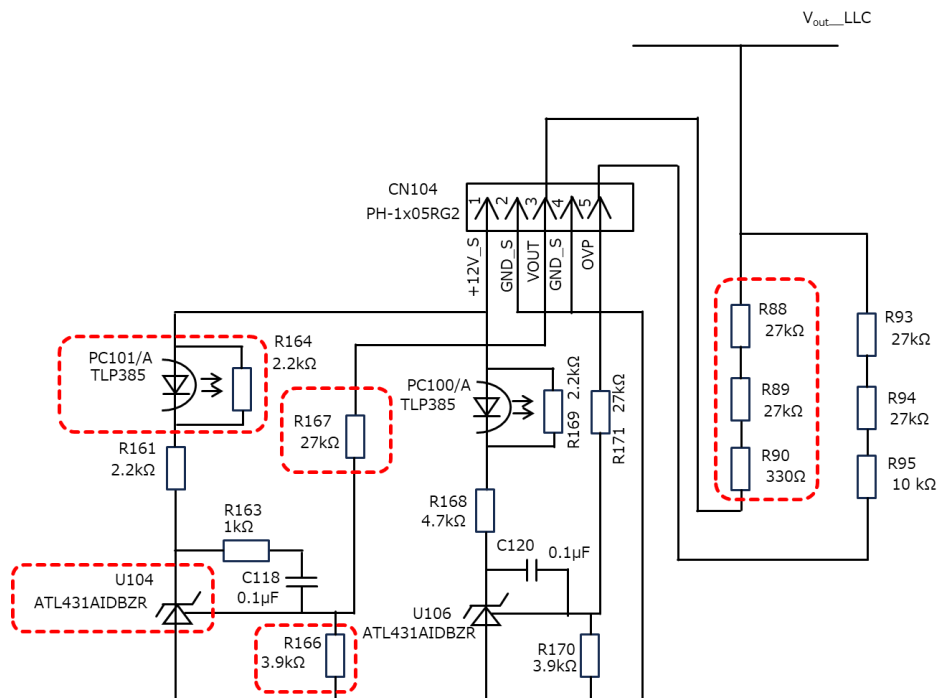

**Fig. 4.14 Output Voltage Setting Circuit**


### Overvoltage protection

Fig. 4.15 shows the overvoltage protection setting circuit. The overvoltage protection voltage  $V_{ovp\_LLC}$  is set with the external resistors (R93, R94, R95, R171 and R170) and the shunt regulator (U106).

The following equation is used to calculate  $V_{ovp\_LLC}$ , where  $I_{bias\_LLC}$  (30nA) is the bias current to the shunt regulator REF pin voltage.

$$V_{ovp\_LLC} = \frac{V_{ref\_LLC} \times (R93 + R94 + R95 + R171 + R170)}{R170} + I_{bias\_LLC} \times (R93 + R94 + R95 + R171)$$


In this design,  $R93 = 27k\Omega$ ,  $R94 = 27k\Omega$ ,  $R95 = 10k\Omega$ ,  $R171 = 27k\Omega$ ,  $R170 = 3.9k\Omega$  are selected, to set  $V_{ovp\_LLC} = 64V$ .

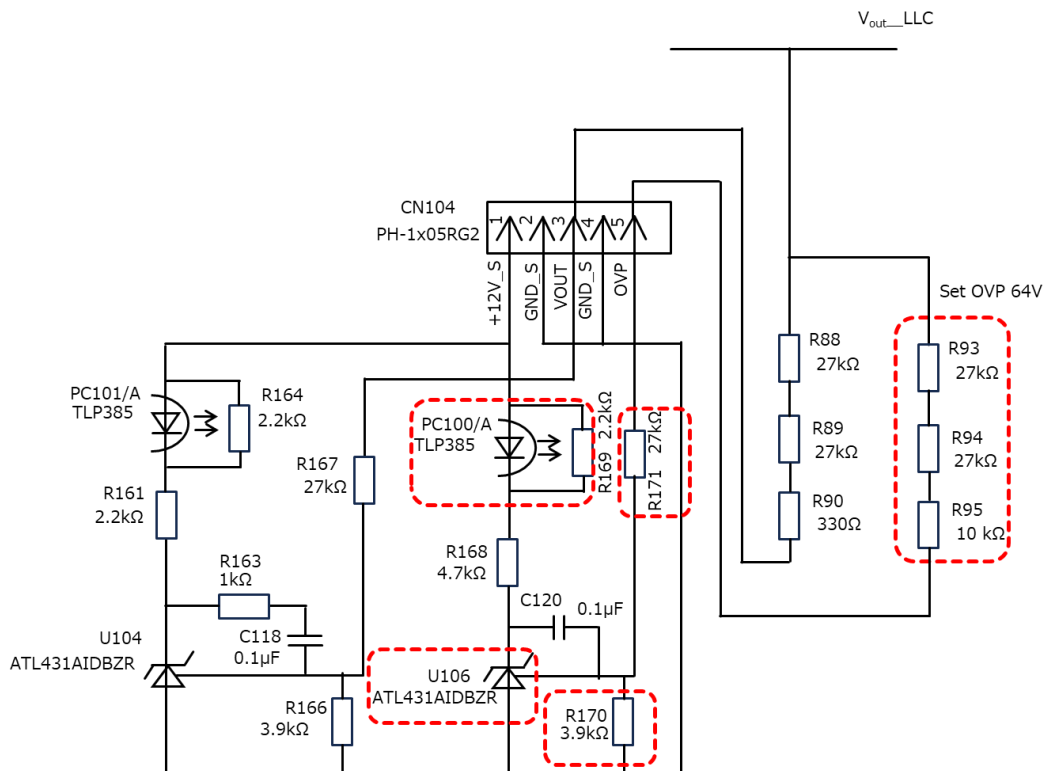

**Fig. 4.15 Overvoltage Protection Setting Circuit**

### Soft start

The soft-start function is required to prevent a large current from flowing during startup. Soft-start capacitor CSS (C110) connected to the Soft-start discharge pin CSS(dis) of LLC controller to set the soft-start duration. When the controller starts to operate, the soft-start capacitor CSS is completely discharged, and its charging starts from Rt pin. Soft-start operation takes place until CSS is fully charged.

 


**Fig. 4.16 Soft-Start Setting Circuit**

### Gate drive circuit

Fig. 4.17 shows the gate drive circuit. The gate-series resistors (R59, R60 and R55, R61) can be used to adjust the turn-on speed and turn-off speed of MOSFET independently.

First, the adjustments related to the high-side MOSFET (Q6) are described. The turn-on and turn-off speeds can be reduced at the same time by increasing R59. Only turn-on speed can be reduced by increasing R60. The adjustments for the low-side MOSFET (Q7) can be done in the same way using R55, R61.

Increasing the resistance may reduce the switching speed of MOSFET, which may also reduce the power supply efficiency. Check that the power supply efficiency specifications and heat radiation specifications satisfy the required specifications.

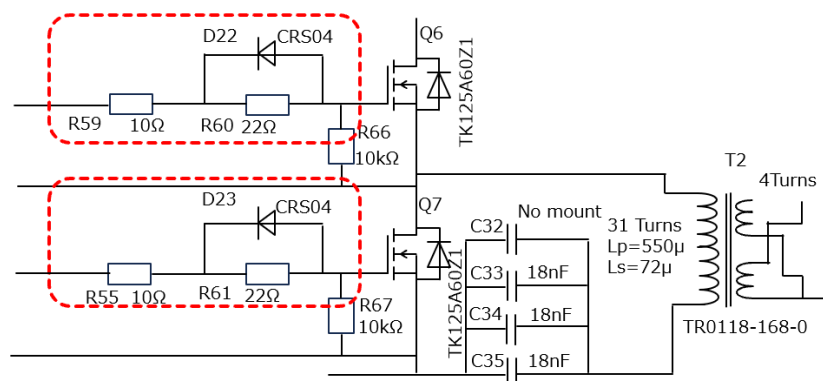

**Fig. 4.17 Gate Drive Circuit**

### Frequency setting

LLC control is capable of switching-frequency operation from 50kHz to 500kHz. The minimum frequency is set using the resistor  $R_{Fmin}$  placed between  $R_t$  pin and GND, and the maximum frequency is set using the resistor  $R_{Fmax}$  placed between  $F_{max}$  pin and GND.

In this design,  $R_{151} = 39k\Omega$  is selected for  $R_{Fmin}$  and  $R_{148} = 8.2k\Omega$  is selected for  $R_{Fmax}$ , with the minimum frequency setting set to 50kHz and the maximum frequency set to 200kHz.

 


Fig. 4.18 Frequency Setting Circuit

### Dead time setting

The dead time is set by the resistor  $R_{DT}$  connected between DT pin and GND. In this design,  $R_{DT}$  is selected as  $R_{147} = 18k\Omega$ , and the deadtime is set to approximately 444ns.

 


Fig. 4.19 Dead Time Setting Circuit



### Output capacitors

Fig. 4.20 shows the output capacitor peripheral circuit. The output capacitor value  $C_{out}$  is set so that the output voltage ripple  $V_{ripple}$  meets the requirements. When  $V_{ripple}$  is 2180mV and the maximum output current is  $I_{max}$ , ESR required for the output capacitor is calculated by the following equation.

$$ESR = \frac{V_{ripple}}{\frac{2 \times \pi}{4} \times I_{max}}$$

Because  $I_{max}$  is 29.4A, ESR becomes 44.2mΩ.

In this design, three capacitors that capacitance is 1200μF and ESR is 20mΩ are placed in parallel (C68, C69, C70) with a combined ESR of approximately 7mΩ.

Following points must also be checked:

1. The output terminal undershoot/overshoot that occurs when the load changes suddenly is within the specified voltage range.
2. The allowable ripple current of the output capacitor must be secured.
3. Output capacitor tolerances and aging must be considered.

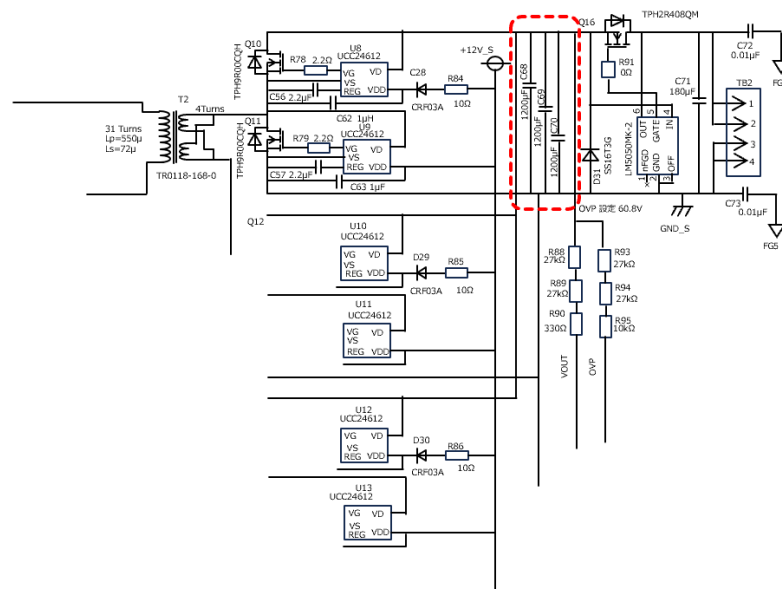



Fig. 4.20 Output Capacitors

**4.6. 3-Phase LLC Resonant DC-DC Converter Design**

This section describes the design of the 3-phase LLC resonant DC-DC converter section (resonant design, transformer design, etc.).

**4.6.1. Calculation of Output Voltage and Output Power of Individual Transformers**

Fig. 4.21 shows an outline of the 3-phase LLC resonant DC-DC converter section of this design. The primary side performs half-bridge switching with 120-degree phase shift, and the secondary side is a power supply configuration with Y-connection at the transformer end.

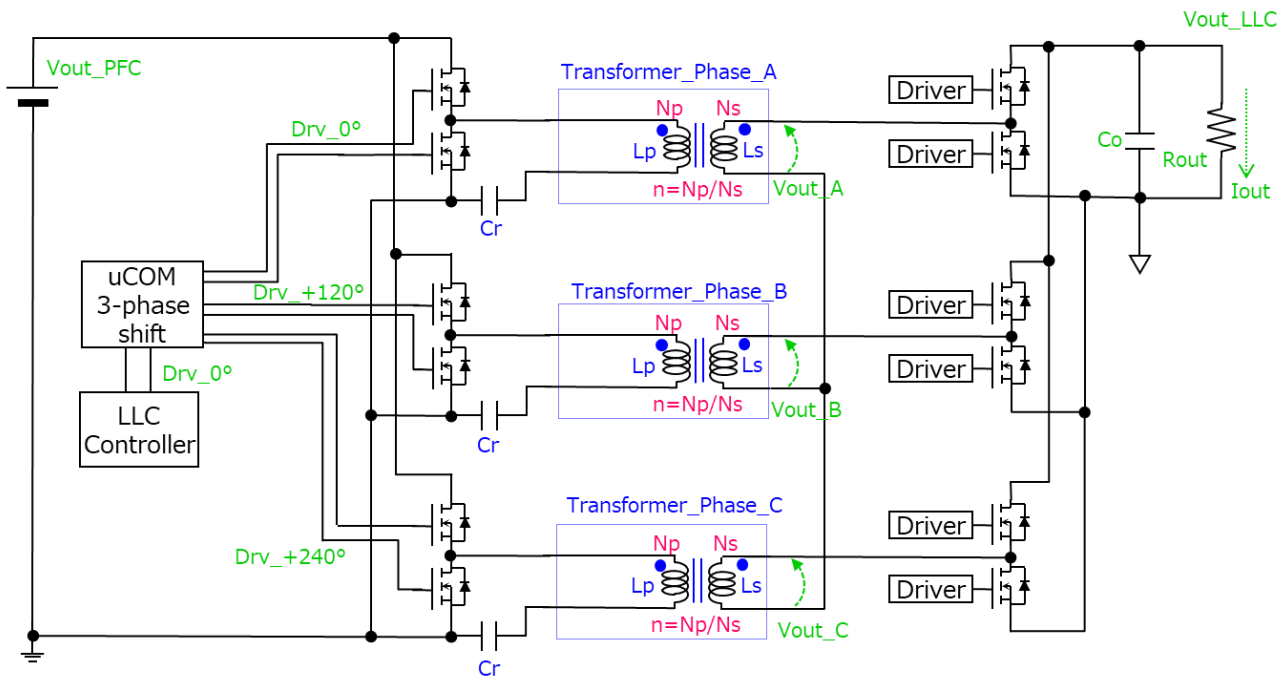

**Fig. 4.21 3-Phase LLC resonant DC-DC Converter Circuit**

Transformer designs are performed by the First Harmonic Approximation (FHA) method. Since the FHA is designed on the assumption that a single transformer is used for the resonant circuit, the output power and output voltage of the transformer alone in this design are calculated.

The specifications of this design are the output-voltage 54.5V and the max. output power 1600W. As described in 3.2, two-phase transformers are connected in series at all times in a 3-phase Y-connection, and 54.5V is output. Therefore, the secondary-side output of the transformer alone is half 27.25V of 54.5V. The maximum output power 1600W means that the maximum output current is  $1600W/54.5V = 29.4A$ . Since 29.4A is divided into 3 phases, the mean output current of one transformer itself is  $29.4A/3 = 9.79A$ .

From above explanation, for each transformer the output voltage is 27.25V and the output power is 266.67W ( $= 27.25 \times 9.79$ ). This information is used for proceeding with the resonant transformer design with FHA. For designing, Phase\_A is used as an example (show in Fig. 4.21). Phase\_B and Phase\_C have similar design values.

### 4.6.2. Transformer Design (Resonant Design)

#### Turn ratio determination

The turn ratio  $n$  is calculated by the following equation using the output voltage  $V_{out\_PFC}$  of PFC and the output voltage  $V_{out\_LLC}$  of LLC ( $= 2 \times V_{out\_A}$ ).

$$n = \frac{V_{out\_PFC}}{2 \times V_{out\_A}}$$

Assigning  $V_{out\_PFC} = 390 \text{ V}$  and  $V_{out\_A} = 27.25\text{V}$  results in  $n = 7.16$ . In this design,  $n = 7.75$  is selected.

#### Resonant circuit voltage gain determination

The FHA is used to develop design based on the gain between the inputs and outputs of the LLC circuit. The voltage-gain required for LLC resonator needs to be calculated. The maximum voltage gain  $Mg\_nom\_max$  required by LLC resonator under normal conditions is calculated using the following equation.

$$Mg\_nom\_max = \frac{n \times V_{out\_A\_max}}{V_{out\_PFC\_min} / 2}$$

If the accuracy of output voltage  $V_{out\_LLC} = 54.5\text{V}$  is  $\pm 5\%$ , the accuracy of output voltage  $V_{out\_A} = 27.25\text{V}$  of the transformer alone is also  $\pm 5\%$ , and the value of  $V_{out\_A\_max} = 28.61\text{V}$ . And if the accuracy of output voltage  $V_{out\_PFC} = 390\text{V}$  is  $\pm 5\%$ , the minimum voltage value is  $370.5\text{V}$ , but by considering the margins  $V_{out\_PFC\_min} = 360\text{V}$ . Since  $n$  is  $7.75$ ,  $Mg\_nom\_max = 1.23$ . After including margin in maximum load, at 105% load the voltage gain meets  $Mg\_nom\_max = 1.23$ .

Next, calculate the max. voltage-gain  $Mg\_hold\_max$  required by LLC resonating circuit at the momentary power failure of AC. In the event of an instantaneous power failure, if the voltage gain at which LLC output voltage can satisfy the minimum specification at the max. load, it shall be deemed to be satisfactory and calculated using the following equation.

$$Mg\_hold\_max = \frac{n \times V_{out\_A\_min}}{V_{out\_PFC\_hold} / 2}$$

If  $n$  is  $7.75$ , the output voltage  $V_{out\_A\_min}$  of the transformer alone with the output voltage lower limit of this power supply (rated output-5%) =  $25.89\text{V}$ , and PFC output voltage lower limit at instantaneous power failure be  $V_{out\_PFC\_hold} = 300\text{V}$ . Thus,  $Mg\_hold\_max = 1.34$ .

From the above, the required voltage gain for LLC resonant circuit is  $Mg\_nom\_max = 1.23$  for 105% load and  $Mg\_hold\_max = 1.34$  for 100% load. In the following calculations, the voltage gain required for LLC resonant circuit is set as follows:  $Mg\_nom\_max$  at 105% load =  $1.23$ , and the final stage of the design is to ensure that the voltage gain at 105% load is  $Mg\_nom\_max = 1.23$ .


Next, the minimum-voltage-gain value  $Mg\_min$  required by LLC resonator is calculated using the following equation.

$$Mg\_min = \frac{n \times V_{out\_A\_min}}{V_{out\_PFC\_max} / 2}$$

If  $n$  is  $7.75$ ,  $V_{out\_A\_min} = 25.89\text{V}$ , and the maximum value of  $V_{out\_PFC}$   $V_{out\_PFC\_max} = 420 \text{ V}$ , then  $Mg\_min = 0.96$ .


### Equivalent load resistance calculation

The FHA transforms LLC resonant circuit into a simple equivalent circuit. Fig. 4.22 shows the circuit diagram for extracting LLC resonant circuit of a single transformer from the 3-phase Y-connection circuit of this design.

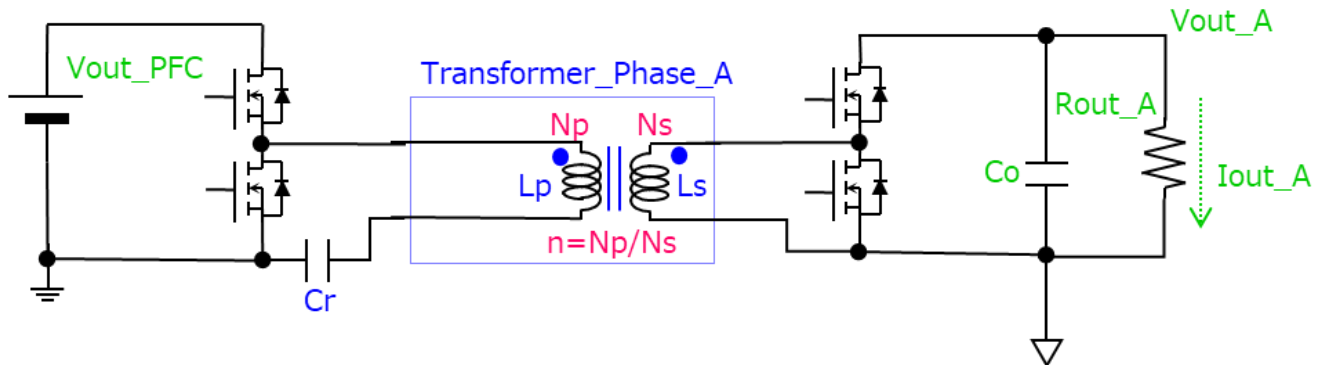

**Fig. 4.22 Single LLC Resonant Circuit Extracted from 3-Phase Y-Connection Circuit**

Here,  $N_p$  is the number of windings of the primary winding of the resonant transformer,  $N_s$  is the number of turns of the secondary winding,  $n$  is the turns ratio,  $L_p$  is the primary inductance (open inductance),  $L_s$  is the secondary inductance,  $C_r$  is the resonant capacitor,  $C_o$  is the output capacitor,  $R_{out\_A}$  is the load resistance of a single transformer,  $V_{out\_A}$  is the output voltage, and  $I_{out\_A}$  is the output current. The equivalent circuit considering the transformer excitation inductance and leakage inductance is shown in Fig. 4.23.

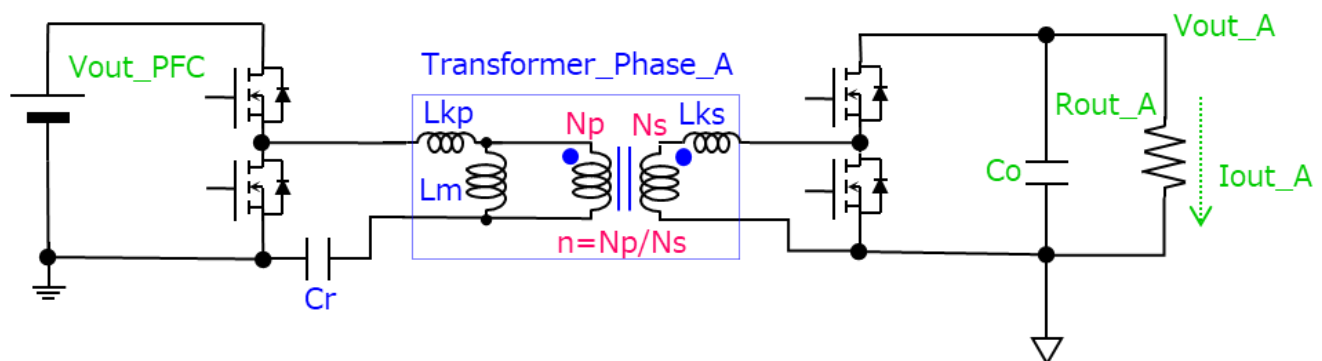

**Fig. 4.23 LLC Resonant Circuit Considering Excitation Inductance and Leakage Inductance of Transformer**

Since the transformer coupling factor is the same for the primary and secondary sides, the relation between the primary side leakage inductance  $L_{kp}$  and the secondary side leakage inductance  $L_{ks}$  is expressed by the following equations.

$$L_{kp} = n^2 L_{ks}$$

When the excitation inductance is  $L_m$  and the short inductance that is measured by shorting the resonant transformer secondary side is taken as  $L_x$ , the open inductance  $L_p$  and the primary leakage inductance  $L_{kp}$  are expressed by the following equations.

$$L_p = L_m + L_{kp}$$

$$L_x = L_{kp} + \frac{L_{kp} * L_m}{L_{kp} + L_m}$$

In LLC resonant circuit, there are two resonant frequencies: the resonant frequency  $f_p$  of the open inductance  $L_p$  and the resonant capacitor  $C_r$ , and the resonant frequency  $f_0$  of the short inductance  $L_x$  and the resonant capacitor  $C_r$ . The relationship between them is as follows.

$$f_p = \frac{1}{2\pi\sqrt{L_p * C_r}}$$

$$f_0 = \frac{1}{2\pi\sqrt{L_x * C_r}}$$

In LLC resonant circuit, the switching-frequency  $f_{sw}$  operates based on  $f_0$ . If the switching frequency  $f_{sw}$  is less than  $f_p$ , LLC will deviate from the resonance. This results in hard switching, which may lead to a drop in power conversion efficiency and damage to the devices. Therefore, it must be operated at a switching-frequency higher than  $f_p$ .


Fig. 4.24 shows an equivalent circuit when the secondary-side leakage inductance  $L_{ks}$  is converted to the primary side. Fig. 4.25 shows a simplified equivalent circuit of LLC resonant circuit.

The following shows the relation between the load  $R_{out\_A}$  of LLC resonant circuit and the equivalent load resistor  $R_{Le}$  in LLC resonant simplified equivalent circuit.


$$R_{Le} = \frac{8n^2}{\pi^2} R_{out\_A}$$

In LLC resonant simplified equivalent circuit of the single transformer, with the output voltage  $V_{out\_A} = 27.25V$  and the output power  $P_{out\_A} = 266.67W$ , the equivalent load-resistance  $R_{Le}$  is as follows.

$$R_{Le} = \frac{8n^2}{\pi^2} R_{out\_A} = \frac{8n^2}{\pi^2} * \frac{(V_{out\_A})^2}{P_{out\_A}} = 135.57\Omega$$

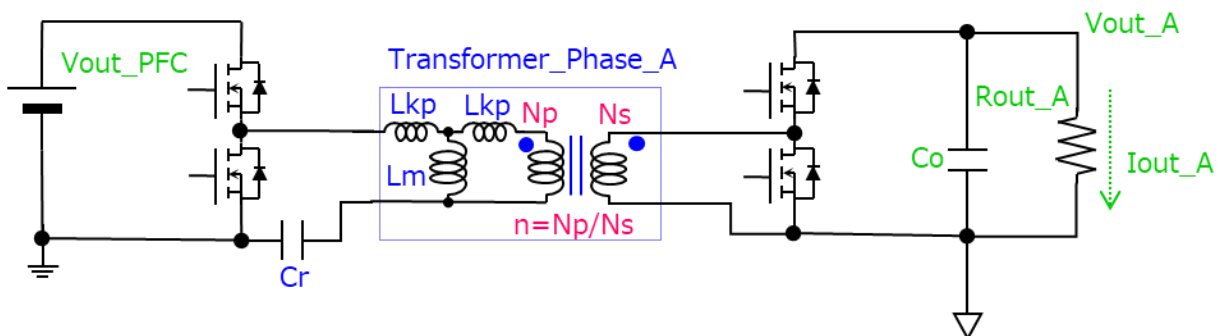


**Fig. 4.24 LLC Resonant Circuit With Secondary Leakage Inductance of Resonant Transformer Converted to Primary Side**

 

**Fig. 4.25 LLC Resonant Simplified Equivalent Circuit**

## Resonant circuit quality factor derivation

Fig. 4.26 shows the relation between the maximum gain of LLC resonant circuit  $Mg\_max$  and quality factor  $Qe$  of the resonant circuit in the FHA. In this diagram,  $L_n$  is the ratio of the exciting inductance  $L_m$  of the resonant transformer to the leakage inductance  $L_k$  ( $L_n = L_m/L_k$ ). If  $L_n = 12$ , the quality factor  $Qe$  is 0.28 when  $Mg\_max = 1.23$ .

 

**Fig. 4.26 LLC Resonant Circuit: Max. Voltage Gain and Quality Factor Relation Diagram**

From the above, the quality factor should be set near  $Qe = 0.28$  to ensure  $Mg\_nom\_max = 1.23$  at 105% load including margins at maximum load. In the FHA, the resonant transformer is defined as an ideal transformer, so the leakage inductance  $L_k$  is assumed to be the same as the short-circuit inductance  $L_x$ .

However, when the resonant transformer leakage inductance is used to construct an LLC resonant circuit, the primary leakage inductance  $L_{kp}$  and the short-circuit inductance  $L_x$  do not become the same value, but have the relation shown below. Where  $L_m$  is the excitation inductance.

$$L_x = L_{kp} + \frac{L_{kp} * L_m}{L_{kp} + L_m}$$

The reference operating switching frequency  $f_0$  of LLC resonant circuit is the resonant frequency of the short inductance  $L_x$  and the resonant capacitor  $C_r$ . Therefore, the ratio between the excitation inductance  $L_m$  of the resonant transformer and the leakage inductance  $L_k$  ( $L_n = L_m/L_k$ ) defined in the relation diagram (Fig. 4.26) between  $M_{g\_max}$  and the quality factor  $Q_e$  in the FHA is different from the ratio between the actual excitation inductance  $L_m$  and the short-circuit inductance  $L_x$ . However, this value is useful for calculating the approximate value of the excitation inductance  $L_m$ .

The quality factor  $Q_e$  is given by the following equation.  $R_{Le}$  is the equivalent load-resistance value of the simple equivalent circuit of LLC resonant circuit.

$$Q_e = \frac{\sqrt{L_x/C_r}}{R_{Le}}$$

### Cr, Lx, Lm, Lkp calculation

Relation between resonant capacitor  $C_r$  and short inductance  $L_x$ , resonant frequency  $f_0$ , equivalent load resistance  $R_{Le}$ , and quality factor  $Q_e$  is shown below.

$$C_r = \frac{1}{2 * \pi * f_0 * R_{Le} * Q_e}$$

When  $f_0$  is 80kHz,  $R_{Le} = 135.57\Omega$  and  $Q_e = 0.28$ , the  $C_r$  is calculated to be  $C_r = 52.41\text{nF}$ . This time, three 18nF are used in parallel to make  $C_r = 54\text{nF}$ .

The following shows the relational expression and calculation of the short inductance  $L_x$ ,  $C_r$ ,  $f_0$ .

$$L_x = \frac{1}{(2 * \pi * f_0)^2 * C_r} = 73.29(\mu\text{H})$$

The relation between  $L_x$  and  $L_{kp}$  is:

$$L_x = L_{kp} + \frac{L_{kp} * L_m}{L_{kp} + L_m} = 73.29(\mu\text{H})$$

$L_n$  is the ratio of the excitation inductance  $L_m$  and primary leakage inductance  $L_{kp}$  set by resonant-circuit quality factor derivation.

$$L_n = \frac{L_m}{L_{kp}} = 12$$

Relation between open inductance  $L_p$  and exciting inductance  $L_m$  and primary leakage inductance  $L_{kp}$  is:

$$L_p = L_m + L_{kp}$$

The excitation inductance  $L_m$ , primary leakage inductance  $L_{kp}$ , and open inductance  $L_p$  are calculated from these values as shown below.

$L_{kp} = 38.11\mu\text{H}$ ,  $L_m = 457.33\mu\text{H}$ ,  $L_p = 495.44\mu\text{H}$

**n, Lp, Lx, Cr determination, and Lm, Lkp, Lks, k, fp, f0 calculation**

The specifications of the resonant transformer and the resonant capacitor based on the above calculation results are determined below.

Resonant transformer turns ratio:  $n = 7.75$  ( $N_p:N_s = 31:4$ )

Resonant transformer open inductance:  $L_p = 480\mu\text{H}$

Resonant transformer short inductance:  $L_x = 70\mu\text{H}$

Resonant capacitor:  $C_r = 54\text{nF}$

Following are the calculation results of excitation inductance, leakage inductance, transformer coupling coefficient, and resonant frequency of the resonant transformer.

Resonant transformer excitation inductance:  $L_m = 443.62\mu\text{H}$

Resonant transformer primary leakage inductance:  $L_{kp} = 36.38\mu\text{H}$

Resonant transformer secondary leakage inductance:  $L_{ks} = L_{kp}/n^2 = 605.7\text{nH}$

Resonant transformer coupling factor:  $a = L_m/L_p = 0.92$

Resonant frequency of a resonant transformer with open inductance  $L_p$  and a resonant capacitor  $C_r$ :  $f_p = 30.22\text{kHz}$

Resonant Frequency of a resonant transformer with short inductance  $L_0$  and resonant capacitor  $C_r$ :  $f_0 = 81.86\text{kHz}$



### 4.6.3. Resonant Circuit Voltage Gain Confirmation

It must be confirmed that the switching frequency transitions properly within the assumed range in the resonant circuit using the designed resonant transformer and resonant capacitor. An LLC converter transfer graph is used to describe the relation between the switching frequency and the voltage gain of the resonant circuit.

#### LLC Converter Transfer Function M calculation

LLC converter transfer function M is calculated by the following equation. The value of M indicates the relationship between the switching frequency of the resonant circuit and the voltage gain according to the load.

$$M = \frac{2n * V_{oe}}{V_{out\_PFC}} = \frac{1}{\sqrt{\left(\frac{1}{a} \left(1 - \frac{1-a^2}{f_{sw}^2} * f_0^2\right)\right)^2 + \left(\frac{Q_e}{a} \left(\frac{f_{sw}}{f_0} - \frac{f_0}{f_{sw}}\right)\right)^2}}$$

$Q_e$  in the above equations is the variable-quality factor due to the load. The following shows the relation between  $Q_e$  and the secondary-side load  $P_{out\_A}$  of the transformer.

$$Q_e = \frac{\sqrt{Lx/Cr}}{RLe} = \sqrt{Lx/Cr} * \frac{\pi^2}{8n^2 * R_{out\_A}} = \sqrt{Lx/Cr} * \frac{\pi^2}{8n^2} * \frac{P_{out\_A}}{(V_{out\_A})^2}$$

Where no-load  $P_{out\_A\_min} = 0W$ , max-load  $P_{out\_A\_max} = 266.67W$ ,

The calculation result of  $Q_e$  at each load is shown from  $P_{out\_A\_max} +5\%$  at the maximum load  $+5\% = 280W$ .

At no-load:  $Q_{e\_min} = 0$

At maximum load:  $Q_{e\_max} = 0.27$


At maximum load at  $+5\%$ :  $Q_{e\_max+5\%} = 0.28$

From the above calculation,  $Q_e$  transits between 0.00 and 0.28. In addition, in the Resonant Circuit Quality Factor Derivation section, it is approximated to  $Q_e = 0.28$  calculated at maximum load, which confirms that it is appropriate for LLC resonant designs.

In the next section, the relation between LLC converter transfer function M and the switching frequency  $f_{sw}$  for each  $Q_e$  is used to check whether the switching frequency transition area is appropriate.

**Resonant circuit voltage gain confirmation and switching frequency transition range confirmation**

Fig. 4.27 shows the relation between the switching-frequency  $f_{sw}$  and the voltage gain of a resonant circuit using a transformer and a resonant capacitor.

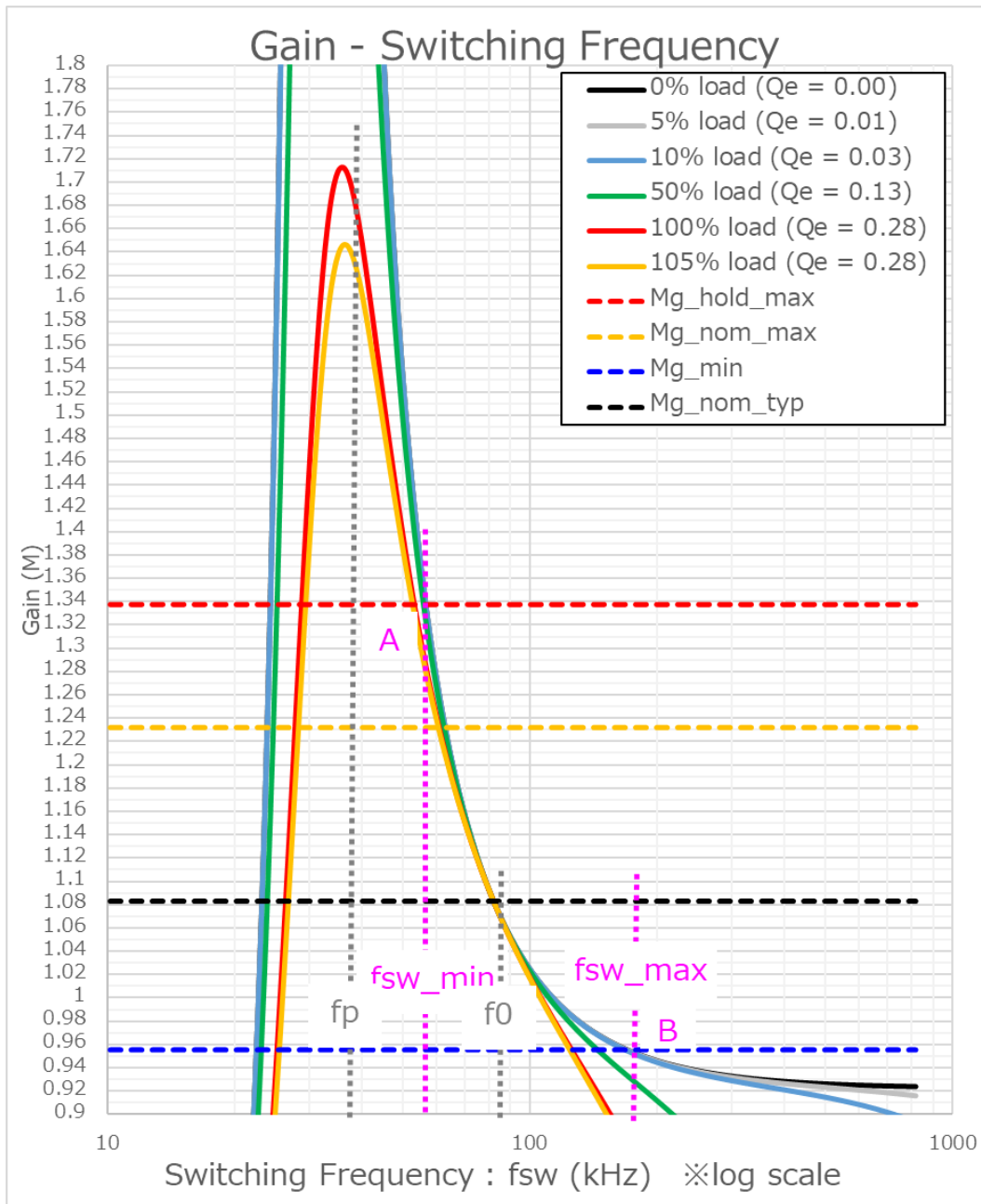


**Fig. 4.27 LLC Resonant Circuit Voltage Gain and Switching Frequency Relation Diagram**

Since the gain curve of  $Q_e = 0.28$  at 105% load including the margin for the maximum load reaches the maximum required voltage gain  $Mg_{nom\_max} = 1.23$ , so it can be confirmed that the required gain is secured at the maximum load +5%. In addition, since the gain curve  $Q_e = 0.27$  at the maximum load reaches the required gain at instantaneous power failure  $Mg_{hold\_max} = 1.34$ , it is also possible to confirm that the required voltage gain is secured at the instantaneous power failure under the maximum load condition. The switching frequency obtained at the intersection of the gain curve and  $Mg_{hold\_max}$  (point A in the diagram) is the minimum switching frequency  $f_{sw\_min}$  of LLC power supply. Since  $f_{sw\_min}$  is smaller than the resonant frequency  $f_p$  of the

resonant transformer with open inductance  $L_p$  and resonant capacitor  $C_r$ , it can be confirmed that this LLC power supply does not deviate from the soft-switching operation area due to resonance at both maximum load and instantaneous stop.

The maximum switching frequency  $f_{sw\_max}$  of LLC power supply is obtained at the intersection of the gain curve  $Q_e = 0.00$  at the minimum load and the minimum required gain  $M_{g\_min} = 0.96$  (point B in the diagram).

Fig. 4.28 shows the relation between the switching frequency (fsw) and the voltage gain near the required maximum voltage gain.

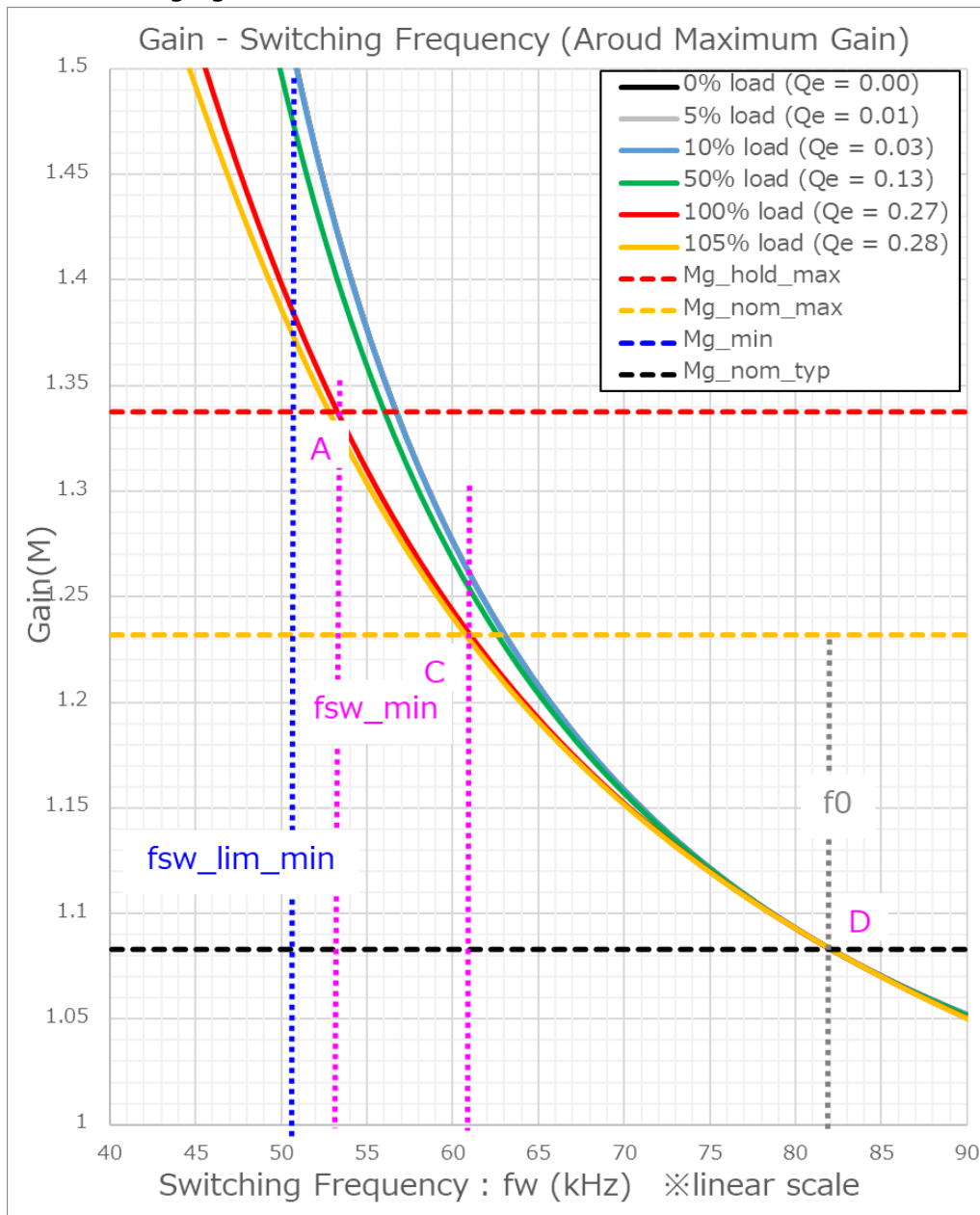


**Fig. 4.28 LLC Resonant Circuit Voltage Gain and Switching Frequency Relation Diagram (Expansion Near Required Maximum Gain, Frequency Axis in Linear Scale)**

The minimum switching frequency in the steady state is 60.5kHz from the intersection of the gain curve (Point C in figure) between the maximum voltage gain required at maximum load +5% in steady state  $Mg\_nom\_max = 1.23$  and the gain curve of  $Qe = 0.28$  at the maximum load +5% in the steady state. Also, since the required voltage-gain at instantaneous power failure  $Mg\_hold\_max = 1.34$  is larger than that of  $Mg\_nom\_max$ , the minimum switching frequency  $fsw\_min$  of the LLC power supply is 53.0kHz from the intersection of the gain curves  $Qe = 0.27$  and  $Mg\_hold\_max =$  at maximum load (point A in the diagram).It is confirmed that this circuit operates correctly in designated condition, because the 53kHz is higher than the 50kHz which is the minimum switching frequency set by the LLC controller.

The intersection of the voltage gain  $Mg\_nom\_typ = 1.08$  and the gain curve  $Qe = 0.27$  at full load (point D in the figure) at the center value of  $Vout\_PFC\_typ = 390\text{ V}$  and  $Vout\_A\_typ = 27.25\text{ V}$  for both input voltage and output voltage is almost the same as the resonant frequency  $f_0$  of the resonant transformer with short inductance  $L_0$  and the resonant capacitor  $C_r$ . In the LLC resonant circuit, the most stable operation is achieved when the switching frequency  $f_{sw}$  is  $f_0$ , so it can be confirmed that the input / output voltage center value is set so that the current LLC power supply operation is set to be the most stable.

Fig. 4.29 shows the relation between the switching frequency ( $f_{sw}$ ) and the voltage gain in the vicinity of the required minimum voltage gain.

 

**Fig. 4.29 LLC Resonant Circuit Voltage Gain and Switching Frequency Relation Diagram (Near Required Minimum Gain Expansion, Frequency Axis in Linear Scale)**

From the intersection of the gain curve of  $Mg_{\min} = 0.96$  required for the minimum load in steady state and  $Q_e = 0.00$  at minimum load (point B in the diagram), the maximum switching frequency  $fsw_{\max}$  of the LLC power supply is 170.0kHz. It is below the upper limit of the switching frequency of the LLC part of this design, which is  $fsw_{\lim_{\max}} = 200.0$  kHz, which was set in the LLC controller peripheral circuit design, and normal operation within the limit range can be confirmed.

From the above confirmation, it can be confirmed that the switching frequency transition range of LLC resonant power supply is as follows, and is within the switching frequency limit range set in the LLC controller peripheral design.

Minimum switching frequency:  $fsw_{\min} = 53\text{kHz}$

Maximum switching frequency:  $fsw_{\max} = 170\text{kHz}$

#### 4.6.4. Resonant Transformer Current Calculation and ZVS (Zero Volt Switching) Confirmation

This section shows the calculation of the current of the designed resonant transformer and the confirmation of the ZVS establishment conditions of soft switching.

##### Current calculation of the resonant transformer

Calculation of the maximum current  $I_{out\_A\_max}$  in Fig. 4.24. In this case, the output voltage accuracy is  $\pm 5\%$ , the minimum output voltage  $V_{out\_A\_min} = 25.89\text{V}$ , and the maximum power  $P_{out\_A\_max} = 266.67 \times 1.05 = 280\text{W}$ , including a margin of  $+5\%$  at the maximum load.

$$I_{out\_A\_max} = \frac{P_{out\_A\_max}}{V_{out\_A\_min}} = 10.81(A)$$

The peak load current value  $I_{s\_A\_peak\_max}$  flowing in the secondary winding and the peak load current value  $I_{p\_A\_peak\_max}$  flowing in the primary winding are calculated on the assumption that sinusoidal current flows in the secondary winding.

$$I_{s\_A\_peak\_max} = \frac{\pi}{2} * I_{out\_A\_max} = 16.98(A_{peak})$$

$$I_{p\_A\_peak\_max} = \frac{\pi}{2n} * I_{out\_A\_max} = 2.19(A_{peak})$$

The load current effective value  $I_{s\_A\_rms\_max}$  that flows in the secondary winding and the load current effective value  $I_{p\_A\_rms\_max}$  that flows in the primary winding are calculate below.

$$I_{s\_A\_rms\_max} = \frac{1}{\sqrt{2}} I_{s\_A\_peak\_max} = \frac{\pi}{2\sqrt{2}} * I_{out\_A\_max} = 12.01(A_{rms})$$

$$I_{p\_A\_rms\_max} = \frac{1}{\sqrt{2}} I_{p\_A\_peak\_max} = \frac{\pi}{2n\sqrt{2}} * I_{out\_A\_max} = 1.55(A_{rms})$$

The primary side has an excitation current that flows through the excitation inductor in addition to the above. The peak value  $I_{m\_A\_peak\_max}$  and the rms value  $I_{m\_A\_rms\_max}$  of the excitation current is calculated using the following formula. In this case, the maximum output voltage  $V_{out\_A\_max} = 28.61\text{V}$  from the excitation inductance  $L_m = 443.62\mu\text{H}$ , the minimum switching frequency  $fsw_{\min} = 53.00\text{kHz}$ , and the output voltage accuracy is  $\pm 5\%$ .

$$I_{m\_A\_peak\_max} = \frac{n}{4 * L_m * f_{sw\_min}} * V_{out\_A\_max} = 2.36(A_{peak})$$

$$I_{m\_A\_rms\_max} = \frac{1}{\sqrt{2}} I_{m\_A\_peak\_max} = \frac{n}{4\sqrt{2} * L_m * f_{sw\_min}} * V_{out\_A\_max} = 1.67(A_{rms})$$

The total peak current  $I_{total\_A\_peak\_max}$  and the total rms current  $I_{total\_A\_rms\_max}$  on the primary side are calculated as follows.

$$I_{total\_A\_peak\_max} = \sqrt{(I_{p\_A\_peak\_max})^2 + (I_{m\_A\_peak\_max})^2} = 3.22(A_{peak})$$

$$I_{total\_A\_rms\_max} = \sqrt{(I_{p\_A\_rms\_max})^2 + (I_{m\_A\_rms\_max})^2} = 2.28(A_{rms})$$

$I_{total\_A\_peak\_max}$  and  $I_{total\_A\_rms\_max}$  are equivalent to the maximum current flowing through the resonant capacitor.

### **Zero volt switching confirmation**

LLC resonant power supply achieves high-efficiency ZVS by charging and discharging the switching MOSFET's output capacitance with the energy stored by the excitation current of the transformer. In order to achieve ZVS in a wide range of loading conditions, ZVS condition must be satisfied even under the condition that the excitation current  $I_{m\_A\_rms}$  is minimal. ZVS is satisfied when the energy stored by the exciting current of the transformer exceeds the energy required to charge/discharge MOSFET output capacitance. When the excitation current is at minimum, the maximum switching frequency  $f_{sw\_max} = 170.00\text{kHz}$ , and the minimum output voltage  $V_{out\_A\_min} = 25.89\text{V}$ , the minimum excitation current  $I_{m\_A\_rms\_min}$  is calculated as follows.

$$I_{m\_A\_rms\_min} = \frac{1}{\sqrt{2}} I_{m\_A\_peak\_min} = \frac{n}{4\sqrt{2} * L_m * f_{sw\_max}} * V_{out\_A\_min} = 0.47(A_{rms})$$

At this time, the minimum energy value  $E_{p\_min}$  stored in the transformer on the primary side is calculated as follows.

$$E_{p\_min} = \frac{1}{2} L_p * (I_{m\_A\_rms\_min})^2 = 53.09(\mu\text{J})$$


ZVS can be achieved if the output capacitance of the switching MOSFET can be charged and discharged with the energy calculated above. The maximum energy required for charging/discharging a single MOSFET TK125A60Z1  $E_{zvs\_max}$  is calculated as follows when the output capacitance energy equivalent effective capacitance value  $C_{o\_er} = 70\text{pF}$  and the input maximum voltage  $V_{out\_PFC\_max} = 420\text{V}$ .

$$E_{zvs\_max} = \frac{1}{2} C_{o\_er} * (V_{out\_PFC\_max})^2 = 6.17(\mu\text{J})$$

There are two switching MOSFETs, one on high side and another on low side. Therefore, in order to achieve ZVS with this LLC resonant power supply, it is necessary to double the maximum energy required for charging/discharging  $E_{zvs\_max}$ . Since the minimum energy stored in the primary side of the transformer  $E_{p\_min} = 53.09\mu\text{J}$ , is more than 2 times the maximum energy required for charging and discharging the switching MOSFET TK125A60Z1  $E_{zvs\_max} * 2 = 12.34\mu\text{J}$ , it can be confirmed that ZVS can be established even under the worst situation with the minimum excitation current and maximum energy required for ZVS.

### 4.7. ORing Circuit

Fig. 4.30 shows ORing circuit. ORing Controller LM5050-1 (made by Texas Instruments) operates as an ideal diode rectifier in conjunction with an external MOSFET when connected in series with a power supply. GATE is deactivated if  $V_{IN} > V_{OUT}$ . In addition, the MOSFET can be turned off by setting the OFF pin high.

 

**Fig. 4.30 ORing Circuit**

- \* Arm, Cortex are registered trademarks of Arm Limited (or its subsidiaries).
- \* Company names, product names, and service names may be trademarks of their respective companies.



## Terms of Use

This terms of use is made between Toshiba Electronic Devices and Storage Corporation ("We") and Customer who downloads or uses this Reference Design. Customer shall comply with this terms of use. This Reference Design means all documents and data in order to design electronics applications on which our semiconductor device is embedded.

### **Section 1. Restrictions on usage**

1. This Reference Design is provided solely as reference data for designing electronics applications. Customer shall not use this Reference Design for any other purpose, including without limitation, verification of reliability.
2. Customer shall not use this Reference Design for sale, lease or other transfer.
3. Customer shall not use this Reference Design for evaluation in high or low temperature, high humidity, or high electromagnetic environments.
4. This Reference Design shall not be used for or incorporated into any product or system whose manufacture, use, or sale is prohibited under any applicable laws or regulations.

### **Section 2. Limitations**

1. We reserve the right to make changes to this Reference Design without notice.
2. This Reference Design should be treated as a reference only. WE ARE NOT RESPONSIBLE FOR ANY INCORRECT OR INCOMPLETE DATA AND INFORMATION.
3. Semiconductor devices can malfunction or fail. When designing electronics applications by referring to this Reference Design, Customer is responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of semiconductor devices could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Customer must also refer to and comply with the latest versions of all relevant our information, including without limitation, specifications, data sheets and application notes for semiconductor devices, as well as the precautions and conditions set forth in the "Semiconductor Reliability Handbook".
4. Designing electronics applications by referring to this Reference Design, Customer must evaluate the whole system sufficiently. Customer is solely responsible for applying this Reference Design to Customer's own product design or applications. WE ASSUME NO LIABILITY FOR CUSTOMER'S PRODUCT DESIGN OR APPLICATIONS.
5. WE SHALL NOT BE RESPONSIBLE FOR ANY INFRINGEMENT OF PATENTS OR ANY OTHER INTELLECTUAL PROPERTY RIGHTS OF THIRD PARTIES THAT MAY RESULT FROM THE USE OF THIS REFERENCE DESIGN. NO LICENSE TO ANY INTELLECTUAL PROPERTY RIGHT IS GRANTED BY THIS TERMS OF USE, WHETHER EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE.
6. THIS REFERENCE DESIGN IS PROVIDED "AS IS". WE (a) ASSUME NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (b) DISCLAIM ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO THIS REFERENCE DESIGN, INCLUDING WITHOUT LIMITATION, WARRANTIES OR CONDITIONS OF FUNCTION AND WORKING, WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.

### **Section 3. Terms and Termination**

It is assumed that Customer agrees to any and all this terms of use if Customer downloads or uses this Reference Design. We may, at its sole and exclusive discretion, change, alter, modify, add, and/or remove any part of this terms of use at any time without any prior notice. We may terminate this terms of use at any time and without any cause. Upon termination of this terms of use, Customer shall eliminate this Reference Design. Furthermore, upon our request, Customer shall submit to us a written confirmation to prove elimination of this Reference Design.

### **Section 4. Export Control**

Customer shall not use or otherwise make available this Reference Design for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). This Reference Design may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Act and the U.S. Export Administration Regulations. Export and re-export of this Reference Design is strictly prohibited except in compliance with all applicable export laws and regulations.

### **Section 5. Governing Laws**

This terms of use shall be governed and construed by laws of Japan, without reference to conflict of law principle.

### **Section 6. Jurisdiction**

Unless otherwise specified, Tokyo District Court in Tokyo, Japan shall be exclusively the court of first jurisdiction for all disputes under this terms of use.