

Notes in use of TB67Z83xxFTG/Z85xxFTG

Description

TB67Z83xxFTG/TB67Z85xxFTG series have a built-in circuit that can drive three phases of high-side and low-side MOSFETs. Gate drive current of external MOSFETs can be set from 10 mA to 1 A(peak) for source current and from 20 mA to 2 A (peak) for sink current. VM supply voltage can be used in a wide operating range from 8 to 75V and VDRAIN voltage can be used in a wide operating range from 6 to 75V. TB67Z833xFTG/TB67Z853xFTG devices incorporate three gain-adjustable amplifiers, which can be used for shunt current sensing.

Toshiba Electronic Devices & Storage Corporation

The contents described in the application note are references for evaluating the product. Therefore, the contents described cannot be guaranteed. As for detailed specifications, please refer to the datasheet.

Table of Contents

Description	1
Table of Contents	2
1. Main differences between TB67Z83xxFTG, TB67Z85XXFTG.....	5
2. Power Supply Voltage	6
2.1. Operating Range of Power Supply Voltage	6
2.2. Power-on Sequence with Control Input Signals.....	6
3. Output Current.....	8
4. Control inputs	13
4.1. ENABLE signal input	13
4.2. INHx/INLx input	13
4.2.1. 6-PWM input mode	13
4.2.2. 3-PWM input mode	14
4.2.3. Hall input mode	14
4.2.4. Independent PWM mode	15
4.3. Hardware Control interface	16
4.4. SPI Control interface	16
5. DVDD output	17
6. Charge pump.....	17
7. Application Circuit Example	18
8. Power Dissipation.....	19
8.1. Heat dissipation design	20
9. Reference land pattern	21
10. Layout Example.....	22
10.1. B67Z833xFTG / Z853xFTG.....	22
10.2. TB67Z830xFTG / Z850xFTG	22
Notes on Contents.....	23
IC Usage Considerations.....	23
Notes on Handling of ICs.....	23
Points to Remember on Handling of ICs.....	24
RESTRICTIONS ON PRODUCT USE.....	25

List of Figures

Figure 2.1	Power-on sequence (nFAULT is pull-up to DVDD)	6
Figure 2.2	Power Supply Configuration Examples	7
Figure 2.3	Example of supplying VM through a resistor.....	7
Figure 3.1	I _{source} = 1 A, H-side, Positive current	9
Figure 3.2	I _{source} = 1 A, H-side, Negative current.....	9
Figure 3.3	I _{source} = 120 mA, H-side, Positive current.....	9
Figure 3.4	I _{source} = 120 mA, H-side, Negative current	9
Figure 3.5	I _{source} = 30 mA, H-side, Positive current.....	9
Figure 3.6	I _{source} = 30 mA, H-side, Negative current	9
Figure 3.7	I _{source} = 1 A, L-side, Positive current.....	10
Figure 3.8	I _{source} = 1 A, L-side, Negative current	10
Figure 3.9	I _{source} = 120 mA, L-side, Positive current.....	10
Figure 3.10	I _{source} = 120 mA, L-side, Negative current.....	10
Figure 3.11	I _{source} = 30 mA, L-side, Positive current.....	10
Figure 3.12	I _{source} = 30 mA, L-side, Negative current.....	10
Figure 3.13	I _{sink} = 2 A, H-side, Positive current.....	11
Figure 3.14	I _{sink} = 2 A, H-side Negative current	11
Figure 3.15	I _{sink} = 240 mA, H-side, Positive current	11
Figure 3.16	I _{sink} = 240 mA, H-side, Negative current.....	11
Figure 3.17	I _{sink} = 60 mA, H-side, Positive current	11
Figure 3.18	I _{sink} = 60 mA H-side Negative current.....	11
Figure 3.19	I _{sink} = 2 A, L-side, Positive current	12
Figure 3.20	I _{sink} = 2 A, L-side, Negative current.....	12
Figure 3.21	I _{sink} = 240 mA, L-side, Positive current.....	12
Figure 3.22	I _{sink} = 240 mA, L-side, Negative current	12
Figure 3.23	I _{sink} = 60 mA, L-side, Positive current.....	12
Figure 3.24	I _{sink} = 60 mA, L-side, Negative current	12
Figure 4.1	6-PWM input mode waveform example.....	13
Figure 4.2	3-PWM input mode waveform example.....	14
Figure 4.3	Hall signal pull-up example.....	14
Figure 4.4	SPI read waveform example.....	16
Figure 4.5	SPI write waveform example	16
Figure 6.1	Charge pump circuit.....	17
Figure 6.2	Charge pump waveform example.....	17
Figure 6.3	Relationship between VCP and VM (reference date).....	17
Figure 7.1	Application circuit example	18
Figure 8.1	Power dissipation	20
Figure 9.1	Reference land pattern	21
Figure 10.1	Layout example (WQFN40).....	22

Figure 10.2 Layout example (VQFN32)..... 22

List of Tables

Table 1.1 Product comparison..... 5

Table 2.1 Operating range of power supply voltage 6

Table 3.1 SPI I/F Gate drive current setting register..... 8

Table 3.2 Gate drive current capability setting..... 8

Table 4.1 6-PWM input mode..... 13

Table 4.2 3-PWM input mode..... 14

Table 4.3 Independent PMW mode..... 15

1. Main differences between TB67Z83xxFTG, TB67Z85XXFTG

Main differences are shown in table below.

Table 1.1 Product comparison

Product Name	Built-in regulator voltage	Number of current sense amplifiers	Interface	Package
TB67Z830HFTG	3.3 V	0 ch	Hardware	P-VQFN32-0505-0.50-007
TB67Z830SFTG			SPI	
TB67Z833HFTG		3 ch	Hardware	P-WQFN40-0606-0.50-003
TB67Z833SFTG			SPI	
TB67Z850HFTG	5 V	0 ch	Hardware	P-VQFN32-0505-0.50-007
TB67Z850SFTG			SPI	
TB67Z853HFTG		3 ch	Hardware	P-WQFN40-0606-0.50-003
TB67Z853SFTG			SPI	

2. Power Supply Voltage

2.1. Operating Range of Power Supply Voltage

Table 2.1 Operating range of power supply voltage

Characteristic	Symbol	Operating Voltage Range	Absolute Maximum Ratings	Unit
VM supply voltage	V_{VM}	8 ~ 75	80	V
VDRAIN voltage	V_{VDR}	6 ~ 75	80	V

The absolute maximum ratings of a semiconductor device are a set of ratings that must not be exceeded, even for a moment. Do not exceed any of these ratings.

2.2. Power-on Sequence with Control Input Signals

The IC supports single power supply operation. To prevent malfunction when the supply voltage is low, it incorporates an undervoltage lockout (UVLO) circuit.

During unstable power supply conditions, such as power-up or power-down (transient regions), it is recommended to keep the motor in the OFF state. Operate the motor only after the supply voltage has stabilized and then switch the input signals. Similarly, it is recommended to turn off the power only after the motor has completely stopped.

Example of power-on sequence is shown below.

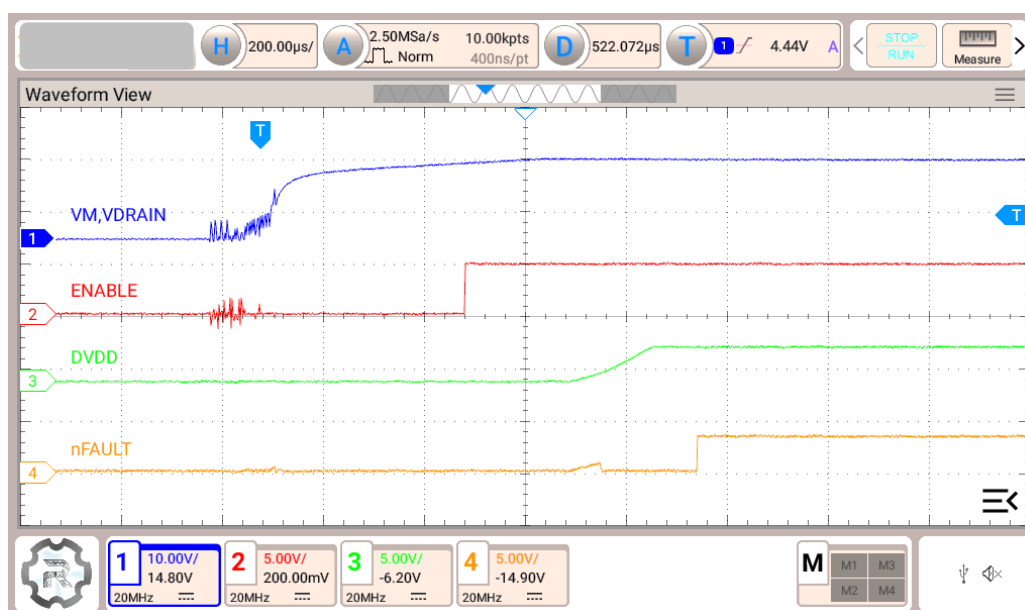


Figure 2.1 Power-on sequence (nFAULT is pull-up to DVDD)

Please input the motor control signal only after nFAULT goes High.

It is also possible to apply separate power supplies to VM and VDRAIN. In this case, the IC is powered from VM, while the reference voltage for the charge pump is VDRAIN. When the system supply voltage is high, using a dual-supply configuration can reduce the IC's power consumption and heat generation.

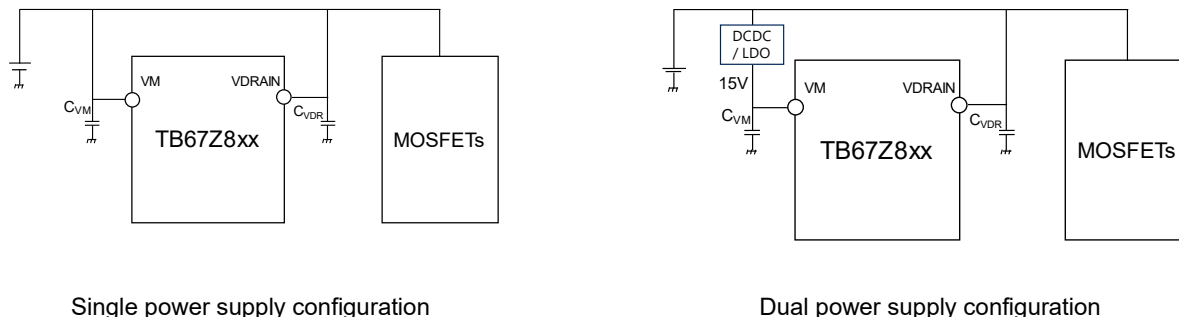


Figure 2.2 Power Supply Configuration Examples

For a dual-supply configuration, to ensure sufficient gate drive voltage for the external MOSFETs, a VM voltage of approximately 15 V is recommended. The VM voltage can be generated using a DC-DC converter or a linear regulator, or it can be supplied simply through a resistor from the power source.

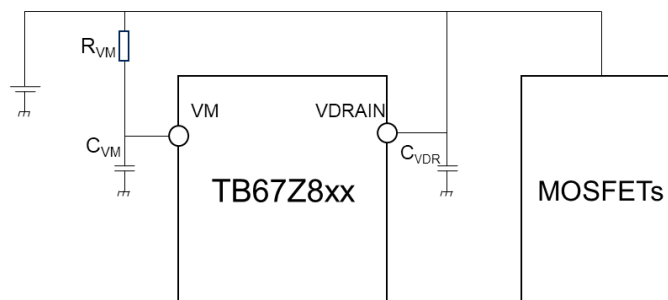


Figure 2.3 Example of supplying VM through a resistor

Select the resistor so that the VM pin voltage is approximately 15 V, taking into account the IC's VM current consumption and voltage fluctuations on the power line.

For example, if the power line voltage is 48 V and the VM current consumption is 15 to 20 mA, inserting a 1.5 kΩ resistor will result in a VM voltage of 18 to 22.5 V (excluding power line voltage variations).

In this case, the resistor's power dissipation is $(20 \text{ mA})^2 \times 1.5 \text{ k}\Omega = 0.6 \text{ W}$, therefore, a resistor with a power rating of at least 1 W is recommended.

3. Output Current

To control the ON, OFF speed of external MOSFETs, the IC incorporates a function to adjust the gate drive current (source and sink current) capability. The source current capability can be set from 10 mA to 1 A, and the sink current capability can be set from 20 mA to 2 A.

In the SPI interface version, the gate drive current capability can be configured via registers. In the hardware interface version, it can be configured through the IDRIVE pin.

Table 3.1 SPI I/F Gate drive current setting register

Register	Setting contents
IDRIVEP_HS	High-side gate drive source current capability
IDRIVEN_HS	High-side gate drive sink current capability
IDRIVEP_LS	Low-side gate drive source current capability
IDRIVEN_LS	Low-side gate drive sink current capability

Table 3.2 Gate drive current capability setting

Source current capability (mA)	Sink current capability (mA)	SPI I/F Register value	Hardware I/F IDRIVE
10	20	0000b	Mode 1
30	60	0001b	Mode 2
60	120	0010b	Mode 3
80	160	0011b	—
120	240	0100b	Mode 4
140	280	0101b	—
170	340	0110b	—
190	380	0111b	—
260	520	1000b	Mode 5
330	660	1001b	—
370	740	1010b	—
440	880	1011b	—
570	1140	1100b	Mode 6
680	1360	1101b	—
820	1640	1110b	—
1000	2000	1111b	Mode 7

Set the gate drive current according to the characteristics of the external MOSFET.

First, to ensure that the external MOSFET can be reliably turned ON and OFF within the drive time, the required source and sink current capability can be estimated using the following formula:

$$I_{\text{Drive}}(\text{min}) = Q_g / (t_{\text{DRIVE}} - t_{\text{PD}}) \quad (\text{Eq.3.1})$$

Q_g : Gate charge of the external MOSFET

t_{DRIVE} : Drive time

t_{PD} : Input propagation delay

Example: Driving TPH1R204PB, since the MOSFET's Q_g is 44 nC (typ.),

When the drive time is set to the maximum of 4000 ns, $I_{\text{Drive}}(\text{min}) = 11.5 \text{ mA}$

When the drive time is set to the minimum of 600 ns, $I_{\text{Drive}}(\text{min}) = 103.5 \text{ mA}$

When turning the MOSFET ON, the source current capability decreases as the gate voltage rises; when turning it OFF, the sink current capability decreases as the gate voltage falls. In addition, drive current should be set with sufficient margin, taking into account variations in drive time, input propagation delay,

and MOSFET gate charge.

If the drive current is too small, the MOSFET may not turn ON/OFF reliably within the drive time, and a gate drive voltage fault may be detected. Conversely, if the drive current is too large, there is a risk of ringing, oscillation, and degraded EMI noise performance. Always evaluate thoroughly on actual hardware and set an appropriate drive current capability.

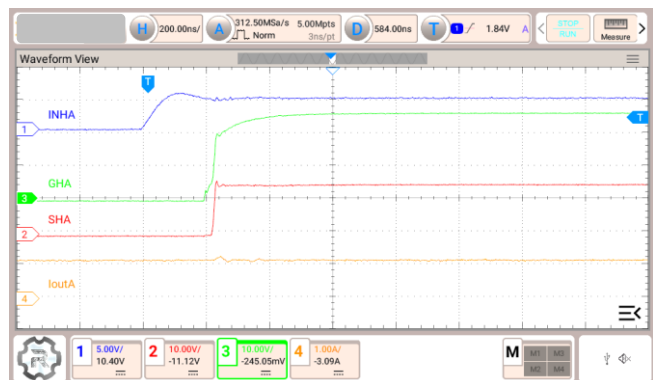


Figure 3.1 Isource = 1 A, H-side, Positive current

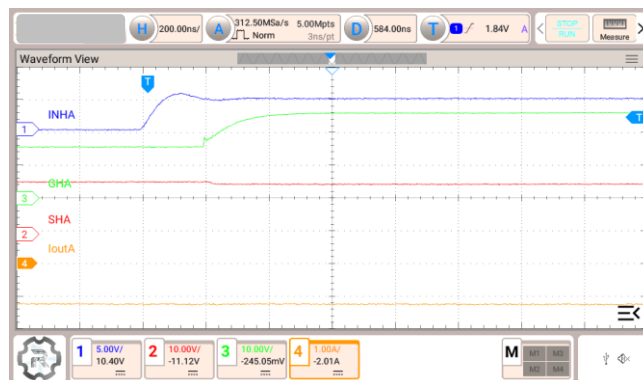


Figure 3.2 Isource = 1 A, H-side, Negative current



Figure 3.3 Isource = 120 mA, H-side, Positive current



Figure 3.4 Isource = 120 mA, H-side, Negative current

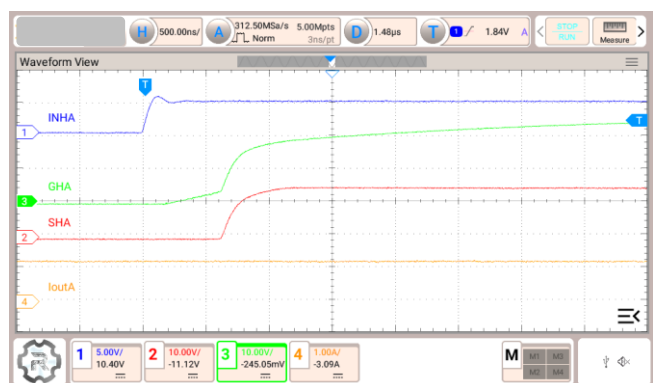


Figure 3.5 Isource = 30 mA, H-side, Positive current



Figure 3.6 Isource = 30 mA, H-side, Negative current

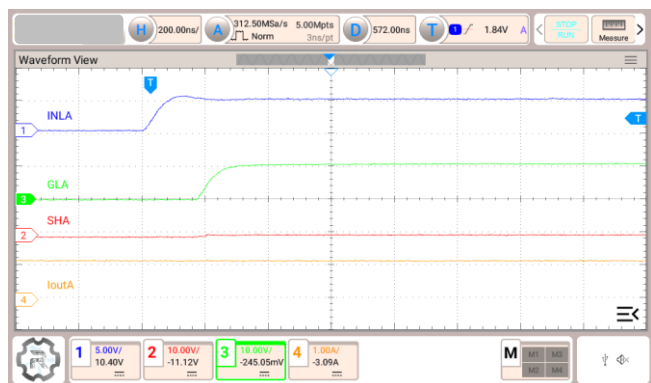


Figure 3.7 Isource = 1 A, L-side, Positive current

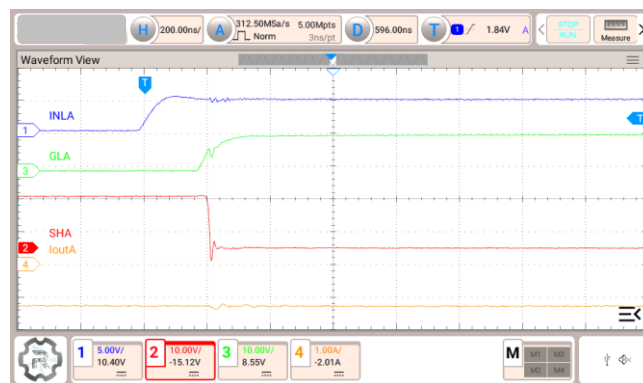


Figure 3.8 Isource = 1 A, L-side, Negative current

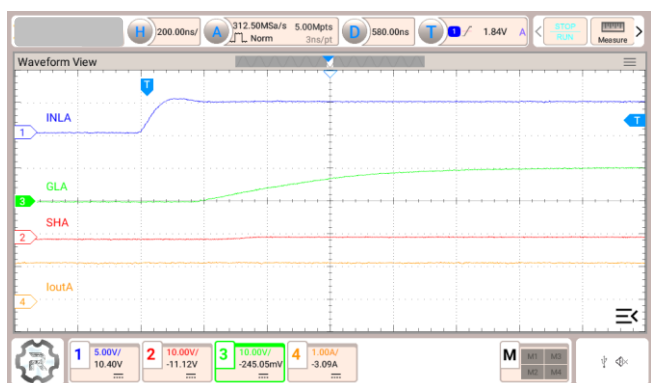


Figure 3.9 Isource = 120 mA, L-side, Positive current



Figure 3.10 Isource = 120 mA, L-side, Negative current



Figure 3.11 Isource = 30 mA, L-side, Positive current



Figure 3.12 Isource = 30 mA, L-side, Negative current



Figure 3.13 $I_{\text{sink}} = 2 \text{ A}$, H-side, Positive current



Figure 3.14 $I_{\text{sink}} = 2 \text{ A}$, H-side Negative current



Figure 3.15 $I_{\text{sink}} = 240 \text{ mA}$, H-side, Positive current



Figure 3.16 $I_{\text{sink}} = 240 \text{ mA}$, H-side, Negative current



Figure 3.17 $I_{\text{sink}} = 60 \text{ mA}$, H-side, Positive current



Figure 3.18 $I_{\text{sink}} = 60 \text{ mA}$ H-side Negative current



Figure 3.19 Isink = 2 A, L-side, Positive current

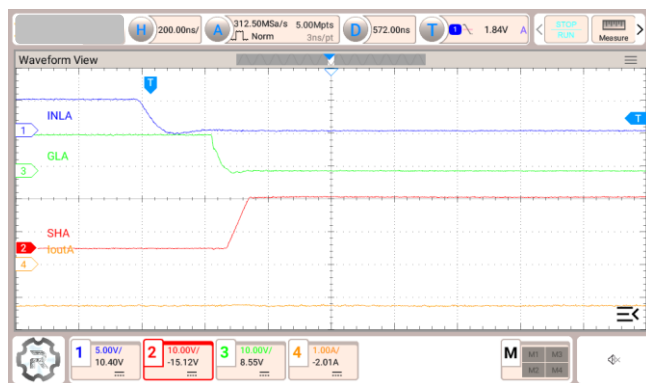


Figure 3.20 Isink = 2 A, L-side, Negative current

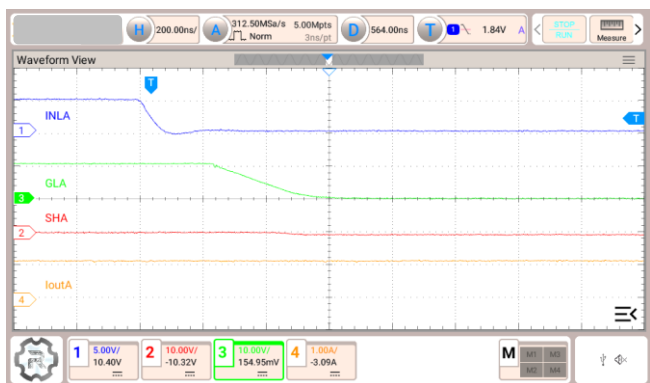


Figure 3.21 Isink = 240 mA, L-side, Positive current

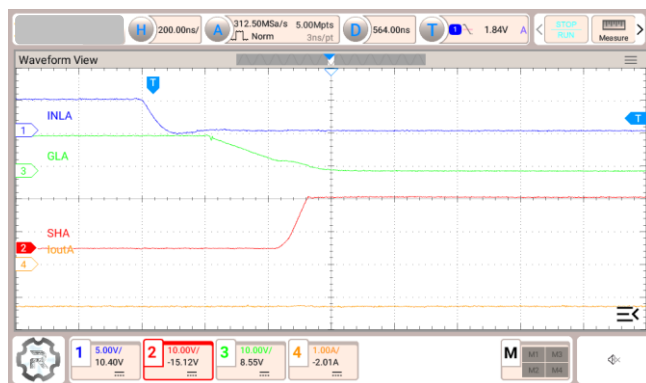


Figure 3.22 Isink = 240 mA, L-side, Negative current



Figure 3.23 Isink = 60 mA, L-side, Positive current

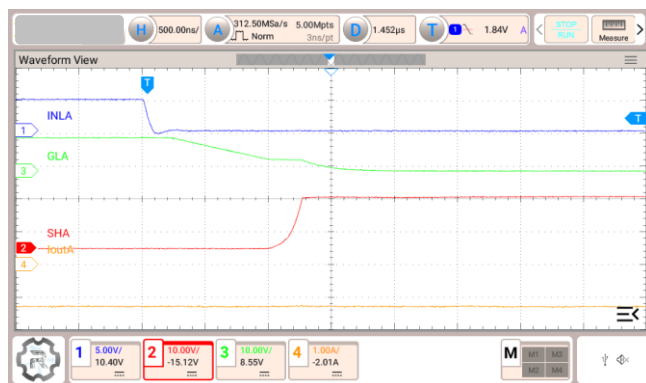


Figure 3.24 Isink = 60 mA, L-side, Negative current

4. Control inputs

4.1. ENABLE signal input

The IC enters standby mode If the ENABLE pin remains Low for 40 μ s or longer. If the Low period of the ENABLE pin is between 5 and 40 μ s, it is recognized as an error reset pulse, which clears the fault flag without transitioning to standby mode.

Note that the above timing depends on the internal oscillator frequency (f_{OSC}). When f_{OSC} is 20 MHz, the time recognized as an error reset pulse is 5 to 40 μ s. If f_{OSC} is higher, this time becomes shorter. Control the ENABLE signal while considering the variation range of f_{OSC} .

4.2. INHx/INLx input

The states of each gate drive output terminal (GHx / GLx) can be controlled via the INHx and INLx pins. This IC supports four types of control modes.

4.2.1. 6-PWM input mode

6-PWM input mode is a commonly used mode, in this mode, each of the three half-bridges can be controlled independently. The state of each half-bridge can be controlled to Low, High, and High impedance (Hi-Z) through the inputs of the INHx and INLx pins.

Table 4.1 6-PWM input mode

INLx	INHx	GLx	GHx	SHx
L	L	L	L	Hi-Z
L	H	L	H	H
H	L	H	L	L
H	H	L	L	Hi-Z

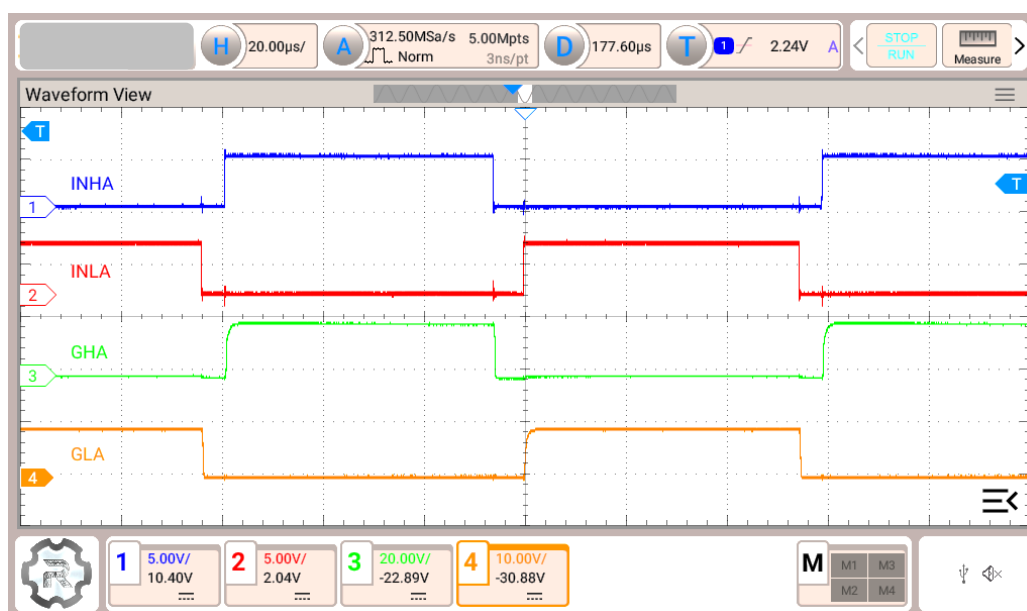


Figure 4.1 6-PWM input mode waveform example

As a noise countermeasure for the INHx/INLx pins, consider adding a capacitor (approximately 1000 pF) between the pins and GND.

4.2.2. 3-PWM input mode

In 3-PWM input mode, each half-bridge can be controlled to either Low or High state via the INHx pin. The INLx pin can be used to set the half-bridge to a high-impedance (Hi-Z) state.

Table 4.2 3-PWM input mode

INLx (ENABLE)	INHx (PWM)	GLx	GHX	SHx
L	X	L	L	Hi-Z
H	L	H	L	L
H	H	L	H	H

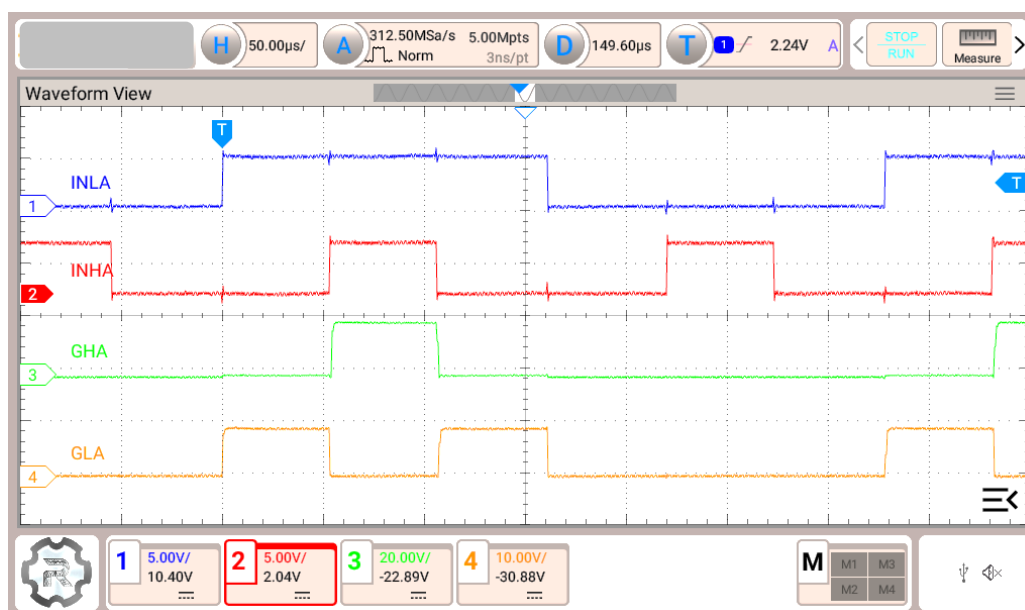


Figure 4.2 3-PWM input mode waveform example

As a noise countermeasure for the INHx/INLx pins, consider adding a capacitor (approximately 1000 pF) between the pins and GND.

4.2.3. Hall input mode

In Hall input mode, by inputting the three-phase Hall signals to the INLA, INHB, and INLB pins, and providing the PWM frequency and PWM duty to the INHA pin and the rotation direction signal to the INHC pin, rectangular wave drive (120° conduction) can be easily achieved. Additionally, the INLC pin can be used to control the BRAKE function. For details, refer to the datasheet section “11.1.1.3. Hall Input Mode.”

When using Hall signals from an open collector output Hall IC, a pull-up circuit is required. Also, as a noise countermeasure, consider adding a capacitor (100–1000 pF) to GND.

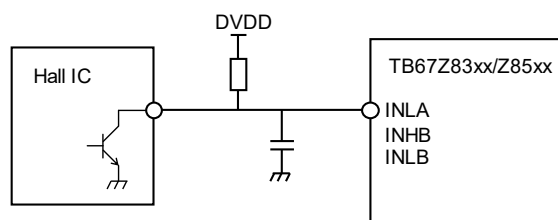


Figure 4.3 Hall signal pull-up example

4.2.4. Independent PWM mode

In independent PWM mode, high-side and low-side gate drive is controlled separately.

Table 4.3 Independent PMW mode

INLx	INHx	GLx	GHX
L	L	L	L
L	H	L	H
H	L	H	L
H	H	H	H

When using both the high-side and low-side of the same half-bridge simultaneously in Independent PWM mode, please disable the VDS over current detection function to avoid false detection.

As a noise countermeasure for the INHx/INLx pins, consider adding a capacitor (approximately 1000 pF) between the pins and GND.

4.3. Hardware Control interface

In the Hardware I/F version, the functions of the IC are controlled using four pins: GAIN, IDRIIVE, MODE, and VDS. Additionally, functions can be configured by shorting to IC's DVDD and AGND or connect through a resistor, eliminating the need to directly apply external voltage.

As a noise countermeasure for the pins, consider adding a capacitor (approximately 1000 pF) between the pins and GND.

4.4. SPI Control interface

In the SPI I/F version, communication with the IC and control of its functions are performed using four pins: nCS, SCLK, SDI, and SDO.

nCS is the chip select pin, and communication is enabled when it is Low. SCLK is the clock signal input pin, SDI is the data input pin, and SDO is the data output pin.

While nCS is High, inputs to SCLK and SDI are ignored, and the SDO pin is Hi-Z state. During transitions of nCS from High to Low or Low to High, SCLK must be held Low. Additionally, nCS should remain High for at least 400 ns between two communications.

The input data from SDI consists of 1-bit command, 4-bit address, and 11-bit data. The first 1-bit (RW) indicates the read/write command, RW = 0b for write, RW = 1b for read. The next 4 bits specify the target register address, and the final 11 bits represent the data content.

The output data from SDO consists of the first 5 bits as "Don't care" bits, and the remaining 11 bits as the register content.

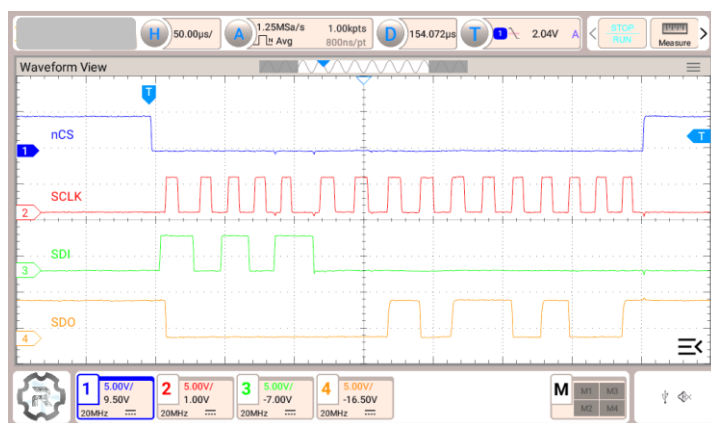


Figure 4.4 SPI read waveform example

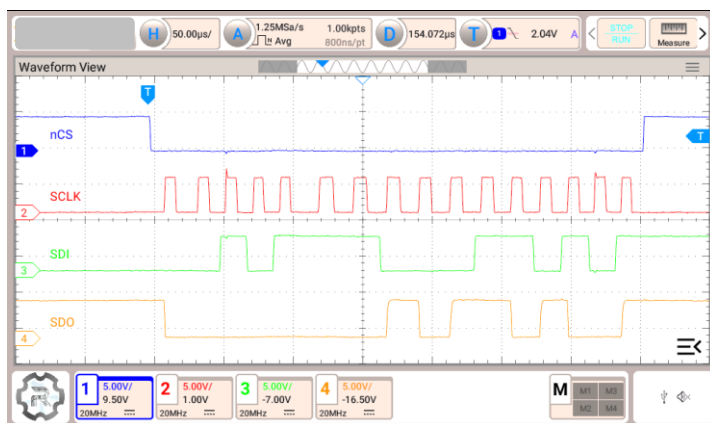


Figure 4.5 SPI write waveform example

5. DVDD output

The DVDD pin is the output of the internal regulator. For the TB67Z83xxFTG, the output voltage is 3.3 V (typ.), and for the TB67Z85xxFTG, it is 5 V (typ.).

To stabilize the internal regulator, add a ceramic capacitor with a capacitance of 1 μF , a withstand voltage of 6.3 V or more, and a temperature characteristic of X5R or X7R, between the DVDD and AGND pins, and place it as close to the device as possible.

If the regulator is used as a power source for external circuits, the output current must be limited to 30 mA. Also, note that the IC may generate heat depending on the regulator's power consumption, so please pay attention to the absolute maximum temperature rating.

6. Charge pump

To generate the power supply for driving the high-side external MOSFET, a charge pump circuit is built into the IC. The operation of the charge pump is as follows:

First, as indicated by the blue arrows in the diagram, electric charge supplied from VDRAIN is charged into C1 (flying capacitor). Next, as indicated by the red arrows, the lower terminal of C1 (CPL) is boosted up to the VM voltage level. Since the potential difference across C1 is already charged and maintained, the upper terminal (CPH) is also boosted by the same amount as CPL, and this voltage is then charged into C2. When the voltage at the VCP pin exceeds $\text{VDRAIN} + 11 \text{ V}$, the charge pump operation stops.

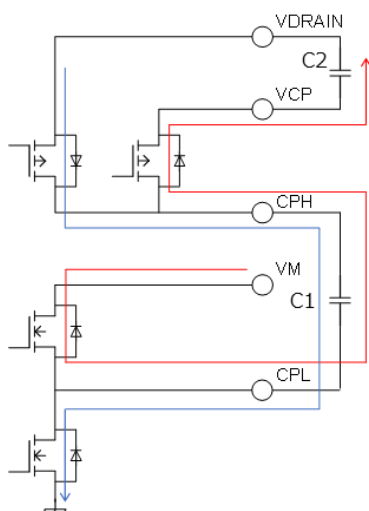


Figure 6.1 Charge pump circuit

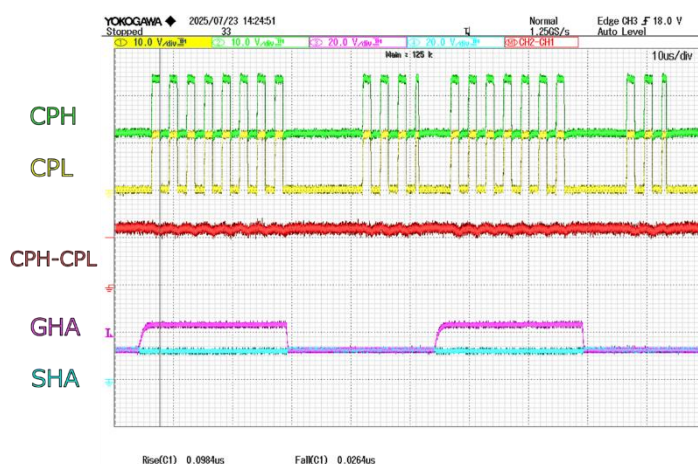


Figure 6.2 Charge pump waveform example

The charge pump voltage depends on the VM voltage. If the VM voltage is below 12 V, the charge pump voltage decreases accordingly.


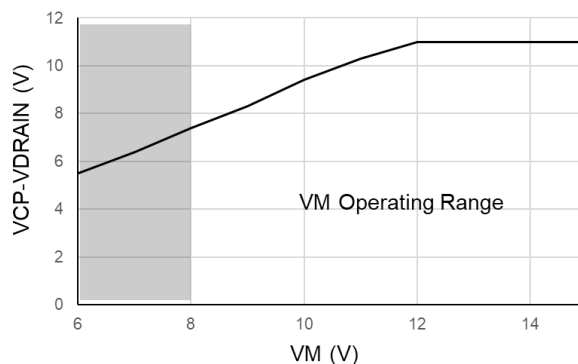


Figure 6.3 Relationship between VCP and VM (reference date)

7. Application Circuit Example

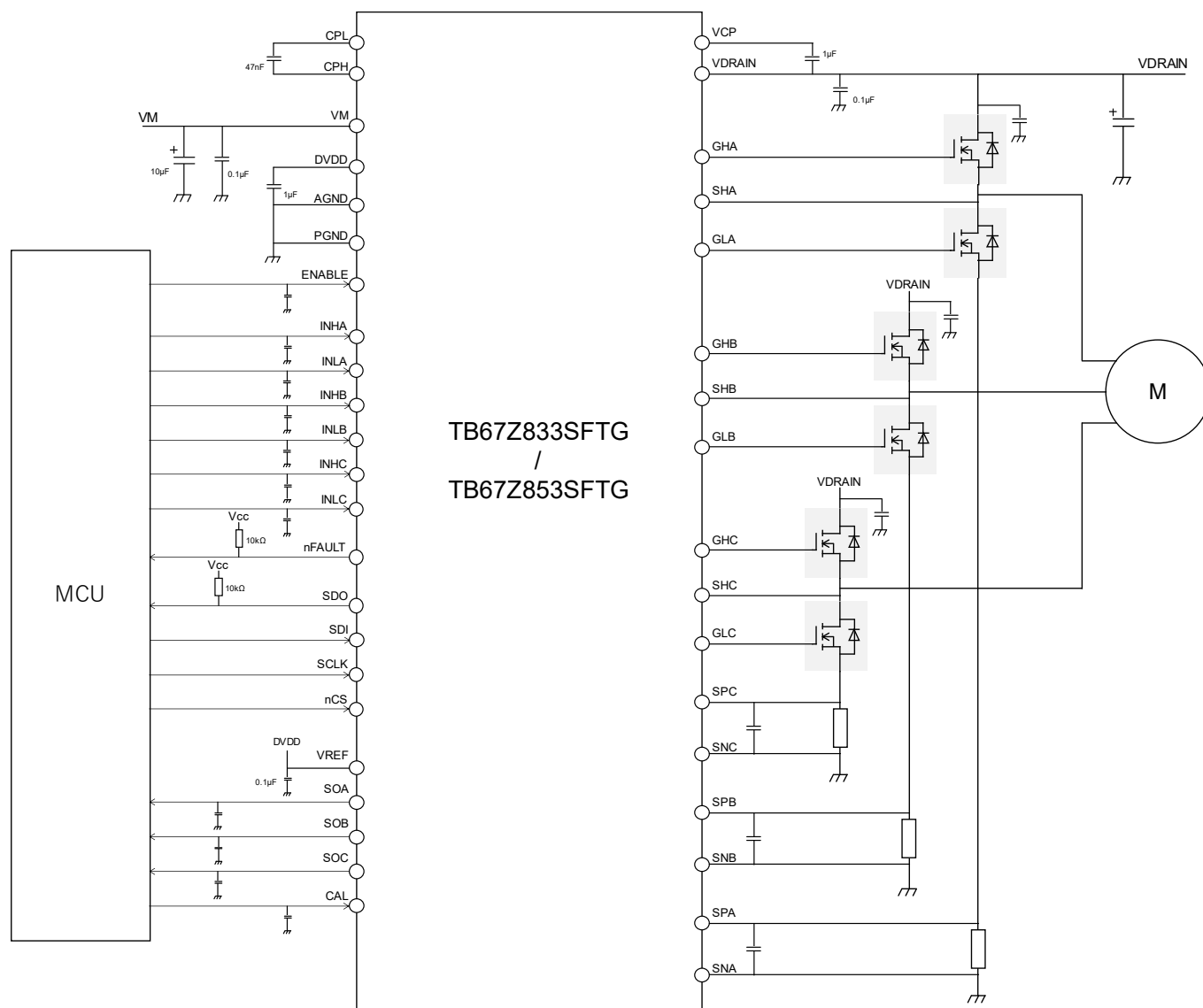

Note: Add capacitors for noise rejection to the input pins as required.

Note: In the event of a short circuit between pins, or a ground/supply fault in output, there is a possibility that device is destroyed or ignited, or over-voltage or over-current may be applied to peripheral components. Therefore, be especially careful when designing the output lines, VM lines, VRAIN lines and ground lines. In addition, rotary insertion (reverse insertion) of the device may also cause breakdown or ignition.

Note: The application circuit examples are not guaranteed for mass production design. Thorough evaluation is required, especially at the mass production design stage. Providing these application circuit examples does not grant a license for industrial property rights.

Figure 7.1 Application circuit example

8. Power Dissipation

Regarding the power consumption of the IC, it can be broadly divided into three components:

1. Power consumed by internal logic and analog circuits
2. Power consumed by the gate driver
3. Power consumed by the regulator

This can be expressed as:

$$P_{(Total)} = P_{(Inter)} + P_{(Gate)} + P_{(DVDD)}$$

Power consumed by internal logic and analog circuits can be estimated using the following formula:

$$\begin{aligned} P_{(Inter)} &= P_{(VM)} + P_{(VDRAIN)} \\ &= V_{VM} \times I_{VM} + V_{VDRAIN} \times I_{VDRAIN} \end{aligned} \quad (\text{Eq.8.1})$$

Power consumed by the gate driver can be estimated using the following formula:

$$\begin{aligned} P_{(Gate)} &= P_{(HS)} + P_{(LS)} \\ &= V_{VCP} \times I_{GATE_HS} + V_{VM} \times I_{GATE_LS} \end{aligned} \quad (\text{Eq.8.2})$$

The average gate drive current, I_{GATE_xx} , depends on the MOSFET's gate charge (Q_g), the PWM frequency (f_{PWM}), and the drive method.

For rectangular wave drive with synchronous rectification (120° commutation): $I_{GATE_xx} = Q_g \times f_{PWM}$

For two-phase modulated sine wave drive (180° commutation): $I_{GATE_xx} = 2 \times Q_g \times f_{PWM}$

Please ensure that I_{GATE_xx} remains within the operating range of 25 mA.

For a PWM frequency of 20 kHz, in the case of rectangular wave drive (120° commutation), use MOSFETs with $Q_g < 1250$ nC, in the case of two-phase modulated sine wave drive (180° commutation), use MOSFETs with $Q_g < 625$ nC.

Power consumed by the regulator can be estimated using the following formula:

$$P_{(DVDD)} = (V_{VM} - V_{DVDD}) \times I_{DVDD} \quad (\text{Eq.8.3})$$

Example:

under the conditions where TB67Z83xxFTG is used with $V_M = V_{DRAIN} = 24$ V, an external MOSFET TPH1R204PB ($Q_g = 44$ nC), 20 kHz two-phase modulated sine wave drive, and 5 mA current supplied externally from DVDD, the IC's power consumption can be estimated as follows:

$$P_{(Inter)} = 24 \text{ V} \times 15 \text{ mA} + 24 \text{ V} \times 4 \text{ mA} = 0.45 \text{ W}$$

$$P_{(Gate)} = (24 \text{ V} + 11 \text{ V}) \times (2 \times 44 \text{ nC} \times 20 \text{ kHz}) + 24 \text{ V} \times (2 \times 44 \text{ nC} \times 20 \text{ kHz}) = 0.10 \text{ W}$$

$$P_{(DVDD)} = (24 \text{ V} - 3.3 \text{ V}) \times 5 \text{ mA} = 0.10 \text{ W}$$

$$P_{(Total)} = P_{(Inter)} + P_{(Gate)} + P_{(DVDD)} = 0.66 \text{ W}$$

8.1. Heat dissipation design

When using ICs, ensure that proper heat dissipation design is implemented so that the specified junction temperature (T_j) is never exceeded under any circumstances.


$$T_j = P_{(Total)} \times R_{th(j-a)} + T_a$$

$R_{th(j-a)}$: Thermal resistance between junction and ambient.

T_a : Ambient temperature.

Please note that the $R_{th(j-a)}$ will be affected due to the circumstances around the device.

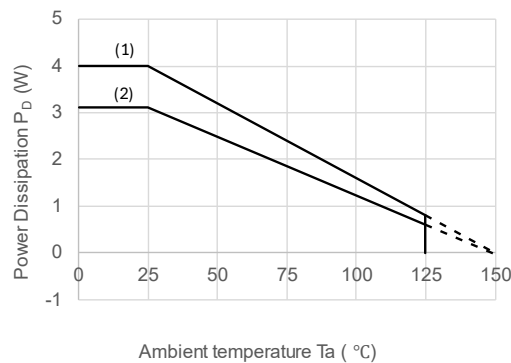Based on the above calculation values, please ensure thorough implementation evaluation for thermal design on the PCB and other components, and design with sufficient margin.




- (1) WQFN40. On PCB (JEDEC 4 layers) and $T_a=25$ °C, $R_{th(j-a)} = 31$ °C/W
 (2) VQFN32, On PCB (JEDEC 4 layers) and $T_a=25$ °C. $R_{th(j-a)} = 40$ °C/W

Figure 8.1 Power dissipation

9. Reference land pattern

P-WQFN40-0606-0.50-003

unit: mm

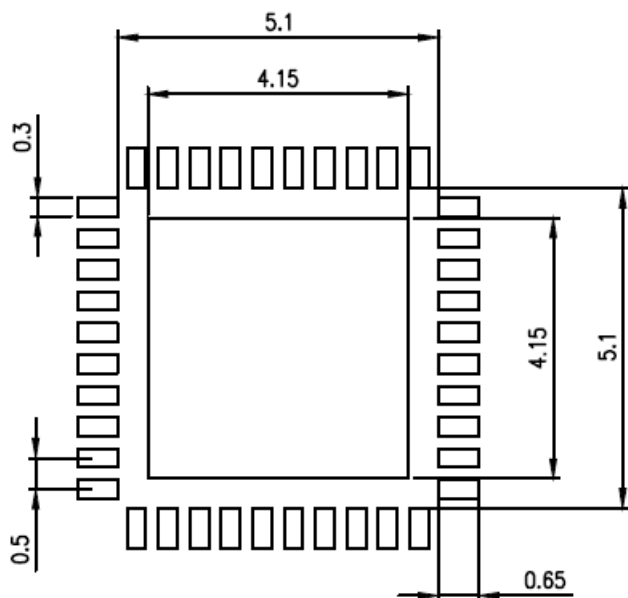

P-VQFN32-0505-0.50-007

unit: mm

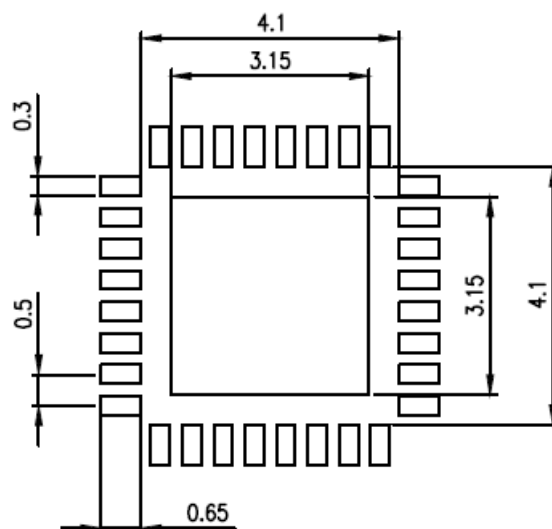


Figure 9.1 Reference land pattern

Notes

- All linear dimensions are given in millimeters unless otherwise specified.
- This drawing is based on JEITA ET-7501 Level3 and should be treated as a reference only. TOSHIBA is not responsible for any incorrect or incomplete drawing and information.
- You are solely responsible for all aspects of your own land pattern, including but not limited to soldering processes.
- The drawing shown may not accurately represent the actual shape or dimensions.
- Before creating and producing design and using, customers must also refer to and comply with the latest versions of all relevant TOSHIBA information and the instructions for the application that Product will be used with or for.

10. Layout Example

10.1. B67Z833xFTG / Z853xFTG

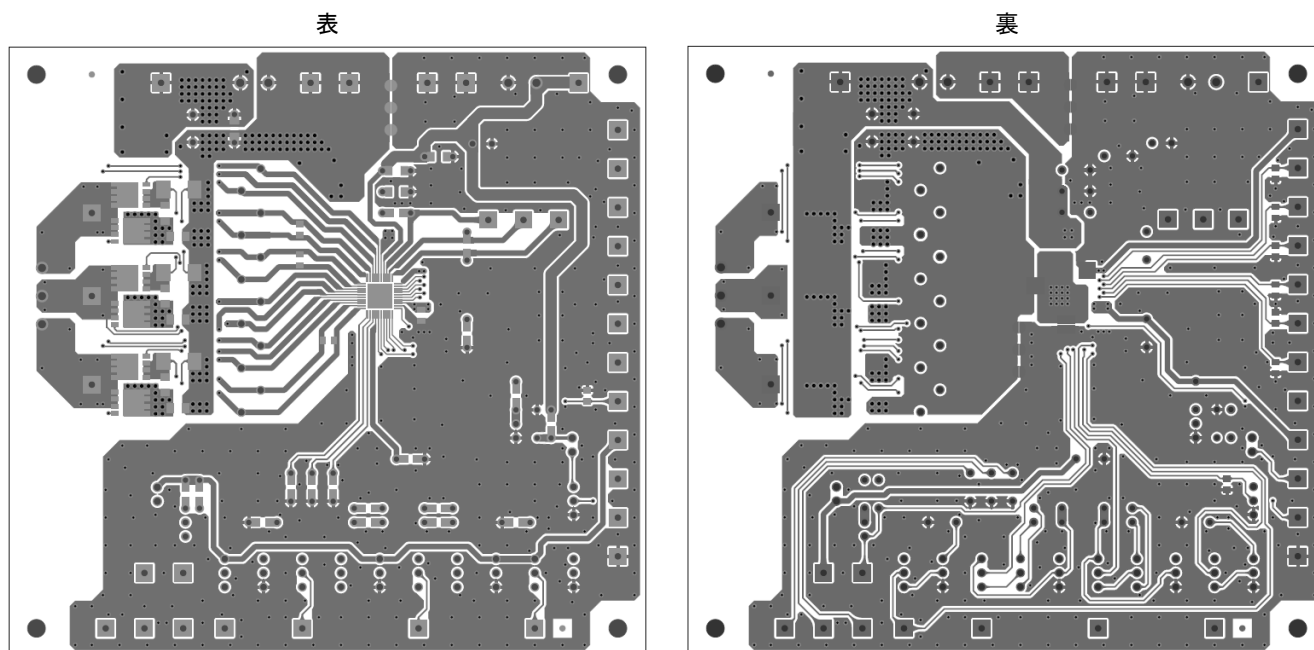


Figure 10.1 Layout example (WQFN40)

10.2. TB67Z830xFTG / Z850xFTG

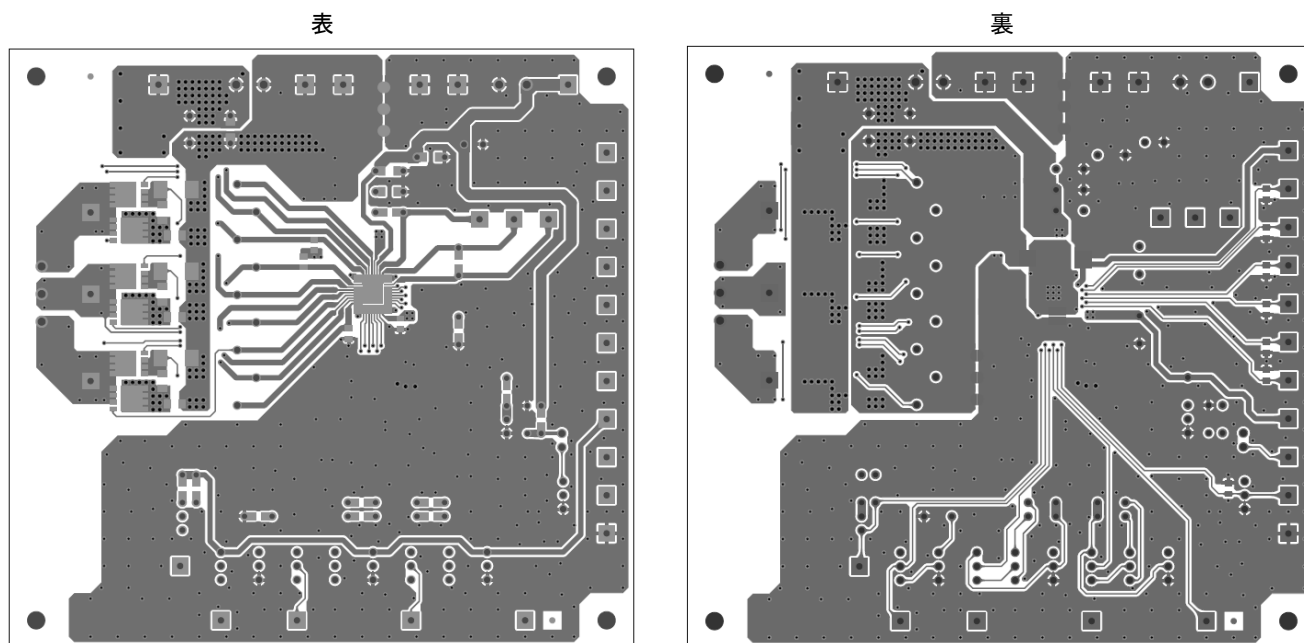


Figure 10.2 Layout example (VQFN32)

Notes on Contents

1. Block Diagrams

Some of the functional blocks, circuits, or constants in the block diagram may be omitted or simplified for explanatory purposes.

2. Equivalent Circuits

The equivalent circuit diagrams may be simplified or some parts of them may be omitted for explanatory purposes.

3. Timing Charts

Timing charts may be simplified for explanatory purposes.

4. Application Circuits

The application circuits shown in this document are provided for reference purposes only. Thorough evaluation is required, especially at the mass production design stage. Toshiba does not grant any license to any industrial property rights by providing these examples of application circuits.

IC Usage Considerations

Notes on Handling of ICs

- (1) The absolute maximum ratings of a semiconductor device are a set of ratings that must not be exceeded, even for a moment. Do not exceed any of these ratings. Exceeding the rating(s) may cause the device breakdown, damage, or deterioration, and may result in injury by explosion or combustion.
- (2) Use an appropriate power supply fuse to ensure that a large current does not continuously flow in case of over current and/or IC failure. The IC will fully break down when used under conditions that exceed its absolute maximum ratings, when the wiring is routed improperly or when an abnormal pulse noise occurs from the wiring or load, causing a large current to continuously flow and the breakdown can lead smoke or ignition. To minimize the effects of the flow of a large current in case of breakdown, appropriate settings, such as fuse capacity, fusing time and insertion circuit location, are required.
- (3) If your design includes an inductive load such as a motor coil, incorporate a protection circuit into the design to prevent device malfunction or breakdown caused by the current resulting from the inrush current at power ON or the negative current resulting from the back electromotive force at power OFF. IC breakdown may cause injury, smoke or ignition. Use a stable power supply with ICs with built-in protection functions. If the power supply is unstable, the protection function may not operate, causing IC breakdown. IC breakdown may cause injury, smoke, or ignition.
- (4) Do not insert devices in the wrong orientation or incorrectly. Make sure that the positive and negative terminals of power supplies are connected properly. Otherwise, the current or power consumption may exceed the absolute maximum rating and exceeding the rating(s) may cause the device breakdown, damage or deterioration, and may result injury by explosion or combustion. In addition, do not use any device that has been powered on while inserted in the wrong orientation or incorrectly even just one time.

Points to Remember on Handling of ICs

- (1) Over current Protection Circuit
Over current protection circuits do not necessarily protect ICs under all circumstances. If the over current protection circuits operate against the over current, clear the over current status immediately. Depending on the method of use and usage conditions, such as exceeding absolute maximum ratings can cause the over current protection circuit to not operate properly or IC breakdown before operation. In addition, depending on the method of use and usage conditions, if overcurrent continues to flow for a long time after operation, the IC may generate heat resulting in breakdown.
- (2) Thermal Shutdown Circuit
Thermal shutdown circuits do not necessarily protect ICs under all circumstances. If the thermal shutdown circuits operate against the over temperature, clear the heat generation status immediately. Depending on the method of use and usage conditions, such as exceeding absolute maximum ratings can cause the thermal shutdown circuit to not operate properly or IC breakdown before operation.
- (3) Heat Radiation Design
In using an IC with large current flow such as power amp, regulator or driver, please design the device so that heat is appropriately radiated, not to exceed the specified junction temperature (T_j) at any time and condition. These ICs generate heat even during normal use. An inadequate IC heat radiation design can lead to decrease in IC life, deterioration of IC characteristics or IC breakdown. In addition, please design the device taking into consideration the effect of IC heat radiation with peripheral components.
- (4) Back-EMF
When a motor rotates in the reverse direction, stops or slows down abruptly, a current flow back to the motor's power supply due to the effect of back-EMF. If the current sink capability of the power supply is small, the device's motor power supply and output pins might be exposed to conditions beyond absolute maximum ratings. To avoid this problem, take the effect of back-EMF into consideration in system design.

RESTRICTIONS ON PRODUCT USE

Toshiba Corporation and its subsidiaries and affiliates are collectively referred to as "TOSHIBA". Hardware, software and systems described in this document are collectively referred to as "Product".

- TOSHIBA reserves the right to make changes to the information in this document and related Product without notice.
- This document and any information herein may not be reproduced without prior written permission from TOSHIBA. Even with TOSHIBA's written permission, reproduction is permissible only if reproduction is without alteration/omission.
- Though TOSHIBA works continually to improve Product's quality and reliability, Product can malfunction or fail. Customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of Product could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Before customers use the Product, create designs including the Product, or incorporate the Product into their own applications, customers must also refer to and comply with (a) the latest versions of all relevant TOSHIBA information, including without limitation, this document, the specifications, the data sheets and application notes for Product and the precautions and conditions set forth in the "TOSHIBA Semiconductor Reliability Handbook" and (b) the instructions for the application with which the Product will be used with or for. Customers are solely responsible for all aspects of their own product design or applications, including but not limited to (a) determining the appropriateness of the use of this Product in such design or applications; (b) evaluating and determining the applicability of any information contained in this document, or in charts, diagrams, programs, algorithms, sample application circuits, or any other referenced documents; and (c) validating all operating parameters for such designs and applications. **TOSHIBA ASSUMES NO LIABILITY FOR CUSTOMERS' PRODUCT DESIGN OR APPLICATIONS.**
- **PRODUCT IS NEITHER INTENDED NOR WARRANTED FOR USE IN EQUIPMENTS OR SYSTEMS THAT REQUIRE EXTRAORDINARILY HIGH LEVELS OF QUALITY AND/OR RELIABILITY, AND/OR A MALFUNCTION OR FAILURE OF WHICH MAY CAUSE LOSS OF HUMAN LIFE, BODILY INJURY, SERIOUS PROPERTY DAMAGE AND/OR SERIOUS PUBLIC IMPACT ("UNINTENDED USE").** Except for specific applications as expressly stated in this document, Unintended Use includes, without limitation, equipment used in nuclear facilities, equipment used in the aerospace industry, lifesaving and/or life supporting medical equipment, equipment used for automobiles, trains, ships and other transportation, traffic signaling equipment, equipment used to control combustions or explosions, safety devices, elevators and escalators, and devices related to power plant. **IF YOU USE PRODUCT FOR UNINTENDED USE, TOSHIBA ASSUMES NO LIABILITY FOR PRODUCT.** For details, please contact your TOSHIBA sales representative or contact us via our website.
- Do not disassemble, analyze, reverse-engineer, alter, modify, translate or copy Product, whether in whole or in part.
- Product shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.
- The information contained herein is presented only as guidance for Product use. No responsibility is assumed by TOSHIBA for any infringement of patents or any other intellectual property rights of third parties that may result from the use of Product. No license to any intellectual property right is granted by this document, whether express or implied, by estoppel or otherwise.
- **ABSENT A WRITTEN SIGNED AGREEMENT, EXCEPT AS PROVIDED IN THE RELEVANT TERMS AND CONDITIONS OF SALE FOR PRODUCT, AND TO THE MAXIMUM EXTENT ALLOWABLE BY LAW, TOSHIBA (1) ASSUMES NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (2) DISCLAIMS ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO SALE, USE OF PRODUCT, OR INFORMATION, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.**
- Do not use or otherwise make available Product or related software or technology for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). Product and related software and technology may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export and re-export of Product or related software or technology are strictly prohibited except in compliance with all applicable export laws and regulations.
- Please contact your TOSHIBA sales representative for details as to environmental matters such as the RoHS compatibility of Product. Please use Product in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. **TOSHIBA ASSUMES NO LIABILITY FOR DAMAGES OR LOSSES OCCURRING AS A RESULT OF NONCOMPLIANCE WITH APPLICABLE LAWS AND REGULATIONS.**