TB67S269 Usage considerations

Summary

The TB67S269 is a two-phase bipolar stepping motor driver using a PWM chopper. The clock in decoder is built in. Fabricated with the BiCD process, rating is 50 V/2.0 A.

© 2016-2017 Toshiba Electronic Devices & Storage Corporation

Contents

Summary	1
1. Power supply voltage	4
1.1. Power supply voltage and usage range	4
1.2. Power supply sequence	4
2. Output current	4
3. Control input	4
4. PWM control	5
5. ADMD control	7
6. Switching characteristics	10
7. Function explanation	10
8. Application circuit (Example)	12
9. Power consumption of the IC	17
10. Power dissipation	18
11. Reference foot pattern (Example)	19
12. Board dimensions	20
12.1. Input	20
12.2. Main part	21
12.3. Options	22
IC Usage Considerations	23
Notes on handling of ICs	23
Points to remember on handling of ICs	24
RESTRICTIONS ON PRODUCT USE	25

Contents of figures

Figure 1.1	Power supply voltage and usage range	4
Figure 4.1	OSCM oscillation frequency	5
Figure 4.2	Chopping frequency (100 kHz)	6
Figure 4.3	Chopping frequency (50 kHz)	6
Figure 5.1	ADMD control	7
Figure 5.2	ADMD waveform	7
Figure 5.3	ADMD current waveform	8
Figure 5.4	ADMD current waveform (When Charge period is more than 1 fchop cycle)	8
Figure 5.5	ADMD current waveform (When the next current step is lower)	9
Figure 5.6	ADMD current waveform (When the Fast continues past 1 fchop cycle)	9
Figure 6.1	Switching characteristics	0
Figure 8.1	Example of application circuit	2
Figure 8.2	Dead band time of thermal shutdown circuit1	5
Figure 8.3	Dead band time of ISD10	6
Figure 10.1	Power dissipation18	8
Figure 11.1	QFN48 foot pattern19	9
Figure 12.1	Input	0
Figure 12.2	Main part2	1
Figure 12.3	Options22	2

Contents of tables

Table 6.1	Switching characteristics	.10
Table 7.1	CLK function	.10
Table 7.2	ENABLE function	.10
Table 7.3	CW/CCW function	. 11
Table 7.4	DMODE function	. 11
Table 8.1	Recommended capacitor values for power supply terminal	.13
Table 8.2	Recommended resistance values for current detection	.13
Table 8.3	Recommended resistance for monitor terminal	.14

1. Power supply voltage

1.1. Power supply voltage and usage range

In using the TB67S269, the voltage should be applied to the terminals of VM, VREFA, and VREFB. The maximum rating of VM supply voltage is 50 V. Usage range of the power supply voltage is 10 to 47 V.

The maximum rating of VREF voltage is 5 V. Usage range of the voltage is 0 to 3.6 V.

As for the voltage of VREF, the voltage of the internal regulator of the IC (VCC) can be also used. (However, if the current is pulled up exceeding the capability of the internal regulator, the regulation of VCC may not be kept. When the voltage of VREF is applied by dividing the voltage of VCC, the total of the voltage-dividing resistance should not be less than 10 k Ω .

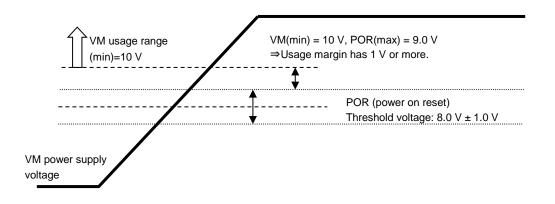


Figure 1.1 Power supply voltage and usage range

1.2. Power supply sequence

There are no special procedures of inputting a power supply and shutdown because the TB67S269 incorporates the power on reset (POR). However, under the unstable state of inputting the power supply (VM) and shutdown, it is recommended to turn off the motor operation. Please operate the motor by switching the input signal after the power supply becomes in the stable state.

2. Output current

Motor usage current should be 2.0 A or less. The maximum current of the actual usage is limited depending on the usage conditions (the ambient temperature, the wiring pattern of the board, the radiation path, and the exciting design). Configure the most appropriate current value after calculating the heat and evaluating the board under the operating environment.

3. Control input

When the logic input signal is inputted under the condition that the voltage of VM is not supplied, the electromotive force by inputting signal is not generated. However, configure the input signal low level before the power supply is applied by referring to the description of the "1.2. Power supply sequence".

4. PWM control

The TB67S269 can adjust the internal oscillation frequency (fOSCM) and the chopping frequency (fchop) with the constant number of the external parts connecting to OSCM terminal.

The relation equations of the OSCM oscillation frequency (fOSCM) and the chopping frequency (fchop) are as follows;
 fOSCM = 1 / [0.56 × {C × (R1 + 500)}]

 $fOSCM = 1 / [0.56 \times {C \times (R1 + 500)}]$ fchop = fOSCM / 16

※ C, R1: external constant number for OSCM (C = 270 pF, R1 = 5.1 kΩ: fOSCM=about 1.12MHz(typ.), fchop: about 70kHz(typ.))


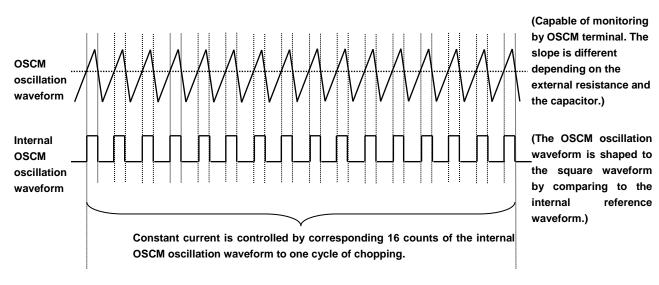


Figure 4.1 OSCM oscillation frequency

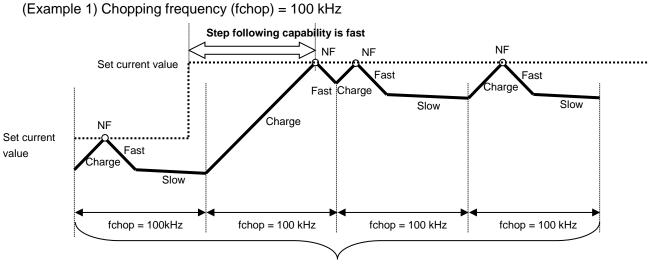
When the chopping frequency is increased, the motor can rotate faster because the following capability of the current steps increases. However, switching loss and heat increase may occur because the number of switching of output MOSFET is larger than the case of low frequency of the chopping.



The number of chopping is large (\Rightarrow Switching loss and heat are large)

Figure 4.2 Chopping frequency (100 kHz)

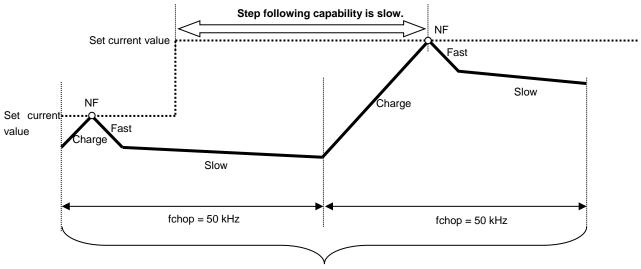(Example 2) Chopping frequency (fchop) = 50 kHz




The number of chopping is small (⇒ Switching loss and heat are small)

Figure 4.3 Chopping frequency (50 kHz)

Generally, it is recommended to configure the frequency in the range of 50 kHz to 100 kHz on the basis of 70kHz.

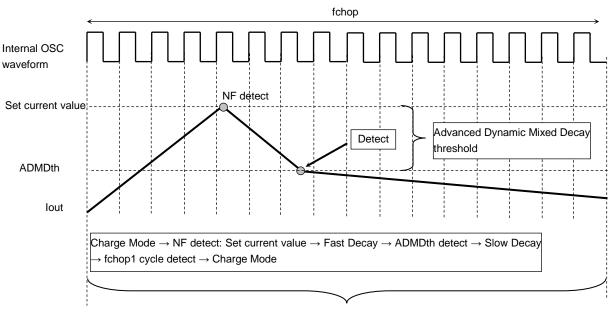
5. ADMD control

The Advanced Dynamic Mixed Decay threshold, which determines the current ripple level during current feedback control, is a unique value.



fchop1 cycle : 16 clk



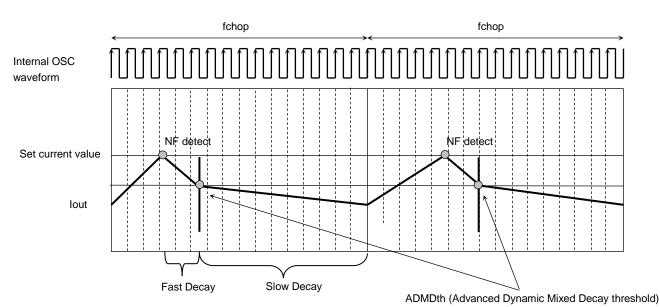

ADMD waveform (current waveform)

Timing charts may be simplified for explanatory purpose.



ADMD current waveform

• When the next current step is higher:

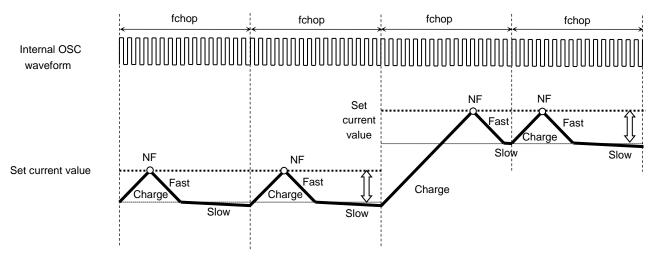


Figure 5.3 ADMD current waveform

• When Charge period is more than 1 fchop cycle:

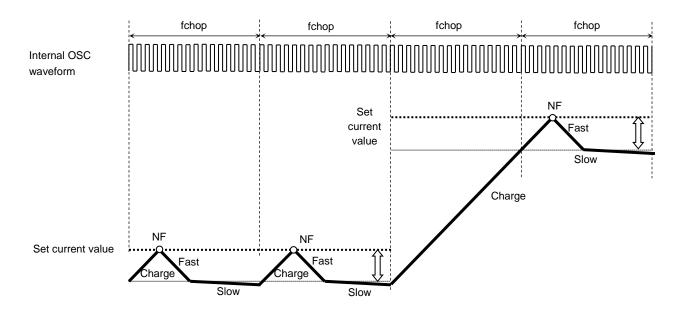


Figure 5.4 ADMD current waveform (When Charge period is more than 1 fchop cycle)

When the Charge period is longer than fchop cycle, the Charge period will be extended until the motor current reaches the

NF threshold. Once the current reaches the next current step, then the sequence will go on to decay mode.

• When the next current step is lower:



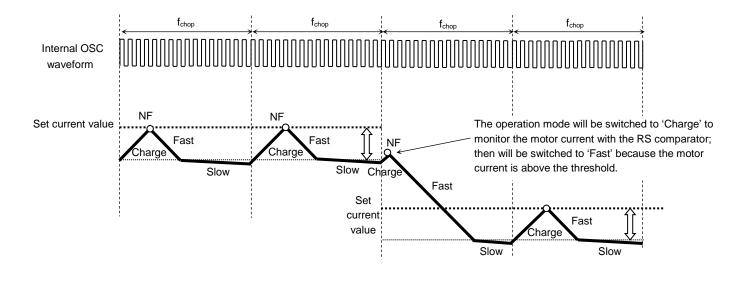


Figure 5.5 ADMD current waveform (When the next current step is lower)

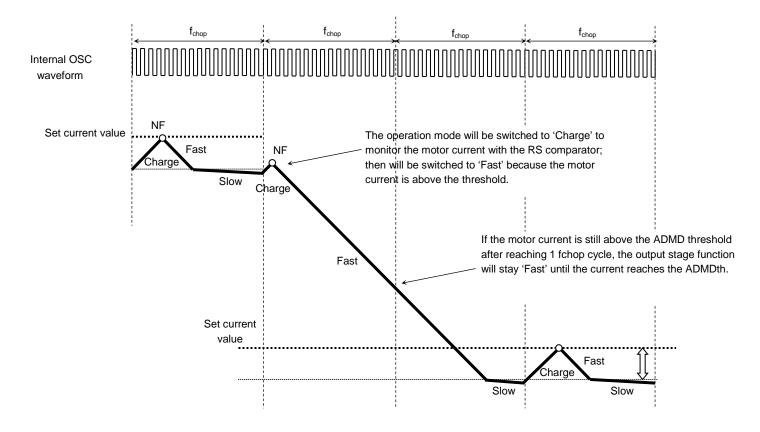
• • When the Fast continues past 1 fchop cycle (the motor current not reaching the ADMD threshold during 1 fchop cycle)



 



6. Switching characteristics

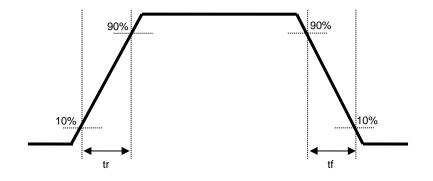



$T_a = 25^{\circ}C$, VM = 24 V, No load				
ltem	Item Typ. Unit			
tr	80	ns		
tf	90	ns		

7. Function explanation

(1) CLK function

Each up-edge of the CLK signal will shift the motor's electrical angle per step.

Table 7.1 CLK function

CLK input	Function	
Up-edge	Shifts the electrical angle per step.	
Down-edge	-(State of the electrical angle does not change.)	

(2) ENABLE function

The ENABLE terminal controls the ON and OFF of the corresponding output stage. This terminal serves to select if the motor is stopped in Off (High impedance) mode or activated. Please set the ENABLE terminal to 'L' during VM power-on and power-off sequence.

ENABLE Input	Function
Н	Output stage='ON' (Normal operation mode)
L	Output stage='OFF) (High impedance mode)

Table 7.2 ENABLE function

(3) CW/CCW function and the output terminal function (Output logic at the time of a charge start)

The CW/CCW terminal controls the rotation direction of the motor. When set to 'Clockwise', the current of OUTA is output first, with a phase difference of 90° . When set to 'Counter clockwise'', the current of OUTB is output first with a phase difference of 90° .

CW/CCW Input	OUT (+)	OUT (-)
H: Clockwise operation(CW)	Н	L
L: Counter clockwise operation(CCW)	L	Н

Table 7.3 CW/CCW function

(4) Step resolution select function


Table 7.4DMODE function

DMODE0	DMODE1	DMODE2	Function	
L	L	L	Standby mode (the OSCM is disabled and the output stage is set to 'OFF' status)	
L	L	Н	Full step resolution	
L	Н	L	Half step resolution(Type (A))	
L	Н	Н	Quarter step resolution	
Н	L	L	Half step resolution(Type (B))	
Н	L	Н	1/8 step resolution	
Н	Н	L	1/16 step resolution	
Н	Н	Н	1/32 step resolution	


*After STANDBY MODE is released, do not input a signal until the internal circuit becomes stable. (1 ms passes after the release of STANDBY MODE is the indication)

When switching the DMODE0,1,2; setting the RESET signal to Low (will set the electrical angle to the initial status), is recommended.

8. Application circuit (Example)

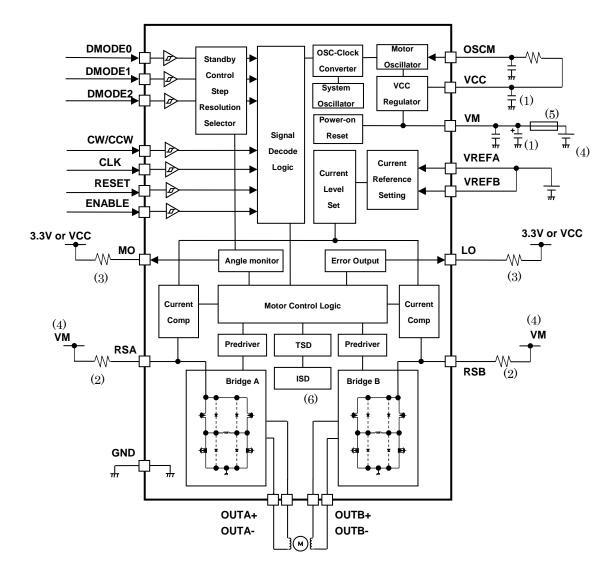

 The application circuits shown in this document are provided for reference purposes only. Thorough evaluation is required, especially at the mass-production design stage.



(1) Capacitor for power supply terminal

To stabilize the power supply voltage of the IC and reduce the noise, connect the appropriate capacitor to each terminal. It is recommended to connect the capacitor as close to the IC as possible. Especially, by connecting the ceramic capacitor near the IC, the change of the power supply at the high frequency range and the noise can be reduced.

ltem	Parts	Тур.	Recommended range
VM-GND	Electrolytic capacitor	100 µF	47 to 100 µF
VIVI-GIND	Ceramic capacitor	0.1 µF	0.01 to 1 µF
VCC-GND Ceramic / Electrolytic capacitor		0.1 µF	0.01 to 1 µF
(VREF-GND)	Ceramic capacitor	0.1 µF	0.01 to 1 µF

 Table 8.1
 Recommended capacitor values for power supply terminal

* VREF-GND: Connect the capacitor in necessary depending on the usage environment.

* It is possible to use the capacitor, which is not the recommended capacitor, depending on the motor load condition and the design pattern of the board.

(2) Resistance of current detection

This IC configures the threshold of the constant current detection by connecting the resistance of current detection between VM and RS terminals. The detection resistance is recommended to connect near the IC. (The motor can be controlled with the accurate current because the influence of the wire resistance of the board can be reduced.)

Table 8.2 F	Recommended re	esistance values	for current detection
-------------	----------------	------------------	-----------------------

Item	Parts	Тур.	Recommended range
VM-RS	Chip / Lead resistance	0.22 Ω (1.5 to 2.0 A)	0.22 to 1.0 Ω
VM-RS	Chip / Lead resistance	0.51 Ω (0 to 1.5 A)	0.22 to 1.0 Ω

The relation equation of the threshold of the constant current detection, Vref voltage, and the resistance of RS detection is as follows;

 $lout(max) = Vref(gain) \times \frac{Vref(V)}{RRS(\Omega)}$

Vref(gain): Vref decay ratio is 1 / 5.0(typ.).

As for the resistance of current detection, the constant number which is out of recommended range can be adopted. In this case, please pay attentions to the followings when the used resistance is high and low.

- When the detection resistance is low, the difference voltage between VM and RS comparing to the internal reference voltage becomes small. So, the current may be largely different from the configured current value.
- When the detection resistance is high, the power applied to the detection resistance increases in motor operation (P=I^2×R). So, in case the same current flows as the case of low resistance, the power dissipation should be larger.

(3) Resistance for monitor terminal

This IC has two open-drain terminals of MO and LO. When internal MOSFET is turned off, it is high impedance as a terminal level. In order to operate the IC with accurate high and low levels, connect the pull-up resistance to the power supply of 3.3 V or 5 V in using.

Table 8.3	Recommended resistance for monitor terminal
-----------	---

ltem	Parts	Тур.	Recommended range
MO,LO- (3.3V or VCC)	Chip / Lead resistance	10 kΩ	10 to 100 kΩ

(4) Wiring pattern for power supply and GND

Since large current may flow in VM, RS, and GND pattern especially, design the appropriate wiring pattern to avoid the influence of wiring impedance. It is very important for surface mounting package to radiate the heat from the heat sink of the back side of the IC to the GND. So, design the pattern by considering the heat design.

(5) Fuse

Use an appropriate power supply fuse for the power supply line to ensure that a large current does not continuously flow in the case of over-current and/or IC failure.

The IC will fully break down when used under conditions that exceed its absolute maximum ratings, when the wiring is routed improperly or when an abnormal pulse noise occurs from the wiring or load, causing a large current to continuously flow and the breakdown can lead to smoke or ignition. To minimize the effects of the flow of a large current in the case of breakdown, appropriate settings, such as fuse capacity, fusing time and insertion circuit location, are required.


This IC incorporates over current detection circuit (ISD) that turns off the output of the IC when over current is detected in the IC. However, it does not necessarily protect ICs under all circumstances. If the Over current detection circuits operate against the over current, clear the over current status immediately. Depending on the method of use and usage conditions, such as exceeding absolute maximum ratings can cause the over current detection circuit to not operate properly or IC breakdown before operation. In addition, depending on the method of use and usage conditions, if over current continues to flow for a long time after operation, the IC may generate heat resulting in breakdown. To avoid above IC destruction and malfunctions caused by noise, the over current detection circuit has a dead band time. So, it is concerned that the over current detection circuit may not operate depending on the output load conditions because of the dead band time. Therefore, in order to avoid continuing this abnormal state, use the fuse for the power supply line.

(6) Abnormality detection function

• Thermal shutdown circuit (TSD)

When the IC detects an over temperature, the internal circuit turns off the output MOSFETs. It has a dead band time to avoid TSD misdetection, which may be triggered by external noise. Reassert the VM power supply or use the standby mode by DMODE terminal to release this function. The TSD is triggered when the device is over heated irregularly. Make sure not to use the TSD function aggressively.

Dead band time of TSD

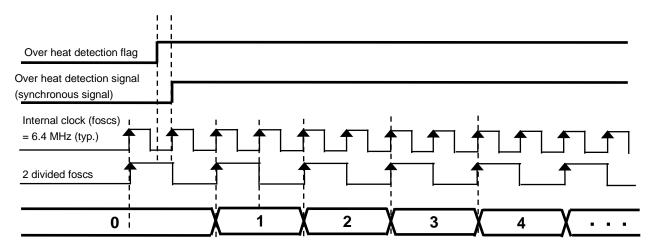

Timing charts may be simplified for explanatory purposes.


Figure 8.2 Dead band time of thermal shutdown circuit

Thermal shutdown circuit has a dead band time to avoid false detection. This dead band time is configured by counting up the internal counter by the fixed frequency (6.4 MHz(typ.)) in the IC.

% foscs = 6.4 MHz(typ.) internal clock 1 / (foscs / 2) × 7 to 8 clk = 1 / foscs × 14 to 16 clk (2.5 to 2.8 μs) • Over current detection (ISD)

When the IC detects an over current, the internal circuits turns off the output MOSFETs. It has a dead band time to avoid ISD misdetection, which may be triggered by external noise. Reassert the VM power supply or use the standby mode by DMODE terminal to release this function.

Dead band time of ISD

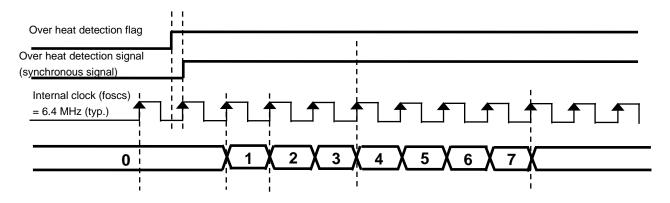

Timing charts may be simplified for explanatory purposes.

Figure 8.3 Dead band time of ISD

ISD has a dead band time to avoid false detection caused by spike current in switching. This dead band time is configured by counting up the internal counter by the fixed frequency (6.4 MHz(typ.)) in the IC.

% foscs = 6.4 MHz(typ.) internal clock 1 / foscs \times 7 to 8 clk (1.09 to 1.25 µs)

9. Power consumption of the IC

Power of the IC is consumed by the transistor of the output block and that of the logic block mainly.

P(total) = P(out) + P(bias)

• Power consumption of the motor output block Power of the output block (P(out)) is consumed by MOSFET of upper and lower H-Bridge.

P(out) =Number of H-Bridge × Iout (A) × VDS (V) = 2 (ch) × Iout (A) × Iout (A) × Ron (Ω).....(1)

When the current waveform of the motor output corresponds to the ideal waveform (2-phase excitation / square wave), average power of output block can be provided as follows;

When Ron = 0.8Ω , Iout (peak: Max) = 1.0 A, VM = 24 VP(out) = $2 \text{ (ch) } \times 1.0 \text{ (A) } \times 1.0 \text{ (A) } \times 0.8(\Omega)$(2) = 1.6 (W)

When the maximum resolution capability of the TB67S269 (8W1-2 phase, 32 steps) is configured by using μ -stepping function, the average power is about 71% (= $1/\sqrt{2}$) and P(out) is 0.8 (W).

• Power consumption of logic and IM systems. Power consumptions of logic and IM systems are calculated by separating the states (operating and stopping).

I (IM3) = 5.5 mA (typ.): Operating I (IM2) = 3.5 mA (typ.): Stopping

Output system is connected to VM (24V). (Output system: Current consumed by the circuit connected to VM + Current consumed by switching output steps)

Power consumption is calculated as follows;

 $P(bias) = 24 (V) \times 0.0055 (A)....(3)$ = 0.132 (W)

• Power consumption Total power consumption P(total) is calculated from the values of formula (2) and (3).

P(total) = P(out) + P(bias) = 1.6 + 0.132 = 1.732 (W)

Standby mode is released. The power consumption in non-operation mode of the motor (waiting mode) is calculated as follows;

 $P = 24 (V) \times 0.0035 (A) = 0.084 (W)$

In actual motor operation, the average current becomes lower than the calculated value because of transition time of the current steps and the ripple of the constant current PWM. Refer to the above equations, evaluate the heat design of the board by the actual board enough, and configure the appropriate margin.

10. Power dissipation

Relation equation of the ambient temperature (T_a) , junction temperature (T_j) , and the heat resistance $(R_{th(j-a)})$ between junction temperature to ambient temperature is as follows;

 $T_j = T_a + P \times R_{th(j \text{-}a)}$

(Example) When 4-layer mounting board ($R_{th(j-a)} = 25^{\circ}C/W$), $T_a = 25^{\circ}C$, P(total) = 1.732 W ($I_{out} = 1.0 \text{ A}$, 2-phase excitation) $T_j = 25 (^{\circ}C) + 25 (^{\circ}C/W) \times 1.732 (W) = 68.3^{\circ}C$

(Reference) Relation between the power dissipation and the ambient temperature

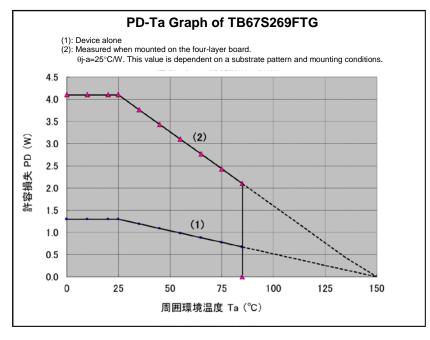


Figure 10.1 Power dissipation

% Pay attention that T_a , $R_{th(j-a)}$, and P(total) depend on the usage environment. When ambient temperature is high, the allowable power consumption decreases.

11. Reference foot pattern (Example)

(1) QFN48 foot pattern (unit: mm)

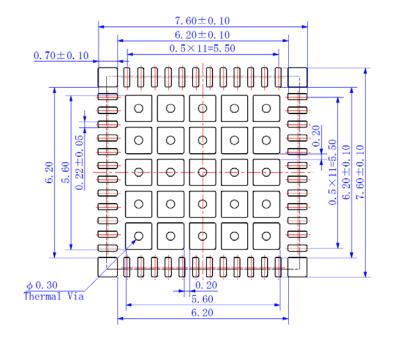


Figure 11.1 QFN48 foot pattern

Toshiba does not guarantee the data for mass production. Please use the data as reference data for customer's application.

Note: In determining the size of mounting board, design the most appropriate pattern by considering the solder bridge, the solder connecting strength, the pattern accuracy in making board, the heat sink of leads, and the mounting accuracy of the IC board.

12. Board dimensions

12.1. Input

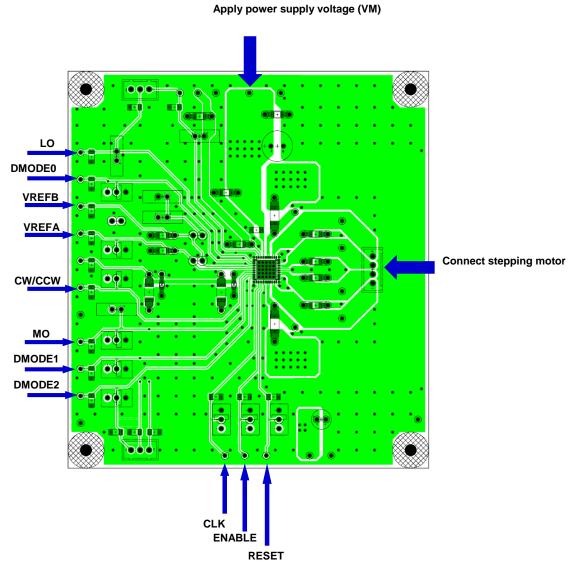


Figure 12.1 Input

Input each power supply and control signal according to above figure.



12.2. Main part


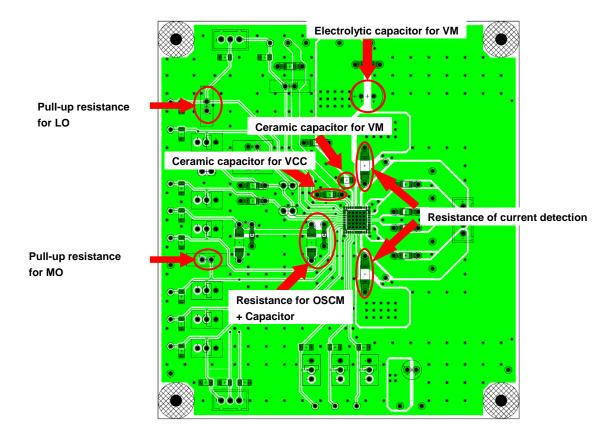



Figure 12.2 Main part

Connect each part referring to "8. Application circuit".

for switch.

12.3. Options

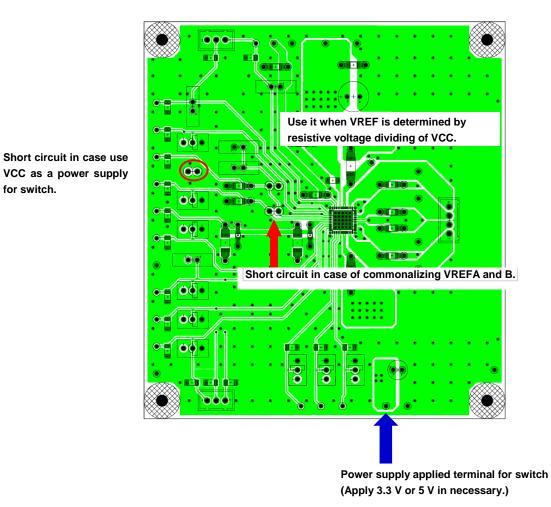

 



Notes on Contents

Block Diagrams

Some of the functional blocks, circuits, or constants in the block diagram may be omitted or simplified for explanatory purposes.

Equivalent Circuits

The equivalent circuit diagrams may be simplified or some parts of them may be omitted for explanatory purposes.

Timing Charts

Timing charts may be simplified for explanatory purposes.

Application Circuits

The application circuits shown in this document are provided for reference purposes only. Thorough evaluation is required, especially at the mass-production design stage.

Toshiba does not grant any license to any industrial property rights by providing these examples of application circuits.

Test Circuits

Components in the test circuits are used only to obtain and confirm the device characteristics. These components and circuits are not guaranteed to prevent malfunction or failure from occurring in the application equipment.

IC Usage Considerations

Notes on handling of ICs

- (1) The absolute maximum ratings of a semiconductor device are a set of ratings that must not be exceeded, even for a moment. Do not exceed any of these ratings.Exceeding the rating(s) may cause device breakdown, damage or deterioration, and may result in injury by explosion or combustion.
- (2)

Use an appropriate power supply fuse to ensure that a large current does not continuously flow in the case of overcurrent and/or IC failure. The IC will fully break down when used under conditions that exceed its absolute maximum ratings, when the wiring is routed improperly or when an abnormal pulse noise occurs from the wiring or load, causing a large current to continuously flow and the breakdown can lead to smoke or ignition. To minimize the effects of the flow of a large current in the case of breakdown, appropriate settings, such as fuse capacity, fusing time and insertion circuit location, are required.

- (3) If your design includes an inductive load such as a motor coil, incorporate a protection circuit into the design to prevent device malfunction or breakdown caused by the current resulting from the inrush current at power ON or the negative current resulting from the back electromotive force at power OFF. IC breakdown may cause injury, smoke or ignition. Use a stable power supply with ICs with built-in protection functions. If the power supply is unstable, the protection function may not operate, causing IC breakdown. IC breakdown may cause injury, smoke or ignition.
- (4) Do not insert devices in the wrong orientation or incorrectly. Make sure that the positive and negative terminals of power supplies are connected properly.

Otherwise, the current or power consumption may exceed the absolute maximum rating, and exceeding the rating(s) may cause device breakdown, damage or deterioration, and may result in injury by explosion or combustion.

In addition, do not use any device inserted in the wrong orientation or incorrectly to which current is applied even just once.

(5) Carefully select external components (such as inputs and negative feedback capacitors) and load components (such as speakers), for example, power amp and regulator. If there is a large amount of leakage current such as from input or negative feedback condenser, the IC output DC voltage will increase. If this output voltage is connected to a speaker with low input withstand voltage, overcurrent or IC failure may cause smoke or ignition. (The overcurrent may cause smoke or ignition from the IC itself.) In particular, please pay attention when using a Bridge Tied Load (BTL) connection-type IC that inputs output DC voltage to a speaker directly.

Points to remember on handling of ICs

Overcurrent detection Circuit

Overcurrent detection circuits (referred to as current limiter circuits) do not necessarily protect ICs under all circumstances. If the overcurrent detection circuits operate against the overcurrent, clear the overcurrent status immediately.

Depending on the method of use and usage conditions, exceeding absolute maximum ratings may cause the overcurrent detection circuit to operate improperly or IC breakdown may occur before operation. In addition, depending on the method of use and usage conditions, if overcurrent continues to flow for a long time after operation, the IC may generate heat resulting in breakdown.

Thermal Shutdown Circuit

Thermal shutdown circuits do not necessarily protect ICs under all circumstances. If the thermal shutdown circuits operate against the over-temperature, clear the heat generation status immediately. Depending on the method of use and usage conditions, exceeding absolute maximum ratings may cause the thermal shutdown circuit to operate improperly or IC breakdown to occur before operation.

Heat Radiation Design

When using an IC with large current flow such as power amp, regulator or driver, design the device so that heat is appropriately radiated, in order not to exceed the specified junction temperature (TJ) at any time or under any condition. These ICs generate heat even during normal use. An inadequate IC heat radiation design can lead to decrease in IC life, deterioration of IC characteristics or IC breakdown. In addition, when designing the device, take into consideration the effect of IC heat radiation with peripheral components.

Back-EMF

When a motor rotates in the reverse direction, stops or slows abruptly, current flows back to the motor's power supply owing to the effect of back-EMF. If the current sink capability of the power supply is small, the device's motor power supply and output terminals might be exposed to conditions beyond the absolute maximum ratings. To avoid this problem, take the effect of back-EMF into consideration in system design.

RESTRICTIONS ON PRODUCT USE

Toshiba Corporation and its subsidiaries and affiliates are collectively referred to as "TOSHIBA". Hardware, software and systems described in this document are collectively referred to as "Product".

- TOSHIBA reserves the right to make changes to the information in this document and related Product without notice.
- This document and any information herein may not be reproduced without prior written permission from TOSHIBA. Even with TOSHIBA's written permission, reproduction is permissible only if reproduction is without alteration/omission.
- Though TOSHIBA works continually to improve Product's quality and reliability, Product can malfunction or fail. Customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of Product could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Before customers use the Product, create designs including the Product, or incorporate the Product into their own applications, customers must also refer to and comply with (a) the latest versions of all relevant TOSHIBA information, including without limitation, this document, the specifications, the data sheets and application notes for Product and the precautions and conditions set forth in the "TOSHIBA Semiconductor Reliability Handbook" and (b) the instructions for the applications, including but not limited to (a) determining the appropriateness of the use of this Product in such design or applications; (b) evaluating and determining the applicability of any information contained in this document, or in charts, diagrams, programs, algorithms, sample application circuits, or any other referenced documents; and (c) validating all operating parameters for such designs and applications. TOSHIBA ASSUMES NO LIABILITY FOR CUSTOMERS' PRODUCT DESIGN OR APPLICATIONS.
- PRODUCT IS NEITHER INTENDED NOR WARRANTED FOR USE IN EQUIPMENTS OR SYSTEMS THAT REQUIRE EXTRAORDINARILY HIGH LEVELS OF QUALITY AND/OR RELIABILITY, AND/OR A MALFUNCTION OR FAILURE OF WHICH MAY CAUSE LOSS OF HUMAN LIFE, BODILY INJURY, SERIOUS PROPERTY DAMAGE AND/OR SERIOUS PUBLIC IMPACT ("UNINTENDED USE"). Except for specific applications as expressly stated in this document, Unintended Use includes, without limitation, equipment used in nuclear facilities, equipment used in the aerospace industry, medical equipment, equipment used for automobiles, trains, ships and other transportation, traffic signaling equipment, equipment used to control combustions or explosions, safety devices, elevators and escalators, devices related to electric power, and equipment used in finance-related fields. IF YOU USE PRODUCT FOR UNINTENDED USE, TOSHIBA ASSUMES NO LIABILITY FOR PRODUCT. For details, please contact your TOSHIBA sales representative.
- Do not disassemble, analyze, reverse-engineer, alter, modify, translate or copy Product, whether in whole or in part.
- Product shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.
- The information contained herein is presented only as guidance for Product use. No responsibility is assumed by TOSHIBA for any infringement of patents or any other intellectual property rights of third parties that may result from the use of Product. No license to any intellectual property right is granted by this document, whether express or implied, by estoppel or otherwise.
- ABSENT A WRITTEN SIGNED AGREEMENT, EXCEPT AS PROVIDED IN THE RELEVANT TERMS AND CONDITIONS OF SALE FOR PRODUCT, AND TO THE MAXIMUM EXTENT ALLOWABLE BY LAW, TOSHIBA (1) ASSUMES NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (2) DISCLAIMS ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO SALE, USE OF PRODUCT, OR INFORMATION, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.
- Do not use or otherwise make available Product or related software or technology for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). Product and related software and technology may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export and re-export of Product or related software or technology are strictly prohibited except in compliance with all applicable export laws and regulations.
- Please contact your TOSHIBA sales representative for details as to environmental matters such as the RoHS compatibility of Product. Please
 use Product in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without
 limitation, the EU RoHS Directive. TOSHIBA ASSUMES NO LIABILITY FOR DAMAGES OR LOSSES OCCURRING AS A RESULT OF
 NONCOMPLIANCE WITH APPLICABLE LAWS AND REGULATIONS.

TOSHIBA ELECTRONIC DEVICES & STORAGE CORPORATION