

# TOSHIBA

## **Tips and Hints for Using eFuse ICs** **—Useful functions available with eFuse ICs**

Toshiba Electronic Devices & Storage Corporation


# Contents

- 01 Introduction: Review of the basics of eFuse ICs
- 02 Application examples and usage
- 03 Current and future requirements for eFuse ICs
- 04 Latest eFuse IC products
- 05 Summary

# 01

## Introduction

Review of the basics of eFuse ICs

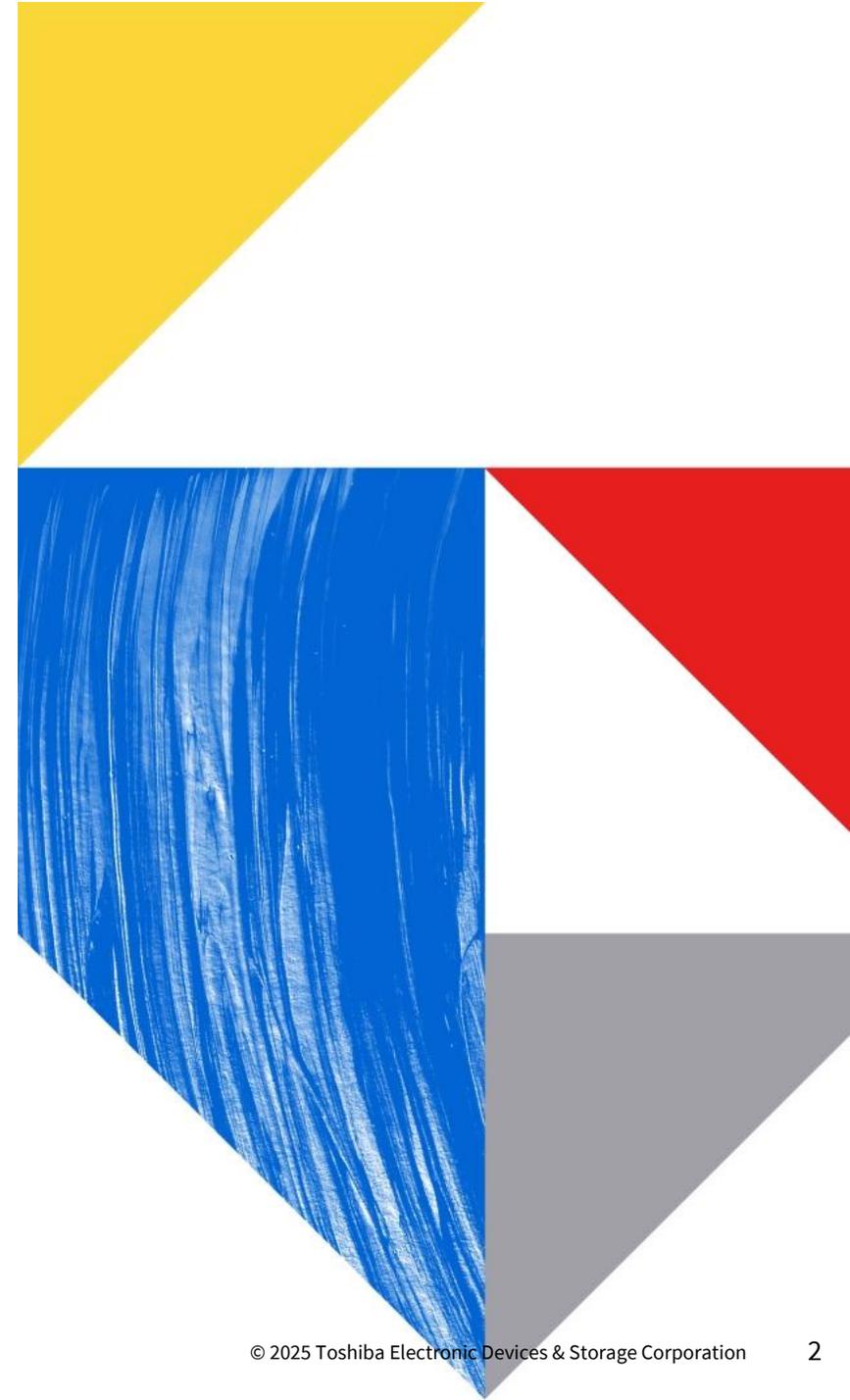

### eFuse ICs provide three major advantages.

- ◆ Being semiconductor devices, eFuse ICs can be used repeatedly.
- ◆ eFuse ICs provide better protection performance than conventional mechanical fuses.
- ◆ eFuse ICs help simplify the process of obtaining certification for IEC 62368-1, a new safety standard.

## eFuse ICs can be used repeatedly


### Mechanical fuse

The mechanical fuse relies on the irreversible melting process.




### eFuse IC

Electronic control

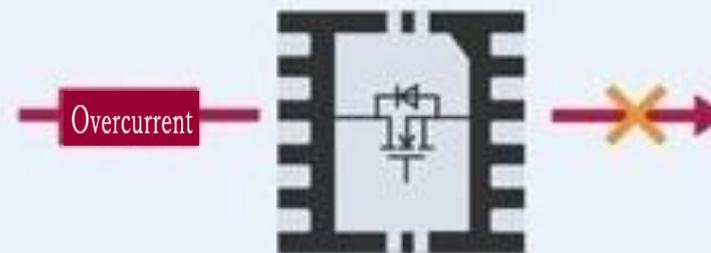

# Advantages of eFuse ICs (2)

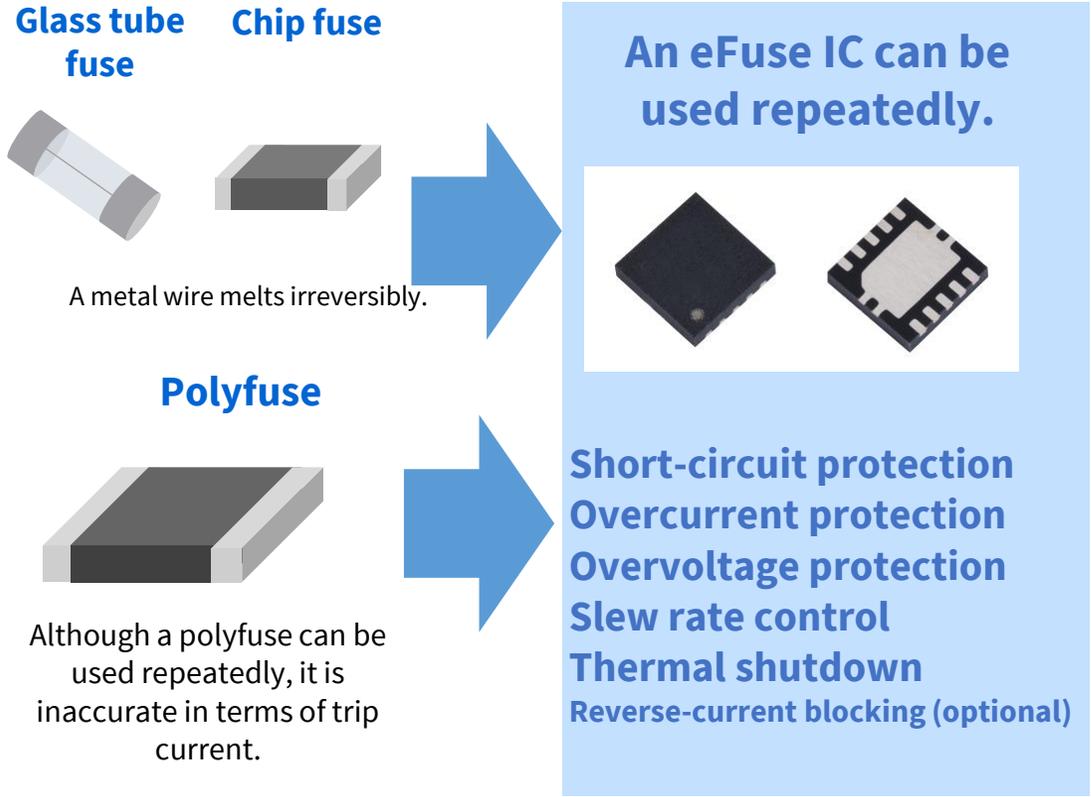**eFuse ICs provide better protection performance than conventional mechanical fuses.**



	Glass tube fuses	Chip fuses	Polyfuses	Electronic fuses eFuse ICs
<b>Repeated use</b>	Impossible	Impossible	Possible but with constraints	Possible without any constraints
<b>Speed and accuracy of overcurrent protection</b>	Slow	Slow	Slow	Fast
<b>Additional protection features</b>	N/A	N/A	N/A	Available
<b>Sensitivity to ambient temperature</b>	Large (adverse)	Large (adverse)	Large (adverse)	Small
<b>Fuse footprint</b>	Large	Small	Large	Moderate
<b>Total footprint required, including protection circuitry</b>	Large	Large	Large	Small
<b>Fuse cost</b>	Moderate	Low	Very high	Moderate
<b>Total cost, including costs of protection circuitry and maintenance</b>	Very high	Very high	Very high	Very low

## Advantages of eFuse ICs (3)

**eFuse ICs help reduce the workload required to obtain IEC 62368-1 certification for an electronic system.**

Withdrawn in December 2020

Enforced in December 2020

**IEC 60950-1**

**Safety standard for information technology equipment**

**IEC 60065**

**Safety standard for audio, video and similar electronic apparatus**

**IEC 62368-1**

**New safety standard for audio/video, information and communication technology equipment**

IEC 62368-1 is a new safety standard developed based on the principles of hazard-based safety engineering (HBSE) that emphasizes the protection of the human body from harm.

### **IEC 62368-1 G9**

#### **Tests for integrated circuit (IC) current limiters**

- Continuous operation test under the maximum load
  - Continuous operation test with the output short-circuited
  - Continuous output short-circuit test
  - Continuous operation test in overcurrent protection mode
- etc.

**Using certified fuses helps reduce the workload required to obtain IEC 62368-1 certification for an electronic system.**

# Examples of applications using electronic fuses



Notebook  
PCs



SSDs/HDDs



Servers



Printers




Video players  
and recorders



Game consoles



VR and AR  
goggles

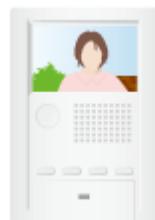

Smart speakers



Headsets

Many other I/O devices


**Electronic fuses have diverse applications.**

## Summary of eFuse ICs

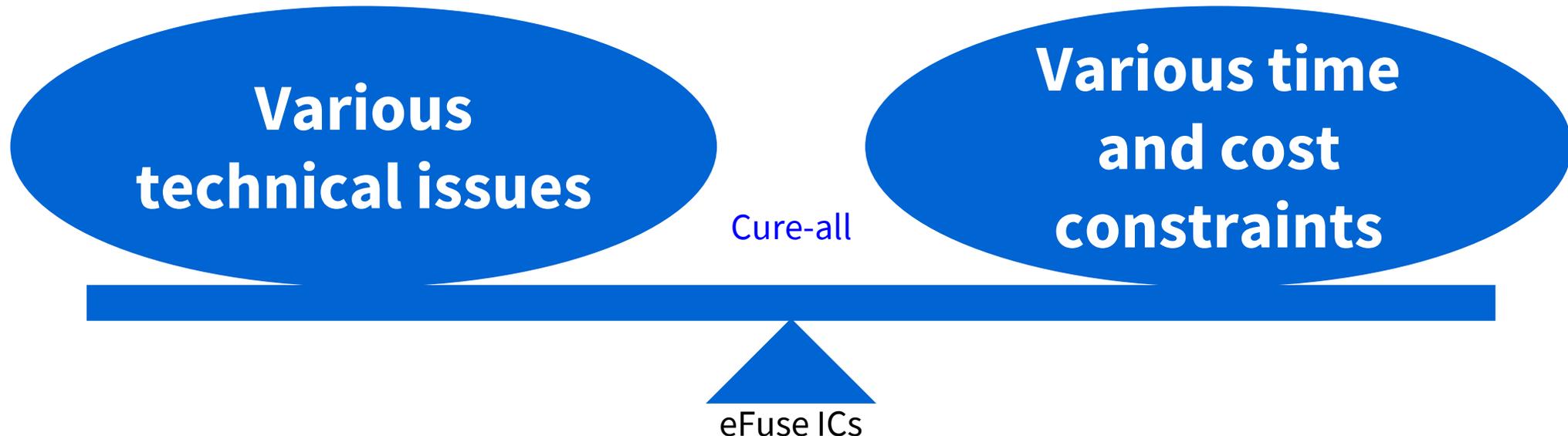**eFuse ICs provide solutions for various technical issues while meeting time and cost constraints.**

- ✓ Voltage and current specifications
- ✓ Power and heat dissipation
- ✓ Protection operation
- ✓ Requirements of reliability tests and various technical standards


- ✓ Part count
- ✓ Board area requirement
- ✓ Time
- ✓ Cost




# 02

## Application examples and usage

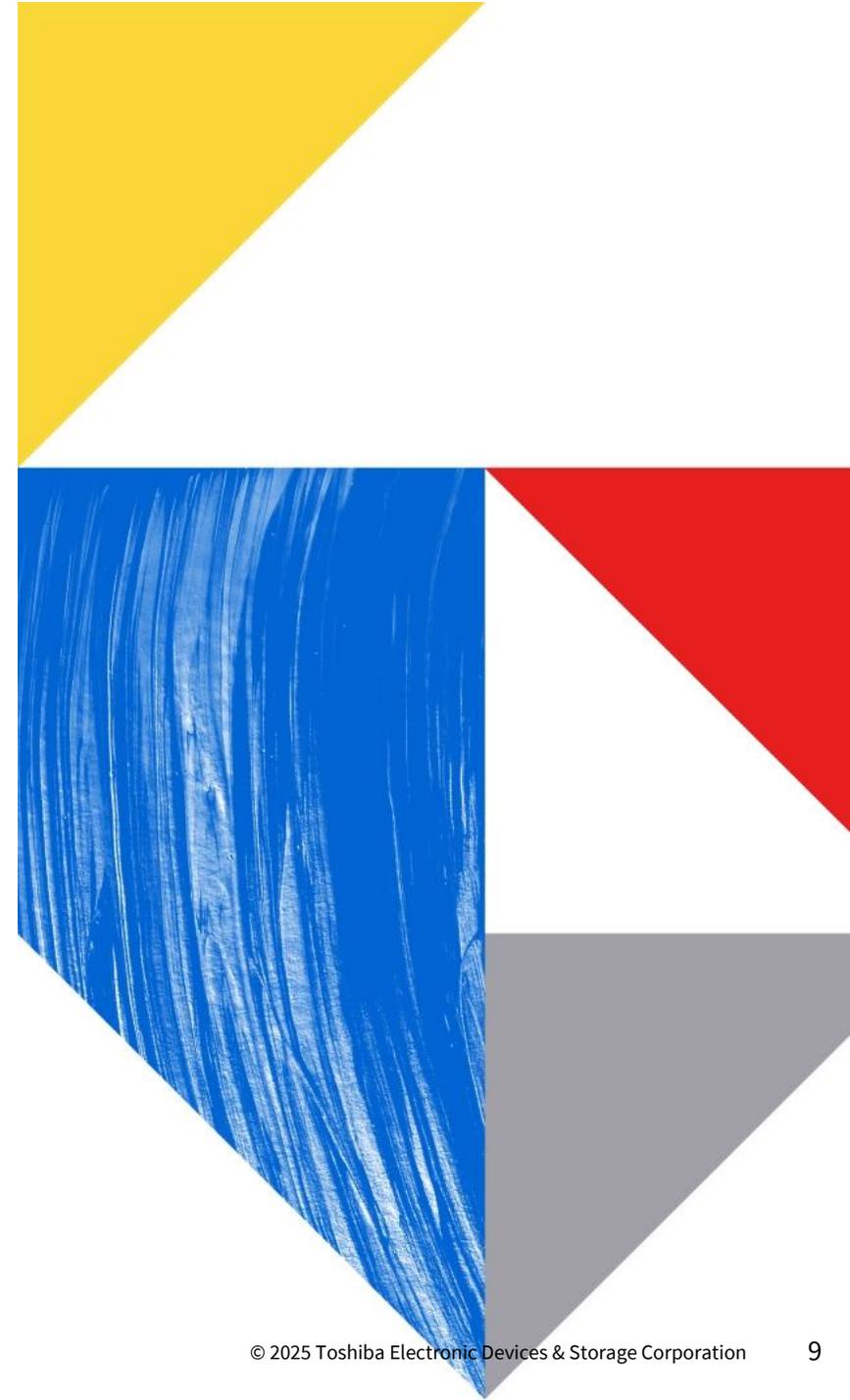1. Protection of power rails from hot plugging
2. System fault detection and power rail protection using the FLAG output
3. Multiplexing and protection of two power rails



# Basic usage of eFuse ICs

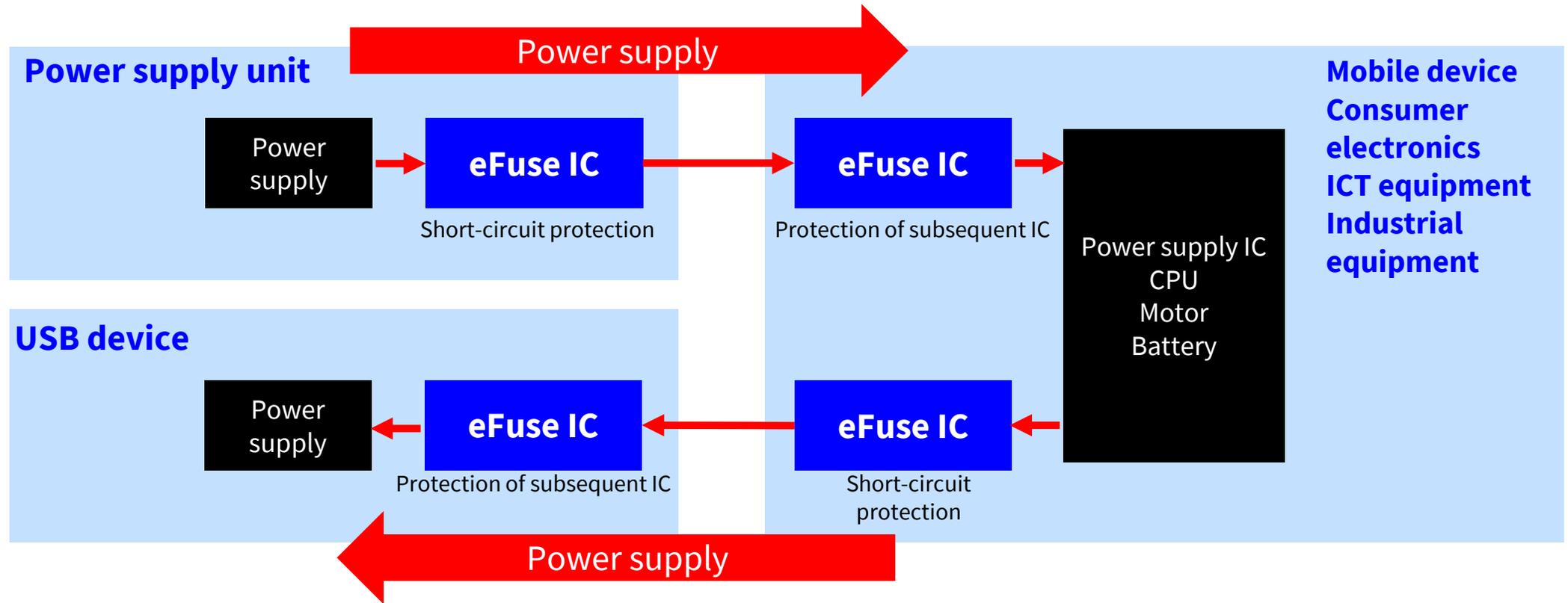

This section shows the basic usage of eFuse ICs.

### 3 application examples using some of the features available with eFuse ICs.

1. Protection of power rails from hot plugging
2. System fault detection and power rail protection using the FLAG output
3. Multiplexing and protection of two power rails

## 1. Protection of power rails from hot plugging


# Protection of power rails from hot plugging

## What is hot plugging?

Insertion and removal of a component to/from a running system

### Examples of hot-swapping/hot-plugging

Plugging a cable into  
a notebook PC

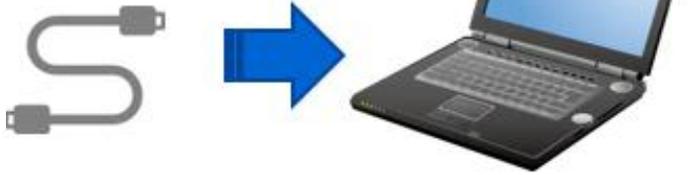

Replacing an  
HDD/SSD of a server



Considerations for power rails during hot plugging


- ◆ **Short-circuiting** of a power supply port due to dust, etc.
- ◆ **Chatter** or **inrush current** upon electrical contact
- ◆ Unexpected application of **excessive voltage** due to wrong connections

# Three benefits of using eFuse ICs along power rails vulnerable to hot-plug events


## eFuse ICs simplify hot-plug protection.

Short-circuit and overcurrent protection

Short-circuit protection

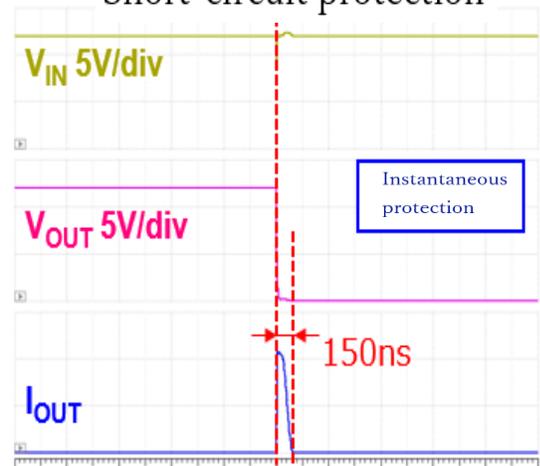


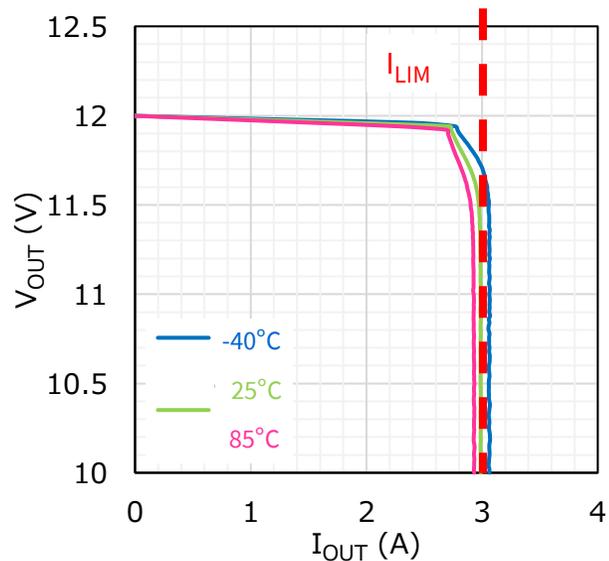This is a simulated waveform of the TCKE8 series.




Inrush current suppression

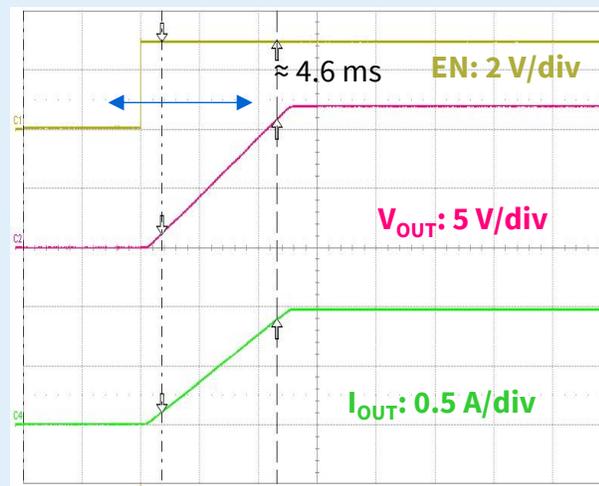$V_{IN} = 12\text{ V}, C_{dv/dT} = 1\text{ nF}$



Time: 2 ms/div

Overvoltage protection

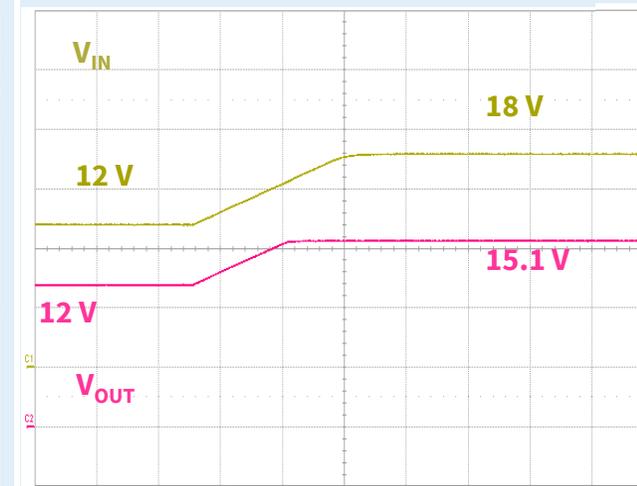


Time: 5 ms/div

# Protection of power rails from hot plugging

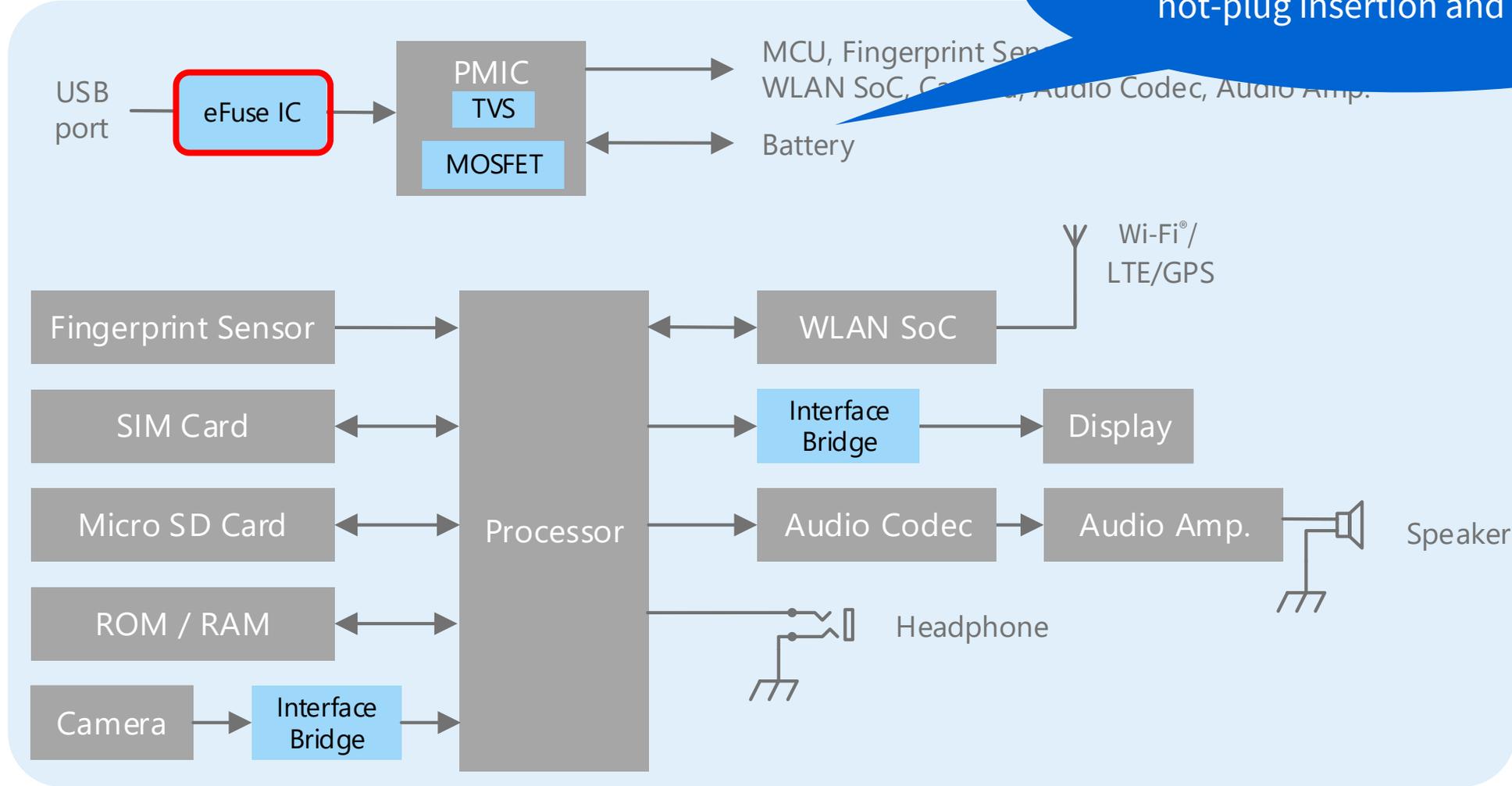Example: Application block diagram of a tablet

For example, USB ports support hot-plug insertion and removal.




◆ Applications web page: [Click](#)

## 2. System fault detection and power rail protection using the FLAG output

# System fault detection and power rail protection using the FLAG output

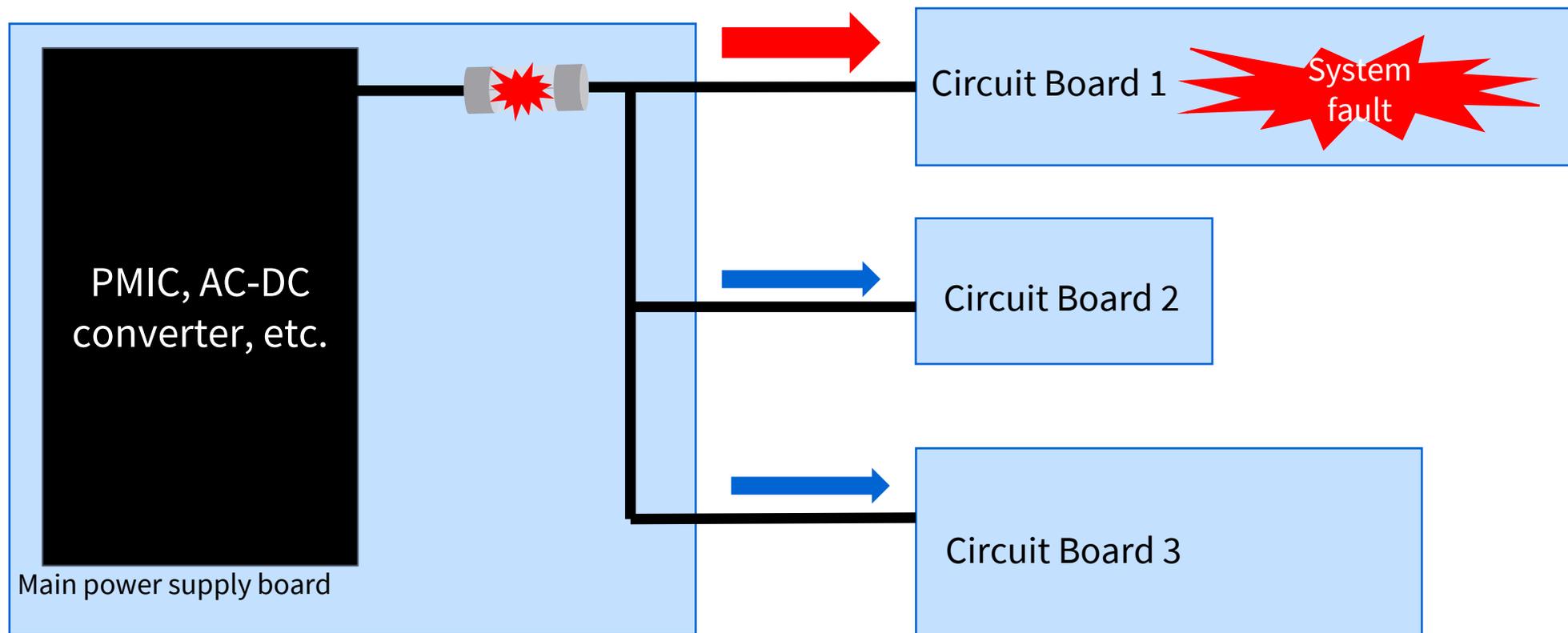
## Example of a circuit configuration using a mechanical fuse



**The mechanical fuse cannot identify where a system fault occurred.**

# System fault detection and power rail protection using the FLAG output


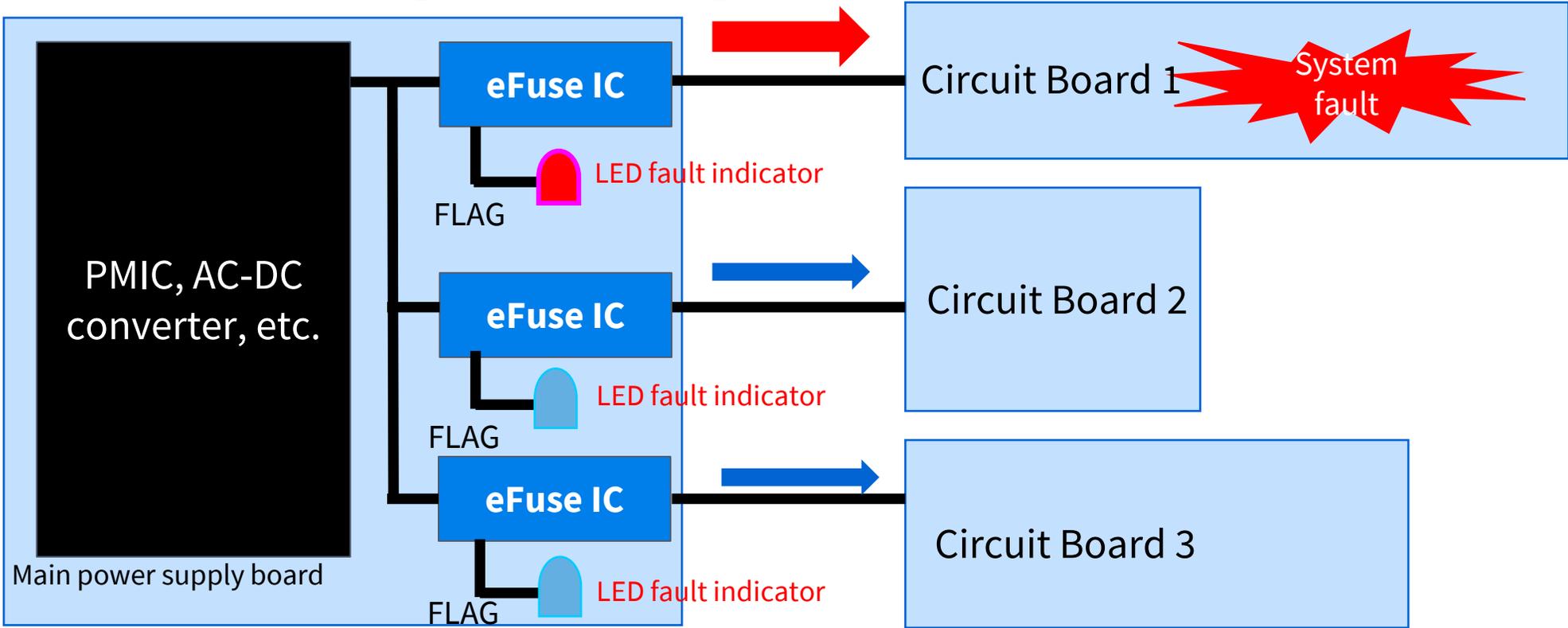
## Example of a circuit configuration using the FLAG output of eFuse ICs



**In addition to protecting power rails, eFuse ICs can detect system faults.**

# Configuration and operation of an application circuit using the FLAG output

## Example using the TCKE712BNL

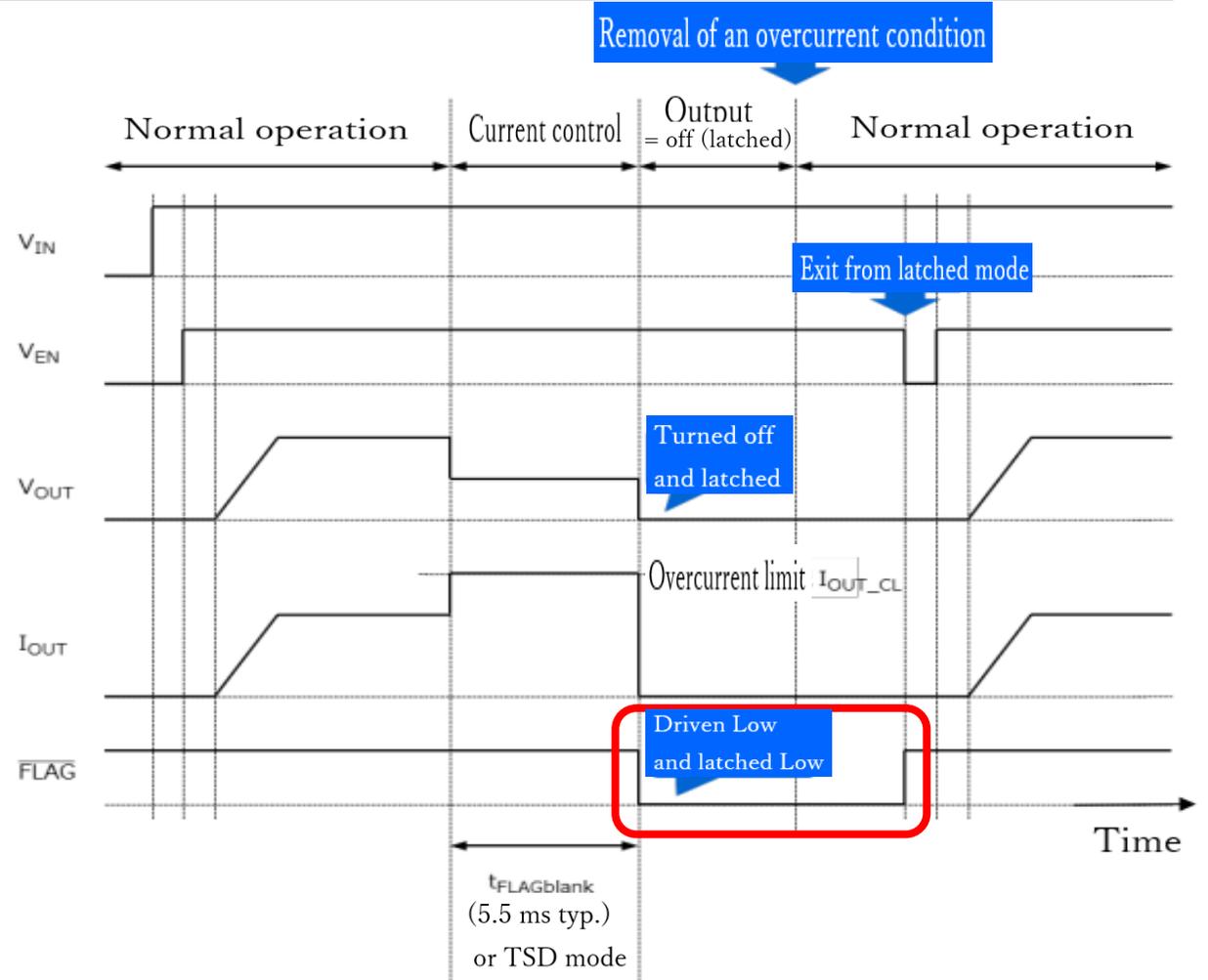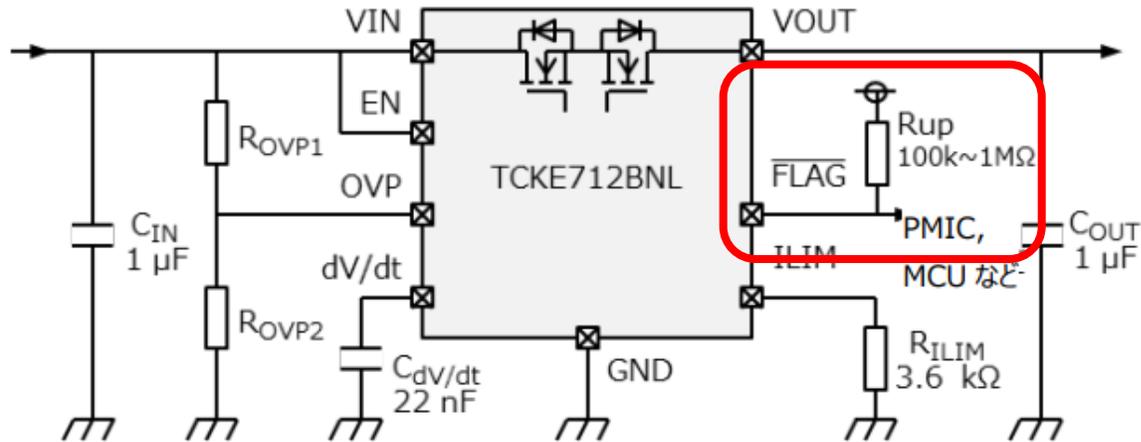


The FLAG output is driven to an active state upon detection of a system fault (e.g., upon tripping of overcurrent protection and thermal shutdown).

## 3. Multiplexing and protection of two power rails

# Multiplexing and protection of two power rails

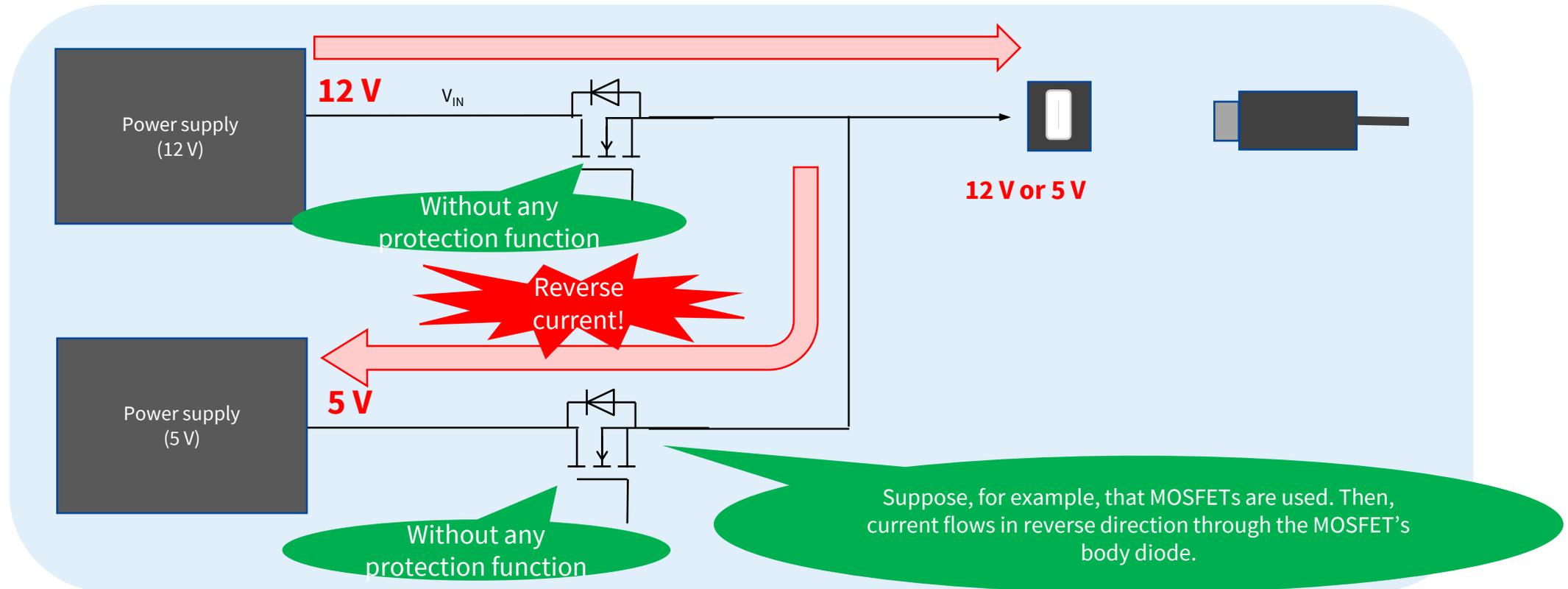
## Example of a circuit configuration using discrete MOSFETs



**Current flows in reverse direction when the circuit switches between two power rails.**

# Multiplexing and protection of two power rails


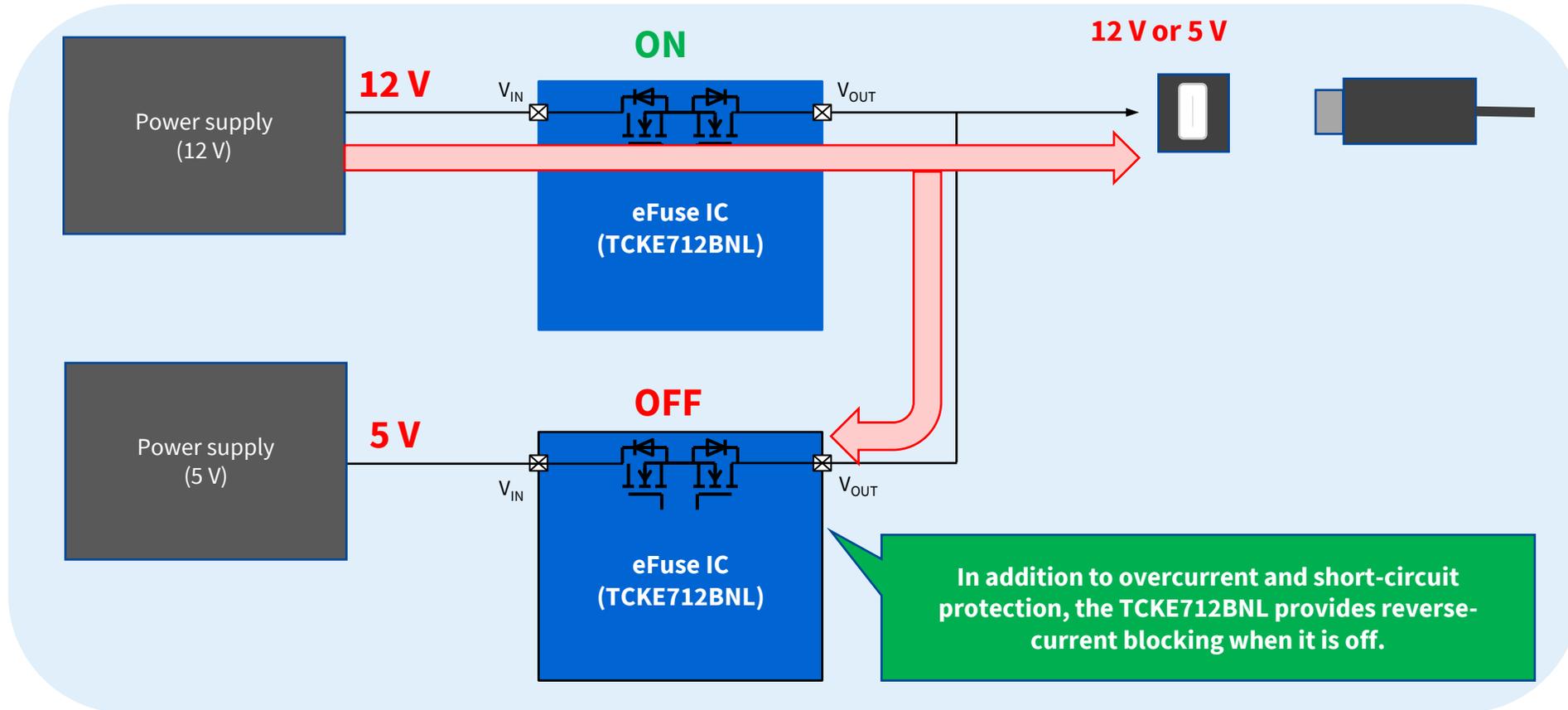
## Example of a circuit configuration using eFuse ICs with a reverse-current blocking



**eFuse ICs with a reverse-current blocking function  
simplify 2-to-1 power multiplexing.**

# Multiplexing and protection of two power delivery paths
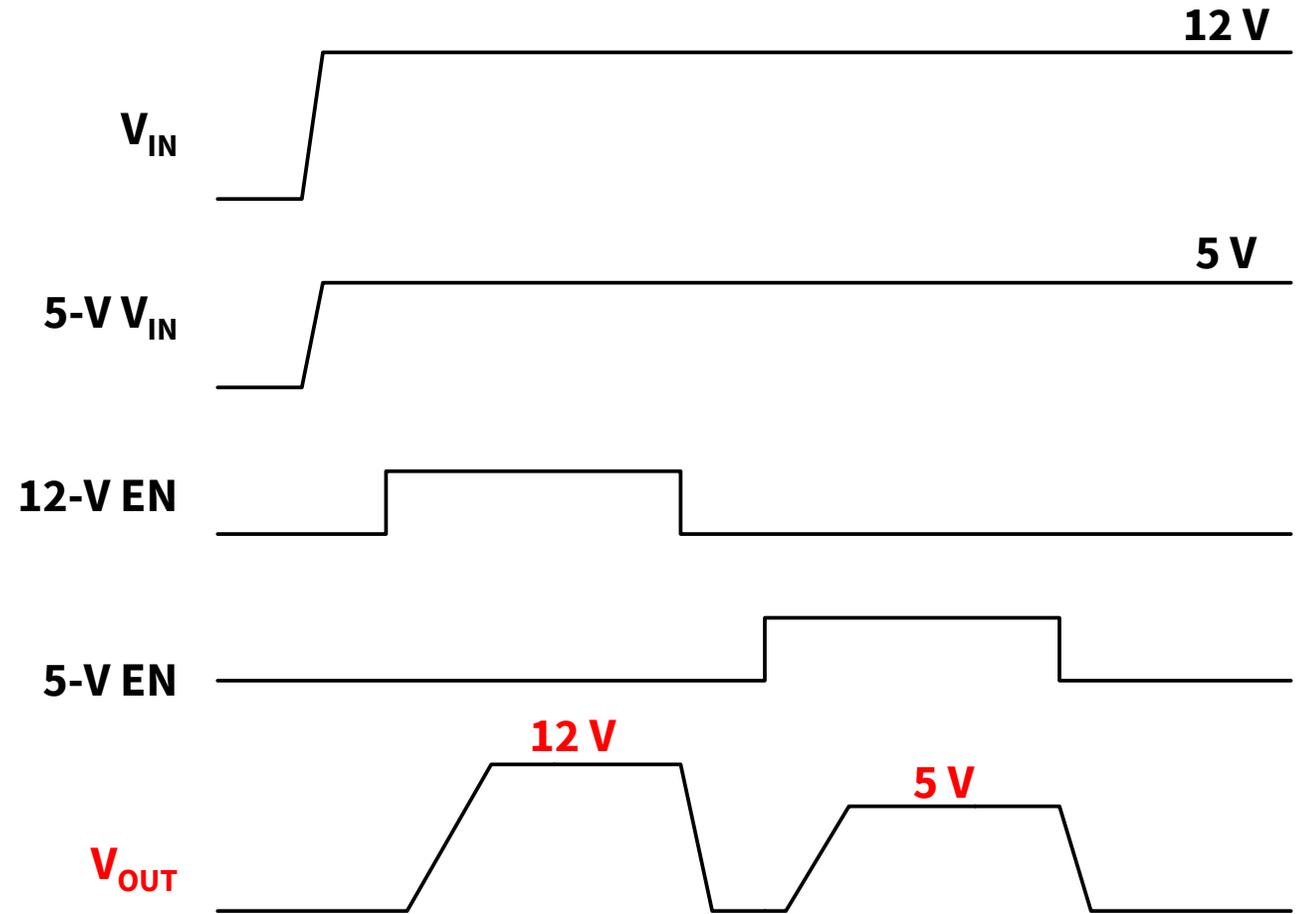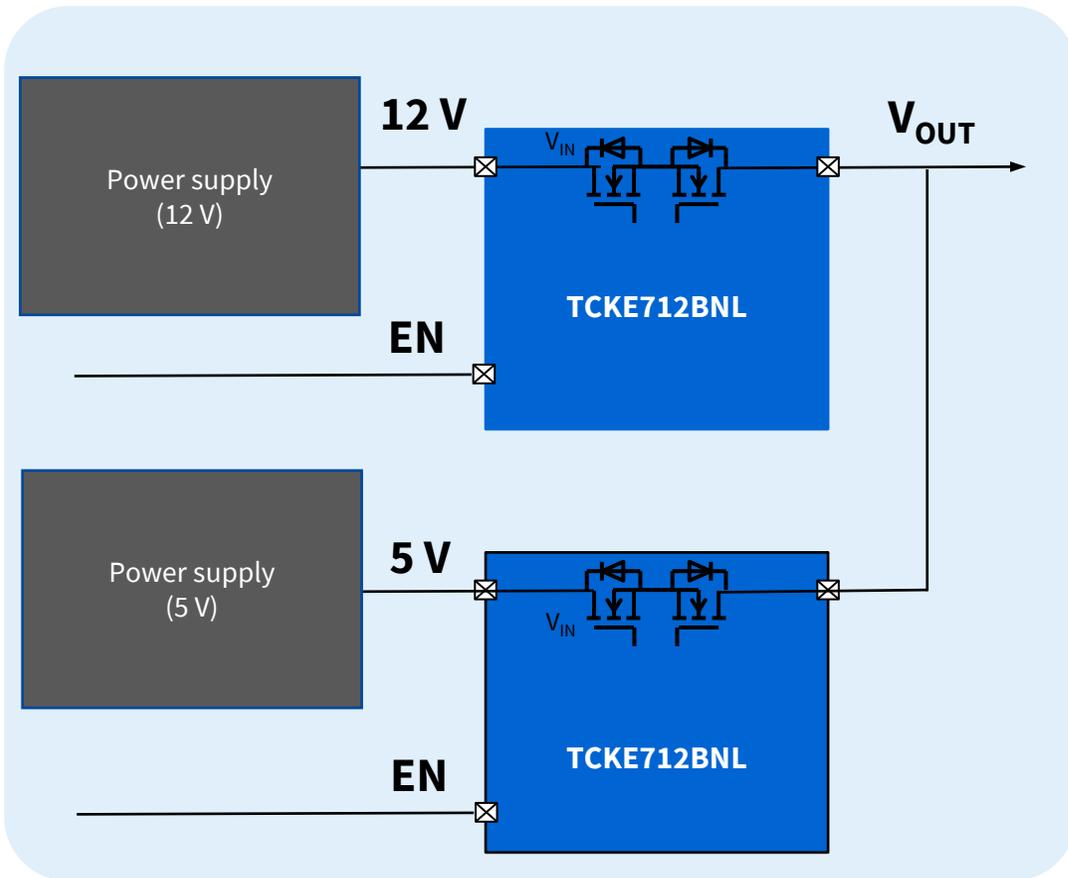
## Example of a circuit configuration using the TCKE712BNL with a reverse-current blocking function




# 03

## Current and future requirements for eFuse ICs

# Current and future requirements for eFuse ICs
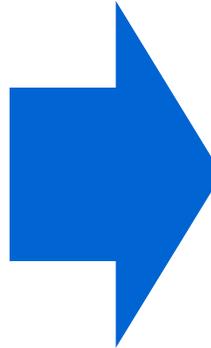
## Applications in which eFuse ICs are currently used



## Applications in which eFuse ICs are expected to be used in the future



**eFuse ICs are expected to expand their application fields.**

# Current and future requirements for eFuse ICs

## Market requirements

- ◆ Enhanced ruggedness and safety
- ◆ Low power loss
- ◆ Cost reduction
- ◆ Stable availability
- ◆ Size reduction




## Future requirements for eFuse ICs

- ◆ An increase in protection performance and withstand voltage
- ◆ A reduction in on-resistance via a driver configuration
- ◆ Integration of more functions to reduce the number of external parts required
- ◆ General-purpose eFuse ICs to support Mult sourcing

**Toshiba is developing eFuse ICs to expand their application fields.**

# 04

## Latest eFuse IC products

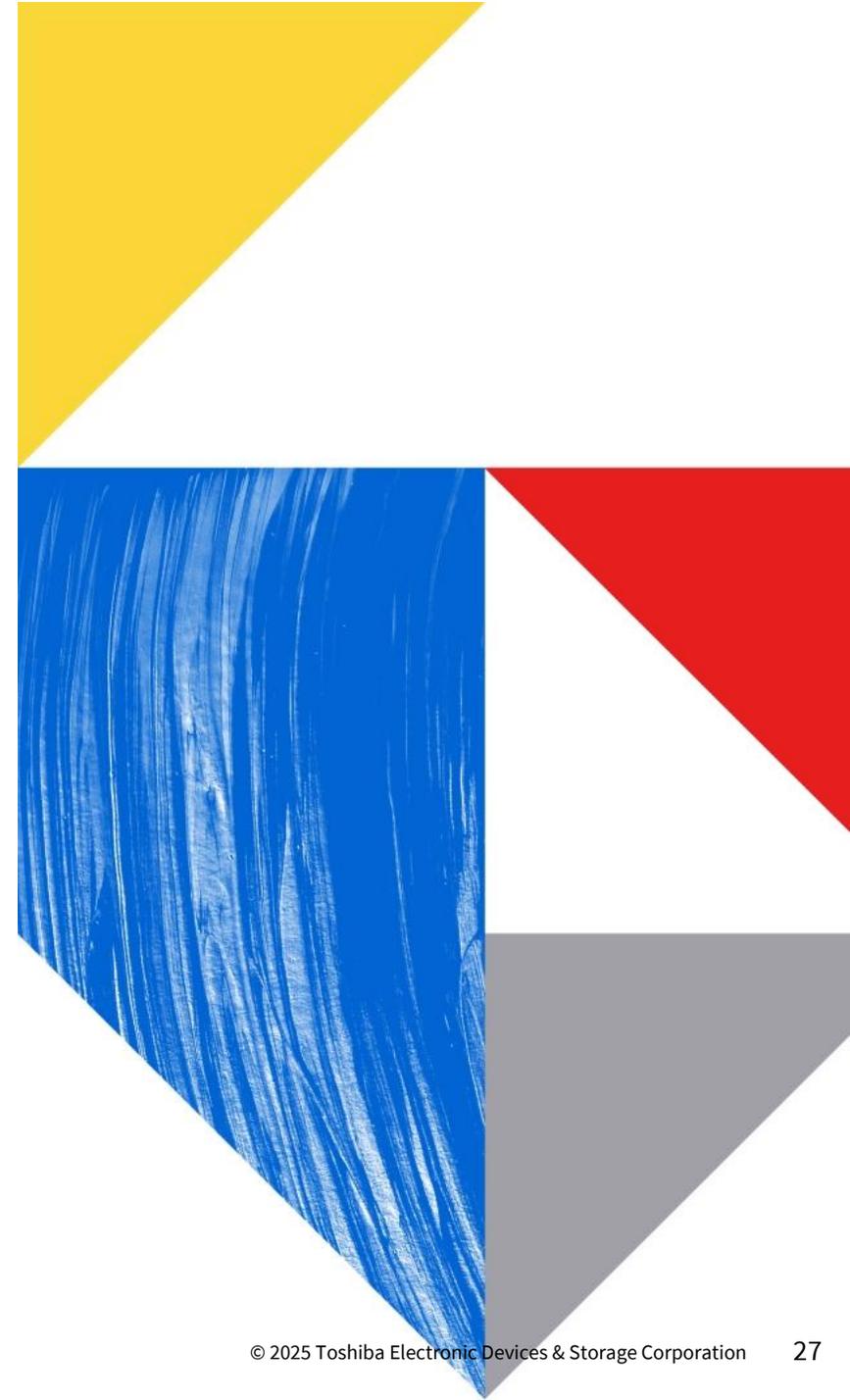


# 18-V/5-V eFuse ICs with variable overcurrent threshold and slew rate

## TCKE800, TCK805, and TCK812 series 18-V/5-V eFuse ICs in a small package

Input voltage: 4.4 to 18 V

- Low  $R_{ON}$ : **28 mΩ (typ.)**, WSON10B
- Programmable OCP threshold via an external resistor: 0.5 to 5.0 A
- OCP threshold accuracy: **±11%**
- OVC threshold accuracy: **±7%**
  - TCKE805: 6 V (typ.)
  - TCKE805: 15 V (typ.)
  - TCKE800: No OVC
- Adjustable slew rate control via an external capacitor
- Reverse-current blocking via an external MOSFET (EN = Off)
- Thermal shutdown threshold: 160°C (typ.)
- Auto recovery: Auto retry / latched

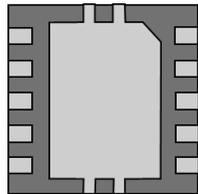


WSON10B  
3.0 × 3.0 mm

IEC 62368-1-  
certified

Part Number	Overvoltage Protection	Recovery Operation
<a href="#">TCKE805NA</a>	6.04 V	Auto retry
<a href="#">TCKE805NL</a>	6.04 V	Latched
<a href="#">TCKE812NA</a>	15.1 V	Auto retry
<a href="#">TCKE812NL</a>	15.1 V	Latched
<a href="#">TCKE800NA</a>	N/A	Auto retry
<a href="#">TCKE800NL</a>	N/A	Latched


### Typical applications

Power supply protection (unidirectional)

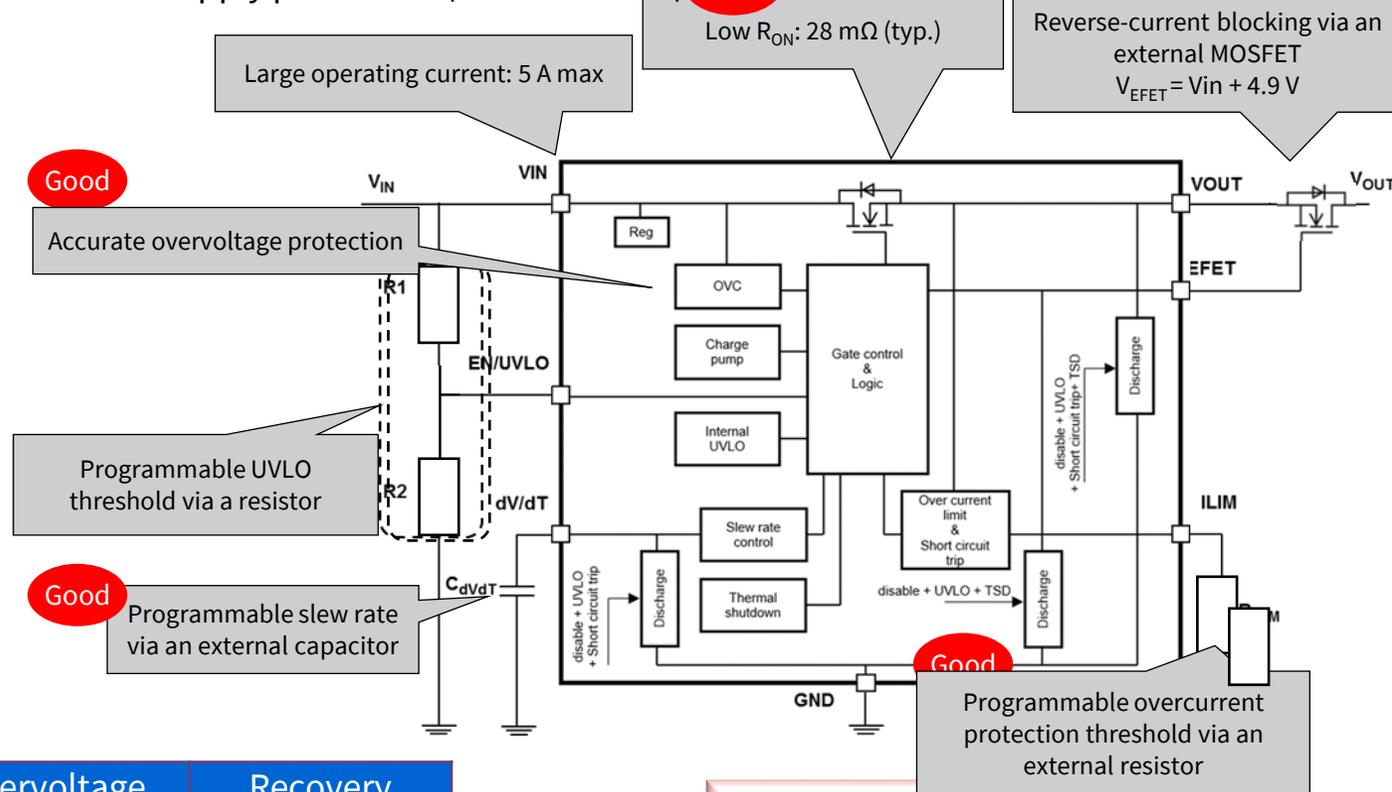

Up to 18 V

Up to 5.0 A

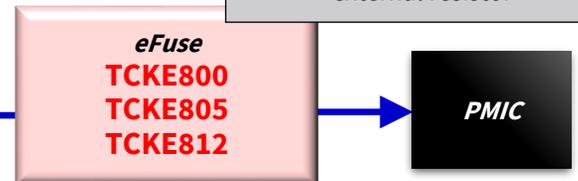

5-V power rail: TCKE805 OVC = 6.04 V (typ.)  
12-V power rail: TCKE812 OVC = 15.1 V (typ.)

# eFuse IC with a reverse-current-blocking MOSFET and programmable OVP and OCP thresholds

## TCKE712BNL

(with the FLAG output, programmable OVP and OCP thresholds, and a reverse-current-blocking MOSFET)


- Maximum input voltage: 18 V
- Operating voltage range: 4.4 to 13.2 V
- Low  $R_{ON}$ : 53 m $\Omega$  (typ.)
- **Programmable overcurrent protection (OCP) threshold via an external resistor: 0.51 to 3.65 A  $\pm$  20%**

Input voltage	Programmable OCP threshold range
9.9 to 13.2 V	0.51 to 2 A (typ.)
5.5 to 9.9 V	0.51 to 2.58 A (typ.)
4.4 to 5.5 V	0.51 to 3.65 A (typ.)


- **Programmable overvoltage protection (OVP) threshold via an external resistor**
- **Programmable slew rate via an external capacitor**
- Quick short-circuit protection: 320 ns
- **Reverse-current blocking via an internal MOSFET (EN = off)**
- **FLAG output**
- Thermal shutdown: 134°C (typ.)
- Latched recovery
- To be certified for IEC 62368-1

### Typical applications


Power supply protection (unidirectional)

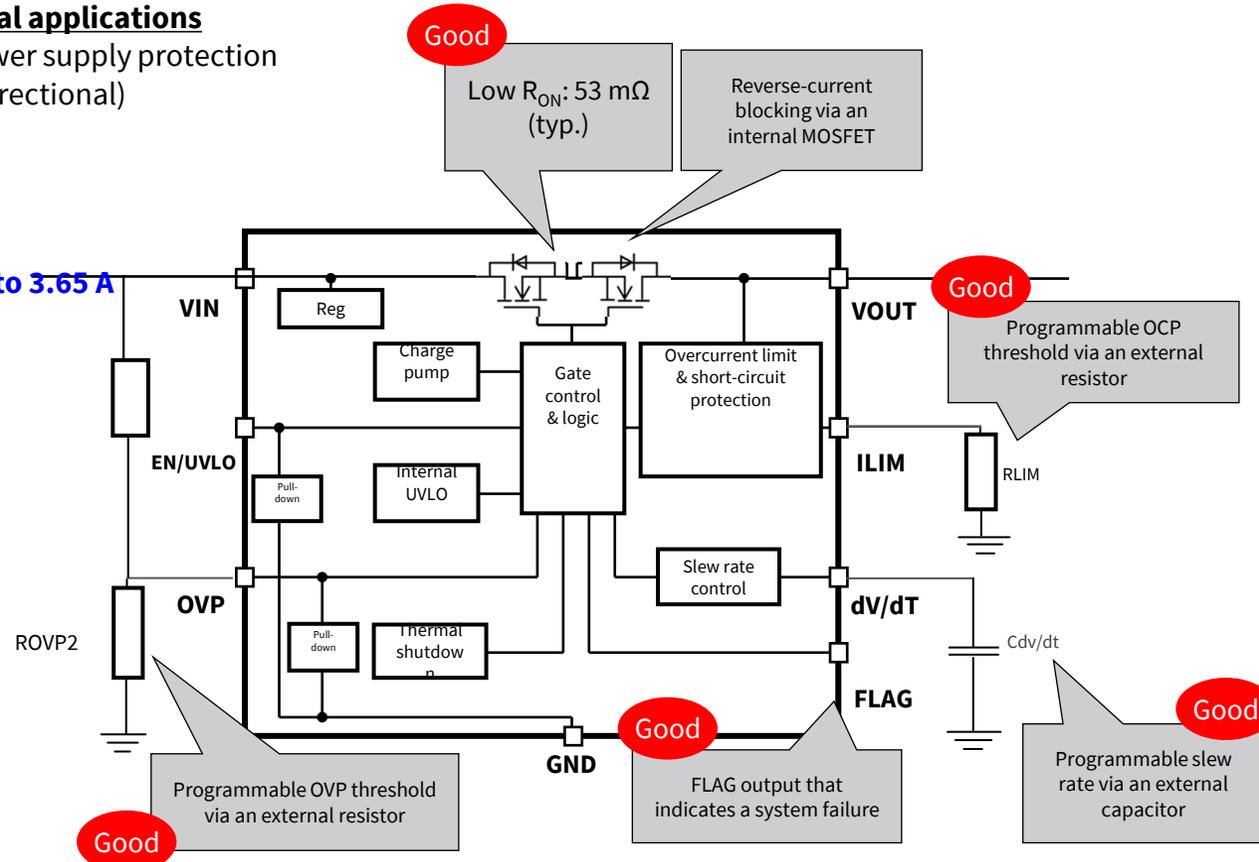

Available in production quantities

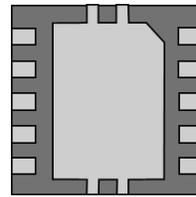

WSON10  
3.0 × 3.0 mm

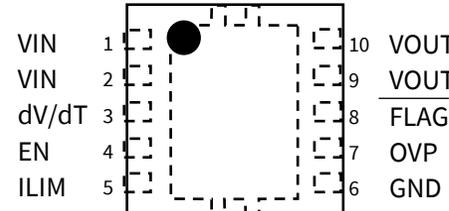

### Application example for an eFuse IC




# 25-V/4-A eFuse ICs with a Adjustable overcurrent protection threshold in a small package

## TCKE903/905/912 and 920 series Small 25-V/4-A eFuse ICs


- High input voltage:  $V_{IN} = 25.0 \text{ V (Max)}$
- Low ON resistance  $R_{ON}$ :  $34 \text{ m}\Omega$  (Typ.)
- Adjustable overcurrent limit:  $0.5 \text{ A}$  to  $4.0 \text{ A}$
- Fixed over voltage clamp
  - TCKE903:  $VOVC = 3.87 \text{ V}$  (Typ.)
  - TCKE905:  $VOVC = 5.7 \text{ V}$  (Typ.)
  - TCKE912:  $VOVC = 13.7 \text{ V}$  (Typ.)
  - TCKE920:  $VOVC = 22.2 \text{ V}$  (Typ.)
- Adjustable slew rate control by external capacitance for inrush current reduction
- Adjustable under voltage lockout by external resistor
- Thermal shutdown
- Quick output discharge: TCKE903QNA, TCKE905QNA
- Small package : WSON8 (2.0 mm (Typ.) x 2.0 mm (Typ.), t: 0.8 mm (Max)).
- IEC62368-1 (G9: Integrated circuit (IC) current limiters) Certified (Under planning)
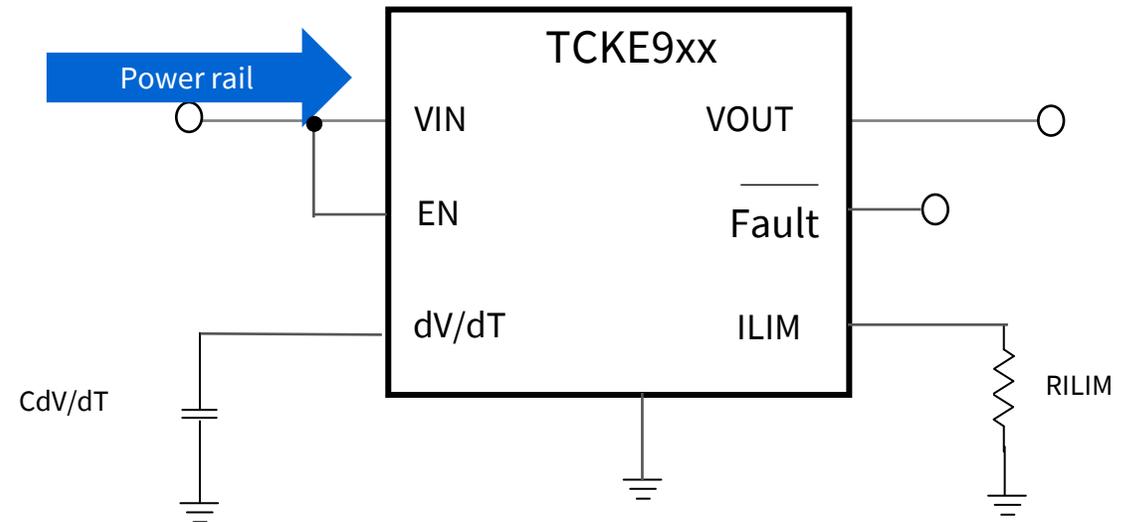
### Typical applications

Power supply protection  
(unidirectional)



Ultra-small

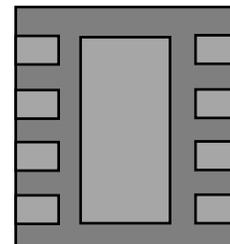


WSON8  
2.0 × 2.0 mm

### Application example of eFuse



# 05

Summary of today's webinar

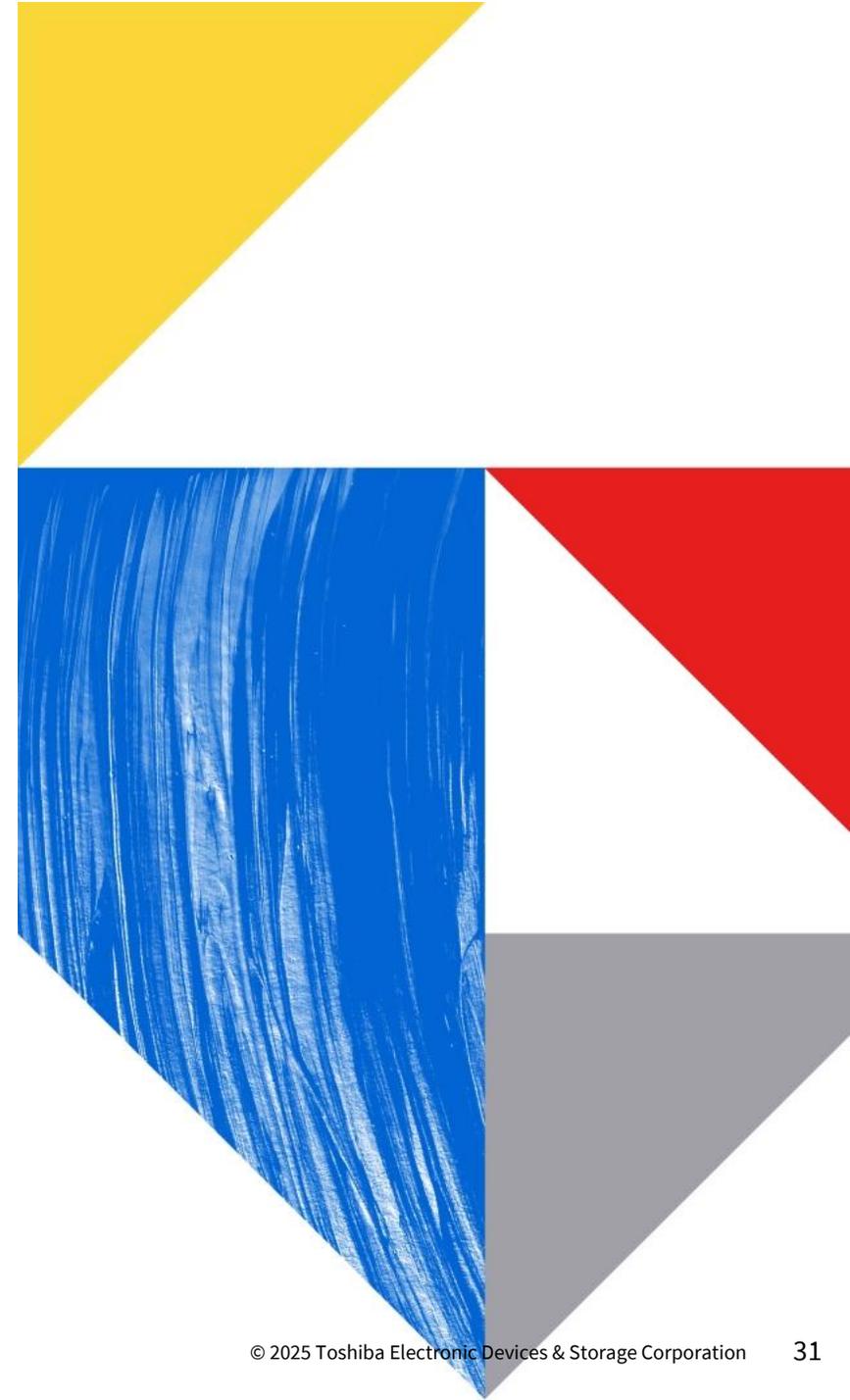


# Summary of today's webinar

## Protection of power rails from hot plugging




Toshiba's eFuse ICs
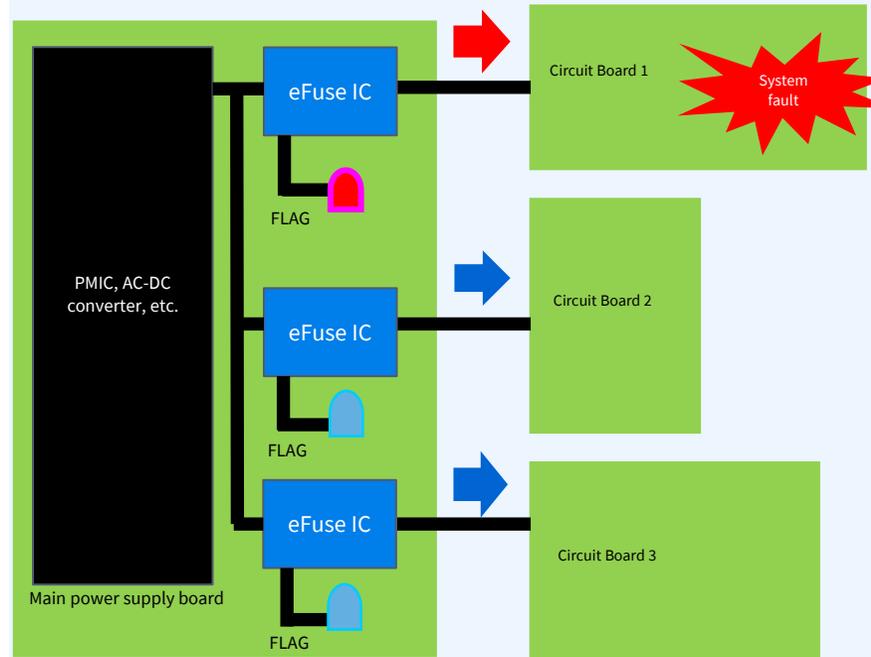
## Accurate system fault detection using the FLAG output



TCKE712BNL  
TCKE9xx series (under development)
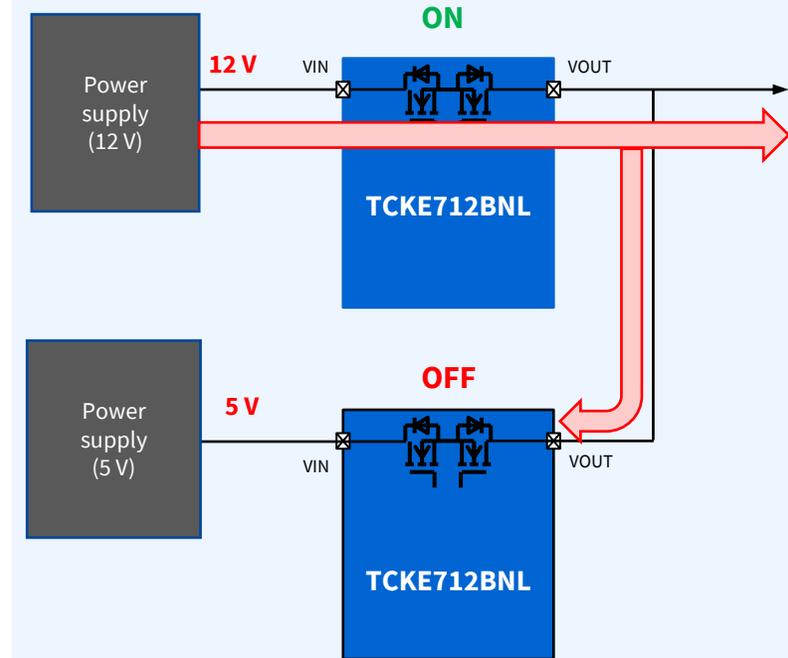
## Power multiplexing using the reverse-current blocking function



TCKE712BNL  
TCKE8xx series (optional)

**In addition to accurate overcurrent protection, eFuse ICs provide various features that simplify circuit protection for a wide range of applications.**

# Summary of today's webinar

- ◆ Toshiba is expanding its portfolio of eFuse ICs to support protection of high-voltage, high-current power rails.
- ◆ Toshiba's eFuse ICs simplify accurate power rail protection for a wide range of applications while reducing the board area requirement.
- ◆ You can purchase all the eFuse ICs shown today from the following site:

[Online distributor inventory search & low-volume purchase](#)

[Click](#)

# TOSHIBA

Thank you for your attention.

\* Wi-Fi is a registered trademark of Wi-Fi Alliance.

\* Other company names, product names, and service names mentioned herein may be trademarks of respective companies.