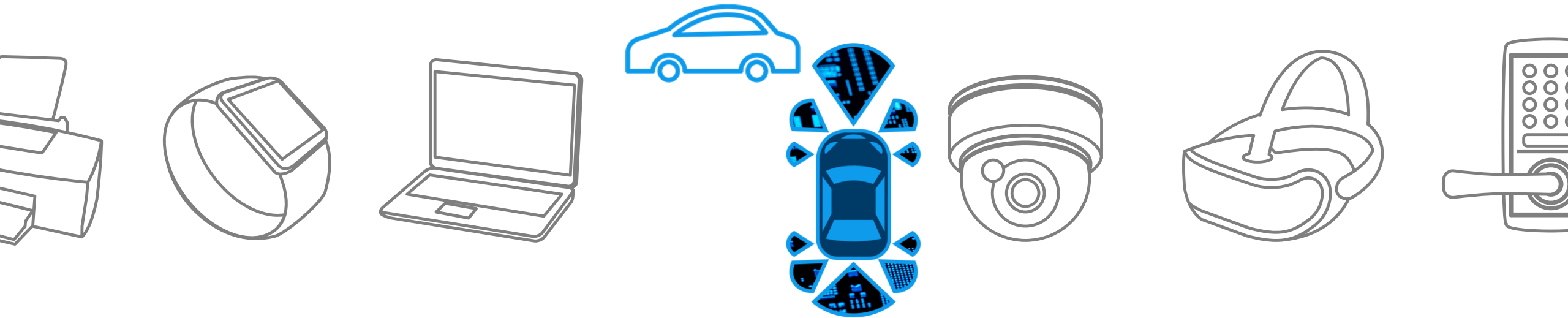



TOSHIBA

Automotive ADAS

Solution Proposal by Toshiba


R22



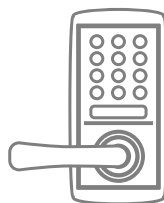

Toshiba Electronic Devices & Storage Corporation provides comprehensive device solutions to customers developing new products by applying its thorough understanding of the systems acquired through the analysis of basic product designs.

Block Diagram

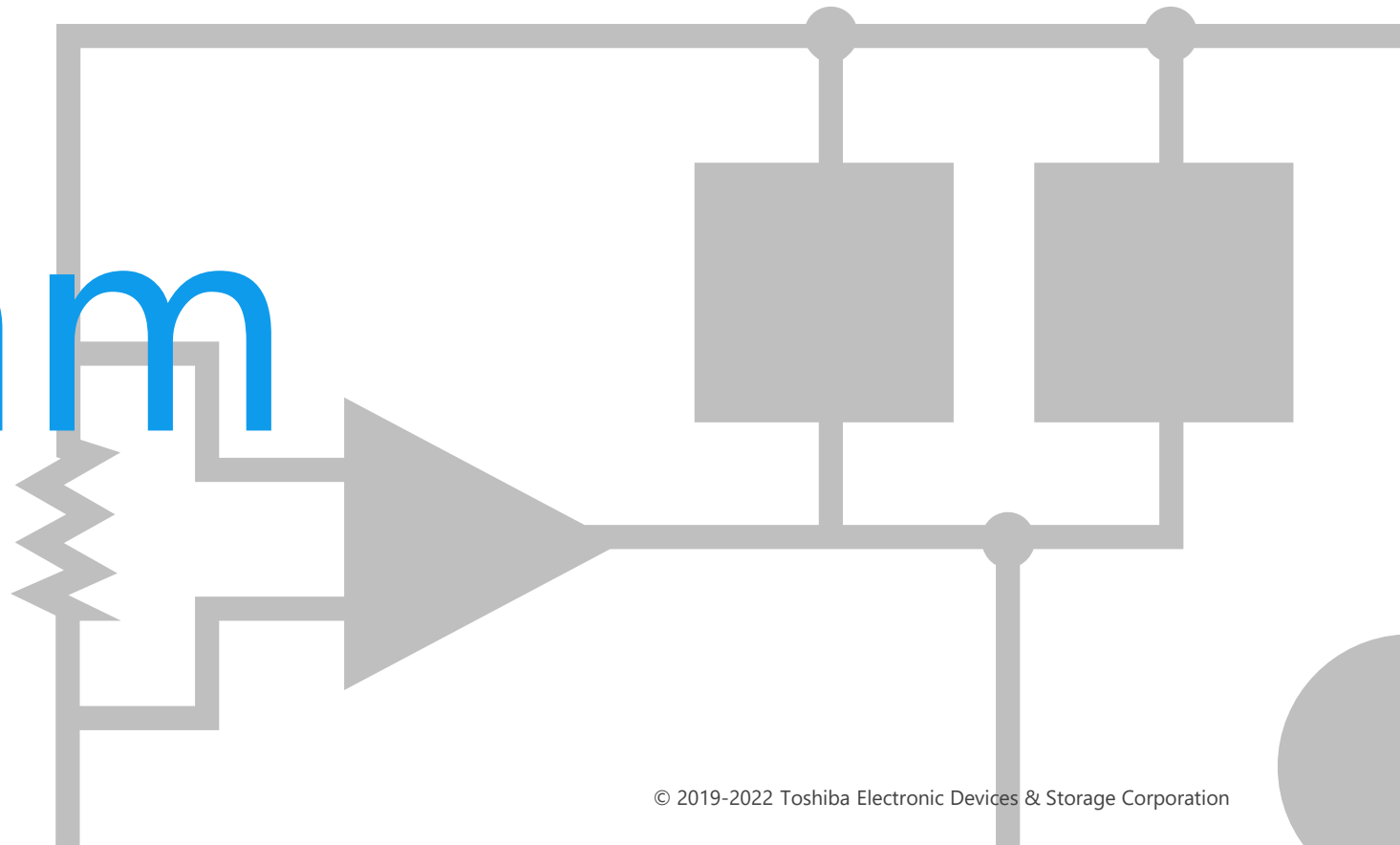

ADAS Overall block diagram

Video Input


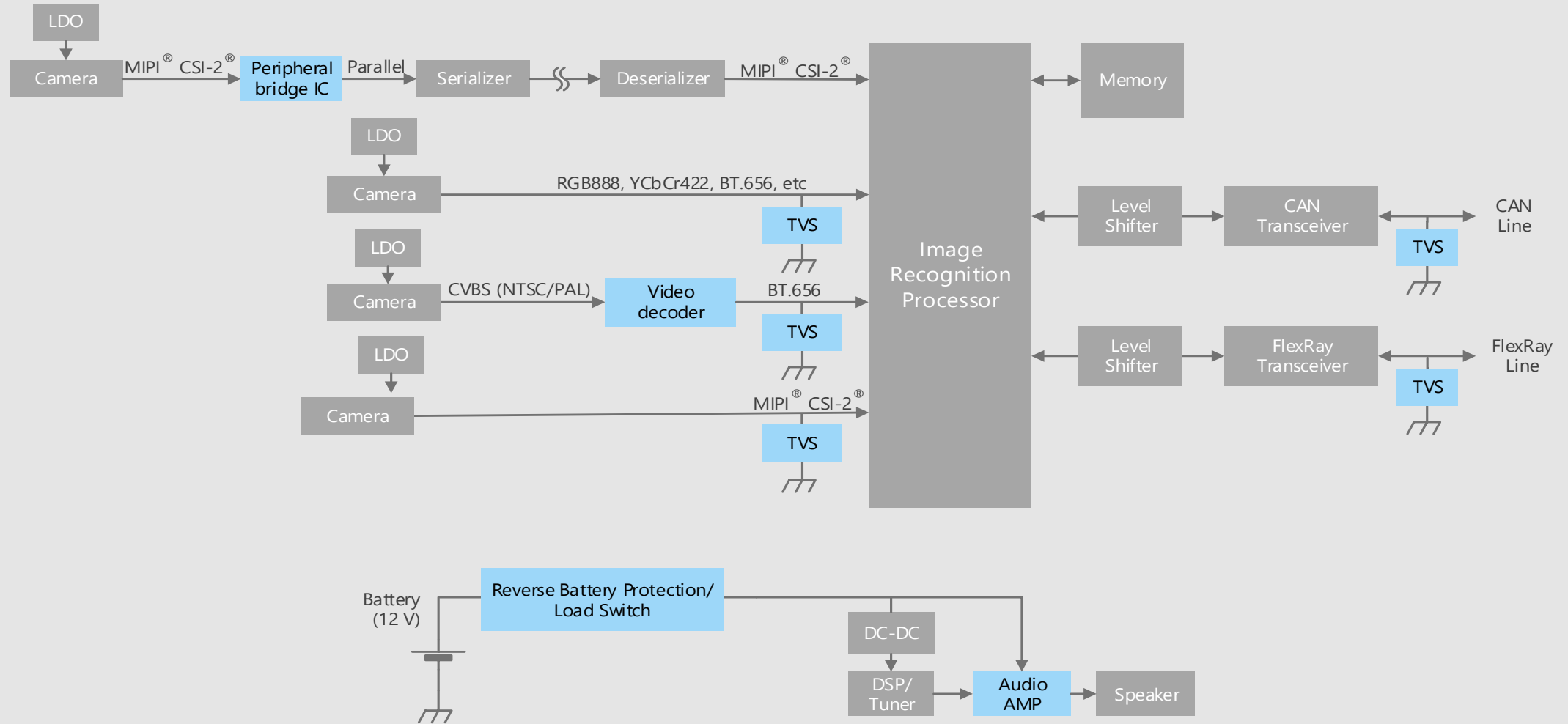


Image input unit

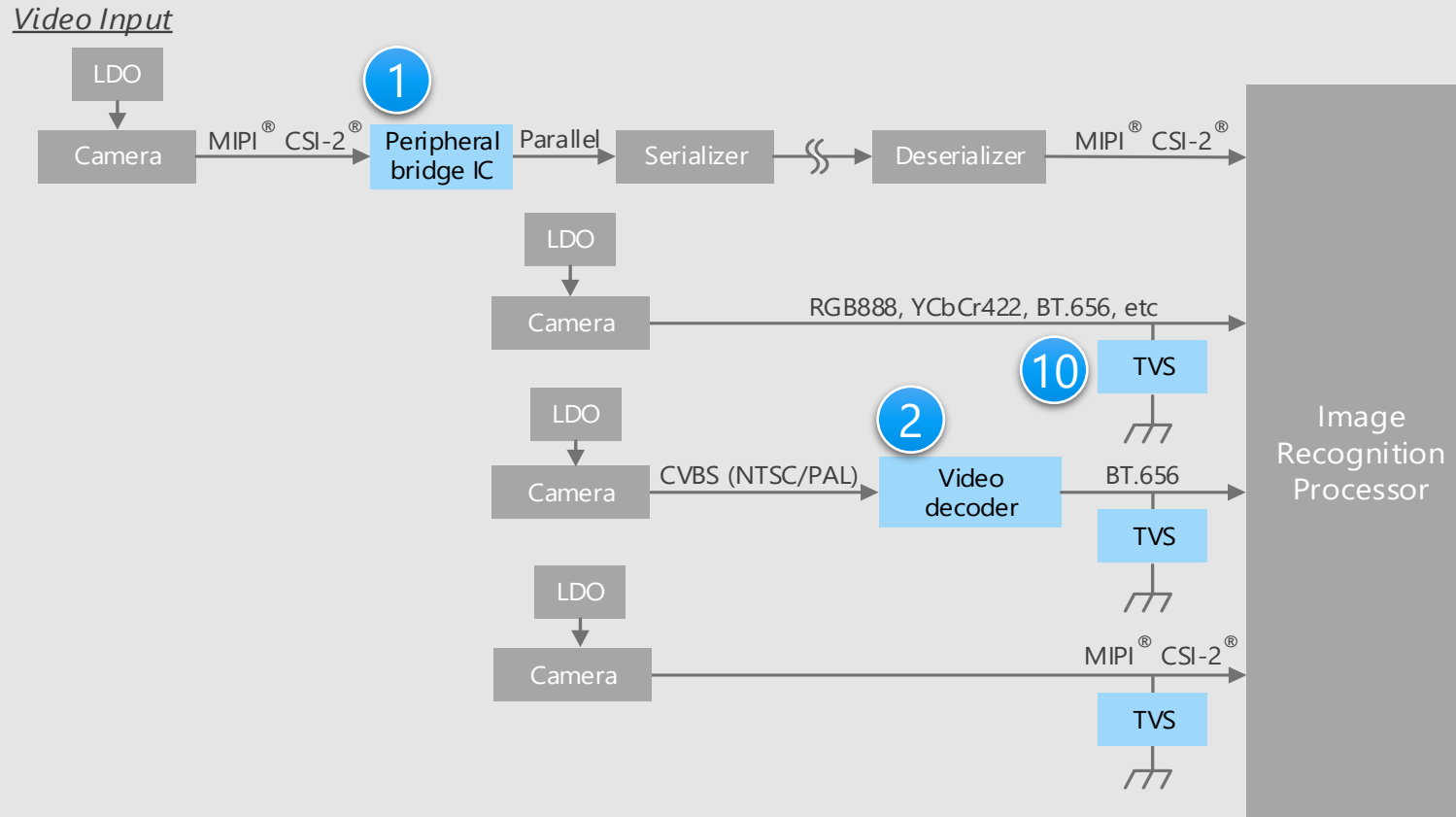

* Click on the numbers in the circuit diagram to jump to the detailed descriptions page


Criteria for device selection

- Employing noise resistant interfaces help to reduce position constraints of camera.
- To use under various environments, video decoders need to have enhanced visual recognition capabilities.

Proposals from Toshiba

- **Resolve differences between interfaces**
Peripheral bridge IC **1**
- **Built-in visual enhancement function**
Video decoder **2**
- **Suitable for ESD protection**
TVS diode (for high speed communication) **10**

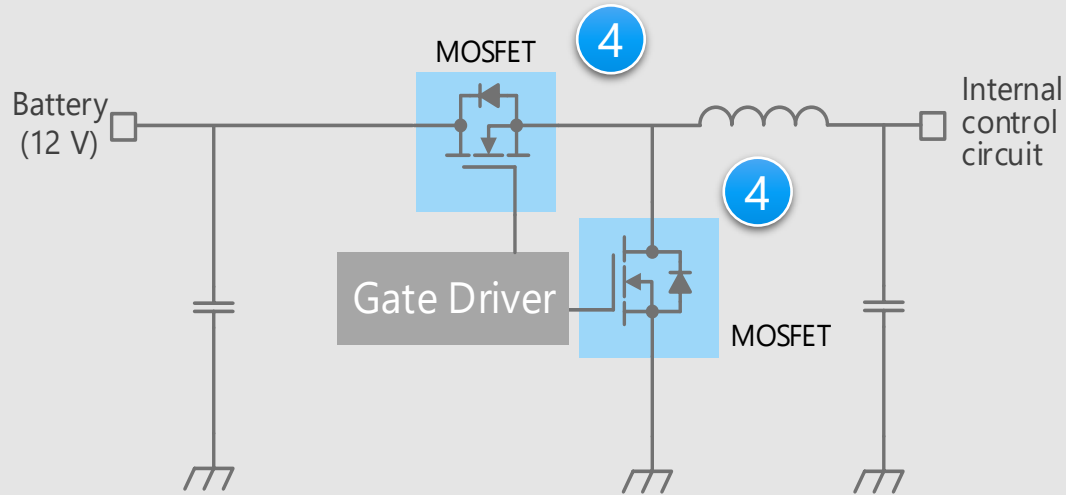DC-DC converter circuit (non-isolated buck type)



* [Click on the numbers in the circuit diagram to jump to the detailed descriptions page](#)

Criteria for device selection

- It is necessary to select the product with the suitable voltage and current ratings for each application.
- A small surface mount package is suitable for realizing miniaturization of the ECU.
- It is necessary to select high speed MOSFETs to prevent short through current.


Proposals from Toshiba

- **Low on-resistance contributes to low power consumption of the system**


U-MOS Series 40 V N-ch MOSFET

4

CAN / FlexRay transmission section

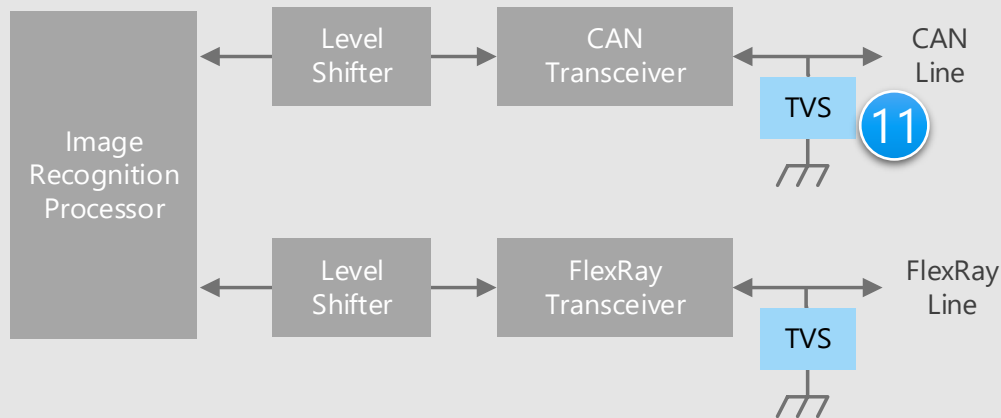

Audio output section

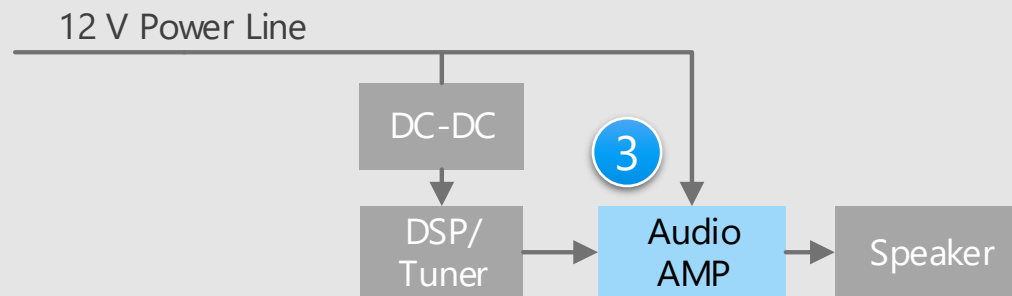

* Click on the numbers in the circuit diagram to jump to the detailed descriptions page

Criteria for device selection

- The TVS diode needs to be selected according to the ESD protection characteristics and capacitance value suitable for transmission speed.


Proposals from Toshiba

- **High output power with low heat generation is realized**
Audio power amplifier IC
- **Suitable for ESD protection**
TVS diode (for CAN communication)

3

11

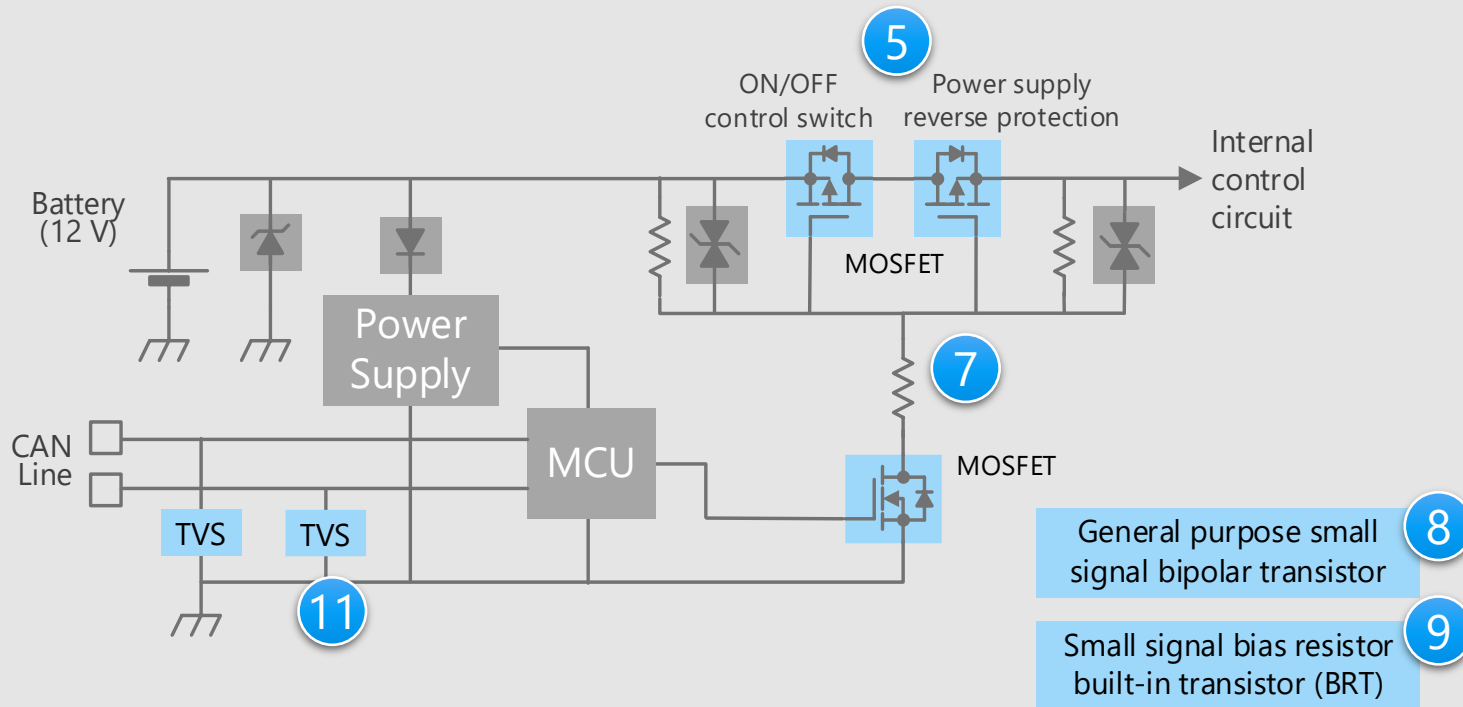Power supply ON/OFF control and reverse connection protection circuit (P-ch type)



* Click on the numbers in the circuit diagram to jump to the detailed descriptions page


Criteria for device selection

- It is necessary to select the product with the suitable voltage and current ratings for each application.
- It is necessary to select a gate driver according to the characteristics of the switching device to be driven.
- A small surface mount package is suitable for realizing miniaturization of the ECU.

Proposals from Toshiba

- **Low on-resistance contributes to low power consumption of the system**
U-MOS Series -40 V / -60 V P-ch MOSFET (5)
- **Extensive product lineup**
General purpose small signal MOSFET (7)
General purpose small signal bipolar transistor (8)
Small signal bias resistor built-in transistor (BRT) (9)
- **Suitable for ESD protection**
TVS diode (for CAN communication) (11)

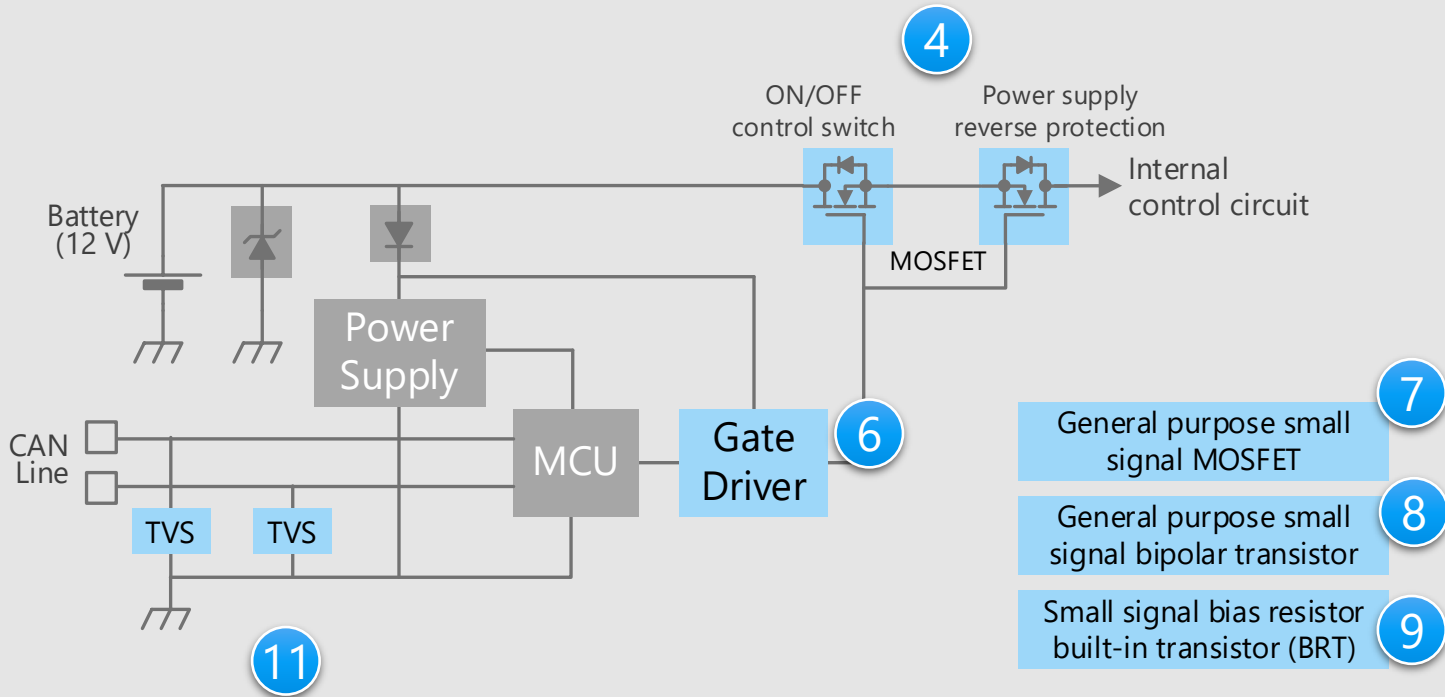Power supply ON/OFF control and reverse connection protection circuit (N-ch type)



* Click on the numbers in the circuit diagram to jump to the detailed descriptions page


Criteria for device selection

- It is necessary to select the product with the suitable voltage and current ratings for each application.
- It is necessary to select a gate driver according to the characteristics of the switching device to be driven.
- A small surface mount package is suitable for realizing miniaturization of the ECU.

Proposals from Toshiba


- **Low on-resistance contributes to low power consumption of the system**
U-MOS Series 40 V N-ch MOSFET
- **Gate driver with protection and diagnosis functions**
Gate driver (for switch)
- **Extensive product lineup**
General purpose small signal MOSFET
General purpose small signal bipolar transistor
Small signal bias resistor built-in transistor (BRT)
- **Suitable for ESD protection**
TVS diode (for CAN communication)

Recommended Devices

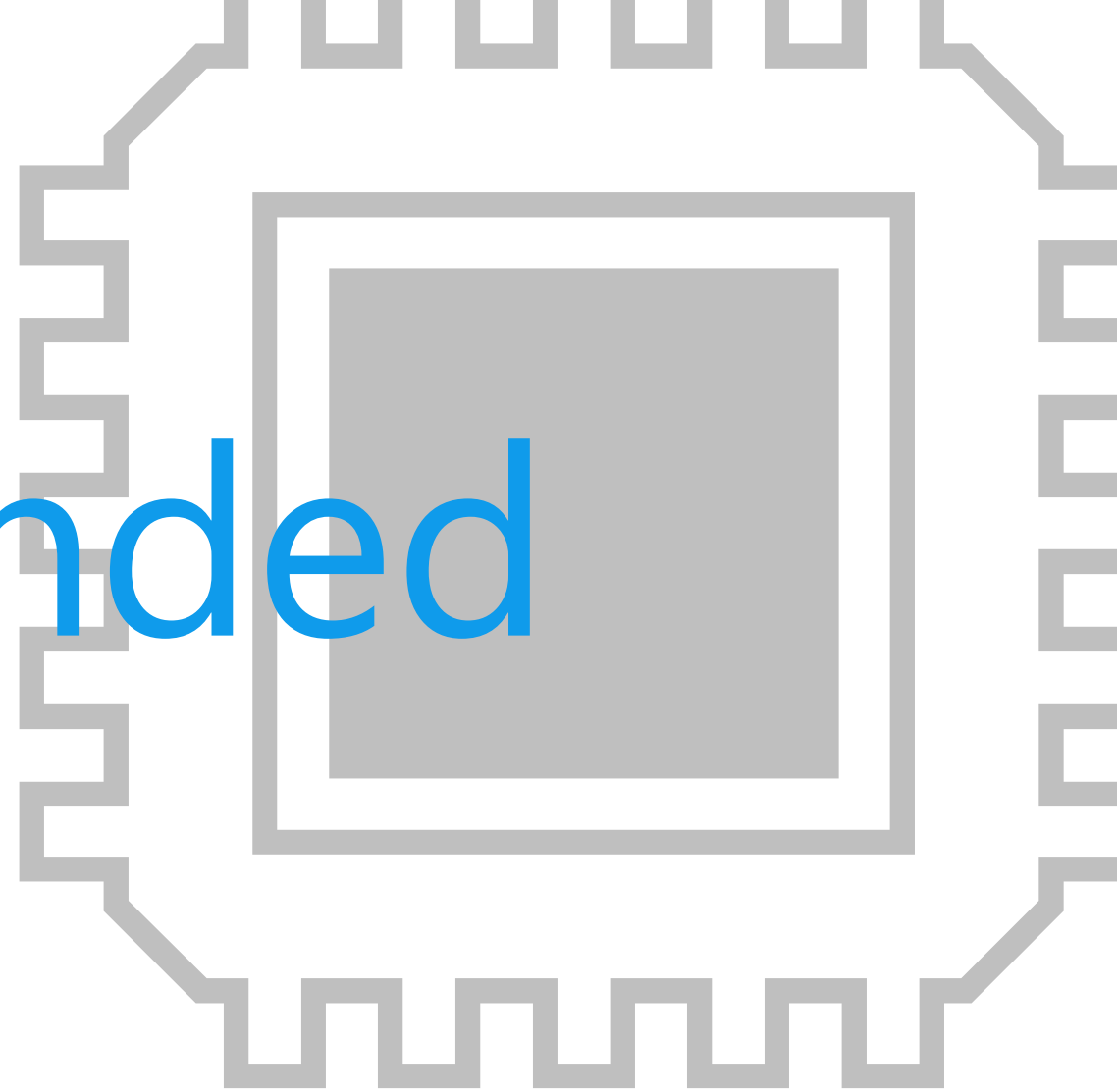

Device solutions to address customer needs

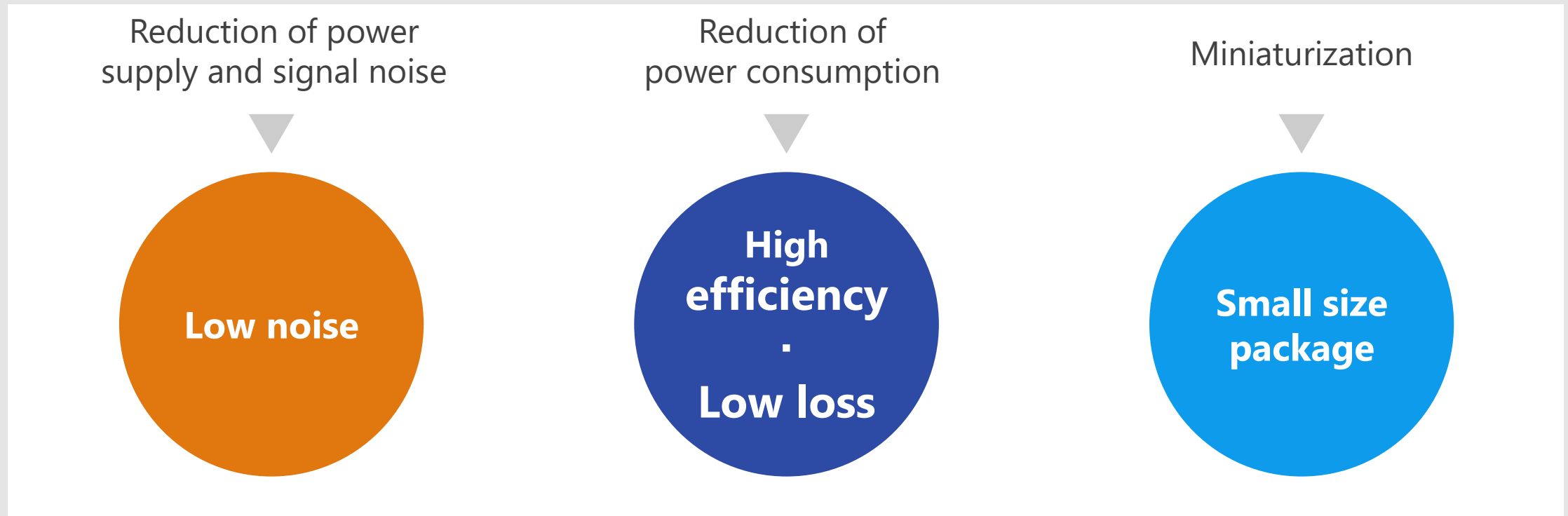As described above, in the design of ADAS, “**Reduction of power supply and signal noise**”, “**Reduction of power consumption**” and “**Miniaturization**” are important factors. Toshiba’s proposals are based on these three solution perspectives.



Device solutions to address customer needs



	Low noise	High efficiency · Low loss	Small size package
1 Peripheral bridge IC	●		
2 Video decoder	●	●	
3 Audio power amplifier IC	●	●	
4 U-MOS Series 40 V N-ch MOSFET		●	●
5 U-MOS Series -40 V / -60 V P-ch MOSFET		●	●
6 Gate driver (for switch)	●		●
7 General purpose small signal MOSFET		●	●
8 General purpose small signal bipolar transistor			●
9 Small signal bias resistor built-in transistor (BRT)			●
10 TVS diode (for high speed communication)	●		●
11 TVS diode (for CAN communication)	●		●

Value provided

Resolve gaps of interface standard between host and peripheral devices.

1 Increase the choice of parts

By using a peripheral bridge IC, it is possible to connect to various types of peripheral devices.


2 Reduce noise

Converting parallel bus line to serial improves noise immunity. That also suppresses the generation of own noise.


3 Reduce disconnection risk

Converting parallel bus line to serial reduces the number of wires on a board, and so reduce the risk of disconnection.

■ Display interface

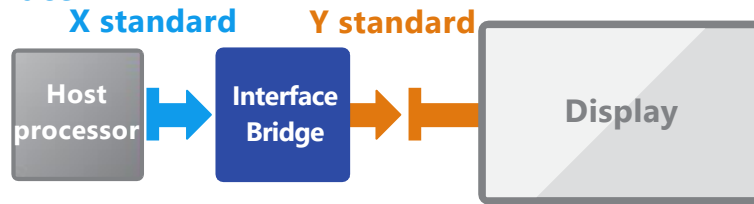

■ Camera interface bridge

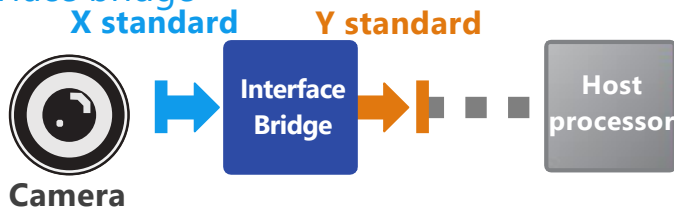

Part number	Camera I/F Bridge		Display I/F Bridge			
	TC9590XBG	TC9591XBG	TC9592XBG	TC9593XBG	TC9594XBG	TC9595XBG
Package	P-LFBGA64-0707-0.80-002	P-VFBGA80-0707-0.65-001	P-VFBGA49-0505-0.65-001	P-VFBGA64-0606-0.65-001	P-VFBGA80-0707-0.65-001	P-VFBGA80-0707-0.65-001
Input	HDMI™1.4a	(1) MIPI® CSI-2® (2) Parallel 24bit @166 MHz	MIPI DSI® 4lanes x 1ch		Parallel input 24bit @166 MHz	MIPI DSI 4lanes x 1ch / MIPI DPI SM (24bit)
Output	MIPI CSI-2 4lanes x 1ch	(1) Parallel 24bit @100 MHz (2) MIPI CSI-2	LVDS Single Link		MIPI DSI 4lanes x 1ch	DisplayPort™ 1.1a x 2ports / MIPI DPI (24bit)

[Return to Block Diagram TOP](#)

Value provided

Built-in image enhancement functions designed for automotive cameras.

1 HDV enhancer

In addition to conventional horizontal and vertical edge emphasis, diagonal emphasis has been added, to enable stronger edge emphasis without increasing discomfort to the eyes.

2 Color management

This function emphasizes a specific selected color (saturation). Emphasizing certain color can improve visibility.

3 Dynamic YC gamma


Applying optimized YC gamma to the images reduces blackout and whiteout, and improves visibility.



Dynamic YC gamma



Color management (blue-cyan emphasis)

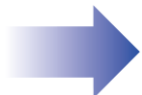

Lineup

Part number	TC90107FG
Package	LQFP64-P-1010-0.50E
AD converter	1
New image correction	✓
ITU-R BT.656 output	✓

[Return to Block Diagram TOP](#)

Value provided

These linear amplifier ICs realize same level of power loss and heat generation the class D amplifier.

1 Proprietary high efficiency amplifier (patent registered)

Realizes equivalent efficiency to the class D amplifiers [Note1] at output of 4 W or less. Power consumption of these ICs are about 1/5 of our class AB amplifiers and about 1/2 of our high efficiency linear class KB amplifiers. [Note2]

Note:1 Based on Toshiba research (April 2020) .
Note:2 Class KB = Toshiba original linear amplifier

2 Reduction of external components


Since these ICs operate without switching such as the class D amplifier, the external parts such as low pass filter or components for EMI suppression can be reduced.

3 Built-in fulltime output offset detection (patent registered)


Includes a proprietary speaker burnout prevention system that continuously checks for any abnormal output DC offset regardless of input signal presence and informs the microcomputer.

Power consumption (for 0.8 W x 4 channels)

(Toshiba internal comparison)

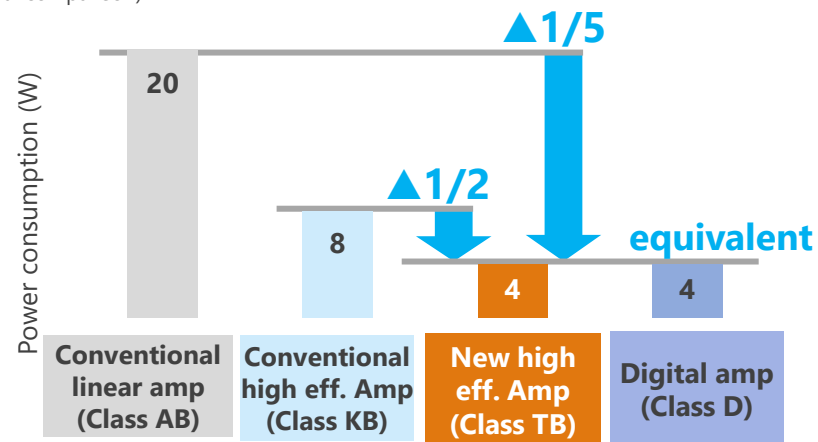

Lineup

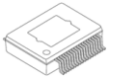Part number	TCB701FNG	TCB702FNG
Package	P-HSSOP36-1116-0.65-001 (36 pin) 	
Maximum output power	49 W x 4ch ($V_{CC} = 15.2 \text{ V}$, $R_L = 4 \Omega$)	45 W x 4ch ($V_{CC} = 15.2 \text{ V}$, $R_L = 4 \Omega$)
Total harmonic distortion (THD)	0.01 % (at $P_{OUT} = 0.4 \text{ W}$)	
Supply voltage	6 to 18 V	
Output noise voltage	60 μVrms (Filter = DIN AUDIO)	

[Return to Block Diagram TOP](#)

Value provided

The latest processes enables low on-resistance and low noise, thereby reducing power consumption.

1 Low loss (reduced on-resistance)



Using low on-resistance chip technology to contribute to reduced power consumption systems.
On-resistance of 61 % reduction per unit area. (compared to Toshiba's U-MOSIV products)

2 Small and low loss package



By adopting a Cu clip structure and a double-sided heat dissipation structure, low loss and high heat dissipation are realized.
Wettable Frank (WF) package contributes good mountability.

3 Low noise (low EMI)

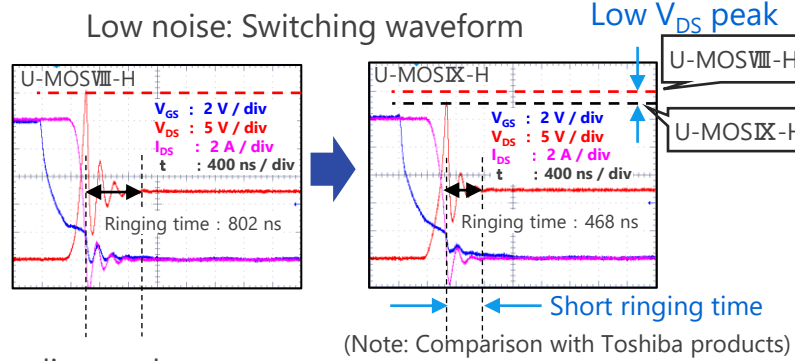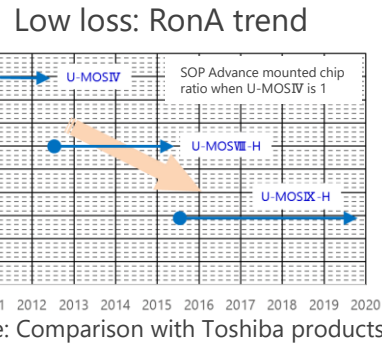Improved chip process reduces surge voltage and ringing time.



Part number	Rated drain current [A]	On-resistance (Max) [mΩ] @V _{GS} = 10 V	Package
XPN3R804NC	40	3.8	TSON Advance(WF)
TK1R4S04PB	120	1.35	DPAK+
XPHR7904PS	150	0.79	SOP Advance(WF)
TPWR7904PB	150	0.79	DSOP Advance(WF)L
XPJR6604PB*	(200)	(0.66)	S-TOGL™
XPQR3004PB	400	0.30	L-TOGL™

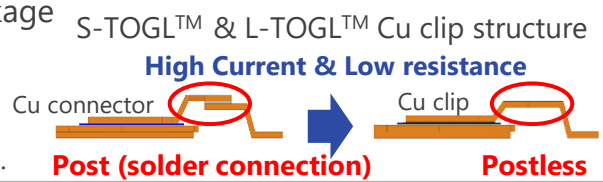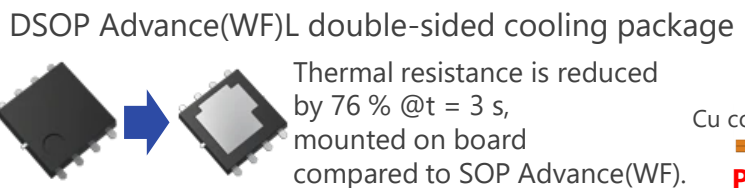

*: Under development (Values enclosed in parentheses are tentative specifications. Specifications are subject to change without notice.)

[Return to Block Diagram TOP](#)

5 U-MOS Series -40 V / -60 V P-ch MOSFET

XPN9R614MC / XPH3R114MC / XPH8R316MC* / TJ90S04M3L

Low noise

High efficiency
Low loss



Small size package

Value provided

Low on-resistance contributes to reduce system power consumption.


1 Low loss (reduced on-resistance) and logic level drive

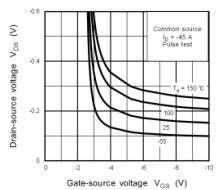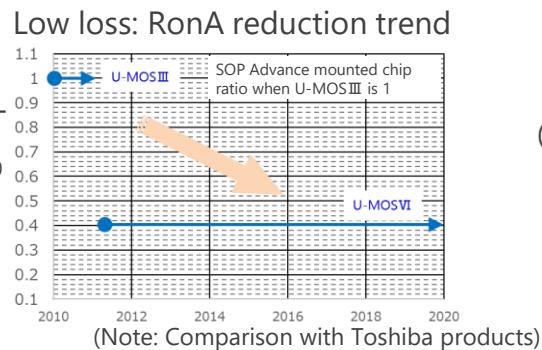Using a low on-resistance technology contributes to reduce system power consumption.
A lineup of logic level drive type is supported.
The on-resistance per area is reduced by 60 %.
(compared to Toshiba's U-MOS^{III} products)



Logic level drive
TJ90S04M3L
 $V_{DS(ON)} - V_{GS}$

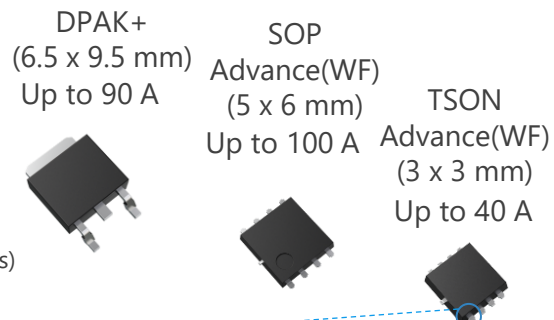Large current, small size, high power dissipation package



2 Small and low loss packages

By adopting a Cu connector structure, a low loss and high power dissipation package is realized.
Wettable Flank (WF) package contributes to good mountability.

Lineup

Part Number	Rated drain-source voltage [V]	Rated drain current [A]	On-resistance (Max) [mΩ] @ $V_{GS} = -10$ V	Package
XPN9R614MC	-40	-40	9.6	TSON Advance(WF)
XPH3R114MC	-40	-100	3.1	SOP Advance(WF)
XPH8R316MC*	-60	(-90)	(8.3)	
TJ90S04M3L	-40	-90	4.3	DPAK+

* Under development (Values enclosed in parentheses are tentative specifications. Specifications are subject to change without notice.)

[Return to Block Diagram TOP](#)

6 Gate driver (for switch)

TPD7104AF / TPD7106F / TPD7107F



Value provided

A charge pump circuit for the N-ch MOSFET gate drive is built in, allowing for easy semiconductor relay configuration.

1 Built-in charge pump circuit

Built-in charge pump circuit enables N-ch MOSFET as high side switch. Easy to configure a semiconductor relay.


2 Can be controlled by logic level voltage

It is possible to be controlled directly by output signal of MCUs or CMOS logic ICs.


3 Small package

The small surface mount packages such as PS-8, SSOP16 and WSON10A contribute to the miniaturization of equipment.

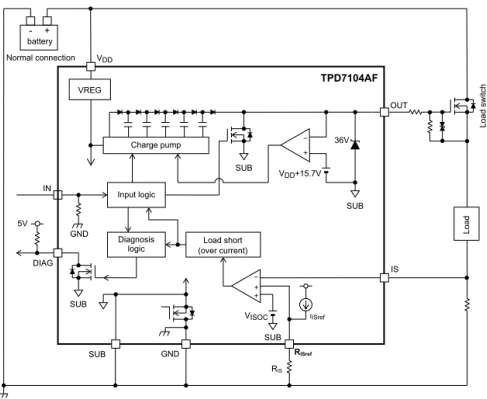Semiconductor relay (switch) application (TPD7104AF)



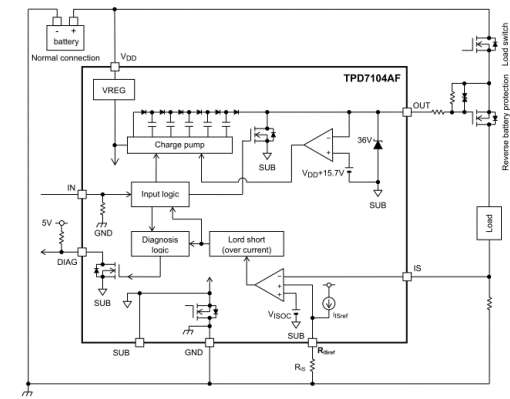Power supply reverse connection protection MOSFET control (TPD7104AF)



Back to back configuration

Lineup

Part number	TPD7104AF	TPD7106F	TPD7107F
Package	PS-8 (2.8 x 2.9 mm)	SSOP16 (5.5 x 6.4 mm)	WSON10A (3 x 3 mm)
Function	High side gate driver	High side gate driver	High side gate driver
Output	1	1	1
Features	<ul style="list-style-type: none"> Operating power supply voltage range: 5 to 18 V Built-in power supply reverse connection protection function (Protective MOSFET control with back-to-back circuitry) 	<ul style="list-style-type: none"> Operating power supply voltage range: 4.5 to 27 V Built-in power supply reverse connection protection function (Protective MOSFET control with back-to-back circuitry) 	<ul style="list-style-type: none"> Operating power supply voltage range: 5.75 to 26 V Current sense output Protective functions; overcurrent, overtemperature, GND disconnect, etc. reverse battery connection Diagnosis output; overcurrent, load open, overtemperature, etc.

[Return to Block Diagram TOP](#)

Value provided

Wide lineup of small packages contribute to reduce the size and power consumption of system.

1 Small package

A lineup of various small packages such as SOT-723 (VESM 1.2 x 1.2 mm package) is available, contributing to reduce mounting area.


2 Low voltage drive

SSM3J66MFV can be driven at low gate-source voltage of 1.2 V. (SSM3J66MFV)




3 AEC-Q101 qualified

AEC-Q101 qualified and can be used for various automotive applications.

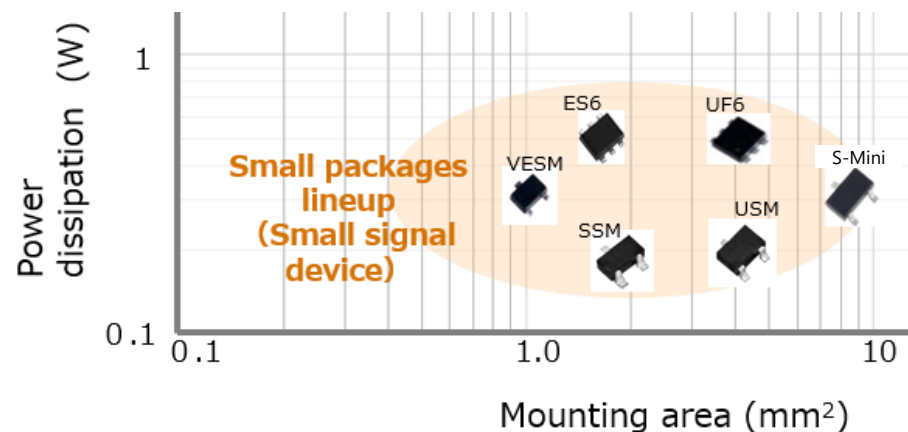Small signal package lineup



Lineup

Part number	SSM3K7002KF	SSM3J168F	SSM3J66MFV
Package	S-Mini (SOT-346) 	S-Mini (SOT-346) 	VESM (SOT-723) 
V_{DSS} [V]	60	-60	-20
I_D [A]	0.4	-0.4	-0.8
$R_{DS(ON)}$ @ $ V_{GS} = 4.5$ V [Ω]	Typ.	1.2	1.4
	Max	1.75	1.9
Drive voltage [V]	4.5	-4.0	-1.2
Polarity	N-ch	P-ch	P-ch

[Return to Block Diagram TOP](#)

Value provided

Extensive product lineup to meet customers' needs.

1 Extensive lineup of packages

Various packages such as 1-in-1, 2-in-1 are provided and suitable products for circuit board design are selectable.



2 Extensive product lineup

Various product lineups, such as general purpose, low noise, low $V_{CE(sat)}$ and high current types are provided. Products can be selected in accordance with the application.

3 AEC-Q101 qualified

AEC-Q101 qualified and can be used for various automotive applications.

Characteristic examples of 2SC2712

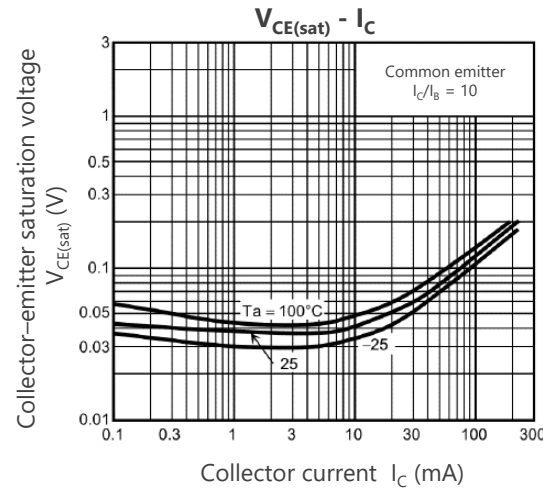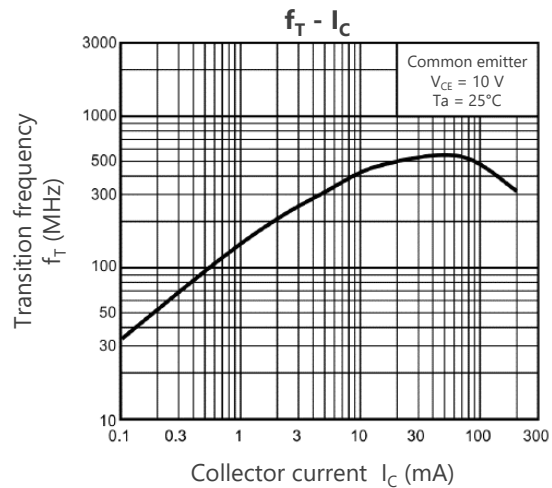

Lineup

Package			SOT-23F		USM (SOT-323) UFM (SOT-323F)*		S-Mini (SOT-346)	
Classification	V_{CE0} [V]	I_C [mA]	NPN	PNP	NPN	PNP	NPN	PNP
General purpose	50	150			2SC4116	2SA1586	2SC2712	2SA1162
	50	500					2SC3325	2SA1313
Low noise	120	100			2SC4117	2SA1587	2SC2713	2SA1163
High current	50	1700				2SA2195*		
	50	2000		TTA501				
	50	2500	TTC501					

* indicates UFM package

[Return to Block Diagram TOP](#)

Value provided

Extensive product lineup to meet customers' needs.

1 Built-in bias resistor type (BRT: Bias Resistor built-in Transistor)


The BRTs contribute to reduction of the number of components, assembly workload and mounting area of circuit boards.

2 Extensive lineup of package and pin assignment



Various package lineups, such as 1-in-1, 2-in-1 and various pin assignment type are provided and suitable products for circuit board design are selectable.

3 AEC-Q101 qualified

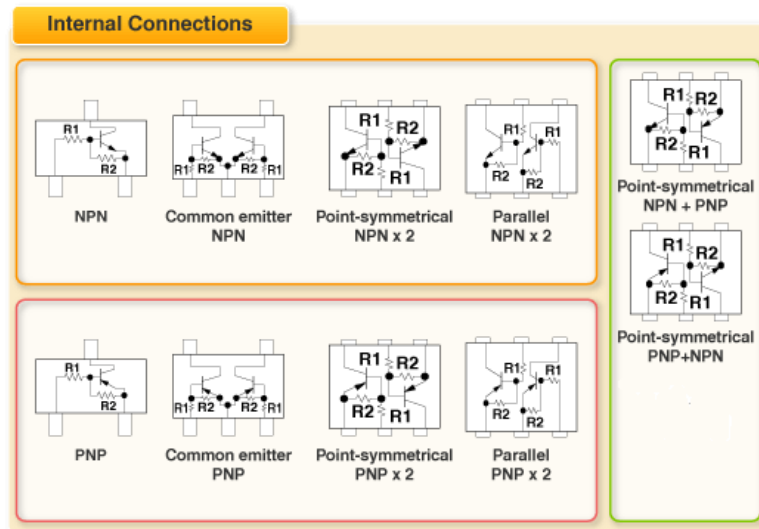AEC-Q101 qualified and can be used for various automotive applications.



Lineup

Part number		NPN (BRT)	PNP (BRT)
Package	ES6 (SOT-563) 	RN1907FE	RN2907FE
	US6 (SOT-363) 	RN1901	RN2901
V_{CE0} [V]		50	-50
I_C [mA]		100	-100

[Return to Block Diagram TOP](#)

Value provided

TVS diodes prevent system damage and malfunction caused by electrostatic discharge (ESD).

1 Improve ESD pulse absorbability

Toshiba proprietary snapback technology (4th-Gen. process) improves ESD pulse absorption compared to Toshiba previous products. (50 % reduction in R_{DYN})



2 Supports Ethernet and LVDS [Note]


These are products applicable to high speed communications (Gbps orders) such as Ethernet and LVDS.

[Note] Low voltage differential signaling

3 High ESD immunity

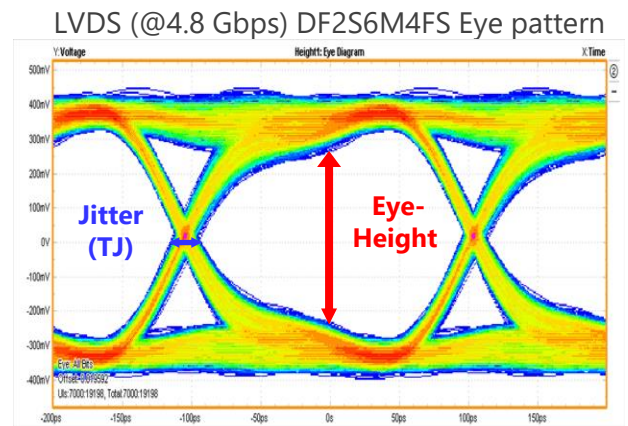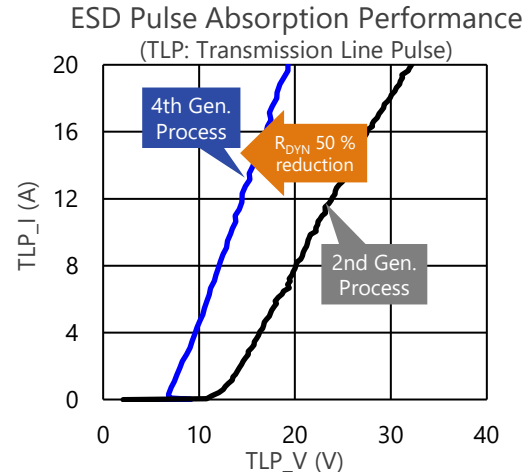$V_{ESD} > \pm 30$ kV @ISO 10605
 $V_{ESD} > \pm 20$ kV @IEC 61000-4-2 (Level 4)



Lineup		
Part number	DF2S5M4FS	DF2S6M4FS
Package	SOD-923 	
V_{ESD} [kV] @ISO 10605	± 30	± 30
V_{RWM} (Max) [V]	3.6	5.5
C_t (Typ. / Max) [pF]	0.45 / 0.55	
R_{DYN} (Typ.) [Ω]	0.35	

(Note: Toshiba internal comparison)
 (Note) This product is an ESD protection diode and cannot be used for purposes other than ESD protection.

[Return to Block Diagram TOP](#)

11 TVS diode (for CAN communication)

DF3D18FU / DF3D29FU / DF3D36FU

Low noise

High efficiency
Low loss

Small size package

Value provided

TVS diodes prevent system damage and malfunction caused by electrostatic discharge (ESD).

1 Improve ESD pulse absorbability

Toshiba proprietary Zener process improves the ESD pulse absorption of TVS diodes.
(Achieving both low dynamic resistance R_{DYN} and low capacitance between terminals C_t)




2 Supports CAN, CAN FD and FlexRay

These are products applicable to in-vehicle LAN communication such as CAN, CAN FD and FlexRay.


3 High ESD immunity

$V_{ESD} > \pm 30$ kV @ISO 10605

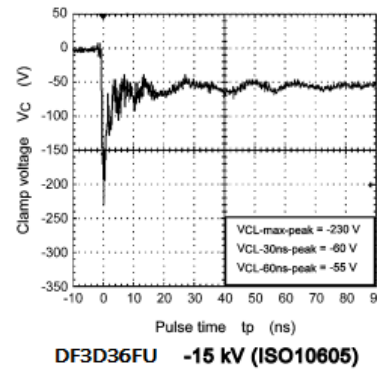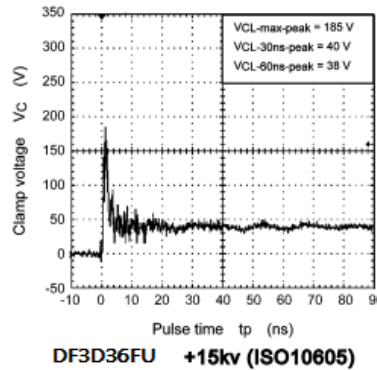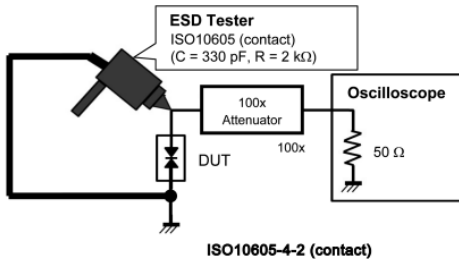$V_{ESD} > \pm 20$ kV @IEC 61000-4-2 (Level 4)



Lineup

Part number	DF3D18FU	DF3D29FU	DF3D36FU
Package	USM (SOT-323) 		
V_{ESD} [kV] @ISO 10605	±30	±30	±20
V_{RWM} (Max) [V]	12	24	28
C_t (Typ. / Max) [pF]	9 / 10		6.5 / 8
R_{DYN} (Typ.) [Ω]	0.8	1.1	1.5

(Note) The above characteristics curves are presented for reference only and not guaranteed by production test, unless otherwise noted.
This product is an ESD protection diode and cannot be used for purposes other than ESD protection.

[Return to Block Diagram TOP](#)

If you are interested in these products and have questions or comments about any of them, please do not hesitate to contact us below:

Contact address: <https://toshiba.semicon-storage.com/ap-en/contact.html>



Terms of use

This terms of use is made between Toshiba Electronic Devices and Storage Corporation ("We") and customers who use documents and data that are consulted to design electronics applications on which our semiconductor devices are mounted ("this Reference Design"). Customers shall comply with this terms of use. Please note that it is assumed that customers agree to any and all this terms of use if customers download this Reference Design. We may, at its sole and exclusive discretion, change, alter, modify, add, and/or remove any part of this terms of use at any time without any prior notice. We may terminate this terms of use at any time and for any reason. Upon termination of this terms of use, customers shall destroy this Reference Design. In the event of any breach thereof by customers, customers shall destroy this Reference Design, and furnish us a written confirmation to prove such destruction.

1. Restrictions on usage

- 1.This Reference Design is provided solely as reference data for designing electronics applications. Customers shall not use this Reference Design for any other purpose, including without limitation, verification of reliability.
- 2.This Reference Design is for customer's own use and not for sale, lease or other transfer.
- 3.Customers shall not use this Reference Design for evaluation in high or low temperature, high humidity, or high electromagnetic environments.
- 4.This Reference Design shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.

2. Limitations

- 1.We reserve the right to make changes to this Reference Design without notice.
- 2.This Reference Design should be treated as a reference only. We are not responsible for any incorrect or incomplete data and information.
- 3.Semiconductor devices can malfunction or fail. When designing electronics applications by referring to this Reference Design, customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of semiconductor devices could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Customers must also refer to and comply with the latest versions of all relevant our information, including without limitation, specifications, data sheets and application notes for semiconductor devices, as well as the precautions and conditions set forth in the "Semiconductor Reliability Handbook".
- 4.When designing electronics applications by referring to this Reference Design, customers must evaluate the whole system adequately. Customers are solely responsible for all aspects of their own product design or applications. WE ASSUME NO LIABILITY FOR CUSTOMERS' PRODUCT DESIGN OR APPLICATIONS.
- 5.No responsibility is assumed by us for any infringement of patents or any other intellectual property rights of third parties that may result from the use of this Reference Design. No license to any intellectual property right is granted by this terms of use, whether express or implied, by estoppel or otherwise.
- 6.THIS REFERENCE DESIGN IS PROVIDED "AS IS". WE (a) ASSUME NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (b) DISCLAIM ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO THIS REFERENCE DESIGN, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.

3. Export Control

Customers shall not use or otherwise make available this Reference Design for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). This Reference Design may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export and re-export of this Reference Design are strictly prohibited except in compliance with all applicable export laws and regulations.

4. Governing Laws

This terms of use shall be governed and construed by laws of Japan.

RESTRICTIONS ON PRODUCT USE

This terms of use is made between Toshiba Electronic Devices and Storage Corporation ("We") and customers who use documents and data that are consulted to design electronics applications on which our semiconductor devices are mounted ("this Reference Design"). Customers shall comply with this terms of use. Please note that it is assumed that customers agree to any and all this terms of use if customers download this Reference Design. We may, at its sole and exclusive discretion, change, alter, modify, add, and/or remove any part of this terms of use at any time without any prior notice. We may terminate this terms of use at any time and for any reason. Upon termination of this terms of use, customers shall destroy this Reference Design. In the event of any breach thereof by customers, customers shall destroy this Reference Design, and furnish us a written confirmation to prove such destruction.

1. Restrictions on usage

- 1.This Reference Design is provided solely as reference data for designing electronics applications. Customers shall not use this Reference Design for any other purpose, including without limitation, verification of reliability.
- 2.This Reference Design is for customer's own use and not for sale, lease or other transfer.
- 3.Customers shall not use this Reference Design for evaluation in high or low temperature, high humidity, or high electromagnetic environments.
- 4.This Reference Design shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.

2. Limitations

- 1.We reserve the right to make changes to this Reference Design without notice.
- 2.This Reference Design should be treated as a reference only. We are not responsible for any incorrect or incomplete data and information.
- 3.Semiconductor devices can malfunction or fail. When designing electronics applications by referring to this Reference Design, customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of semiconductor devices could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Customers must also refer to and comply with the latest versions of all relevant our information, including without limitation, specifications, data sheets and application notes for semiconductor devices, as well as the precautions and conditions set forth in the "Semiconductor Reliability Handbook".
- 4.When designing electronics applications by referring to this Reference Design, customers must evaluate the whole system adequately. Customers are solely responsible for all aspects of their own product design or applications. WE ASSUME NO LIABILITY FOR CUSTOMERS' PRODUCT DESIGN OR APPLICATIONS.
- 5.No responsibility is assumed by us for any infringement of patents or any other intellectual property rights of third parties that may result from the use of this Reference Design. No license to any intellectual property right is granted by this terms of use, whether express or implied, by estoppel or otherwise.
- 6.THIS REFERENCE DESIGN IS PROVIDED "AS IS". WE (a) ASSUME NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (b) DISCLAIM ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO THIS REFERENCE DESIGN, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.

3. Export Control

Customers shall not use or otherwise make available this Reference Design for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). This Reference Design may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export and re-export of this Reference Design are strictly prohibited except in compliance with all applicable export laws and regulations.

4. Governing Laws

This terms of use shall be governed and construed by laws of Japan.

TOSHIBA

- * MIPI[®], CSI-2[®] and DSI[®] are registered service marks of MIPI Alliance, Inc. DPISM is service mark of MIPI Alliance, Inc.
- * HDMI is a trademark or registered trademark of HDMI Licensing Administrator, Inc.
- * DisplayPort and the DisplayPort logo are trademarks owned by the Video Electronics Standards Association (VESA[®]).
- * S-TOGLTM and L-TOGLTM are trademarks of Toshiba Electronic Devices & Storage Corporation.
- * All other company names, product names, and service names may be trademarks of their respective companies.